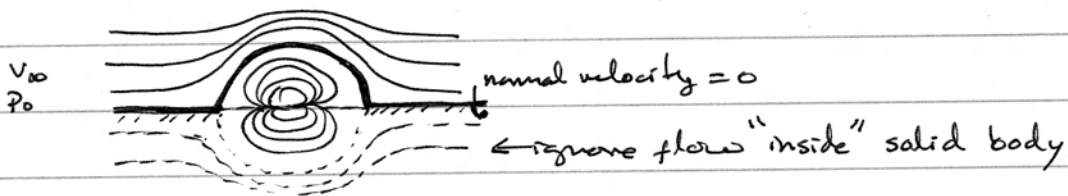


Solutions F10

Flow is a superposition of doublet and uniform (along x)



↳ this reduces to:

the stream function is $\psi = V_{\infty} r \sin \theta \left(1 - \left(\frac{a}{r}\right)^2\right)$

the velocity components are:

$$V_r = \frac{1}{r} \frac{\partial \psi}{\partial \theta} = V_{\infty} \cos \theta \left(1 - \left(\frac{a}{r}\right)^2\right)$$

$$V_{\theta} = -\frac{\partial \psi}{\partial r} = -V_{\infty} \sin \theta \left(1 + \left(\frac{a}{r}\right)^2\right)$$


(a) Along the hump: $r = a$ then $V_r = 0$

$$V_{\theta} = -2V_{\infty} \sin \theta$$

Bernoulli $\Rightarrow \frac{1}{2} \rho V_{\infty}^2 + P_0 = \frac{1}{2} \rho V_{\theta}^2 + P \Rightarrow P = P_0 + \frac{1}{2} \rho V_{\infty}^2 \left(1 - \left(\frac{V_{\theta}}{V_{\infty}}\right)^2\right)$

$$P = P_0 + \frac{1}{2} \rho V_{\infty}^2 (1 - 4 \sin^2 \theta)$$

$P_{\max} = P_0 + \frac{1}{2} \rho V_{\infty}^2$	at $\theta = 0$ and $\theta = \pi$
$P_{\min} = P_0 - \frac{3}{2} \rho V_{\infty}^2$	at $\theta = \pi/2$

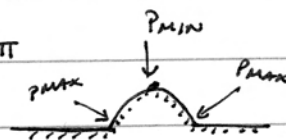

(b) for $\psi = 0$ at $r = a$, then ψ increases for other streamlines from zero.

at $r = 2a, \theta = \frac{\pi}{2}$: $\psi = V_{\infty} 2a \sin \frac{\pi}{2} \left(1 - \left(\frac{a}{2a}\right)^2\right)$

$$= 2V_{\infty} a \left(\frac{3}{4}\right) = \frac{3}{2} V_{\infty} a$$

This means $\psi = \frac{3}{2} V_{\infty} a$ is constant on the streamline,

therefore:


$$\frac{3}{2} V_{\infty} a = V_{\infty} r \sin \theta \left(1 - \left(\frac{a}{r}\right)^2\right) \quad \text{solve for } r:$$

$$\Rightarrow r^2 - \frac{3a}{2 \sin \theta} r - a^2 = 0$$

$$r = \frac{3a}{4 \sin \theta} \left(1 + \sqrt{1 + \frac{16}{9} \sin^2 \theta}\right)$$

Solentrons #11

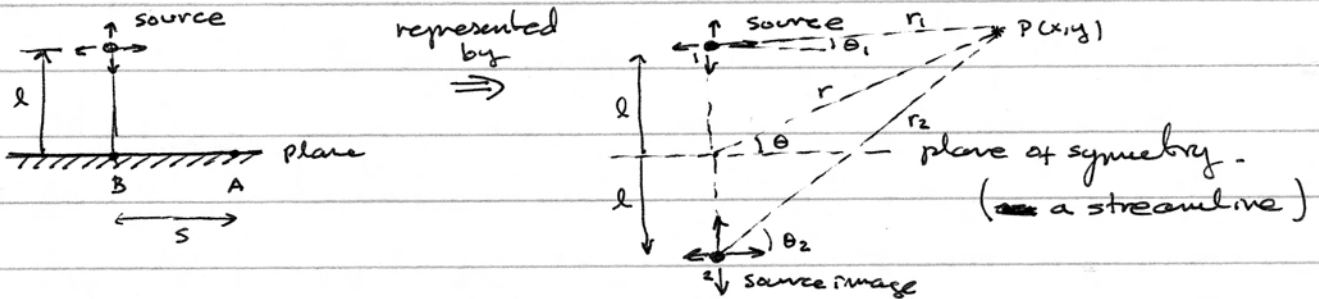To solve this problem, we will use the method of images and place an identical source (pipe) at a symmetric point "inside" the plane surface in order to force the mid-plane be a streamline:




and

the stream function of the source is $\psi = \frac{\Lambda}{2\pi} (\theta_1 + \theta_2)$

and in the most general case we would find ψ at the point (x, y) by finding expressions for $\theta_1 = \theta_1(r, \theta)$ and $\theta_2 = \theta_2(r, \theta)$

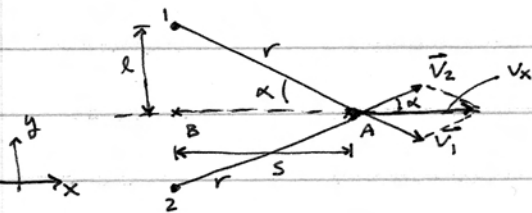In our case, this is not required as we look only for the velocity distribution along the surface. We only need information on the contribution of each source to the velocity: $V_r = \frac{\Lambda}{2\pi r}$



y-components cancel out.

x-component $\Rightarrow V_x = 2V_r \cos \alpha$

$$\text{and } \cos \alpha = \frac{s}{r} \Rightarrow V_x = 2V_r \frac{s}{r} = \frac{\Lambda}{\pi} \frac{s}{r^2}$$

or $V_x = \frac{\Lambda}{\pi} \frac{s}{s^2 + l^2}$, From Bernoulli's: $\frac{1}{2} s V_A^2 + P_A = \frac{1}{2} s V_B^2 + P_B$

and $V_A = V_x$, while $V_B = 0$ (symmetric point).

then $P_B - P_A = \frac{1}{2} s V_x^2 = \frac{1}{2} s \left(\frac{\Lambda}{\pi} \frac{s}{s^2 + l^2} \right)^2$ Values: $\Lambda = \frac{1}{2} \pi (\dot{V}/\text{depth})$

$S = 4 \text{ ft}$

$l = 3 \text{ ft}$

$$P_B - P_A = 0.1984 \frac{\text{lb}}{\text{ft}^2}$$

Signals & Systems.

①

S14

A) From S12 we have

$$\begin{bmatrix} \dot{i}_1 \\ \dot{i}_2 \end{bmatrix} = \begin{bmatrix} -2 & -1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$B) (sI - A) = \begin{bmatrix} s+2 & 1 \\ 1 & s+2 \end{bmatrix}$$

$$|sI - A| = (s+2)^2 - 1 = 0 \Rightarrow s^2 + 4s + 3 = 0$$
$$s_1 = -1, s_2 = -3$$

c) eigen-vectors

$$s = -1 \quad \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} I_1^{s_1} \\ I_2^{s_1} \end{bmatrix} = 0 \quad I_1^{s_1} = -I_2^{s_1}$$
$$I^{s_1} = \begin{bmatrix} -1 \\ 1 \end{bmatrix}$$

$$s = -3 \quad \begin{bmatrix} -1 & 1 \\ 1 & -1 \end{bmatrix} \Rightarrow I^{s_2} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$i_1(t) = -ae^{-t} + be^{-3t}$$
$$i_2(t) = ae^{-t} + be^{-3t}$$

$$i_1(0) = -a + b = 10 \text{ A} \Rightarrow \left. \begin{array}{l} 2b = 10 \\ b = 5 \\ a = -5 \end{array} \right\}$$
$$i_2(0) = a + b = 0 \Rightarrow a = -b$$

$$i_1(t) = 5e^{-t} + 5e^{-3t} \quad i_2(t) = -5e^{-t} + 5e^{-3t}$$

$$a) \quad \tilde{x} = \begin{bmatrix} i_1(t) \\ i_3(t) \end{bmatrix}$$

$$\text{Note: } i_1 + i_2 + i_3 = 0 \Rightarrow i_3 = -i_1 - i_2$$

$$\text{State transformation matrix } T = \begin{bmatrix} 1 & 0 \\ -1 & -1 \end{bmatrix}, \quad \tilde{x} = T x.$$

$$b) \quad T^{-1} = \begin{bmatrix} 1 & 0 \\ -1 & -1 \end{bmatrix}$$

$$\tilde{A} = T A T^{-1} \quad \text{where } A \text{ is } \begin{bmatrix} -2 & -1 \\ -1 & -2 \end{bmatrix}$$

$$\tilde{A} = \begin{bmatrix} -1 & 1 \\ 0 & -3 \end{bmatrix}$$

$$sI - \tilde{A} = \begin{bmatrix} s+1 & -1 \\ 0 & s+3 \end{bmatrix} \quad |sI - \tilde{A}| = (s+1)(s+3) = 0$$

$$s_1 = -1, \quad s_2 = -3$$

$$\text{Eigen-vectors } I^{s_1} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad I^{s_2} = \begin{bmatrix} -1 \\ 2 \end{bmatrix}$$

$$\text{Hence, } i_1(t) = a e^{-t} - b e^{-3t}$$

$$i_2(t) = 2b e^{-3t}$$

Note that $i_3 = -i_1 - i_2$

$$\text{Hence, } i_3(0) = -i_1(0) - i_2(0) = -10\text{A.}$$

$$\begin{aligned} \text{Now } i_1(0) = a - b = 10\text{A} &\Rightarrow a = 10 - b \\ i_3(0) = 2b = -10\text{A} &\Rightarrow b = -5 \\ &\Rightarrow a = 5 \end{aligned}$$

Complete solution:

$$i_1(t) = 5e^{-t} + 5e^{-3t}$$

$$i_3(t) = -10e^{-3t}$$

d) Compare to S14.

$i_1(t)$ is the same ✓

In S14 we obtained i_1 & i_2

$$i_3^{(1)} = -i_1(t) - i_2(t)$$

$$= -5e^{-t} - 5e^{-3t} + 5e^{-t} - 5e^{-3t}$$

$$= -10e^{-3t} \quad \checkmark$$

a) state variables: $v_c(t), i_L(t)$

• Node equations

$$\left. \begin{array}{l} \textcircled{1} \quad i_c + \frac{v_c - v_L}{R} = 0 \\ i_c = C \frac{dv_c}{dt} \end{array} \right\} C \frac{dv_c}{dt} + \frac{v_c}{R} - \frac{v_L}{R} = 0 \quad (*)$$

$$\left. \begin{array}{l} \textcircled{2} \quad i_L + \frac{v_L - v_c}{R} = 0 \\ v_L = L \frac{di_L}{dt} \end{array} \right\} i_L + \frac{L}{R} \frac{di_L}{dt} - \frac{v_c}{R} = 0 \quad (**)$$

Note: $v_L = v_c - i_L \cdot R$

$$(*) \Rightarrow C \frac{dv_c}{dt} + \frac{v_c}{R} - \frac{v_c}{R} + i_L = 0 \Rightarrow \frac{dv_c}{dt} = -\frac{i_L}{C}$$

$$(**) \Rightarrow \frac{di_L}{dt} = \frac{v_c}{L} - i_L \cdot \frac{R}{L}$$

$$\begin{bmatrix} \dot{v}_c \\ i_L \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{C} \\ \frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix}$$

$$\left| sI - A \right| = \begin{vmatrix} s & +1/L \\ -1/L & s + R/L \end{vmatrix} = s(s + R/L) + \frac{1}{LC} = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s_1 = \frac{-R/L + \sqrt{(R/L)^2 - 4/LC}}{2}$$

$$s_2 = \frac{-R/L - \sqrt{(R/L)^2 - 4/LC}}{2}$$

b) $R = \frac{0 \Omega}{1}, L = 2H, C = 2F$

$$s_1 = j/2, \quad s_2 = -j/2, \quad j = \sqrt{-1}$$

possible solutions: $e^{j/2 t}, e^{-j/2 t}$.

$$s_1 = j/2 \Rightarrow sI - A = \begin{bmatrix} j/2 & 1/2 \\ -1/2 & j/2 \end{bmatrix} \begin{bmatrix} E_1^{s_1} \\ E_2^{s_1} \end{bmatrix}$$

$$j/2 E_1 + \frac{1}{2} E_2 = 0 \Rightarrow E_1 = -E_2/j = j \cdot E_2$$

$$E^{s_1} = \begin{bmatrix} j \\ 1 \end{bmatrix}$$

Similarly

$$E^{s_2} = \begin{bmatrix} -j \\ 1 \end{bmatrix}$$

S16 - Cont. (3)

$$V_C(t) = aj e^{j/2 t} - j b e^{-j/2 t}$$

$$i_L(t) = a e^{j/2 t} + b e^{-j/2 t}$$

$$\left. \begin{aligned} V_C(0) &= 10V \\ i_L(0) &= 0A \end{aligned} \right\} \Rightarrow \begin{aligned} aj - bj &= 10 \\ a + b &= 0 \Rightarrow a = -b \end{aligned}$$

$$\Rightarrow -2bj = 10 \Rightarrow b = -5/j = 5j$$

$$a = -5j$$

~~at~~ Solution:

$$V_C(t) = 5 e^{j/2 t} + 5 e^{-j/2 t}$$

$$i_L(t) = -5j e^{j/2 t} + 5j e^{-j/2 t}$$

c) $e^{jB} = \cos(B) + j \sin(B)$

$$\cos(-B) = \cos(B), \sin(-B) = -\sin(B)$$

$$e^{j/2 t} = \cos(t/2) + j \sin(t/2)$$

$$e^{-j/2 t} = \cos(t/2) - j \sin(t/2)$$

$$V_C(t) = 5 (\cos(t/2) + j \sin(t/2)) + 5 (\cos(t/2) - j \sin(t/2))$$

$$= 10 \cos(t/2)$$

$$i_L(t) = -5j [\cos(t/2) + j \sin(t/2)] + 5j [\cos(t/2) - j \sin(t/2)]$$

$$= 10 \sin(t/2)$$

you can now check this answer


$$\frac{dV_C}{dt} = \frac{-i_L}{C} \Rightarrow i_L = -C \frac{dV_C}{dt} \quad C=2$$

$$\frac{d}{dt} 10 \cos\left(\frac{t}{2}\right) = -5 \sin\left(\frac{t}{2}\right)$$

$$\Rightarrow i_L = 10 \sin\left(\frac{t}{2}\right)$$

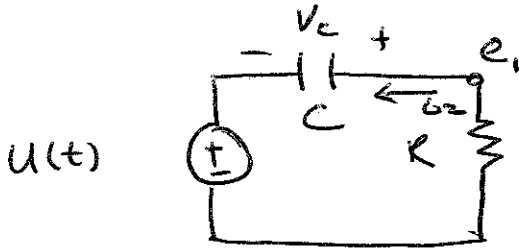d) without a resistor in the circuit ($R=0$) energy does not dissipate in this circuit. As a result energy moves back-and-forth between the inductor and the capacitor, leading to the oscillation in the current and voltage.

$$i_2 = C \frac{dv_c}{dt} \Rightarrow \frac{dv_c}{dt} = \frac{i_2}{C}$$



$$e_1 = u(t) + v_c(t)$$

Node equation at e_1 : $i_2 + \frac{e_1}{R} = 0$

$$\Rightarrow \frac{e_1}{R} = -i_2$$

$$\Rightarrow \frac{u(t) + v_c(t)}{R} = -i_2 = -C \frac{dv_c}{dt}$$

$$\frac{dv_c}{dt} = \frac{-u(t) - v_c(t)}{RC}$$

Homogeneous solution: ~~$v_c = a e^{st}$~~ $u(t) = 0$

$$\Rightarrow \frac{dv_c}{dt} = \frac{-v_c(t)}{RC}$$

$$v_c = a e^{st}$$

$$\Rightarrow a s e^{st} = \frac{-a e^{st}}{RC}$$

$$as + \frac{a}{RC} = 0 \quad a(s + \frac{1}{RC}) = 0 \Rightarrow s = -\frac{1}{RC}$$

$$V_H = a e^{-t/RC}$$

With $u(t) = 1V$ we guess a constant forced response

$$V_F = B, \quad \dot{V}_F = 0$$

$$\textcircled{*} \frac{dV_C}{dt} = \frac{-u(t) - V_C(t)}{RC} = \frac{-1 - B}{RC} = 0 \quad \begin{array}{l} \leftarrow V_C = V_F = B \\ \leftarrow \text{with } V_F = B \\ \dot{V}_F = 0. \end{array}$$

* Note we use $V_C = V_F = B$

$$\Rightarrow B = -1$$

$$V_F = -1$$

$$V_C(t) = V_H + V_F = a e^{-t/RC} - 1$$

$$V_C(0) = 0 \Rightarrow a - 1 = 0$$

$$\Rightarrow a = 1$$

$$\boxed{V_C(t) = (e^{-t/RC} - 1)V}$$

Note that as $t \rightarrow \infty$ $V_C \rightarrow -1V$.

this makes sense because as $t \rightarrow \infty$ the capacitor becomes an open circuit, current stops flowing,

$$\Rightarrow i_c = 0 \Rightarrow V_C = -u(t) = -1V.$$