

# Lect # 3

Note Title

10/26/2008

Next:

- Kirchhoff's Current Law
- Kirchhoff's Voltage Law
- Examples

Objectives:

- Be able to state Ohm's Law, Kirchhoff's Current Law, Kirchhoff's Voltage Law, and be able to use those Laws to analyze simple circuits
- know how to calculate power for each element in a simple circuit and be able to determine (check) whether or not power balances for the whole circuit.

- Kirchhoff's Law

- Kirchhoff's Current Law (KCL)

The algebraic sum of all the currents at any node in a circuit equals zero.

- Kirchhoff's Voltage Law (KVL)

The algebraic sum of all the voltages around any closed path in a circuit equals zero.

Gustav Kirchhoff - 1848

. To use KCL - algebraic sign corresponding to a reference direction must be assigned to every current at a node


+ sign (- sign) to current leaving a node requires  
- sign (+ sign) to current entering a node

- To use KVL - algebraic sign corresponding to a reference direction must be assign to each voltage in a loop.

As we trace a closed path a voltage will appear either as a raise or a drop in the tracing direction.

+ sign (- sign) to a voltage rise requires  
 - sign (+ sign) to a voltage drop.

Example :

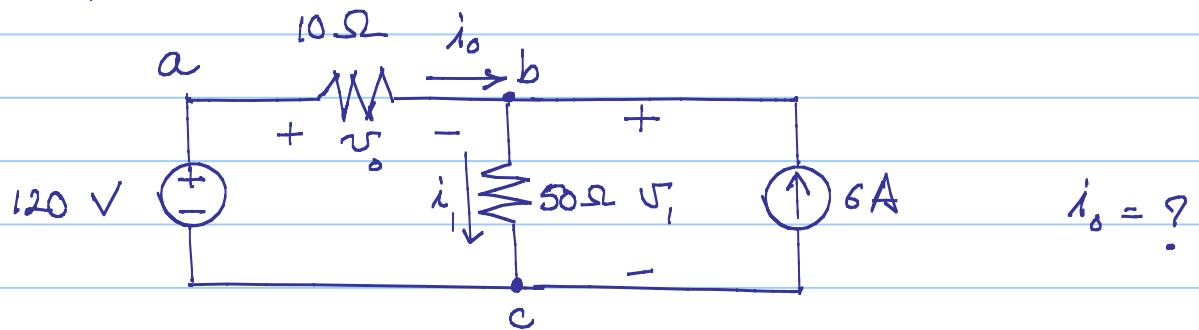

At node b (assigning + to outgoing currents)

$$+) i_1 - i_o - 6 = 0 \quad \text{KCL}$$

Clockwise around the first loop  
(assign + to voltage drops)

$$-120 + 5i_0 + 5i_1 = 0 \quad \text{KVL}$$

1)  $-120 + 10i_0 + 50i_1 = 0 \quad \text{Ohm's Law}$

10  $\times$  i)  $10i_1 - 10i_0 = 60$

2)  $50i_1 + 10i_0 = 120$

+  $60i_1 = 180$

$$i_1 = 3 \text{ Amp}$$

$$i_0 = -3 \text{ Amp}$$

$$V_0 = 10i_0 = -30 \text{ Volts}$$

$$V_1 = 50i_1 = 150 \text{ Volts}$$

Check: Total power generated  
= total power dissipated ?

power dissipated in the resistors :

$$P_{50\Omega} = i_1^2 \cdot 50 = 3^2 \cdot 50 = 450 \text{ Watts}$$

$$P_{10\Omega} = i_2^2 \cdot 10 = (-3)^2 \cdot 10 = 90 \text{ Watts}$$

power delivered to the voltage source

$$P_{120V} = -120 i_3 = -120 (-3) = 360 \text{ Watts}$$

power delivered to the current source


$$P_{6A} = -51 \cdot 6 = -150 \cdot 6 = -900 \text{ Watts}$$

In summary:

The 6A current source is delivering 900 Watts  
120V voltage source is absorbing 360 Watts

total power absorbed is  $360 + 450 + 90 = 900 \text{ Watts}$

Example

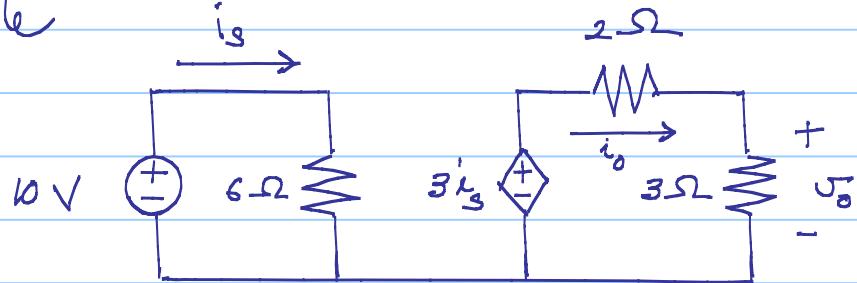

Left Loop

$$1) \quad i_s 6 = 10 \quad (\text{Ohm's Law})$$

Right Loop

$$2) \quad -3i_s + 2i_o + 3i_o = 0$$

$$1) \Rightarrow i_s = \frac{5}{3} \text{ Amp}$$

$$2) \Rightarrow i_o = 1 \text{ Amp}$$

$$v_o = i_o 3 = 3 \text{ Volts}$$

power delivered to independent voltage source

$$P_{\text{cov}} = -25 i_s = -10 \frac{5}{3} = -\frac{50}{3} \text{ Watts}$$

power delivered to dependent voltage source

$$P_3 = -(3 i_s) i_o = -(5) 1 = -5 \text{ Watts}$$

power delivered to the resistors

$$P_{6\Omega} = i_o^2 6 = \left(\frac{5}{3}\right)^2 6 = \frac{50}{3} \text{ Watts}$$

$$P_{2\Omega} = i_o^2 2 = 1^2 2 = 2 \text{ Watts}$$

$$P_{3\Omega} = i_o^2 3 = 1^2 3 = 3 \text{ Watts}$$

Total power delivered by the sources =  $\frac{50}{3} + 5$  Watts

" " absorbed by (dissipated) by the  
resistors =  $\frac{50}{3} + 5$  Watts