

Lect # 6

Note Title

10/26/2008

Next:

- Introduction to the Mesh - Current Method
- The Mesh Current Method and Dependent sources
- The Node Current Method : Some Special Cases


Objectives:

Understand and be able to use mesh-current method to solve a circuit.

Be able to decide whether the node-voltage method or mesh-current method

= The Mesh Current Method.

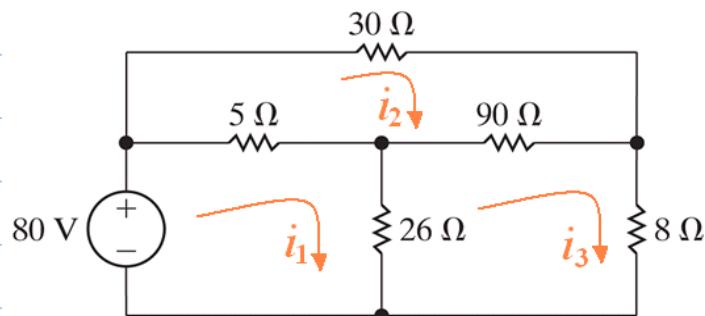- The dual of the node voltage method
 - Use KVL equations around meshes
 - Solve directly for currents
- Find the power associated with the voltage source and $8\ \Omega$ resistor, using the mesh current method.



- KVL equations:

$$i_1 \text{ mesh: } -80 + 5(i_1 - i_2) + 26(i_1 - i_3) = 0$$

$$i_2 \text{ mesh: } 30i_2 + 90(i_2 - i_3) + 5(i_2 - i_1) = 0$$

$$i_3 \text{ mesh: } 8i_3 + 26(i_3 - i_1) + 90(i_3 - i_2) = 0$$

- Standard Forms:

$$i_1(5+26) + i_2(-5) + i_3(-26) = 80$$

$$i_1(-5) + i_2(30+90+5) + i_3(-90) = 0$$


$$i_1(-26) + i_2(-90) + i_3(8+26+90) = 0$$

$$\Rightarrow i_1 = 5 \text{ A}$$

$$i_2 = 2 \text{ A}$$

$$i_3 = 2.5 \text{ A}$$


- Power balance

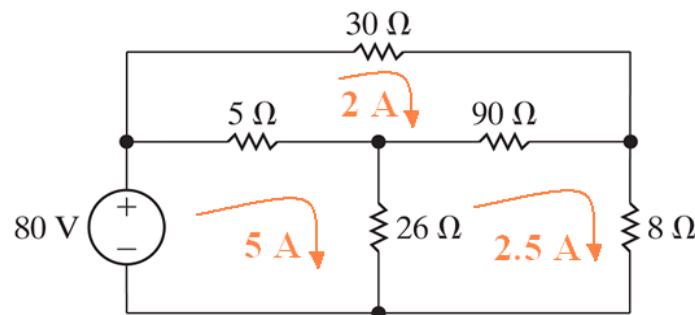

Component	Equation	p [W]
80 V	$-(5)(80)$	-400
5 Ω	$(5 - 2)^2(5)$	45
90 Ω	$(2.5 - 2)^2(90)$	22.5
30 Ω	$(2)^2(30)$	120
26 Ω	$(5 - 2.5)^2(26)$	162.5
8 Ω	$(2.5)^2(8)$	50

- Mesh current method with dependent source

Find v_o using the mesh current method

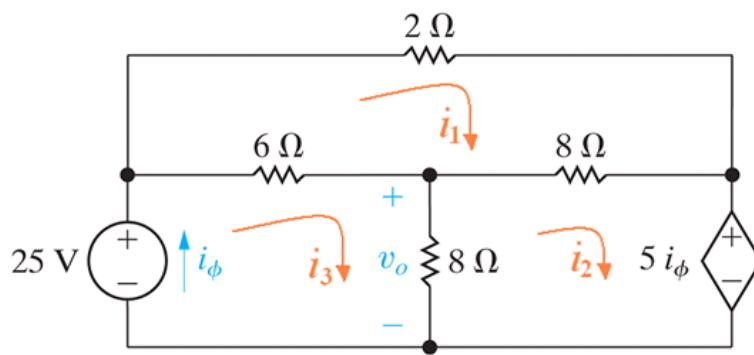

KVL equations:

$$i_1 \text{ mesh: } 2i_1 + 8(i_1 - i_2) + 6(i_1 - i_3) = 0$$

$$i_2 \text{ mesh: } 5i_\phi + 8(i_2 - i_3) + 8(i_2 - i_1) = 0$$

$$i_3 \text{ mesh: } -25 + 6(i_3 - i_1) + 8(i_3 - i_2) = 0$$

constraint equation: $i_\phi = i_3$

Standard Form

$$i_1(2+6+8) + i_2(-8) + i_3(-6) = 0$$

$$i_1(-8) + i_2(8+8) + i_3(5-8) = 0$$


$$i_1(-6) + i_2(-8) + i_3(6+8) = 25$$

$$\Rightarrow i_1 = 2.5 \text{ A}$$

$$i_2 = 2 \text{ A}$$

$$i_3 = i_\phi = 4 \text{ A}$$


- Power balance

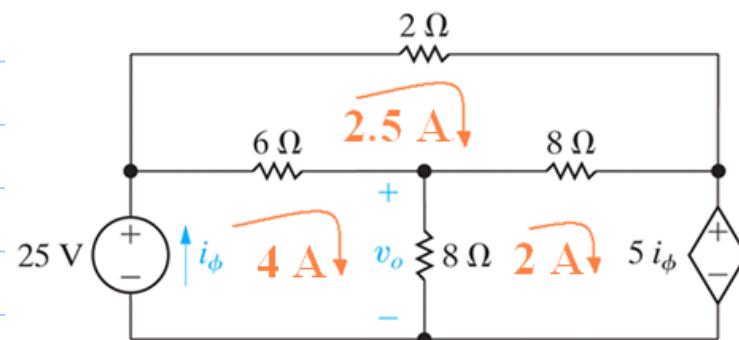


Component	Equation	p [W]
25 V	$-(4)(25)$	-100
Dep. source	$(2)[5(4)]$	40
6Ω	$(4 - 2.5)^2(6)$	13.5
2Ω	$(2.5)^2(2)$	12.5
8Ω (middle)	$(4 - 2)^2(8)$	32
8Ω (right)	$(2 - 2.5)^2(8)$	2

- Mesh current method with current source on the perimeter of a mesh

Find i_a using the mesh current method

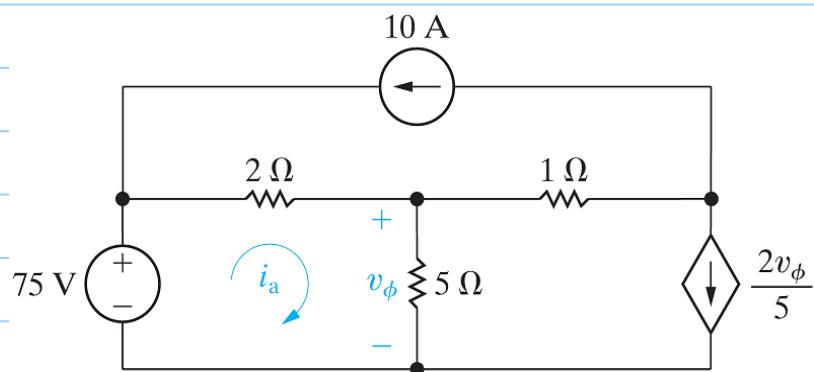

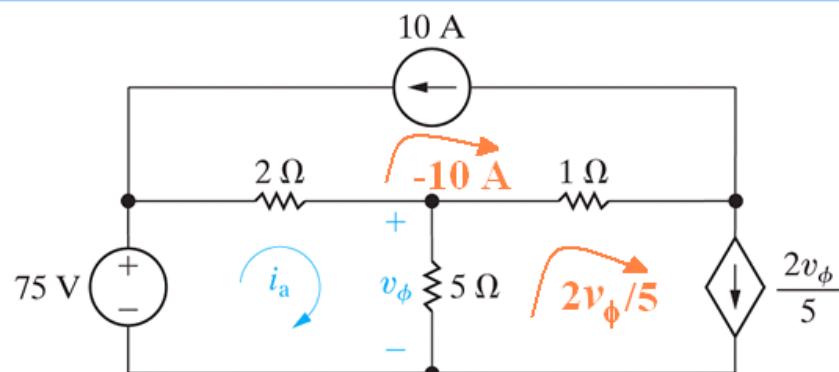If there are current sources on the perimeter of a mesh, then label the mesh currents with the values of the current sources



KVL for i_a mesh:

$$-75 + 2(i_a - (-10)) + 5(i_a - \frac{2}{5}v_\phi) = 0$$

Constraint:

$$v_\phi = 5(i_a - \frac{2}{5}v_\phi)$$

Standard Form


$$i_a(2+5) + v_\phi(-2) = 75 - 20$$

$$i_a(5) + v_\phi(-2-1) = 0$$

$$\Rightarrow i_a = 15 \text{ A}$$

$$v_\phi = 25 \text{ V}$$

- Power balance

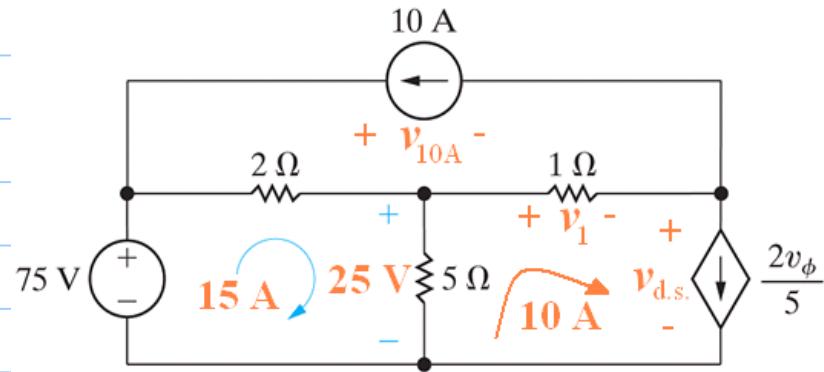

$$v_i = (10 + 10) \cdot 1 = 20 \text{ V}$$

$$v_{ds} = v_\phi - v_i = 25 - 20 = 5 \text{ V}$$

$$v_{10A} = -v_{ds} + 75 = -5 + 75 = 70 \text{ V}$$

Component	Equation	p [W]
75 V	$-(15)(75)$	-1125
Dep. source	$(5)(10)$	50
10 A	$-(70)(10)$	-700
2 Ω	$(15+10)^2(2)$	1250
1 Ω	$(10+10)^2(1)$	400
5 Ω	$25^2/5$	125