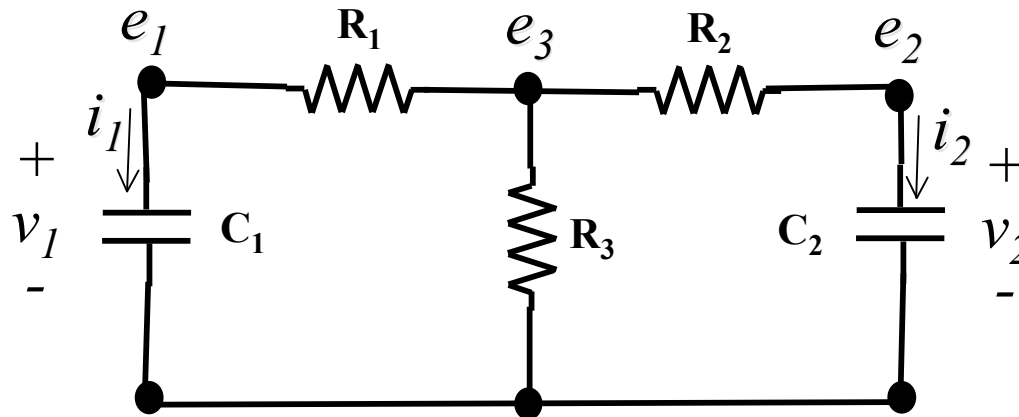

Analysis of RC circuits

Eytan Modiano

Learning Objectives

- **Analysis of basic circuit with capacitors, no inputs**
 - **Derive the differential equations for the voltage across the capacitors**
- **Solve a system of first order homogeneous differential equations using classical method**
 - **Identify the exponential solution**
 - **Obtain the characteristic equation of the system**
 - **Obtain the natural response of the circuit**
 - **Solve for the complete solution using initial conditions**

Second order RC circuits



$$R_1 = R_2 = R_3 = 1\Omega$$

$$C_1 = C_2 = 1F$$

$$i_1 = C_1 \frac{dv_1}{dt} \quad i_2 = C_2 \frac{dv_2}{dt}$$

Node equations :

$$e_1 : i_1 + (e_1 - e_3) / R_1 = 0$$

$$e_2 : (e_2 - e_3) / R_2 + i_2 = 0$$

$$e_3 : (e_3 - e_1) / R_1 + (e_3 - e_2) / R_2 + e_3 / R_3 = 0$$

The differential equations

Note : $v_1 = e_1$; $v_2 = e_2$

Differential equations:

$$C_1 \frac{de_1}{dt} + (e_1 - e_3) / R_1 = 0$$

$$C_2 \frac{de_2}{dt} + (e_2 - e_3) / R_2 = 0$$

$$(e_3 - e_1) / R_1 + (e_3 - e_2) / R_2 + e_3 / R_3 = 0$$

Plugging in values for resistors capacitors :

$$(1) \dot{e}_1 + e_1 - e_3 = 0$$

$$(2) \dot{e}_2 + e_2 - e_3 = 0$$

$$(3) 3e_3 - e_2 - e_1 = 0$$

Guessing a solution

We “guess” that the solution is an exponential of the form:

$$\text{Guess } e_i = E_i e^{st} \Rightarrow \dot{e}_i = E_i s e^{st}$$

$$\left. \begin{aligned} E_1 s e^{st} + E_1 e^{st} - E_3 e^{st} &= 0 \\ E_2 s e^{st} + E_2 e^{st} - E_3 e^{st} &= 0 \\ 3E_3 e^{st} - E_2 e^{st} - E_1 e^{st} &= 0 \end{aligned} \right\} \Rightarrow \begin{aligned} E_1 s + E_1 - E_3 &= 0 \\ E_2 s + E_2 - E_3 &= 0 \\ 3E_3 - E_2 - E_1 &= 0 \end{aligned}$$

$$E_1(1 + s) \quad - E_3 = 0$$

$$E_2(1 + s) \quad - E_3 = 0$$

$$-E_1 \quad -E_2 \quad +3E_3 = 0$$

Solution to homogeneous equations

- If equations are linearly independent we have one unique solution:
 - $E_1=E_2=E_3=0$
 - “trivial” solution
- In order to obtain non-trivial solution, the equations cannot be linearly independent
 - For what values of s are the equations not linearly independent?
- Rewrite equations in the form: $AE = 0$

$$\begin{bmatrix} (1+s) & 0 & -1 \\ 0 & 1+s & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix} = 0$$

- Rows of A are linearly dependent if determinant of $A = 0$
 - Non-trivial solution

The characteristic equation

$\det A = 0$ (The characteristic equation)

see linear algebra primer on taking determinants

$$|A| = 3(1+s)(1+s) - (1+s) - (1+s) = 0$$

$$3s^2 + 4s + 1 = 0 \Rightarrow s = \frac{-4 \pm \sqrt{16 - 12}}{6} = \frac{-4 \pm 2}{6}$$

$$\Rightarrow s_1 = -1, s_2 = -1/3$$

Two solutions :

$$s = -1 \Rightarrow e_i = E_i e^{-t}$$

$$s = -1/3 \Rightarrow e_i = E_i e^{-t/3}$$

Non-trivial solution

- Now we must solve for the values of E_i 's

- Recall $E_1(1+s) - E_3 = 0$

$$E_2(1+s) - E_3 = 0$$

$$-E_1 - E_2 + 3E_3 = 0$$

- For $s = -1$ we have,

$$E_1(0) - E_3 = 0 \Rightarrow E_3 = 0$$

$$E_2(0) - E_3 = 0 \Rightarrow E_3 = 0$$

$$-E_1 - E_2 + 3E_3 = 0 \Rightarrow E_1 = -E_2$$

Solution not unique, choose: $E_2 = 1, E_1 = -1$

$$\Rightarrow e_1 = -1e^{-t}, e_2 = 1e^{-t}, e_3 = 0$$

Non-trivial solution, continued

- Similarly, for $s = -1/3$

$$E_1(2/3) - E_3 = 0 \Rightarrow E_1 = 3/2 E_3$$

$$E_2(2/3) - E_3 = 0 \Rightarrow E_2 = 3/2 E_3$$

$$-E_1 - E_2 + 3E_3 = 0$$

Solution not unique, choose : $E_3 = 1, E_1 = E_2 = 3/2$

$$\Rightarrow e_1 = 3/2 e^{-t/3}, e_2 = 3/2 e^{-t/3}, e_3 = e^{-t/3}$$

- Note that in general we can solve for the E's using row reduction, etc. (see linear algebra notes)

The complete solution

- We now have two possible solutions:

$$(1): e_1 = 3/2 e^{-t/3}, e_2 = 3/2 e^{-t/3}, e_3 = e^{-t/3}$$

$$(2): e_1 = -1 e^{-t}, e_2 = 1 e^{-t}, e_3 = 0$$

- Since the system is linear and homogeneous, any linear combination of these solution is also a solution. Hence,

$$\vec{e}(t) = a \begin{bmatrix} -1 \\ 1 \\ 0 \end{bmatrix} e^{-t} + b \begin{bmatrix} 3/2 \\ 3/2 \\ 1 \end{bmatrix} e^{-t/3}$$

- Where a, and b are constants that depend on initial conditions
 - Given initial values for $e_1 = v_1$ and $e_2 = v_2$ we can solve for a and b

The complete solution, continued

- Suppose we are given the initial voltage values across the capacitors: $e_1(0) = v_1(0)$, $e_2(0) = v_2(0)$
- Plug these into the solution to obtain:
$$\left. \begin{aligned} e_1(0) &= -ae^0 + 3/2be^0 = -a + 3/2b \\ e_2(0) &= ae^0 + 3/2be^0 = a + 3/2b \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow a = \frac{e_2(0) - e_1(0)}{2}, \quad b = \frac{e_1(0) + e_2(0)}{3}$$

Finally,

$$e_1(t) = \frac{e_1(0) - e_2(0)}{2} e^{-t} + \frac{e_1(0) + e_2(0)}{2} e^{-t/3}$$

$$e_2(t) = \frac{e_2(0) - e_1(0)}{2} e^{-t} + \frac{e_1(0) + e_2(0)}{2} e^{-t/3}$$

$$e_3(t) = \frac{e_1(0) + e_2(0)}{3} e^{-t/3}$$