# **General Response of Second Order System**

Eytan Modiano

# **Learning Objectives**

- Learn to analyze a general second order system and to obtain the general solution
  - Identify the over-damped, under-damped, and critically damped solutions
  - Convert complex solution to real solution
  - Suspended "mass-spring-damper" equivalent system

# Second order RC circuit

- System with 2 state variables
  - Described by two coupled first-order differential equations



- States
  - Voltage across the capacitor  $V_1$
  - Current through the inductor i<sub>L</sub>
- What to obtain state equations of the form: x' = Ax
  - Need to obtain expression for  $dv_1/dt$  in terms of  $V_1$  and  $i_L$
  - Need to obtain expression for  $di_1/dt$  in terms of V<sub>1</sub> and  $i_L$

#### **State Differential Equations**

• For the capacitor and inductor we have,

$$\frac{dv_1}{dt} = \frac{i_c}{C}, \ \frac{di_L}{dt} = \frac{v_L}{L} = \frac{v_1}{L}$$

- Above immediately gives us an expression for di<sub>I</sub>/dt in terms of V<sub>1</sub>
- Need to obtain expression for dv<sub>1</sub>/dt in terms of V<sub>1</sub> and i<sub>L</sub>
- Write node equation at v<sub>1</sub> to obtain:

$$i_c + i_L + v_1 / R = 0$$

• Hence the state equations are given by:

(1) 
$$\frac{dv_1}{dt} = \frac{-i_L}{C} - \frac{v_1}{RC}$$
  
(2) 
$$\frac{di_L}{dt} = \frac{v_1}{L}$$

# Solving the state differential equations

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ i_L \end{bmatrix} = \begin{bmatrix} -1/RC & -1/C \\ 1/L & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ i_L \end{bmatrix}$$

$$A$$

$$[sI - A] = \begin{bmatrix} s+1/RC & 1/C \\ -1/L & s \end{bmatrix}$$

$$\phi(s) = characteristic \ eqn = det(sI - A) = 0$$

$$det(sI - A) = s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$$

solve quadratic equation to obtain:

Slide 5

$$s_{1} = \frac{-\frac{1}{RC} + \sqrt{\left(\frac{1}{RC}\right)^{2} - \frac{4}{LC}}}{2}, \quad s_{2} = \frac{-\frac{1}{RC} - \sqrt{\left(\frac{1}{RC}\right)^{2} - \frac{4}{LC}}}{2}$$

# The natural response of RLC circuits

#### • Three cases

Over-damped response:

Characteristic equation has two (negative) real roots

Response is a decaying exponential

No oscillation (hence the name over-damped, because the resistor damps out the frequency of oscillation)

Under-damped response:

Characteristic equation has two distinct complex roots Response is a decaying exponential that oscillates

Critically-damped response:

Characteristic equation has two read, distinct roots Solution no longer a pure exponential Response is on the verge of oscillation

 Analogy to oscillating suspended spring-mass-damper system; where energy is stored in the spring and mass

# **Over-damped response**

$$\frac{1}{\left(RC\right)^2} > \frac{4}{LC}$$

- Characteristic equation has two distinct real roots; s<sub>1</sub>, s<sub>2</sub>
  - Both  $s_1 > 0$ ,  $s_2 > 0$  (why?)
- Solution of the form:

$$v_1 = aE_1^{s_1}e^{s_1t} + bE_1^{s_2}e^{s_2t}$$
  

$$i_l = aE_2^{s_1}e^{s_1t} + bE_2^{s_2}e^{s_2t}$$
  
Over-damped response  

$$\int_{15}^{15}e^{s_1t}e^{s_1t} + bE_2^{s_2}e^{s_2t} = 0$$

# **Critically-damped response**

$$\frac{1}{\left(RC\right)^2} = \frac{4}{LC}$$

- Characteristic equation has two real repeated roots; s<sub>1</sub>, s<sub>2</sub>
  - Both  $s_1 = s_2 = -1/2RC$
- Solution no longer a pure exponential
  - "defective eigen-values" ⇒ only one independent eigen-vector Cannot solve for (two) initial conditions on inductor and capacity
- However, solution can still be found and is of the form:

$$v_1 = a_1 e^{st} + b_1 t e^{st}$$
$$i_l = a_2 e^{s_1 t} + b_2 t e^{s_2 t}$$

• See chapter 5 of Edwards and Penny; or 18.03 notes

#### Critically-damped response, cont.

$$v_1 = ae^{-t/2RC} + bte^{-t/2RC}$$

- Response is on the verge of oscillation
- Known as "critically damped"



### **Under-damped response**

$$\frac{1}{\left(RC\right)^2} < \frac{4}{LC}$$

• Characteristic equation has two distinct complex roots; s<sub>1</sub>, s<sub>2</sub>

$$s_1 = -\alpha + j\beta, \ s_2 = s_1^* = -\alpha - j\beta$$
  
 $\alpha = 1/2RC, \ \beta = \frac{\sqrt{1/(RC)^2 - 4/LC}}{2}$ 

- Two distinct eigenvectors,  $V_1$  and  $V_1^*$ 
  - Complex eigenvalues and eigenvectors
- Solution of the form:

$$v_1 = a_1 e^{s_1 t} + a_1^* e^{s_2 t}$$
$$i_l = a_2 e^{s_1 t} + a_2^* e^{s_2 t}$$

#### Under-damped response, cont.

$$v_1 = a_1 e^{(-\alpha + j\beta)t} + a_1^* e^{(-\alpha - j\beta)t}$$

Euler's formula:  $e^{\alpha + j\beta} = e^{\alpha}(\cos(\beta) + j\sin(\beta))$  $\Rightarrow v_1 = a_1 e^{-\alpha t} (\cos(\beta t) + j \sin(\beta t)) + a_1^* e^{-\alpha t} (\cos(-\beta t) + j \sin(-\beta t))$  $\cos(-\beta) = \cos(\beta), \ \sin(-\beta) = -\sin(\beta)$  $\Rightarrow v_1 = 2e^{-\alpha t} \left[ \operatorname{Re}[a_1] \cos(\beta t) - \operatorname{Im}[a_1] \sin(\beta t) \right]$ 



**Decaying oscillation between** 

# Example of over-damped response (complex eigen-values and eigen-vectors)

- Consider the same circuit with the following values
  - C=1/2 F, L=1/5 H, R=1
  - Initial conditions,  $V_1(0)=1v$ ,  $i_c(0)=1A$

$$\frac{d}{dt}\begin{bmatrix}v_1\\i_L\end{bmatrix} = \begin{bmatrix}-1/RC & -1/C\\1/L & 0\end{bmatrix}\begin{bmatrix}v_1\\i_L\end{bmatrix} = \begin{bmatrix}-2 & -2\\5 & 0\end{bmatrix}\begin{bmatrix}v_1\\i_L\end{bmatrix}$$
$$A$$
$$[sI - A] = \begin{bmatrix}s+2 & 2\\-5 & s\end{bmatrix}$$

$$\begin{bmatrix} s+2 & 2 \\ -5 & s \end{bmatrix} = s^{2} + 2s + 10 = 0$$
  
$$s_{1} = -1 + 3j, \quad s_{2} = -1 - 3j$$

• Now find the eigen-vectors

$$s_{1} = -1 + 3j \implies sI - A = \begin{bmatrix} 1 + 3j & 2 \\ -5 & -1 + 3j \end{bmatrix} \begin{bmatrix} V_{1}^{s1} \\ V_{2}^{s1} \end{bmatrix} = 0$$
$$\implies -5V_{1}^{s1} + (-1 + 3j)V_{2}^{s1} = 0$$
$$\implies V_{1}^{s1} = \begin{bmatrix} -1/5 + 3/5j \end{bmatrix} V_{2}^{s1}$$
$$\implies V_{1}^{s1} = \begin{bmatrix} V_{1}^{s1} \\ V_{2}^{s1} \end{bmatrix} = \begin{bmatrix} -1/5 + 3/5j \\ 1 \end{bmatrix}$$

$$s_{2} = s_{1}^{*} = -1 - 3j$$

$$V^{s2} = \begin{bmatrix} V_{1}^{s1} \\ V_{2}^{s1} \end{bmatrix}^{*} = \begin{bmatrix} -1/5 + 3/5j \\ 1 \end{bmatrix}^{*} = \begin{bmatrix} -1/5 - 3/5j \\ 1 \end{bmatrix}^{*}$$

# The total solution

$$V_1(t) = a_1(-1/5 + 3/5j)e^{(-1+3j)t} + a_2(-1/513/5j)e^{(-1-3j)t}$$
$$i_c(t) = a_1(1)e^{(-1+3j)t} + a_2(1)e^{(-1-3j)t}$$

Use 
$$V_1(0) = 1$$
,  $i_c(0) = 1$  to obtain:  $a_1 = 1/2 - j$ ,  $a_2 = 1/2 + j$   
 $V_1(t) = (1/2 + 1/2j)e^{(-1+3j)t} + (1/2 - 1/2j)e^{(-1-3j)t}$   
 $i_c(t) = (1/2 - j)e^{(-1+3j)t} + (1/2 + j)e^{(-1-3j)t}$ 

to express as real values use,

Euler's formula: 
$$e^{\alpha + j\beta} = e^{\alpha} (\cos(\beta) + j\sin(\beta))$$
  
some algebra  $\Rightarrow \begin{cases} V_1(t) = [\cos(3t) - \sin(3t)]e^{-t} \\ i_c(t) = [\cos(3t) + 2\sin(3t)]e^{-t} \end{cases}$ 

# 2nd order mechanical systems mass-spring-damper



- Force exerted by spring is proportional to the displacement (x) of the mass from its equilibrium position and acts in the opposite direction of the displacement
  - **Fs = -kx**
  - Fs < 0 if x > 0 (l.e., spring stretched)
  - Fs > 0 if x < 0 (spring compressed)</li>
- Damper force is proportional to velocity (v = x') and acts in opposite direction to motion
  - Fr = -bv = -bx'

### Spring-mass-damper system

- If Fr and Fs are the only forces acting on the mass m, then
  - F = ma where a = dv/dt = x''
  - F = m x'' = Fs + Fr = -kx bx'
- So the differential equation for the mass position, x, is given by:

mx'' + bx' + kx = 0

- This is a second order system
- Guessing  $x = Ae^{st}$  for the solution we get,

 $mAs^2e^{st} + bAse^{st} + kAe^{st} = 0$ 

The characteristic equation is thus

$$s^{2} + (b/m)s + k/m = 0$$

$$s_1 = \frac{(-b/m) + \sqrt{(b/m)^2 - 4(k/m)}}{2}, \quad s_2 = \frac{(-b/m) - \sqrt{(b/m)^2 - 4(k/m)}}{2}$$

# **Response of Spring-mass-damper system**

 $x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ 

where  $A_1$  and  $A_2$  are chosen to satisfy initial conditions

- Note that for this system the state can be described by
  - Position, x(t), Velocity, x'(t)
  - Hence, the initial conditions would be x(0) and x'(0)
- Note similarity to RLC circuit response:

$$s_{1} = \frac{\frac{-1}{RC} + \sqrt{\left(\frac{1}{RC}\right)^{2} - \frac{4}{LC}}}{2}, \quad s_{2} = \frac{\frac{-1}{RC} - \sqrt{\left(\frac{1}{RC}\right)^{2} - \frac{4}{LC}}}{2}$$

- Notice relationship between 1/R in RLC circuit and damping factor (b) in spring-mass-damper system
  - $B \sim 0 \Rightarrow$  un-damped system  $\Rightarrow$  oscillation
  - This is the basis for the terminology, over-damped, under-damped, etc.
  - Over-damped system ⇒ damping factor is large and system does not oscillate (just exponential decay)