

Unified Quiz 3S November 5, 2004

Two 8 $\frac{1}{2}$ " x 11" sheets (both sides) of notes allowed.

Calculators are not needed, and may not be used.


No books allowed.

- Put the last 4 digits of your ID on each page of the exam.
- Read all questions carefully.
- Do all work for each problem on the two pages provided.
- Show intermediate results.
- Explain your work --- don't just write equations. Any problem (except multiple choice) without an explanation can receive no better than a "B" grade.
- Partial credit will be given, but only when the intermediate results and explanations are clear.
- Please be neat. It will be easier to identify correct or partially correct responses when the response is neat.
- Show appropriate units with your final answers.
- Box your final answers.

Exam Scoring

#1 (12.5%)	
#2 (12.5%)	
#3 (25%)	
#4 (25%)	
#5 (25%)	
Total	

PROBLEM #1 (12.5%)

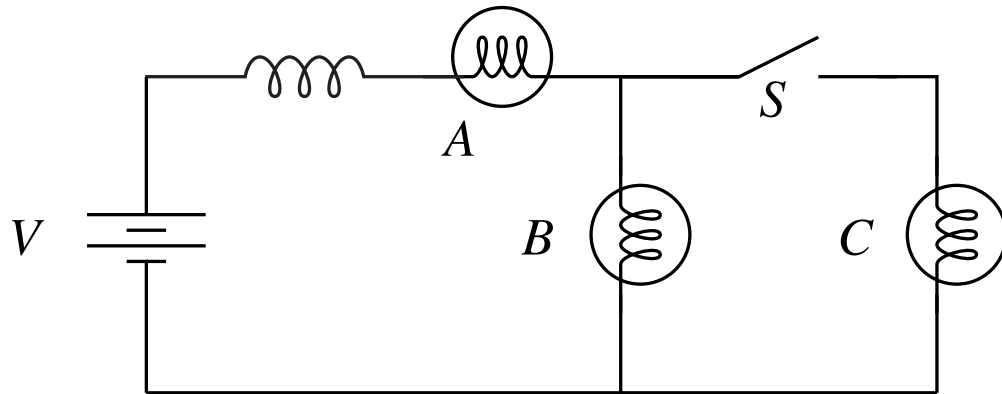


Consider the circuit above with three identical light bulbs, an inductor, and a switch. Initially, the switch is open, and has been open for a long time. When the switch is closed, what happens to the intensity of each bulb?

1. Immediately after the switch is closed, the intensity of bulb A
increases decreases stays the same
2. Immediately after the switch is closed, the intensity of bulb B
increases decreases stays the same
3. After the switch has been closed for a long time, the intensity of bulb A is
greater than less than the same as
the intensity of bulb A before the switch is closed.
4. After the switch has been closed for a long time, the intensity of bulb B is
greater than less than the same as
the intensity of bulb B before the switch is closed.

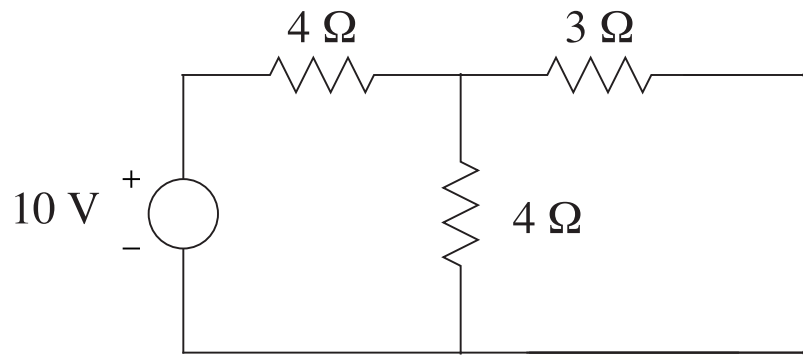PROBLEM #2 (12.5%)

Find the Thevinin equivalent for the circuit below:




Unified Quiz 3S
November 5, 2004

ID number _____

PROBLEM #2 (continued)

PROBLEM #3 (25%)

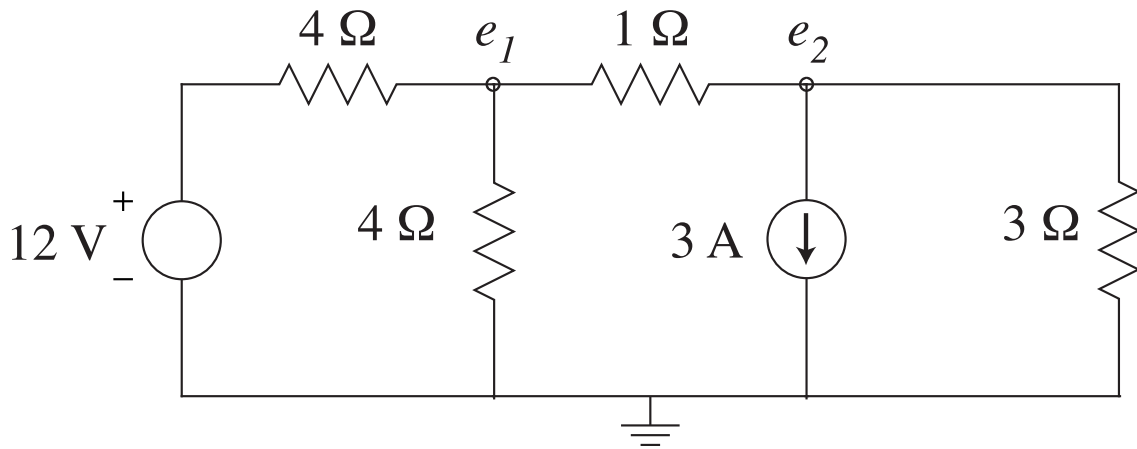

For the circuit above, calculate:

- The node potentials e_1 and e_2 .
- The current in the 3 Ω resistor. Make sure that you specify the direction of the current.

Unified Quiz 3S
November 5, 2004

ID number _____

PROBLEM #3 (continued)

Unified Quiz 3S
November 5, 2004

ID number _____

PROBLEM #4 (continued)

PROBLEM #4 (25%)

A circuit has dynamics described by the state-space equation

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -3 & -1 \\ 2 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

Find $v_1(t)$ and $i_2(t)$ for the initial conditions

$$v_1(0) = 1 \text{ V}$$

$$i_2(0) = 4 \text{ A}$$

Unified Quiz 3S
November 5, 2004

ID number _____


PROBLEM #4 (continued)

Unified Quiz 3S
November 5, 2004

ID number _____

PROBLEM #4 (continued)

PROBLEM #5 (25%)

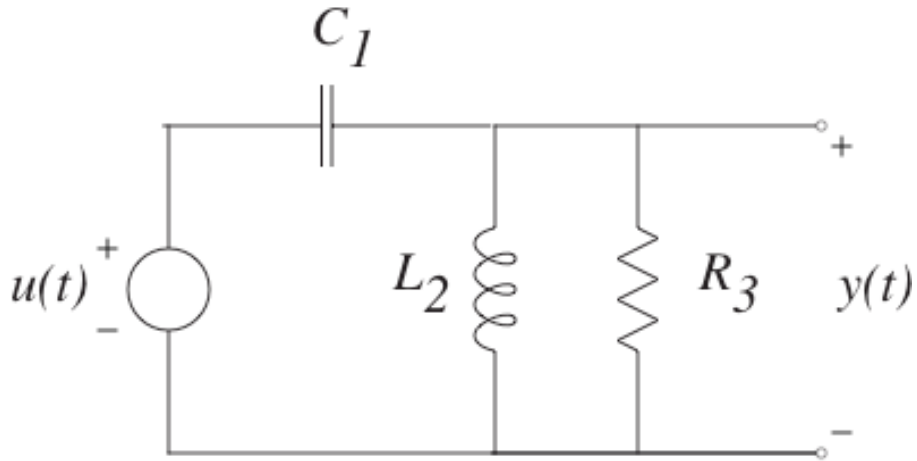

Find the differential equations that describe the input-output behavior of the circuit above, in state-space form,

$$\dot{\underline{x}}(t) = A\underline{x}(t) + Bu(t)$$

$$y(t) = C\underline{x}(t) + Du(t)$$

That is, you must define the state vector \underline{x} , and then derive the matrices A , B , C , and D . The component values are not given, so your answer should be in symbolic form.

Unified Quiz 3S
November 5, 2004

ID number _____

PROBLEM #5 (continued)

Unified Quiz 3S
November 5, 2004

ID number _____

PROBLEM #5 (continued)