

Assigned: Friday, November 9

Due: Friday, November 16

Problem S5.1: Look-ahead to Lectures 11 and 12 (10 points)

Reference: Prof. Hall's linear algebra primer, available on the Signals & Systems webpage; your 18.03 notes.

- (a) Consider the differential equation


$$\frac{d^2y}{dt^2} + y = 0.$$

- (i) Write this differential equation as a system of first-order differential equations in the form

$$\vec{x}' = A\vec{x}.$$

- (ii) Compute the eigenvalues and eigenvectors of your resulting system matrix A .
 (iii) To determine the response of the system, how many and what initial conditions must be specified?
 (iv) What will be the general form of the system response $y(t)$?

- (b) For the following circuit:

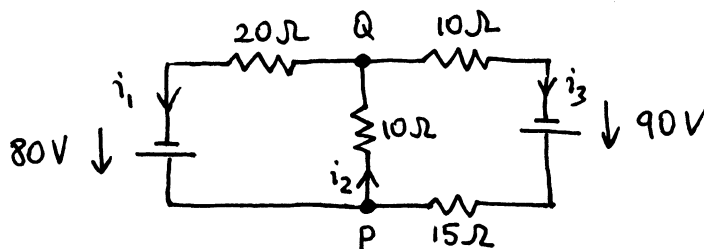

currents i_1, i_2, i_3

- (i) Apply Kirchoff's current law to Node P and Node Q (using the notation and current directions given in the figure).
 (ii) Apply Kirchoff's voltage law to the left loop and the right loop.
 (iii) Write your four equations as a matrix system of the form $A\vec{x} = \vec{b}$, where the unknowns are the currents i_1, i_2 , and i_3 .
 (iv) Apply Gauss elimination to your matrix system to convert it to upper triangular form. Then use back substitution to determine the values of the currents.