

a) $P_1 = 1 \times 10^6 \text{ Pa}$, $T_1 = 200 \text{ K}$, $C_1 = 50 \frac{\text{m}}{\text{s}}$ $\dot{m} = 100 \text{ kg/s}$
 $P_2 = 5 \times 10^6 \text{ Pa}$ via A ρ -s ADiab. process $\therefore P V^\gamma = \text{const.}$
 $C_2 = 50 \frac{\text{m}}{\text{s}}$ $\therefore q = 0$

$$P_1 V_1 = RT_1 \Rightarrow V_1 = 0.052 \frac{\text{m}^3}{\text{kg}} \quad (R = 260 \text{ J/kg}\cdot\text{K})$$

$$P_1 V_1^\gamma = P_2 V_2^\gamma, \quad \gamma = \frac{C_p}{C_v} = 1.1 \Rightarrow V_2 = 0.012 \frac{\text{m}^3}{\text{kg}}$$

SFEE \rightarrow $W_s = h_2 - h_1 + \frac{C_2^2}{2} - \frac{C_1^2}{2}$
 or $W = u_2 - u_1 + \frac{C_2^2}{2} - \frac{C_1^2}{2}$

$$W_f = R(T_2 - T_1) = W - W_s$$

so

$$W = - \left[C_v(T_2 - T_1) + \frac{C_2^2}{2} - \frac{C_1^2}{2} \right], \quad \frac{P_2 V_2}{R} = T_2 = 230.8 \text{ K}$$

$$W = -78.2 \frac{\text{kJ}}{\text{kg}}$$

or

$$\dot{W} = \dot{m} W = -7.8 \text{ MW}$$

$$W_f = 260(230.8 - 200) = 8 \frac{\text{kJ}}{\text{kg}}$$

or

$$\dot{W}_f = \dot{m} W_f = 0.8 \text{ MW}$$

$$W_s = - \left[C_p(T_2 - T_1) + \frac{C_2^2}{2} - \frac{C_1^2}{2} \right] = W - W_f$$

$$W_s = -86.2 \frac{\text{kJ}}{\text{kg}} \quad \text{or} \quad \dot{W}_s = -8.62 \text{ MW}$$

b) $C_2 = 50 \text{ m/s}$, $T_2 = 230.8 \text{ K}$, $P_2 = 5 \times 10^6 \text{ Pa}$ 2 of 2
 $C_3 = 100 \text{ m/s}$, $T_3 = ?$, $P_3 = 5 \times 10^6 \text{ Pa}$ $q_{in} = 1300 \text{ kJ/kg}$

$$q - \cancel{W_s} = C_p (T_3 - T_2) + \frac{C_3^2}{2} - \frac{C_2^2}{2} \quad (\text{NO SHAFT WORK BUT CAN STILL BE FLOW WORK})$$

$$1300 \times 10^3 = 2800 (T_3 - 230.8) + \frac{100^2}{2} - \frac{50^2}{2}$$

$$T_3 = 693.7, \quad v_3 = \frac{RT_3}{P_3} = \frac{260 (693.7)}{5 \times 10^6} = 0.036 \frac{\text{m}^3}{\text{kg}}$$

$$\boxed{W_s = 0} \quad W_f = R(T_3 - T_2)$$

$$\boxed{W_f = 260 (693.7 - 230.8) = 120 \frac{\text{kJ}}{\text{kg}}}$$

or

$$\dot{W}_f = 1.2 \text{ MW}$$

c) $\boxed{W_{s, \text{TURBINE}} = -W_{s, \text{PUMP}} = 86.2 \frac{\text{kJ}}{\text{kg}}}$ or $\dot{W}_s = 8.6 \text{ MW}$

$$\cancel{q} - W_s = C_p (T_4 - T_3) + \frac{C_4^2}{2} - \frac{C_3^2}{2}$$

$$-86.2 \times 10^3 = 2800 (T_4 - 693.7) + \frac{120^2}{2} - \frac{100^2}{2}$$

$$T_4 = 662 \text{ K}$$

$$W_f = R(T_4 - T_3) = 260 (662 - 693.7) = -8.2 \text{ kJ/kg}$$

$$\boxed{W_f = -8.2 \frac{\text{kJ}}{\text{kg}} \quad \text{or} \quad \dot{W}_f = -0.82 \text{ MW}}$$

T12 SOLUTIONS (WATZ)

GIVEN • $C_{pc} = 1000 \text{ J/kg-K}$

• $C_{pt} = 1200 \text{ J/kg-K}$

• $\dot{m}_i = 30 \text{ kg/s}$

• STAGNATION TEMPERATURE & PRESSURE PROFILES

a) POWER TO DRIVE HIGH PRESSURE COMPRESSOR (2C-3)

STEADY FLOW ENERGY EQN: $\dot{Q} - \dot{W}_s = \dot{m}_i (h_{T_{3c}} - h_{T_{2c}})$

$T_{T_{2c}} = 367 \text{ K}$, $T_{T_{3c}} = 810 \text{ K}$ $\dot{W}_s = \dot{m}_i 1000 [367 - 810] = \underline{\underline{-13.3 \text{ MW}}}$

b) HEAT TRANSFER IN COMBUSTOR

$\dot{Q} - \dot{W}_s = \dot{m}_i \Delta h_T = 30 [C_{pt} T_{T_4} - C_{pc} T_{T_3}] = 30 [1200 \cdot 1532 - 1000 \cdot 810]$

$\dot{Q} = \underline{\underline{30.9 \text{ MW}}}$

c) $\beta = \frac{\dot{m}_B}{\dot{m}_c}$, THE FAN IS DRIVEN BY THE LOW PRESSURE TURBINE
ASSUMING BOTH ARE ADIABATIC GIVES:

all mass flow through fan?

$(\dot{m}_c + \dot{m}_B) (C_{pc} T_{T_{2.4}} - C_{pc} T_{T_2}) = \dot{m}_c (C_{pt} T_{T_{5.4}} - C_{pt} T_{T_{5.5}})$


~~$\dot{m}_c (\beta + 1) (C_{pc} T_{T_{2.4}} - C_{pc} T_{T_2}) = \dot{m}_c (C_{pt} T_{T_{5.4}} - C_{pt} T_{T_{5.5}})$~~

$\dot{m}_c (\beta + 1) (C_{pc} T_{T_{2.4}} - C_{pc} T_{T_2}) = \dot{m}_c (C_{pt} T_{T_{5.4}} - C_{pt} T_{T_{5.5}})$

$\beta = \frac{C_{pt}}{C_{pc}} \frac{(T_{T_{5.4}} - T_{T_{5.5}})}{(T_{T_{2.4}} - T_{T_2})} - 1 = \frac{1200}{1000} \frac{(1032 - 865)}{(367 - 300)} - 1 = \underline{\underline{2}}$

d) POWER TO DRIVE FAN = $\dot{m}_c [C_{pt} T_{T_{5.5}} - C_{pt} T_{T_{5.4}}]$
 $= \underline{\underline{-6 \text{ MW}}}$

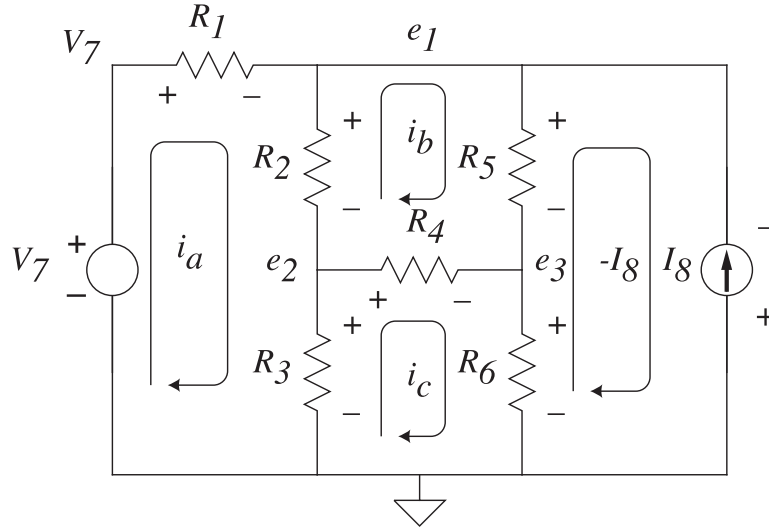Problem S5 (Signals and Systems) SOLUTION



The component values are:

$$\begin{aligned}
 R_1 &= 1 \Omega \\
 R_2 &= 1 \Omega \\
 R_3 &= 4 \Omega \\
 R_4 &= 6 \Omega \\
 R_5 &= 1 \Omega \\
 R_6 &= 6 \Omega \\
 I_8 &= 3 \text{ A} \\
 V_7 &= 5 \text{ V}
 \end{aligned}$$

Draw the loop currents as shown above. Note that there are three unknown currents, i_a , i_b , and i_c . Applying KVL around each loop results in the equations

$$\begin{aligned}
 i_a : & \quad (R_1 + R_2 + R_3)i_a & - R_2i_b & - R_3i_c = V_7 \\
 i_b : & \quad -R_2i_a + (R_2 + R_4 + R_5)i_b & - R_4i_c = -R_5I_8 \\
 i_c : & \quad -R_3i_a & - R_4i_b + (R_3 + R_4 + R_6)i_c = -R_6I_8
 \end{aligned}$$

Plugging in component values (and ignoring units for now), we have

$$\begin{aligned}
 6 i_a - i_b - 4 i_c &= 5 \\
 -i_a + 8i_b - 6 i_c &= -3 \\
 -4 i_a - 6i_b + 16 i_c &= -18
 \end{aligned}$$

Solving by row reduction, or Matlab, gives

$$\begin{aligned}i_a &= -\frac{43}{45} \text{ A} \\i_b &= -\frac{19}{9} \text{ A} \\i_c &= -\frac{97}{45} \text{ A}\end{aligned}$$

We then obtain


$$\begin{aligned}i_1 &= i_a = -\frac{43}{45} \text{ A} \\v_1 &= i_1 R_1 = -\frac{43}{45} \text{ V} \\i_2 &= i_a - i_b = \frac{52}{45} \text{ A} \\v_2 &= i_2 R_2 = \frac{52}{45} \text{ V} \\i_3 &= i_a - i_c = \frac{6}{5} \text{ A} \\v_3 &= i_3 R_3 = \frac{24}{5} \text{ V} \\i_4 &= i_c - i_b = -\frac{2}{45} \text{ A} \\v_4 &= i_4 R_4 = -\frac{4}{15} \text{ V} \\i_5 &= i_b + I_8 = \frac{8}{9} \text{ A} \\v_5 &= i_5 R_5 = \frac{8}{9} \text{ V} \\i_6 &= i_c + I_8 = \frac{38}{45} \text{ A} \\v_6 &= i_6 R_6 = \frac{76}{15} \text{ V} \\i_7 &= -i_a = \frac{43}{45} \text{ A} \\v_7 &= V_7 = 5 \text{ V} \\i_8 &= I_8 = 3 \text{ A} \\v_8 &= -v_5 - v_6 = -\frac{268}{45} \text{ V}\end{aligned}$$

Problem S6 (Signals and Systems) SOLUTION

Find the Thevinin and Norton equivalent circuits for the circuits below. Hint: Add a test current to the terminals, and then determine the voltage at the terminals as a function of the test current. You should find that the terminal voltage can be expressed as

$$v = V_T + R_T I_{\text{test}}$$

1.

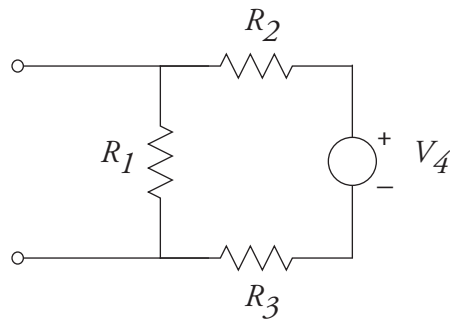

where

$$R_1 = 2 \Omega, \quad R_2 = 4 \Omega, \quad R_3 = 3 \Omega, \quad V_4 = 12 \text{ V}$$


SOLUTION: The circuit is a voltage divider, so the open-circuit voltage is

$$V_{OC} = V_T = \frac{R_1}{R_1 + R_2 + R_3} V_4 = \frac{8}{3} \text{ V}$$

The Thevinin resistance can be found by looking at the equivalent resistance at the terminals, setting all the sources to zero. Since a voltage source of strength zero is a short circuit, we have that

$$R_T = R_1 || (R_2 + R_3) = 2 \Omega || 7 \Omega = \frac{2 \cdot 7}{2 + 7} \Omega = \frac{14}{9} \Omega$$


2.

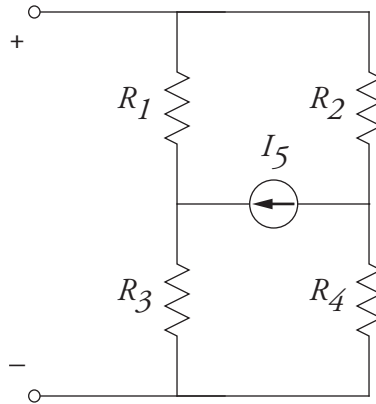

where

$$R_1 = 1 \Omega, \quad R_2 = 3 \Omega, \quad R_3 = 3 \Omega, \quad R_4 = 1 \Omega, \quad I_5 = 8 \text{ A}$$

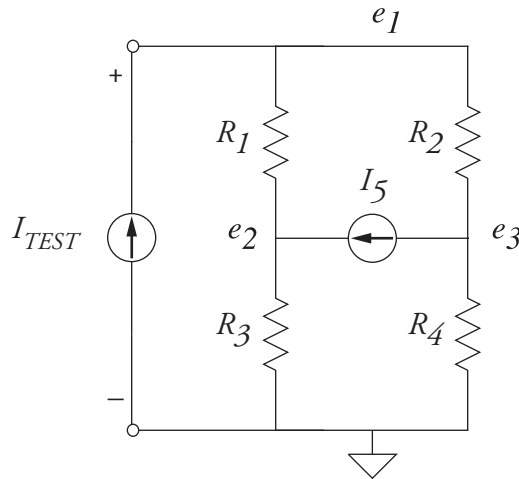SOLUTION: There are several ways to proceed. The most direct is to add a test current, and use the node method to solve. Use the following analysis circuit:



Applying KCL at each node yields the node equations:-G_2

$$\begin{aligned} (G_1 + G_2)e_1 - G_1e_2 - G_2e_3 &= I_{TEST} \\ -G_1e_1 + (G_1 + G_3)e_2 &= I_5 \\ -G_2e_1 + (G_2 + G_4)e_3 &= -I_5 \end{aligned}$$

Plugging in values,

$$\begin{aligned} \frac{4}{3}e_1 - e_2 - \frac{1}{3}e_3 &= I_{TEST} \\ -e_1 + \frac{4}{3}e_2 &= 8 \\ -\frac{1}{3}e_1 + \frac{4}{3}e_3 &= -8 \end{aligned}$$

Solving by row reduction or Matlab yields

$$e_1 = 2I_{TEST} + 8$$

Therefore,

$$V_T = 8 \text{ V}$$

$$R_T = 2 \Omega$$