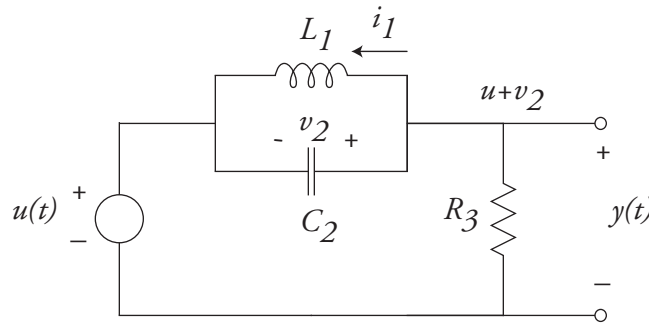


**Problem S13 (Signals and Systems) SOLUTION**

It's easiest to use the node method for this problem. Label the states  $i_1$ , and  $v_2$ , and the nodes as below:



The state vector is defined as

$$\underline{x} = \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

So we need to find  $di_1/dt$ ,  $dv_2/dt$ . Start with the inductor, with

$$\frac{di_1}{dt} = \frac{v_1}{L_1} = \frac{v_2}{L_1}$$

since  $v_2 = v_1$ . For the capacitor,

$$\frac{dv_2}{dt} = \frac{i_2}{C_2}$$

To find  $i_2$ , apply KCL at the  $u + v_2$  node:

$$i_1 + i_2 + \frac{u + v_2}{R_3} = 0$$

Solving for  $i_2$ ,

$$i_2 = -i_1 - \frac{u + v_2}{R_3}$$

Therefore,


$$\frac{dv_2}{dt} = -\frac{i_1}{C_2} - \frac{u + v_2}{R_3 C_2}$$

In state-space form,

$$\begin{aligned} \frac{d}{dt} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} &= \begin{bmatrix} 0 & 1/L_1 \\ -1/C_2 & -1/R_3 C_2 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 0 \\ -1/R_3 C_2 \end{bmatrix} u \\ y &= \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} + [1]u \end{aligned}$$

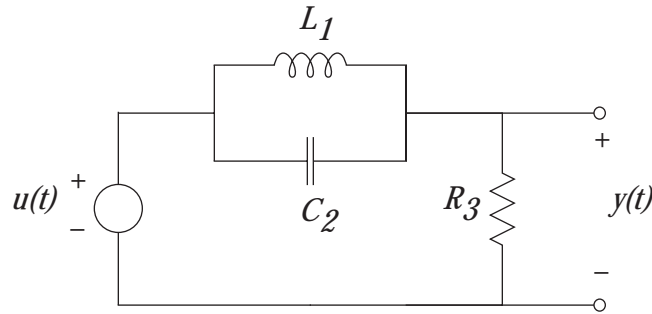Problem S14 (Signals and Systems) SOLUTION

Consider the RLC circuit of Problem S13, shown below:



1. From S13, we found a state-space description to be

$$\frac{d}{dt} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 1/L_1 \\ -1/C_2 & -1/R_3 C_2 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 0 \\ -1/R_3 C_2 \end{bmatrix} u$$

$$y = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} + [1]u$$

Therefore,

$$sI - A = \begin{bmatrix} s & -1/L_1 \\ 1/C_2 & s + 1/R_3 C_2 \end{bmatrix}$$

Inverting,

$$(sI - A)^{-1} = \frac{1}{s^2 + s/R_3 C_2 + 1/L_1 C_2} \begin{bmatrix} s + 1/R_3 C_2 & +1/L_1 \\ -1/C_2 & s \end{bmatrix}$$

Multiplying by  $C$ ,

$$C(sI - A)^{-1} = \frac{1}{s^2 + s/R_3 C_2 + 1/L_1 C_2} \begin{bmatrix} -1/C_2 & s \end{bmatrix}$$

Multiplying by  $B$ ,

$$C(sI - A)^{-1}B = \frac{-s/R_3 C_2}{s^2 + s/R_3 C_2 + 1/L_1 C_2}$$

Adding  $D$ ,

$$G(s) = C(sI - A)^{-1}B + D = \frac{-s/R_3 C_2}{s^2 + s/R_3 C_2 + 1/L_1 C_2} + 1 = \frac{s^2 + 1/L_1 C_2}{s^2 + s/R_3 C_2 + 1/L_1 C_2}$$

2. To find the transfer function using impedance methods, note that the inductor and capacitor have parallel impedance

$$Z_{LC} = Z_L || Z_C = \frac{Z_L Z_C}{Z_L + Z_C} = \frac{Ls \left(\frac{1}{Cs}\right)}{Ls + \frac{1}{Cs}} = \frac{Ls}{LCs^2 + 1}$$

(Note that I have dropped the numerical subscripts, since no confusion can arise.) Then the circuit is a voltage divider, with transfer function

$$G(s) = \frac{R}{Z_{LC} + R} = \frac{R}{\frac{Ls}{LCs^2+1} + R} = \frac{R(LCs^2 + 1)}{R(LCs^2 + 1) + Ls} = \frac{RLCs^2 + R}{RLCs^2 + Ls + R}$$

Dividing numerator and denominator by  $RLC$  gives

$$G(s) = \frac{s^2 + 1/L_1C_2}{s^2 + s/R_3C_2 + 1/L_1C_2}$$

as in part (1).

3. For component values

$$L_1 = 1 \text{ H}, \quad C_2 = 0.25 \text{ F}, \quad R_3 = 10 \text{ } \Omega$$


the transfer function is

$$G(s) = \frac{s^2 + 4}{s^2 + 0.4s + 4}$$

Therefore,

$$G(j\omega) = \frac{-\omega^2 + 4}{-\omega^2 + 0.4j\omega + 4}$$

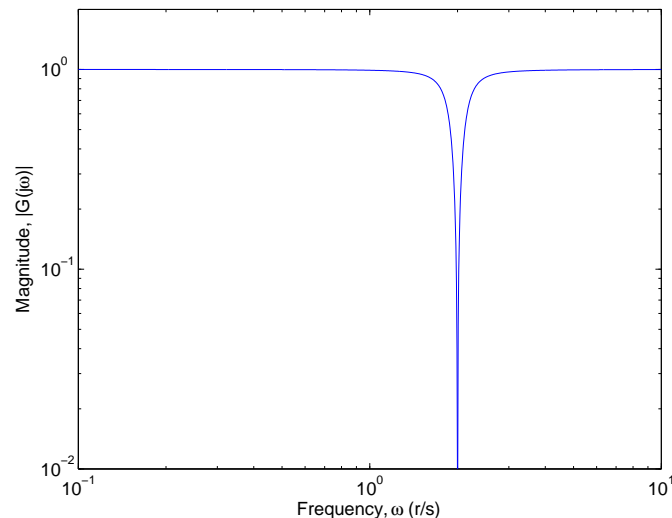You are then to plot the magnitude of this function. This could be done in a spread sheet, by calculating the transfer function frequency by frequency, or by using the Matlab command `bode`. I used Matlab. (Most of you will probably use a spreadsheet, since we haven't used Matlab this term.) My plot is shown below:



Note that I've plotted the magnitude on a log-log scale. (This is how experts always plot transfer functions.) Most of you will probably plot on a linear-linear scale — that's OK. On either scale, it's clear why this is a “notch filter” — graphically, there's a notch in the plot which is otherwise a straight line.

**Problem S15 (Signals and Systems) SOLUTION**

In Problem S14, we found that

$$G(s) = \frac{s^2 + 1/L_1C_2}{s^2 + s/R_3C_2 + 1/L_1C_2}$$

For component values

$$L_1 = 1 \text{ H}, \quad C_2 = 0.25 \text{ F}, \quad R_3 = 10 \text{ } \Omega$$

the transfer function is

$$G(s) = \frac{s^2 + 4}{s^2 + 0.4s + 4}$$

1. For the input

$$u(t) = \cos t$$

the complex frequency is  $s = j\omega$ , where  $\omega = 1$ , and the complex amplitude is  $U = 1$ . Therefore,

$$Y = G(s)U = G(1j) \cdot 1 \approx 0.9825 - 0.1310j$$

The real and imaginary parts of the amplitude correspond to the cosine and (minus) sine amplitudes. Therefore,

$$u(t) \approx 0.9825 \cos t + 0.1310 \sin t$$

2. For the input

$$u(t) = 3 \sin 2t$$

the complex frequency is  $s = j\omega$ , where  $\omega = 2$ , and the complex amplitude is  $U = 3$ . Therefore,

$$Y = G(s)U = G(2j) \cdot 3 = 0$$

The amplitude of  $y$  is identically zero, because the frequency of the input signal is at exactly the notch frequency. Therefore,

$$u(t) = 0$$

3. For the input

$$u(t) = 2 \cos 4t + \sin 4t$$

the complex frequency is  $s = j\omega$ , where  $\omega = 4$ , and the complex amplitude is  $U = 2 - j$ . Therefore,


$$Y = G(s)U = G(4j) \cdot (2 - j) \approx (0.9825 + 0.1310j)(2 - j) \approx 2.0961 - 0.7205j$$

Finally,

$$u(t) \approx 2.0961 \cos 4t + 0.7205 \sin 4t$$

## Problem 4

GIVEN:

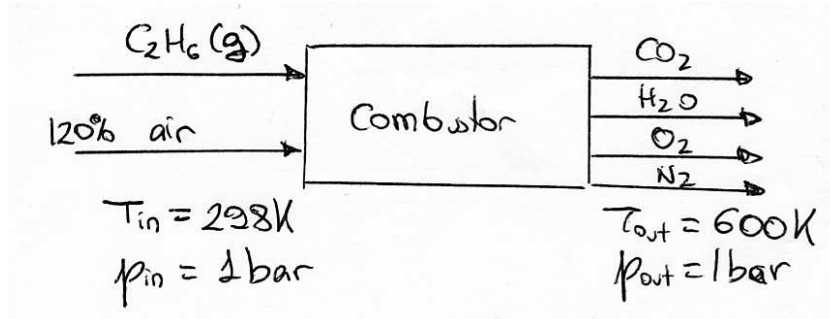


ASSUMPTIONS: • Steady flow.  
• Neglect kinetic and potential energy effects.


CONCEPTS: • Stoichiometry.  
• First Law in CV form.  
• Enthalpy of formation.

SOLUTION:

a) The stoichiometric reaction is:

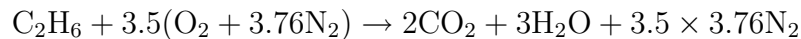

With 20% excess air:

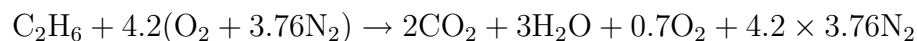

Then, the air/fuel ratio is:

$$\frac{1}{f} = \frac{m_{\text{air}}}{m_{\text{fuel}}} = \frac{4.2(M_{\text{O}_2} + 3.76M_{\text{N}_2})}{M_{\text{C}_2\text{H}_6}} = 19.22$$

b) Per kmol of fuel, the products will be:

- 2 kmol of  $\text{CO}_2$ .
- 3 kmol of  $\text{H}_2\text{O}$ .
- 0.7 kmol of  $\text{O}_2$ .
- 15.79 kmol of  $\text{N}_2$ .

c) The enthalpy of a reaction at the standard conditions is:

$$\begin{aligned} \Delta \bar{h}_{\text{reaction}} &= 2\bar{h}_{f,\text{CO}_2}^0 + 3\bar{h}_{f,\text{H}_2\text{O}}^0 + 0.7\bar{h}_{f,\text{O}_2}^0 + 15.79\bar{h}_{f,\text{N}_2}^0 - \\ &\quad - \bar{h}_{f,\text{C}_2\text{H}_6}^0 - 4.2\bar{h}_{f,\text{O}_2}^0 - 15.79\bar{h}_{f,\text{N}_2}^0 = \\ &= 2\bar{h}_{f,\text{CO}_2}^0 + 3\bar{h}_{f,\text{H}_2\text{O}}^0 - \bar{h}_{f,\text{C}_2\text{H}_6}^0 = -1.428 \times 10^6 \text{ kJ/kmol} \end{aligned}$$

d) The amount of heat transfer per kmol of fuel is obtained from the first law:

$$\bar{q} = \sum_R n_R \bar{h}_R - \sum_P n_P \bar{h}_P$$

The enthalpy of the reactants is:

$$\sum_R n_R \bar{h}_R = \bar{h}_{\text{C}_2\text{H}_6} + 4.2 \bar{h}_{\text{O}_2} + 15.79 \bar{h}_{\text{N}_2} = \bar{h}_{f,\text{C}_2\text{H}_6}^0 + 4.2 \bar{h}_{f,\text{O}_2}^0 + 15.79 \bar{h}_{f,\text{N}_2}^0 = \bar{h}_{f,\text{C}_2\text{H}_6}^0$$

The enthalpy of the products is:

$$\sum_P n_P \bar{h}_P = 2 \bar{h}_{\text{CO}_2} + 3 \bar{h}_{\text{H}_2\text{O}} + 0.7 \bar{h}_{\text{O}_2} + 15.79 \bar{h}_{\text{N}_2},$$

where

$$\begin{aligned} \bar{h}_{\text{CO}_2} &= \bar{h}_{f,\text{CO}_2}^0 + \Delta \bar{h}_{\text{CO}_2}|_{T=600 \text{ K}} \\ \bar{h}_{\text{H}_2\text{O}} &= \bar{h}_{f,\text{H}_2\text{O}}^0 + \Delta \bar{h}_{\text{H}_2\text{O}}|_{T=600 \text{ K}} \\ \bar{h}_{\text{O}_2} &= \bar{h}_{f,\text{O}_2}^0 + \Delta \bar{h}_{\text{O}_2}|_{T=600 \text{ K}} = \Delta \bar{h}_{\text{O}_2}|_{T=600 \text{ K}} \\ \bar{h}_{\text{N}_2} &= \bar{h}_{f,\text{N}_2}^0 + \Delta \bar{h}_{\text{N}_2}|_{T=600 \text{ K}} = \Delta \bar{h}_{\text{N}_2}|_{T=600 \text{ K}} \end{aligned}$$

Then:

$$\sum_P n_P \bar{h}_P = (2 \bar{h}_{f,\text{CO}_2}^0 + 3 \bar{h}_{f,\text{H}_2\text{O}}^0) + (2 \Delta \bar{h}_{\text{CO}_2} + 3 \Delta \bar{h}_{\text{H}_2\text{O}}^0 + 0.7 \Delta \bar{h}_{\text{O}_2} + 15.79 \Delta \bar{h}_{\text{N}_2})|_{T=600 \text{ K}}$$


$\Delta \bar{h}_{\text{CO}_2}$ ,  $\Delta \bar{h}_{\text{H}_2\text{O}}$ ,  $\Delta \bar{h}_{\text{O}_2}$  and  $\Delta \bar{h}_{\text{N}_2}$  are the enthalpy change between the reference state and the substance at the exit conditions ( $T_{\text{out}} = 600 \text{ K}$ ,  $p_{\text{out}} = 1 \text{ bar}$ ). These  $\Delta \bar{h}$  can be found in tables:

$$\begin{aligned} \Delta \bar{h}_{\text{CO}_2} &= 12906 \text{ kJ/kmol} \\ \Delta \bar{h}_{\text{H}_2\text{O}} &= 10499 \text{ kJ/kmol} \\ \Delta \bar{h}_{\text{O}_2} &= 9245 \text{ kJ/kmol} \\ \Delta \bar{h}_{\text{N}_2} &= 8894 \text{ kJ/kmol} \end{aligned}$$

Adding the different enthalpy of the different products and reactants, and using the definition of  $\Delta \bar{h}_{\text{reaction}}$ :

$$\bar{q} = -\Delta \bar{h}_{\text{reaction}} - 2 \Delta \bar{h}_{\text{CO}_2} - 3 \Delta \bar{h}_{\text{H}_2\text{O}}^0 - 0.7 \Delta \bar{h}_{\text{O}_2} - 15.79 \Delta \bar{h}_{\text{N}_2} = 1.224 \times 10^6 \text{ kJ/kmol}$$

TIP SOLUTIONS BY WAITZ

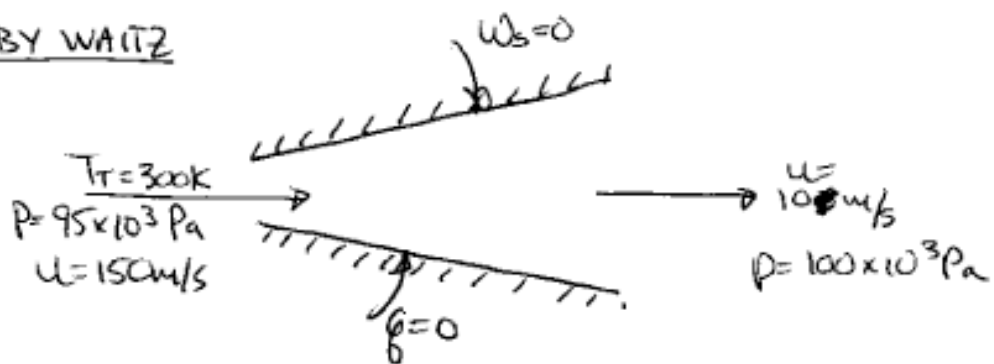

$$a) \quad q - w_s = \left( C_p T_{out} + \frac{C_{out}^2}{2} \right) - \left( C_p T_{in} + \frac{C_{in}^2}{2} \right)$$

$$C_p T_T = C_p T + \frac{C^2}{2} \quad \Rightarrow \quad \frac{1003.5 (300K)}{1003.5} - \frac{(150)^2}{2(1003.5)} = \boxed{T_{in} = 288.8K}$$

$$\frac{T_T}{T} = \left( \frac{P_T}{P} \right)^{\frac{\gamma-1}{\gamma}} \quad \left( \frac{300}{288.8} \right)^{\frac{1}{1.4}} \cdot 95 \times 10^3 = \boxed{P_{T_{in}} = 108546 Pa}$$

$$b) \quad \text{SINCE } q = 0 \text{ \& } w_s = 0, \quad h_{T_{out}} = h_{T_{in}}$$

$$\therefore \boxed{T_{T_{out}} = T_{T_{in}} = 300K} \quad T_{out} = T_{T_{out}} - \frac{C_{out}^2}{2C_p}$$

$$T_{out} = 299.95K$$

$$\left( \frac{T_{out}}{T_{in}} \right)^{\frac{\gamma}{\gamma-1}} \cdot P_{out} = P_{T_{out}}$$

$$\left( \frac{300}{299.95} \right)^{\frac{1.4}{0.4}} \cdot 100 \times 10^3 = \boxed{P_{T_{out}} = 100058 Pa}$$

$$c) \quad \Delta s = C_p \ln \left( \frac{T_2}{T_1} \right) - R \ln \left( \frac{P_2}{P_1} \right) = 1003.5 \ln \left( \frac{299.95}{288.8} \right) - 287 \ln \left( \frac{100 \times 10^3}{95 \times 10^3} \right)$$

$$\Delta s = 23.3 \frac{J}{kg \cdot K}$$

d) IF EXPANDED IN A REVERSIBLE MANNER (gas, adiabatic)

$$\left( \frac{P_{out}}{P_{in}} \right)^{\frac{\gamma-1}{\gamma}} = \left( \frac{T_{out}}{T_{in}} \right)^{\frac{\gamma-1}{\gamma}} \quad \therefore T_{out} = 288.8 \left( \frac{100}{95} \right)^{\frac{1}{1.4}} = 293.06K$$



$T_T = \text{const}$  if adiabatic & no external work

so  $T_{T, \text{out}} = 300 \text{ K}$

$$T_{T, \text{out}} = T_{\text{out}} + \frac{c^2}{2c_p} \implies c_{\text{out}} = 118 \frac{\text{m}}{\text{s}}$$

$$\left(\frac{T_{T, \text{out}}}{T_{\text{out}}}\right)^{\gamma/\gamma-1} = \frac{P_{T, \text{out}}}{P_{\text{out}}} \left(\frac{300}{293.06}\right)^{\gamma/\gamma-1} \cdot 100 \times 10^3 = 108546 \text{ Pa} \checkmark$$

$$P_{T, \text{out}} = P_{T, \text{in}} = 108546 \text{ Pa} \checkmark$$

T13 SOLUTIONS BY WAITZ

a)  $s_2 - s_1 = C_v \ln\left(\frac{T_2}{T_1}\right) + R \ln\left(\frac{V_2}{V_1}\right) = 10085 \ln\left(\frac{270}{300}\right) + 4124 \ln\left(\frac{200}{100}\right)$

$$\Delta s = 1796 \frac{\text{J}}{\text{kg}\cdot\text{K}} \quad \Delta u = q - w \quad w = -C_v \Delta T = -10085(270 - 300)$$

$$w = 32550 \frac{\text{J}}{\text{kg}}$$

b) FOR QUASI-STATIC ADIABATIC  $\frac{T_2}{T_1} = \left(\frac{V_1}{V_2}\right)^{\gamma-1} = \left(\frac{100}{200}\right)^{\left(\frac{14209}{10085} - 1\right)} = 0.753$

$$T_2 = 226 \text{ K}$$

$$w = -10085(226 - 300) = 746290 \frac{\text{J}}{\text{kg}}$$

$$\Delta s = 0$$

c) IRREVERSIBLE PROCESS:  $T_1 = 300\text{K}$ ,  $T_2 = 288\text{K}$   
 $V_1 = 0.0861 \frac{\text{m}^3}{\text{kg}}$ ,  $V_2 = 0.1722 \frac{\text{m}^3}{\text{kg}}$

$$\Delta s = C_v \ln\left(\frac{T_2}{T_1}\right) + R \ln\left(\frac{V_2}{V_1}\right) = 716.5 \ln\left(\frac{288}{300}\right) + 287 \ln\left(\frac{0.1722}{0.0861}\right)$$

$$\Delta s_{\text{irrev.}} = 169.7 \frac{\text{J}}{\text{kg}\cdot\text{K}}$$

REVERSIBLE PROCESS:  $T_1 = 300\text{K}$ ,  $T_2 = 227.4\text{K}$   
 $V_1 = 0.0861 \frac{\text{m}^3}{\text{kg}}$ ,  $V_2 = 0.1722 \frac{\text{m}^3}{\text{kg}}$

$$\Delta s_{\text{REV.}} = 716.5 \ln\left(\frac{227.4}{300}\right) + 287 \ln\left(\frac{0.1722}{0.0861}\right) = 0 \quad \checkmark$$