

2.111J/18.435J Quantum Computation Midterm Quiz Solutions
(Given in class, with a page of notes allowed, on Thursday, October 27, 2005)

1) Classical Logic

Consider a binary function f from n bits to m bits. If one can write $f(\mathbf{x}) = M\mathbf{x} + \mathbf{b}$, where \mathbf{x} is a column vector of length n , M is a $m \times n$ matrix, and \mathbf{b} is a column vector of length m , then f is said to be *affine*. (All multiplication and addition in this problem is mod 2.)

- (a) Let $M = \begin{pmatrix} 1 & 0 & 1 \\ 1 & 1 & 0 \end{pmatrix}$ and $\mathbf{b} = \begin{pmatrix} 0 \\ 1 \end{pmatrix}$. Exhibit a circuit made only of CNOT gates that implements $f(\mathbf{x}) = M\mathbf{x} + \mathbf{b}$. (Your circuit can include more than 3 bits.)
 - (b) Is f one-to-one? How is your answer to this question reflected in the form of your circuit in (a)?
 - (c) Can any affine function f from n bits to m bits be constructed out of CNOT gates alone? (You are free to include more than $\max\{m, n\}$ bits in these hypothetical circuits.) If so, why? If not, why not?
-

2) Single Qubit Operators

Note on Conventions: In this problem, positive rotation angles correspond to counterclockwise rotations, and negative rotation angles correspond to clockwise rotations.


- (a) A qubit is rotated by $\pi/2$ around the x -axis and then rotated by $\pi/2$ around the y -axis. Write down the 2×2 unitary matrix U corresponding to the net rotation.
 - (b) The net rotation U from (a) is expressible as a single rotation. By what angle? Around what axis?
 - (c) To lowest nonzero order in ϵ , write down the 2×2 unitary transformation U_ϵ corresponding to a rotation of ϵ around the x -axis, followed by a rotation of ϵ around the y -axis, then a rotation of $-\epsilon$ around the x -axis, and finally a rotation of $-\epsilon$ around the y -axis.
 - (d) The net approximate rotation U_ϵ from (c) is expressible as a single rotation. By what angle? Around what axis?
-

3) Cluster States

A *controlled phase gate* applies a phase of -1 to $|11\rangle$ and leaves all other logical states unchanged. That is,


$$|00\rangle \rightarrow |00\rangle, \quad |01\rangle \rightarrow |01\rangle, \quad |10\rangle \rightarrow |10\rangle, \quad |11\rangle \rightarrow -|11\rangle$$

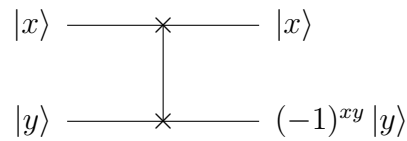We depict controlled phase gates with the following diagram.




[Note that the phase factor $(-1)^{xy}$ can just as well be associated with the output ket $|x\rangle$. Controlled phase gates are symmetric.]

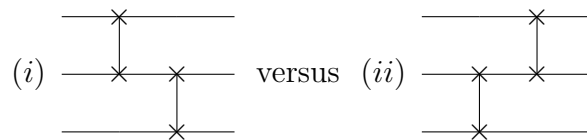
- (a) Show how to construct a CNOT using controlled phase gates and single qubit rotations.
- (b) How do the following two circuits differ in their effect?



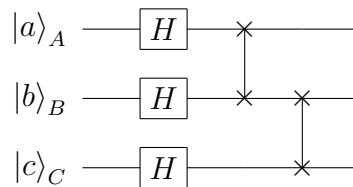- (c) What state is produced by the following circuit?



- (d) Consider extending the circuit in (c) by measuring qubit B in the $\{|0\rangle, |1\rangle\}$ basis and then flipping the qubit C if the result of the measurement is $|1\rangle_B$.

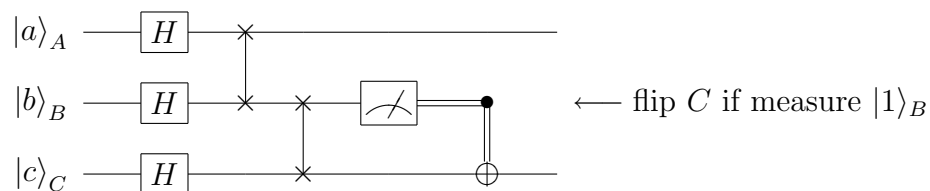

What is the joint state of qubits A and C after this procedure...

- (i) ... if measurement of qubit B yields $|1\rangle_B$?
- (ii) ... if you do not yet know the measurement result for qubit B ?


4) Quantum Phase Estimation for Grover's Algorithm

Let G denote the Grover step:

$$\boxed{G} \iff (\mathbb{I} - 2|s\rangle\langle s|)(2|w\rangle\langle w| - \mathbb{I}),$$

where $N = 2^n$, $|w\rangle$ is the target state, and $|s\rangle = \frac{1}{\sqrt{N}} \sum_{x=0}^{N-1} |x\rangle$.

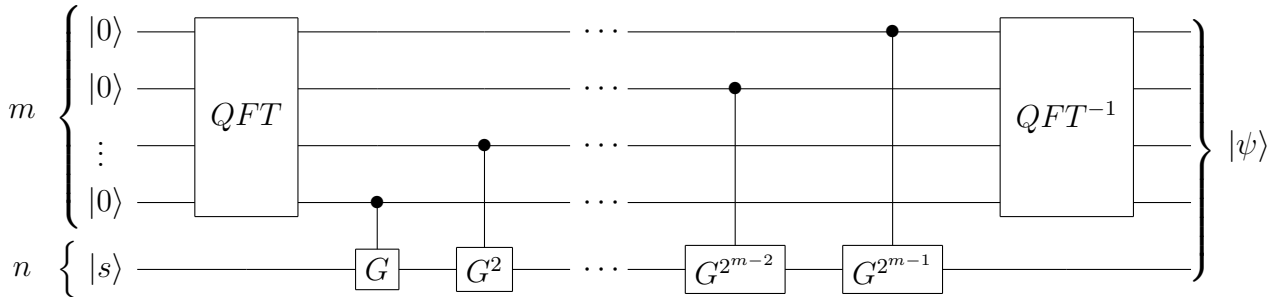(a) What is the output of the following circuit?



(b) Suppose $m = n$. What information do you get by measuring the first m bits of $|\psi\rangle$? After measurement, what state is registered by the second n bits of $|\psi\rangle$?

(c) How do your conclusions for part (b) change if $m \ll n$? If $m \gg n$?