

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Electrical Engineering and Computer Science

6.002 - Electronic Circuits  
Fall 2000

Homework #3  
Handout F00-020

Issued 9/21/2000 - Due 9/29/2000


**Exercise 3.1:** How many different Boolean functions are there of 3 variables? Of  $n$  variables?

**Exercise 3.2:** Do Exercise 6, p.216, parts a, b, and d.

**Exercise 3.3:** Do Exercise 2, p.257 (continues on p.258).

**Problem 2.1:** Do Problem 2, p.217.

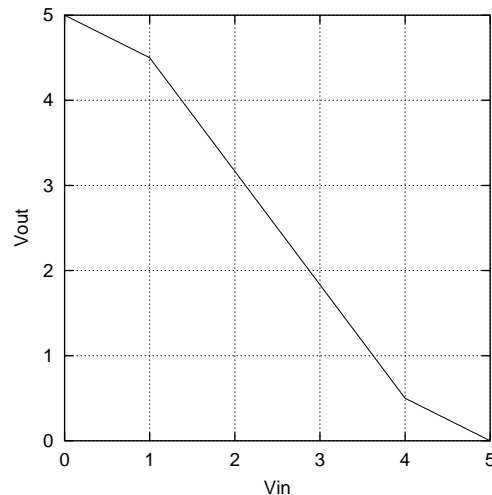**Problem 2.2:** An inverter has the input/output transfer characteristic shown below:



For suitable choices of the voltages  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$ , and  $V_{OH}$  this inverter obeys the static discipline (see Figure 6.7 on page 194 in the notes).

Give values of  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$ , and  $V_{OH}$  that actually achieve the static discipline with a positive noise margin. What is the noise margin you obtained?

**Problem 2.3:** Do Problem 9, p.265, but with the following modification: You need only design an inverter that meets the specification; you need not find a minimum area solution. Also, in calculating the area of your inverter you need to consider only the area taken by the gates of the transistors; you may ignore the area taken by source and drain regions and by interconnect.