

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

6.002 – Electronic Circuits
Fall 2002

Problem Set 1

Issued: September 4, 2002

Due: September 11, 2002

Reading Assignment:

Readings will be assigned from Agarwal and Lang.

- Chapters 1, 2 and Appendix A (for this week).
- 3.1-3.3 for Tuesday, September 10.
- 3.5-3.7 for Thursday, September 12.

Review Exercise 1.1: Let $x(t)$ be the complex function $x(t) = \frac{a+bj}{c+dj}e^{j\omega t}$ where a, b, c, d and ω are constants, and $j = \sqrt{-1}$. Determine M and ϕ such that $\Re\{x(t)\} = M \cos(\omega t + \phi)$, where the symbol $\Re\{z\}$ represents the real part of the complex number z .

Review Exercise 1.2: Determine $x(t)$ for $t \geq 0$ given that $\frac{dx(t)}{dt} + ax(t) = b$ and $x(0) = c$ where a, b and c are constants.

Problem 1.1: Figure 1 shows a circuit with four elements: two resistors, a voltage source, and a current source. The resistances of the resistors and the strengths of the sources are given. Branch voltage circuit variables (v_k) and branch current circuit variables (i_k) are defined for each element, in associated reference directions.

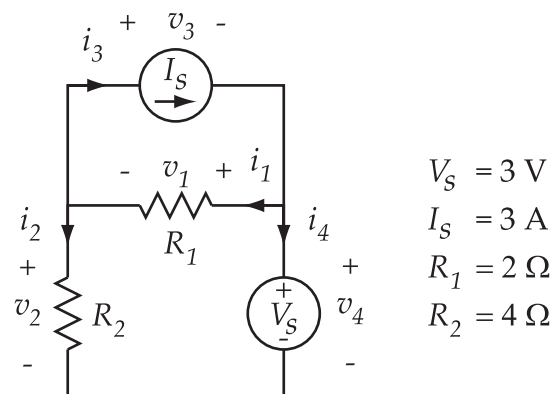


Figure 1: Circuit for Problem 1

- (A) How many nodes are there in the circuit? Write a KCL equation for each node. How many of the KCL equations are independent? (Independent means, “Cannot be derived from the other equations.”)
- (B) How many loops are there in the circuit? Write a KVL equation for each loop. How many of these equations are independent?
- (C) Write an equation expressing the v-i constraint for each element.
- (D) You should now have a set of linear equations in the branch voltage and current variables. If you count only the independent equations, you should have one equation for each unknown branch voltage or current. Solve the equations and fill in the table of results. Compute the power ($v_k i_k$) leaving the circuit by each branch and enter it into your table.

$$v_1 = \quad i_1 = \quad v_1 i_1 =$$

$$v_2 = \quad i_2 = \quad v_2 i_2 =$$

$$v_3 = \quad i_3 = \quad v_3 i_3 =$$

$$v_4 = \quad i_4 = \quad v_4 i_4 =$$

- (E) Now compute the sum of the four powers you computed. It should be exactly zero, or you made an error! Which source supplies power and which absorbs power?

Problem 1.2: Repeat the process you did in Problem 1 for the circuit of Figure 2 below. Notice that the sum of the powers is zero here too.

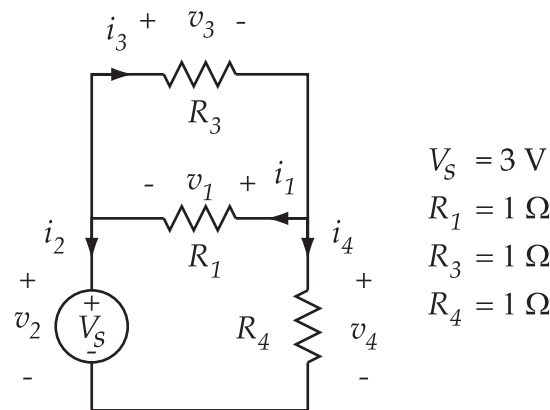


Figure 2: Circuit for Problem 2

Problem 1.3: Make a table of the voltages you computed from Problem 1 paired with the corresponding currents you got in Problem 2 (e.g., get v_1 from the first table and i_1 from the second table). What is the sum of the products of these voltages and the currents? More precisely, compute $v_1 i_1 + v_2 i_2 + v_3 i_3 + v_4 i_4$. The result that you get (assuming that you have done the work correctly) is not an accident but the result of a network theorem called *Tellegen's Theorem*.