

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

6.002 – Electronic Circuits
Fall 2002

Problem Set 4

Issued: September 25, 2002

Due: October 2, 2002

Reading Assignment:

- A&L Section 2.6 for Thursday, September 26.
- A&L Chapter 7 for Tuesday, October 1.

Problem 4.1:

(A) Implement the logical function $A\bar{B} + \bar{A}B$ using

- (i) only NOT and NAND gates.
- (ii) only NOT and NOR gates.

(B) Determine a circuit implementation for the gate configurations found in part (A) using MOSFETs and pull-up resistors. You do not need to determine element values.

Problem 4.2: Design a circuit to implement the Boolean expressions given below using MOSFETs and pull-up resistors. You do not need to determine element values.

(A) $A + \bar{B} + \bar{C}$

(B) $AB\bar{C}$

(C) $AB + C$

In each case the circuit can be implemented by at most four MOSFETs and two resistors. Try to use the minimum number of components.

Problem 4.3: The NOR gate shown in Figure 1 is a member of a family of logic gates that operates with the following voltage thresholds:

$$V_{OL} = 0.5V, \quad V_{IL} = 1.5V, \quad V_{IH} = 4V, \quad V_{OH} = 4.5V$$

Since the voltage V_G is more than one threshold voltage above V_S , the pull-up MOSFET, like the MOSFETs used to implement the NOR gate, operates in the S-R regime with $R_{on} = R_n \frac{L}{W}$ where $R_n = 1k\Omega$ and L and W are the lateral dimensions of the MOSFET channel. Assume that the area of each MOSFET is given by $L \times W$, that the dimensions of each MOSFET can be independently specified, and that the minimum dimension of any MOSFET channel is $0.5\mu m$.

 


Figure 1: Circuit for Problem 4.3

- (A) A random batch of MOSFETs has variability in their threshold voltage values. What is the widest range of V_T values that would be acceptable in implementing the above gate?
- (B) Determine the minimum total MOSFET area required to implement the NOR gate.
- (C) Assume that the NOR gate operates for equal time in each of its four input states. What is the total average power dissipated by the MOSFETs?

Problem 4.4: Figure 2 shows a simplified model of a single-stage amplifier that incorporates a bipolar junction transistor (BJT). Typically the parameter $\beta \approx 100$. Although we will not study BJT's in 6.002, this problem illustrates that the tools we are developing are sufficient to analyze and design circuits containing them, given appropriate models.

 


Figure 2: Circuit for Problem 4.4

- (A) Determine the relationship between v_O and v_I .
- (B) Graph this relationship and indicate a range of validity if the model holds only for $i_B > 0$ and $v_O > 0$. In this range, what is the small-signal gain dv_O/dv_I ?

Problem 4.5:

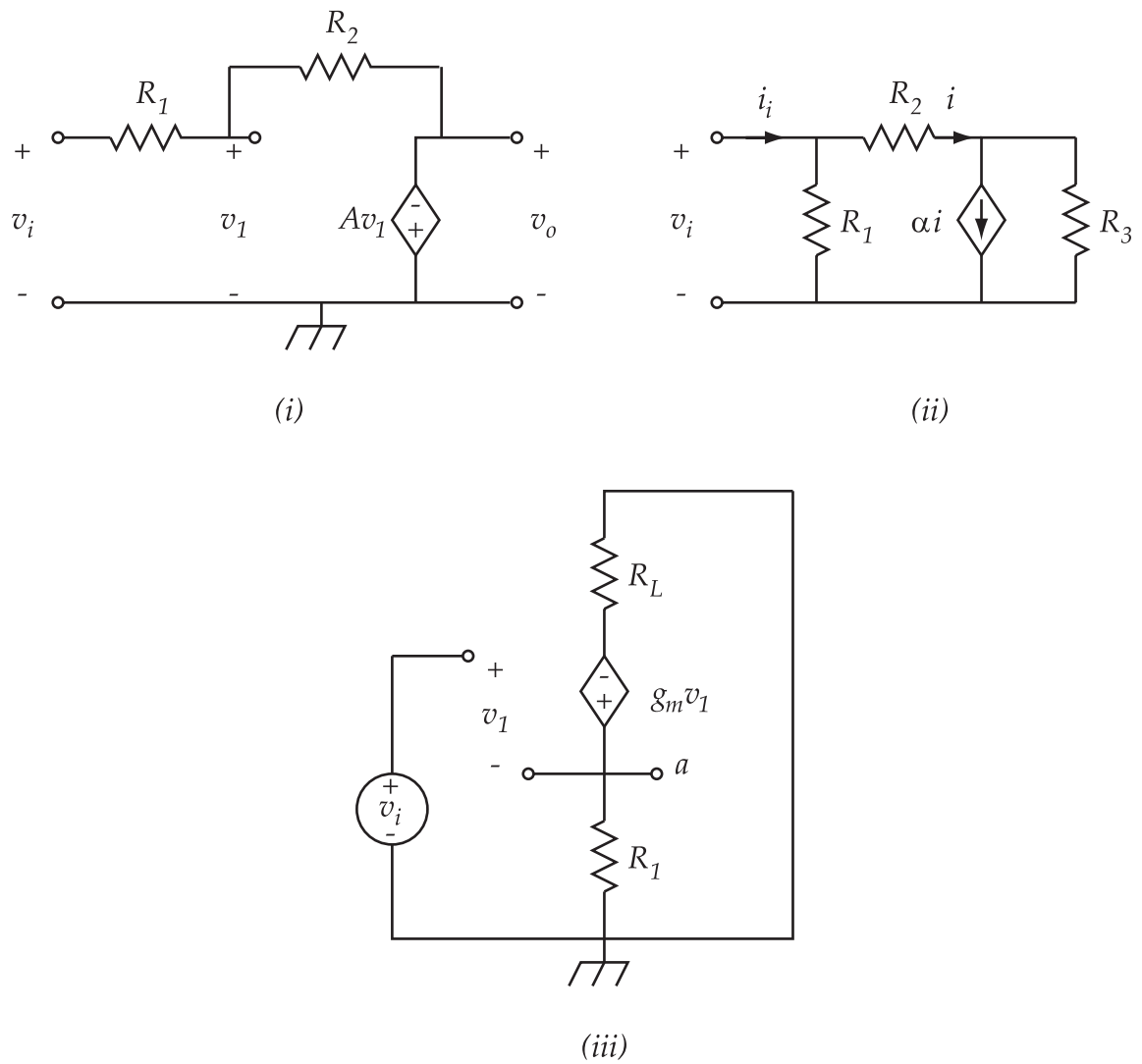


Figure 3: Circuits for Problem 4.5

- Compute the gain $A = v_o/v_i$ in Figure 3(i).
- Compute the Thévenin resistance $R_{Th} = v_i/i_i$ in Figure 3(ii).
- Determine the Thévenin equivalent circuit at the terminal pair formed by a and the ground node in Figure 3(iii).