

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Electrical Engineering and Computer Science

6.002 – Electronic Circuits  
Fall 2002

Problem Set 5

Issued: October 2, 2002

Due: October 9, 2002

Reading Assignment:

- A&L Section 7.7 and Chapter 8 for Thursday, October 3.
- A&L Chapter 8 for Tuesday, October 8.

**Problem 5.1:** Figures 3 and 4, at the end of this problem set, show three amplifier configurations with the MOSFET characteristics.

- Determine  $K$  and  $V_T$  for the MOSFETs used in these circuits.
- In each case, sketch the load line directly on the characteristics clearly indicating the slope and intercepts.
- For each amplifier, determine  $v_O(v_I)$  assuming the MOSFET operates in its saturation region.
- For the amplifiers in (b) and (c), find the small-signal gain in the limit  $v_I - V_T \gg 1/2KR_2$ .
- For each of the amplifiers, determine the range of  $v_I$  and  $v_O$  for which the MOSFET operates in saturation, i.e.,  $V_T < v_{GS} < v_{DS} + V_T$ .

**Problem 5.2:** The MOSFETs M1 and M2 in the circuit of Figure 1 are characterized by  $K = 2\text{mA}/\text{V}^2$  and  $V_T = 2\text{V}$ , while MOSFET M3 has  $K = 1\text{mA}/\text{V}^2$  and  $V_T = 2\text{V}$ .

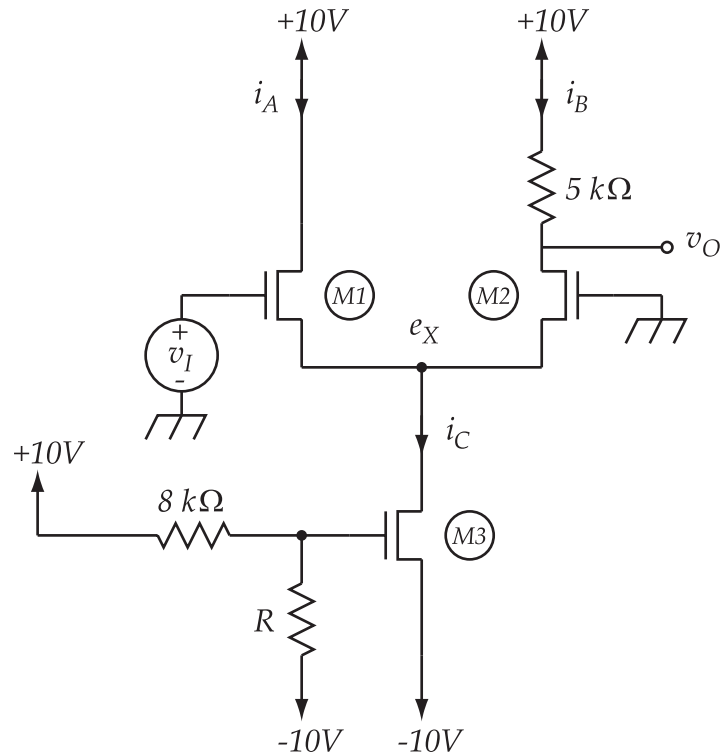


Figure 1: Circuit for Problem 5.2

- For the circuit shown in Figure 1, determine  $R$  so that  $I_C = 2\text{mA}$  with  $v_I = 0$ .
- For the bias condition determined in part (A), what are the currents  $I_A$  and  $I_B$ , and the node voltage  $E_X$ ?
- Now let  $v_I = v_i$ , a small-signal input voltage. Determine  $e_x$ , the small-signal component of the node voltage  $e_X$ , and from that determine the small-signal gain  $v_o/v_i$ .
- Assume now that the above amplifier operates in the large-signal, nonlinear regime. At what value of  $v_I$  will the output MOSFET M2 cutoff, i.e., its current decrease to 0?

**Problem 5.3:** The two MOSFETs in the circuit shown in Figure 2(a) are identical and characterized by the  $i_{DS}$ - $v_{DS}$  relationship shown in Figure 2(b). Note that in the triode region the characteristics are approximated by a single  $i_{DS}$ - $v_{DS}$  relationship that is independent of  $v_{GS}$  and that M1 and M2 are characterized by the same values of  $K$  and  $V_T$  as for the MOSFETs in Problem 5.1.

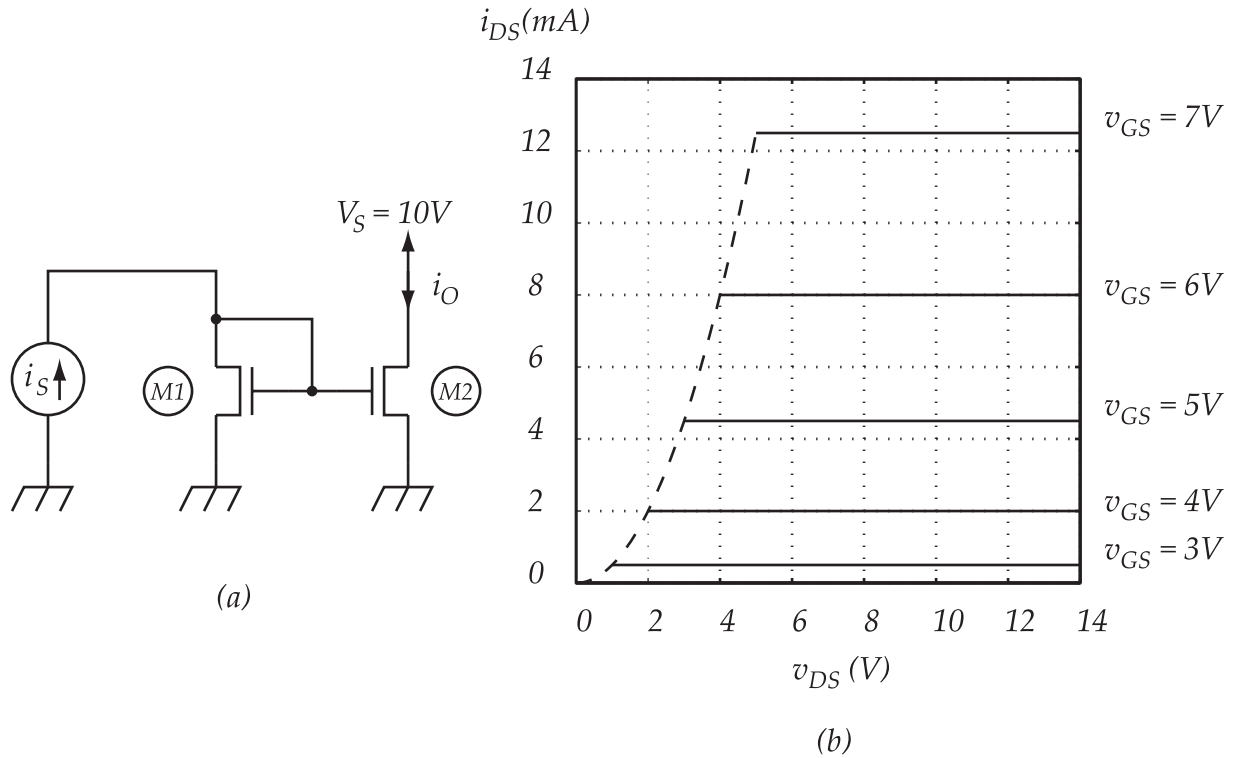


Figure 2: Circuit for Problem 5.3

- (A) Determine and graph  $i_O$  vs.  $i_S$  for  $i_S > 0$ . Explain why this circuit is called a “current mirror”.
- (B) Repeat part (A) with a  $1k\Omega$  load resistor between the drain of M2 and the  $V_S$  rail.

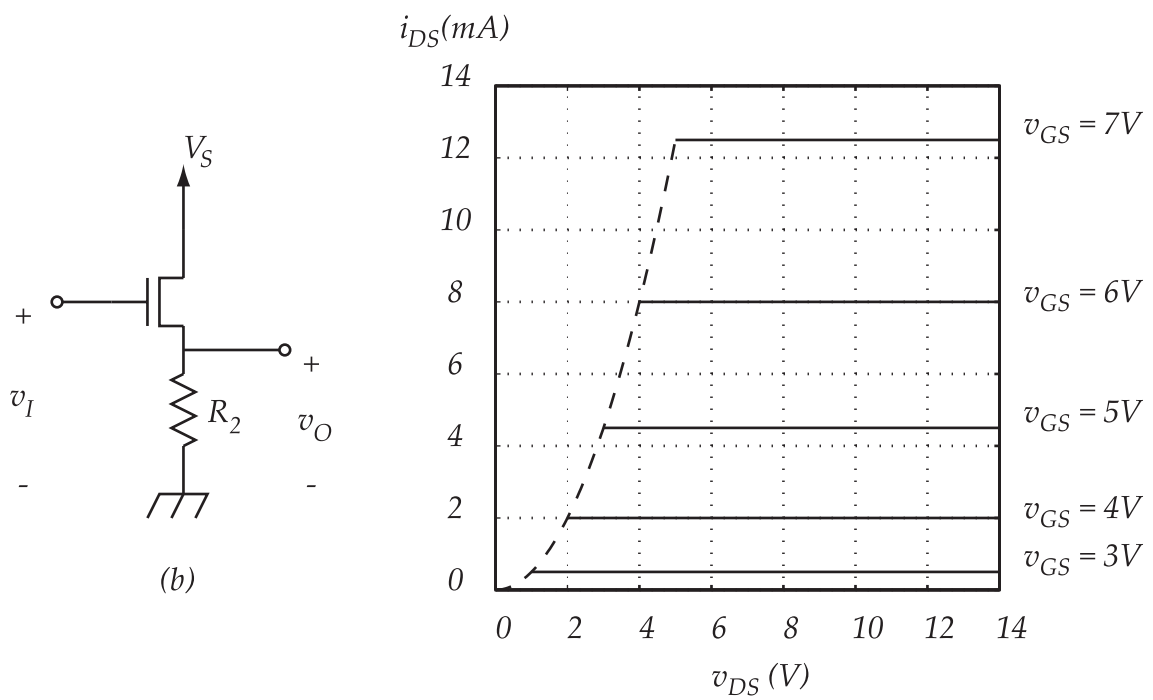
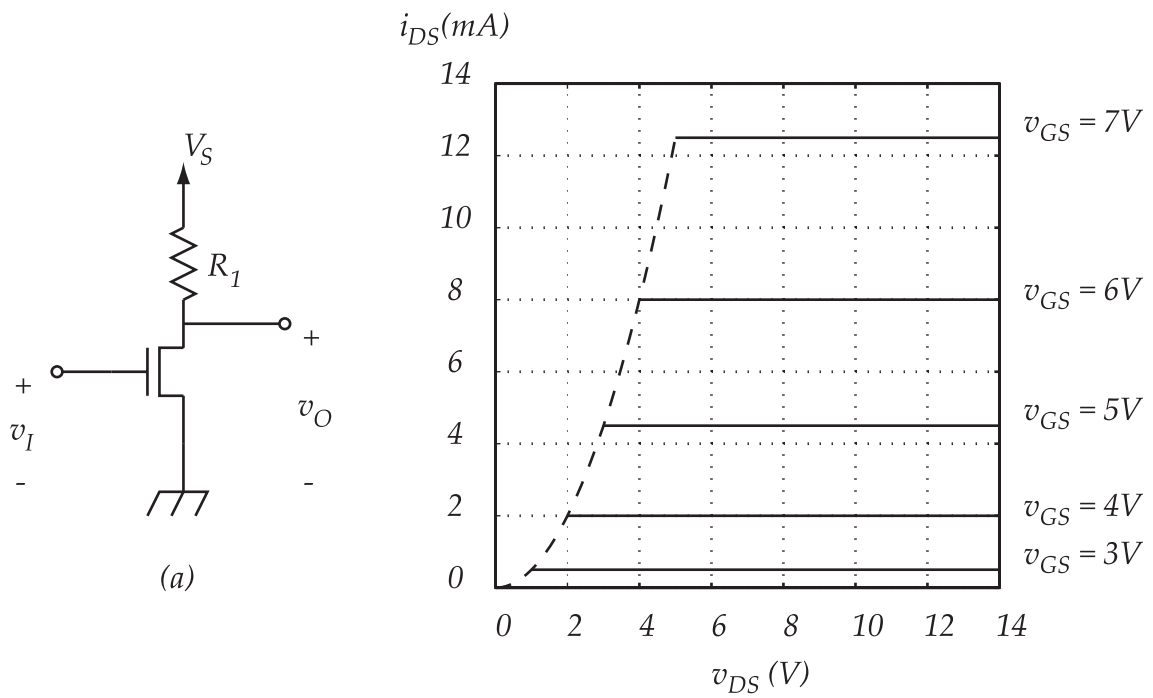


Figure 3: Circuits (a) and (b) for Problem 5.1

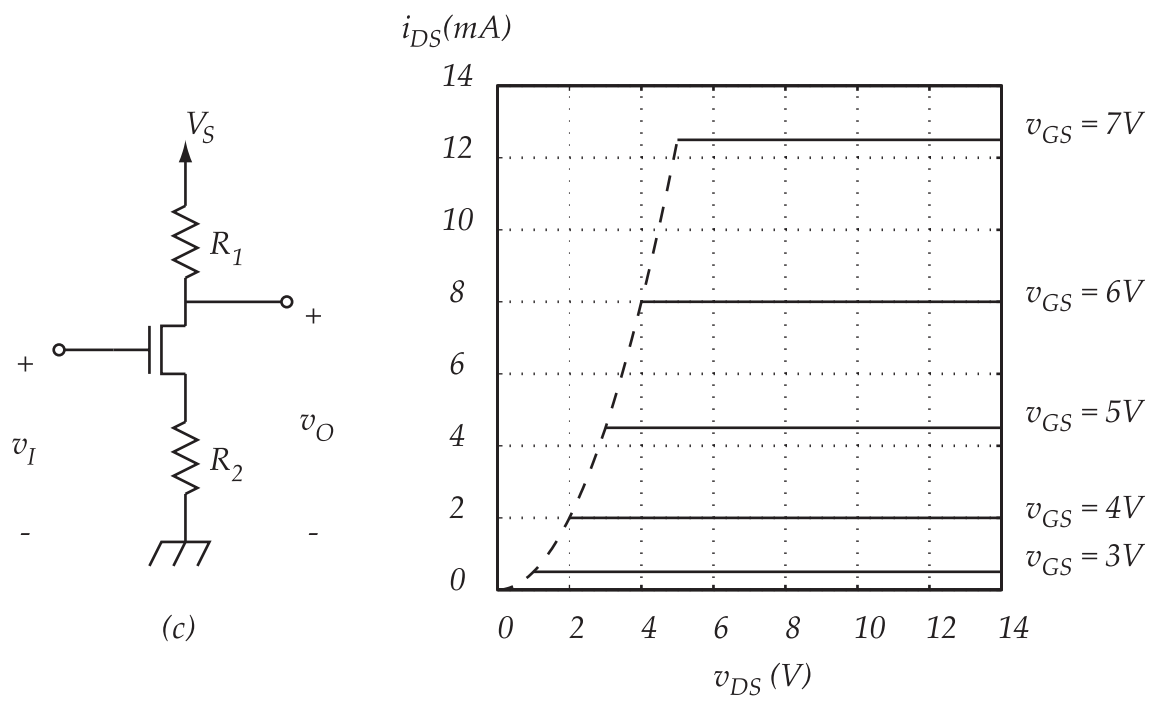


Figure 4: Circuit (c) for Problem 5.1