

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

6.002 – Electronic Circuits
Fall 2002

Quiz 3 Solutions

Name: _____ Recitation Section: _____


Recitation Instructor: _____ Teaching Assistant: _____

Make sure that your name is on all sheets. Enter your answers directly in the spaces provided on the printed pages. You may use the back of the previous page as a worksheet. Answers must be derived or explained, not just simply written down. The quiz is closed book, but **calculators are allowed**.

This quiz contains 8 pages including the cover sheet. Make sure that your quiz contains all 8 pages and that you hand in all 8 pages.

Problem	Points	Grade	Grader
1	30		
2	30		
3	40		
Total	100		

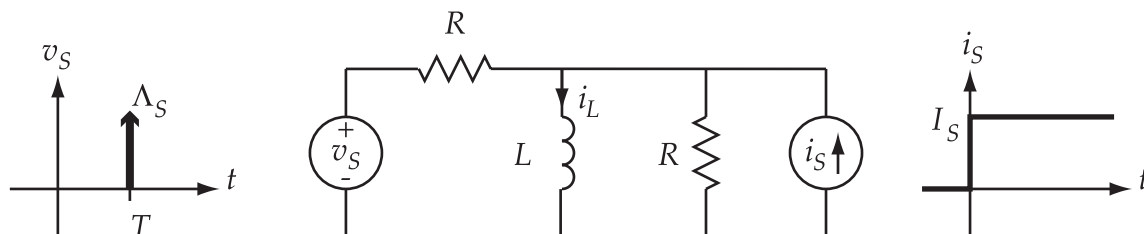Problem 1: (30 points) This problem examines the transient response of the circuit shown below. In the circuit, $i_L = 0$ at $t = 0^-$.



(A) (10 points) Determine an expression for i_L due to $i_S = I_S u(t)$; that is, for $\Lambda_S = 0$.

Since $\Lambda_S = 0$, we replace the voltage source v_S with a short. Recognizing that this is a first order LR circuit, we need to find: 1. $i_L(0^+)$, 2. $i_L(t \rightarrow \infty)$ and 3. $\tau = L/R_{eq}$, where R_{eq} is the Thévenin equivalent resistance seen from the terminals of the inductor L .

1. To find $i_L(0^+)$, we recall that an inductor with $i_L(0^-) = 0$ acts as an open at $t = 0^+$. Thus, the current from the source goes through the two resistors and $i_L(0^+) = 0$.

2. To find $i_L(t \rightarrow \infty)$, we recall that an inductor acts as a short at $t \rightarrow \infty$. Thus, all the current from the source goes through the inductor and $i_L(t \rightarrow \infty) = I_S$.

3. To find $\tau = L/R_{eq}$, we turn off i_S by replacing it with an open. We then find that the Thévenin equivalent resistance seen from the terminals of the inductor L is the two resistors R in parallel, so that $R_{eq} = R/2$. Therefore, $\tau = 2L/R$.

We can construct the answer using the results 1, 2, and 3:

$$i_S(t) = \begin{cases} I_S(1 - e^{-t/\tau}); & \tau = 2L/R \quad t \geq 0 \\ 0 & t < 0 \end{cases}$$

(B) (10 points) Determine an expression for i_L due to $v_S = \Lambda_S \delta(t - T)$; that is, for $I_S = 0$.

Since $I_S = 0$, we replace the current source i_S with an open. Since this is a linear system, the answer to an input shifted to $t = T$ is the answer to that same input at $t = 0$ shifted to $t = T$. Thus, we need to find the response to $v_S = \Lambda_S \delta(t)$ and shift the answer to $t = T$.

Again, recognizing that this is a first order LR circuit, we need to find: 1. $i_L(0^+)$ and 2. $i_L(t \rightarrow \infty)$. The time constant τ is the same independent of the inputs to the circuit; thus, it is as that found in part (A), $\tau = 2L/R$.

1. To find $i_L(0^+)$, we recall that an inductor with $i_L(0^-) = 0$ acts as an open at $t = 0^+$. The voltage flux Λ_S divides equally across the two resistors R and appears across the open terminals of the inductor as $\Lambda_S/2$. This flux generates a current instantly according to $\Lambda_L = Li_L$. Thus, $i_L(0^+) = \Lambda_L/L = \frac{\Lambda_S}{2L}$.

2. To find $i_L(t \rightarrow \infty)$, we recall that an inductor acts as a short at $t \rightarrow \infty$. Thus, the current through the inductor is $i_L(t \rightarrow \infty) = v_S(t \rightarrow \infty)/R$. Since v_S is an impulse, $v_S(t \rightarrow \infty) = 0$, and $i_L(t \rightarrow \infty) = v_S(t \rightarrow \infty)/R = 0$.

We can construct the answer combining the results 1 and 2, and shifting the response to $t = T$:

$$i_S(t) = \begin{cases} \frac{\Lambda_S}{2L} e^{-(t-T)/\tau}; & \tau = 2L/R \quad t > T \\ 0 & t < T \end{cases}$$

Alternatively, we can compute the step response and differentiate it to get the impulse response:

$$\left[\frac{\Lambda_S}{V_S} \frac{d}{dt} \right] V_S u(t - T) = \Lambda_S \delta(t - T)$$


$$\left[\frac{\Lambda_S}{V_S} \frac{d}{dt} \right] \frac{V_S}{R} (1 - e^{-(t-T)/\tau}) = \frac{\Lambda_S}{R} e^{T/\tau} \frac{1}{\tau} e^{-t/\tau} = \frac{\Lambda_S}{2L} e^{-(t-T)/\tau}$$

(C) (10 points) Determine an expression for i_L due to i_S and v_S together.

Applying superposition, the response is the sum of the responses found in parts (A) and (B):

$$i_S(t) = \begin{cases} I_S(1 - e^{-t/\tau}) + \frac{\Lambda_S}{2L} e^{-(t-T)/\tau}; & \tau = 2L/R \quad t > T \\ I_S(1 - e^{-t/\tau}); & \tau = 2L/R \quad 0 \leq t < T \\ 0 & t < 0 \end{cases}$$

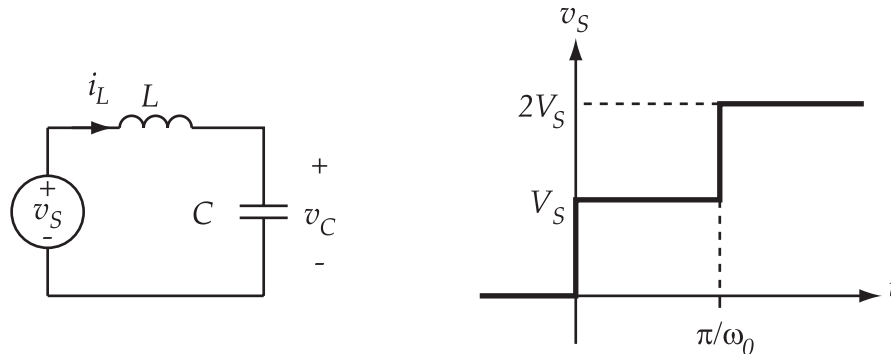Problem 2: (30 points) In the circuit below, $\omega_0 \equiv 1/\sqrt{LC}$, $v_C(0^-) = 0$, and $i_L(0^-) = 0$.



(A) (15 points) Determine an expression for $v_C(t)$ for $t > 0$. If you determine $v_C(t)$ by inspection, state your reasoning CLEARLY.

The input is a sum of two steps, which can be written as $v_S(t) = V_S u(t) + V_S u(t - \pi/\omega_0)$. Using linearity, we can express the solution as $v_C(t) = v'_C(t) + v'_C(t - \pi/\omega_0)$, where $v'_C(t)$ is the response of the circuit to $v_S(t) = V_S u(t)$.

At $t = 0^+$, L is open and C is shorted. Thus, $i_L(0^+) = 0$, and $v'_C(0^+) = 0$. Also, $v'_C(0^+) = i_L(0^+)/C = 0$. The particular solution is $v'_C(t) = V_S$. Since the system is undamped, the general solution takes the form

$$v'_C(t) = A \cos \omega_0 t + B \sin \omega_0 t + V_S$$

Applying the initial conditions,

$$v'_C(t) = V_S(1 - \cos \omega_0 t)$$


Thus, this is the solution for $0 \leq t \leq \pi/\omega_0$. For $t > \pi/\omega_0$, we need to add $v'_C(t - \pi/\omega_0)$ to our original $v'_C(t)$,

$$\begin{aligned} v'_C(t) + v'_C(t - \pi/\omega_0) &= V_S(1 - \cos \omega_0 t) + V_S[1 - \cos \omega_0(t - \pi/\omega_0)] \\ &= V_S(1 - \cos \omega_0 t) + V_S(1 + \cos \omega_0 t) = 2V_S \end{aligned}$$

Combining these results,


$$v_C(t) = \begin{cases} V_S(1 - \cos \omega_0 t) & 0 \leq t \leq \pi/\omega_0 \\ 2V_S & t > \pi/\omega_0 \end{cases}$$

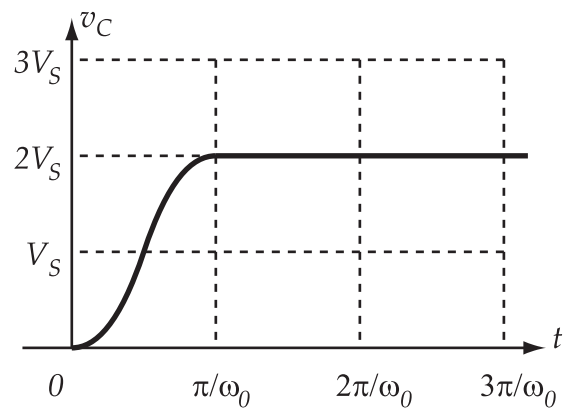(B) (15 points) Sketch and dimension $v_C(t)$ for $t > 0$.



Problem 3: (40 points) All circuits below operate in the sinusoidal steady state. For each circuit, determine the input impedance $Z(j\omega)$, the specified transfer function $H(j\omega)$, and the parameters V_o and ϕ which define $v_o(t) \equiv V_o \cos(\omega t + \phi)$, where V_o is a real, positive number.

(A) (10 points)

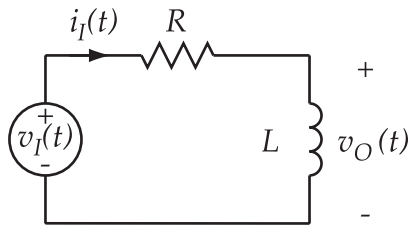

$$v_I(t) = V_i \cos(\omega t)$$


$$Z(j\omega) = \frac{V_i}{\hat{I}_i} = R + Lj\omega$$

$$H(j\omega) = \frac{\hat{V}_o}{V_i} = \frac{Lj\omega}{R + Lj\omega} = \frac{j\frac{L}{R}\omega}{1 + j\frac{L}{R}\omega}$$

$$V_o = \frac{L\omega}{\sqrt{R^2 + (L\omega)^2}} V_i$$

$$\phi = \pi/2 - \tan^{-1} \frac{L\omega}{R} = \tan^{-1} \frac{R}{L\omega}$$

(B) (15 points)

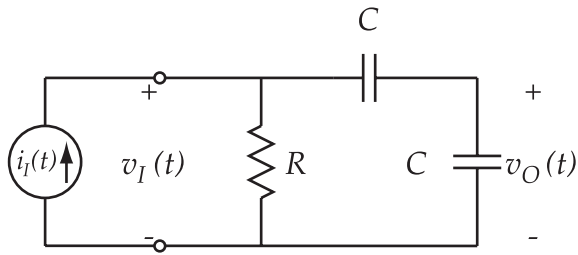

$$i_I(t) = I_i \cos(\omega t)$$


$$Z(j\omega) = \frac{\hat{V}_i}{\hat{I}_i} = R \parallel \left(\frac{1}{Cj\omega} + \frac{1}{Cj\omega} \right) = \frac{2R}{RCj\omega + 2}$$

$$H(j\omega) = \frac{\hat{V}_o}{\hat{I}_i} = \frac{\hat{V}_o}{\hat{V}_i} \frac{\hat{V}_i}{\hat{I}_i} = \frac{\hat{V}_o}{\hat{V}_i} Z(j\omega) = \frac{\frac{1}{Cj\omega}}{\frac{1}{Cj\omega} + \frac{1}{Cj\omega}} Z(j\omega) = \frac{1}{2} Z(j\omega) = \frac{R}{RCj\omega + 2}$$

$$V_o = \frac{R}{\sqrt{4 + (RC\omega)^2}} I_i$$

$$\phi = -\tan^{-1} \frac{RC\omega}{2}$$

(C) (15 points)

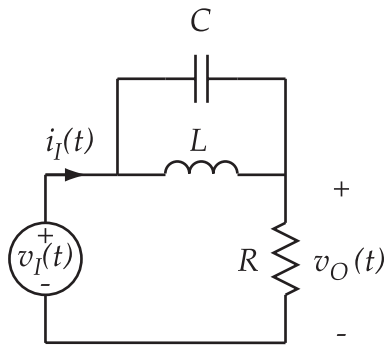

$$v_I(t) = V_i \cos(\omega t)$$

$$\begin{aligned} Z(j\omega) &= \frac{V_i}{I_i} = R + Lj\omega \parallel \frac{1}{Cj\omega} = R + \frac{Lj\omega}{1-LC\omega^2} \\ &= R \left(1 + \frac{\frac{1}{RC}j\omega}{\frac{1}{LC}-\omega^2} \right) = R \left(\frac{\frac{1}{LC}-\omega^2 + \frac{1}{RC}j\omega}{\frac{1}{LC}-\omega^2} \right) \end{aligned}$$

$$H(j\omega) = \frac{\hat{V}_o}{\hat{V}_i} = \frac{R}{R + Lj\omega \parallel \frac{1}{Cj\omega}} = \frac{R - RLC\omega^2}{R - RLC\omega^2 + Lj\omega} = \frac{\frac{1}{LC} - \omega^2}{\frac{1}{LC} - \omega^2 + \frac{1}{RC}j\omega}$$

$$V_o = \frac{|R - RLC\omega^2|}{\sqrt{(R - RLC\omega^2)^2 + (L\omega)^2}} V_i$$

$$\begin{aligned} \phi &= -\tan^{-1} \frac{L\omega}{R - RLC\omega^2} + \tan^{-1} \left(\frac{0}{R - RLC\omega^2} \right) \\ &= -\tan^{-1} \frac{L\omega}{R - RLC\omega^2} + \begin{cases} 0 & \omega < 1/\sqrt{LC} \\ \pi & \omega > 1/\sqrt{LC} \end{cases} \end{aligned}$$

Note:

Since \tan^{-1} is a multi-valued function, its range needs to be specified in order to define a unique solution within a factor of $2n\pi$. One way to do this is to explicitly spell out the numerator and denominator in the argument, a procedure that then defines the angle to be between 0 and 2π or $-\pi$ to $+\pi$. This is the approach taken in lecture and in Appendix C of the notes, and leads to the result given here. Another way is to specify that \tan^{-1} lies between $-\pi/2$ and $\pi/2$ and add π when the angle moves out of this range. In any case, \tan^{-1} must be clearly defined and that was worth 1 point for this part of the problem.