


Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.002 – Electronic Circuits  
Spring 2002


Homework #10

Issued 4/17/02 – Due 4/24/02

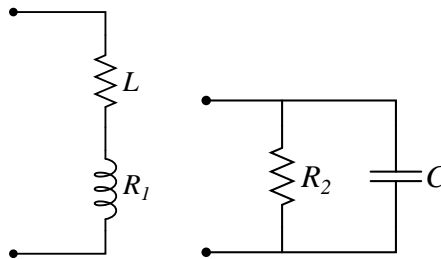**Exercise 10.1:** Determine the impedance of each network shown below. Also, identify the asymptotic dependence of the impedances on frequency for very low frequencies and for very high frequencies, and explain the dependences physically.




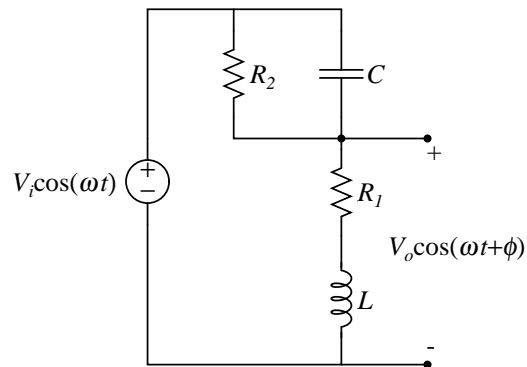**Exercise 10.2:** Assume that the network shown below is operating in sinusoidal steady state. Determine the amplitude  $V_o$  and phase  $\phi$  of the voltage across the series inductor and resistor. Hint: see Exercise 10.1.




**Problem 10.1:** This problem explores the Thevenin and Norton equivalence of networks operating in sinusoidal steady state. All networks considered here are comprised of linear resistors, capacitors and inductors, and voltage and current sources all operating at the same frequency  $\omega$ . Therefore, all branch currents and voltages operate at the frequency  $\omega$ .

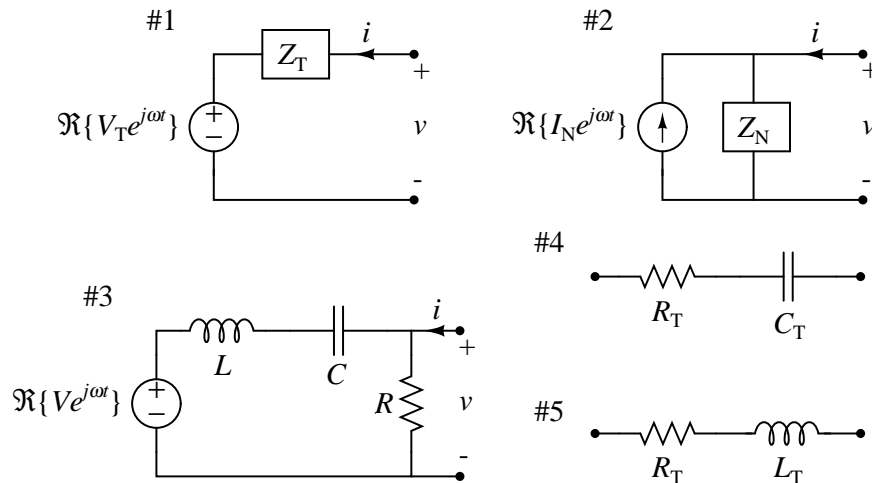- (A) Determine the relations between  $V_T$ ,  $Z_T$ ,  $I_N$  and  $Z_N$  which must exist for the  $i$ - $v$  relations at the terminals of Networks #1 and #2 to be identical when operating in sinusoidal steady state.
- (B) Review the arguments for networks involving only resistors and sources, and then briefly explain why Networks #1 and #2 may serve as the Thevenin and Norton equivalents, respectively, of an arbitrary network operating in sinusoidal steady state.
- (C) Determine  $V_T$  and  $Z_T$  in the Thevenin equivalent of Network #3.
- (D) Suppose  $Z_T$  in Part C is implemented with Networks #4 and #5. Determine  $R_T$  and  $C_T$  in Network #4, and  $R_T$  and  $L_T$  in Network #5, in terms of  $R$ ,  $L$ ,  $C$  and  $\omega$ . Under what circumstances is Network #4 preferred over Network #5, and vice versa?



**Problem 10.2:** This problem examines the very simple tuner for an AM radio shown below. Here, the tuner is the parallel inductor and capacitor. The injection of radio signals into the tuner by the antenna is modeled by a current source, while the Norton resistance of the antenna in parallel with the remainder of the radio is modeled by a resistor. (You will learn about antenna modeling in 6.014.) The AM radio band extends from 540 kHz through 1600 kHz. The information transmitted by each radio station is constrained to be within  $\pm 5$  kHz of its center frequency. (You will learn about AM radio transmission in 6.003.) To prevent frequency overlap of neighboring stations, the center frequency of each station is constrained to be a multiple of 10 kHz. Therefore, the purpose of the tuner is to pass all frequencies within 5 kHz of the center frequency of the selected station, while attenuating all other frequencies.

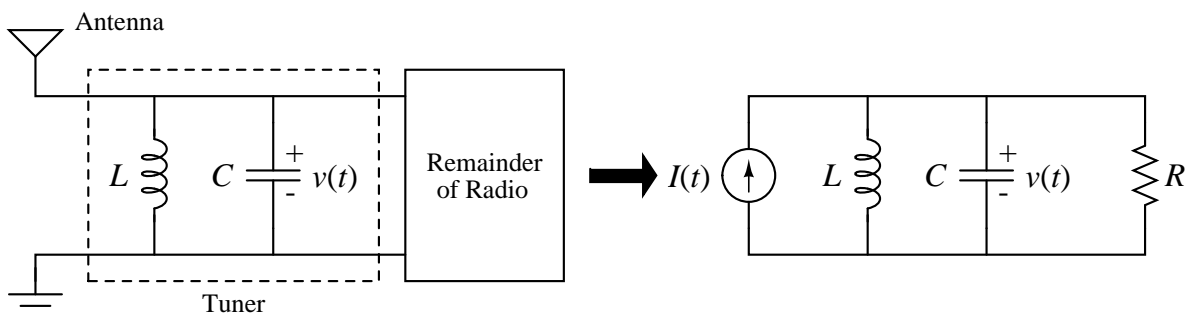- (A) Assume that  $I(t) = I \cos(\omega t)$ . Find  $v(t)$  where  $v(t) = V \cos(\omega t + \phi)$ , and both  $V$  and  $\phi$  are functions of  $\omega$ . Note that  $v(t)$  is the output of the tuner, namely the signal that is passed on to the remainder of the radio.
- (B) For a given combination of  $I$ ,  $C$ ,  $L$  and  $R$ , at what frequency is  $V$  maximized?
- (C) Assume that  $L = 365 \mu\text{H}$ . Over what range of capacitance must  $C$  vary so that the frequency of maximum  $V/I$  may be tuned over the entire AM band. Note that tuning the frequency of maximum  $V/I$  to the center frequency of a particular station tunes in that station.
- (D) As a compromise between passing all frequencies within 5 kHz of a center frequency and rejecting all frequencies outside that band, let the design of  $R$  be such that  $V(1 \text{ MHz} \pm 5 \text{ kHz})/V(1 \text{ MHz}) \approx 0.25$  when the tuner is tuned to 1 MHz. Given this design criterion, determine  $R$ .
- (E) Given your design for  $R$ , determine  $V(1 \text{ MHz} \pm 10 \text{ kHz})/V(1 \text{ MHz})$ . Also, determine  $Q$  for the tuner and its load resistor when the tuner is tuned to 1 MHz.
- (F) Suppose the tuner is tuned to another station and then quickly tuned to the station broadcasting at 1 MHz. Approximately how long will it take for  $v(t)$  to depend primarily on the signal from the station broadcasting at 1 MHz. Assume that both stations broadcast signals of equal strength. Hint: consider the time-domain interpretation of  $Q$ .



**Problem 10.3:** In this problem, a low-voltage sinusoidal source is coupled to a resistive load through an inductor-capacitor network as shown below. The role of the network is to boost the voltage at the load.

- (A) Derive the differential equation that relates  $v_{\text{OUT}}(t)$  to  $v_{\text{IN}}(t)$ .
- (B) Assume that the circuit operates in sinusoidal steady state with  $v_{\text{IN}}(t) = V_I \cos(\omega t)$ . Let  $v_{\text{OUT}}(t)$  take the form  $v_{\text{OUT}} = V_O \cos(\omega t + \phi)$ . Determine  $N \equiv V_O/V_I$  and  $\phi$ .
- (C) For a given  $L$  and  $\omega$ , determine the value of  $C$  which maximizes  $N$ , and for this value of  $C$ , determine  $N$ .
- (D) Suppose that  $v_{\text{IN}}(t)$  is abruptly set to zero in an attempt to remove the voltage at the load. In this case, the amplitude of the load voltage will decay in proportion to  $e^{-t/\tau}$ . Assuming that  $C$  is chosen to maximize  $N$  following the result from Part (C), determine  $\tau$  in terms of  $N$  and  $\omega$ .
- (E) In view of the results of Parts (C) and (D), what is the disadvantage of using an inductor-capacitor network to boost the voltage which excites the load?

