


Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Electronic Circuits
Spring 2002

Homework #2

Issued 2/13/02 – Due 2/20/02

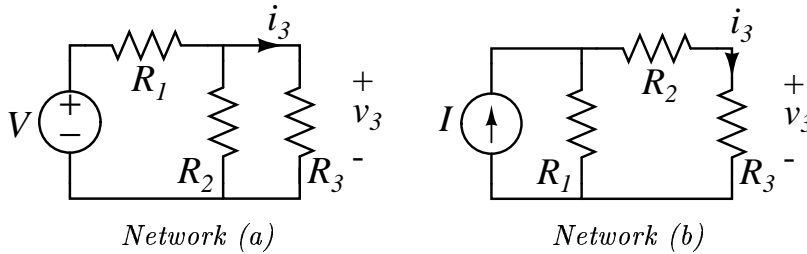
Exercise 2.1: For both networks shown below, determine the voltage v_3 across, and the current i_3 through, R_3 .




Exercise 2.2: Using the node method, develop a set of simultaneous equations for the network shown below that can be used to solve for the three unknown node voltages in the network. Express these equations in the form

$$G \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = S$$


where G is a 3×3 matrix of conductance terms and S is a 3×1 vector of terms involving the sources. You need not solve the set of equations for the node voltages.

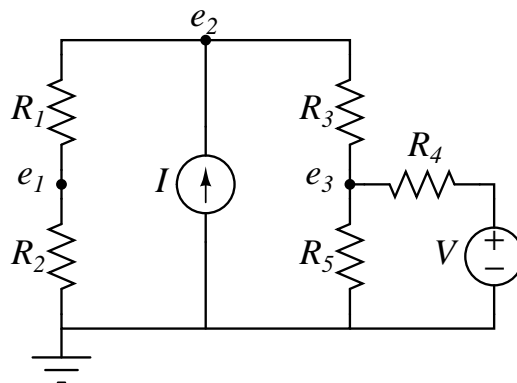

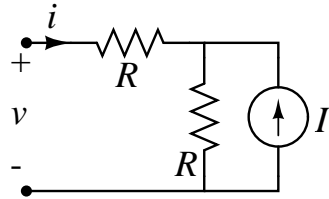
Problem 2.1: Find the Thevenin and Norton equivalents of the following networks, and graph their i - v relations as viewed at their ports.




Network (a)

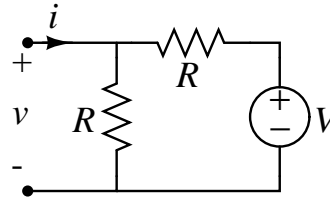

Network (b)

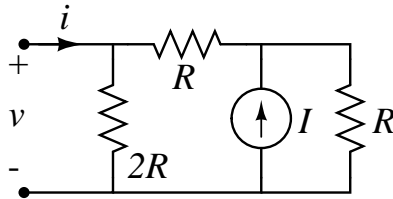


Network (c)

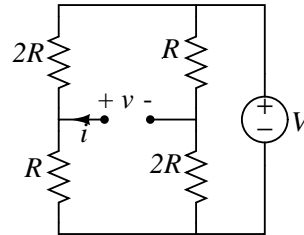



Network (d)

Problem 2.2: Given the network shown below, find v_0 as a function of v_1 , v_2 and v_3 assuming $i_0 = 0$. Hint: use superposition. Also, find the Thevenin equivalent of the network as viewed from its port. Finally, of what electronic circuit might the network be a part?

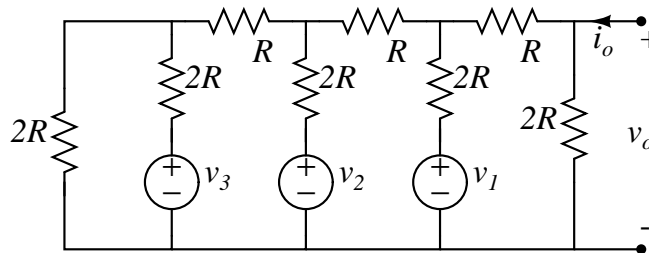

Problem 2.3: Two networks, N1 and N2, are described in terms of their i - v relations, and connected together through a single resistor, as shown below.

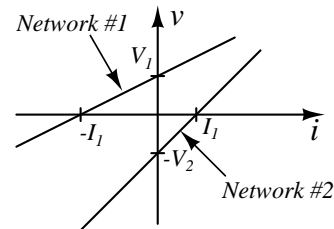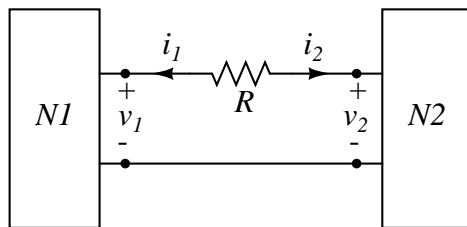- (A) Find the Thevenin and Norton equivalents of N1 and N2.
- (B) Find the voltages v_1 and v_2 that result from the interconnection of N1 and N2 through a resistor as shown below.



Problem 2.4: This problem studies the network shown below. The network contains two current sources and a nonlinear resistor. The nonlinear resistor has the terminal relation $i_N = \alpha|v_N|v_N$, where α is a positive constant with units A/V^2 . One current source produces the current i_A while the second current source produces the current i_B .

- (A) Determine v_N in terms of i_A and i_B .
- (B) Let $i_A = I_A$, where I_A is a constant current, and let $i_B = i_b(t)$. Further, assume that $I_A \gg |i_b(t)| > 0$ so that i_A can be thought of as being only a large-signal bias current, and i_B can be thought of as being only a small-signal time-varying current. Using the result from Part (A), linearize v_N and express it in the form $v_N = V_N + v_n(t)$ where V_N is a constant large-signal bias voltage and $v_n(t)$ is small-signal time-varying voltage proportional to $i_b(t)$.
- (C) Using the result of Part (B), determine R such that $v_n(t) = Ri_b(t)$. Show that R is the incremental resistance of the nonlinear resistor, namely that $R = dv_N/di_N$ evaluated at the bias current I_A .
- (D) From Part (C), it is apparent that the small-signal gain from the input current $i_b(t)$ to the output voltage $v_n(t)$ can be controlled by the bias current I_A . What problem can you see in using the circuit shown below as a controllable gain from the input current $i_b(t)$ to the output voltage $v_n(t)$?

