

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science


6.002 – Electronic Circuits  
Spring 2002

Homework #6

Issued 3/13/02 – Due 3/20/02


**Exercise 6.1:** Consider an amplifier with an input-output relation that takes the form  $v_{\text{OUT}} = V_A(v_{\text{IN}}/V_B)^5$ , where  $V_A$  and  $V_B$  are voltage constants. Determine its output bias voltage  $V_{\text{OUT}}$  and its small-signal gain  $v_{\text{out}}/v_{\text{in}}$  for a given input bias voltage  $V_{\text{IN}}$ .

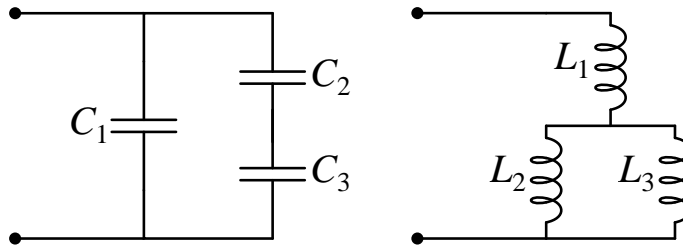**Exercise 6.2:** Find the capacitance of the all-capacitor network, and the inductance of the all-inductor network, shown below.




**Problem 6.1:** This problem studies the propagation delay of digital signals through the inverter shown below. Assume that the MOSFET in the inverter acts as a switch with on-state resistance  $R_{ON}$ . The inverter is loaded with a capacitor, having capacitance  $C_G$ , that models the combined input capacitance of the logic gates connected to its output. Assume that the inverter obeys the static discipline defined in part by  $V_{OL}$  and  $V_{OH}$ .

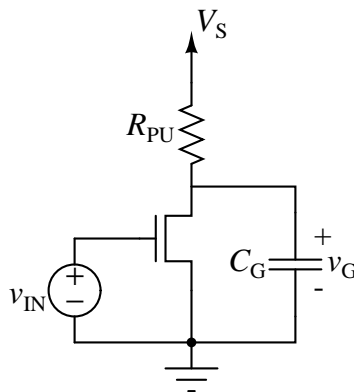- (A) Assume that the MOSFET has been off for a very long time. At  $t = 0$ ,  $v_{IN}$  turns the MOSFET on. Determine  $v_G(t)$  for  $t \geq 0$ .
- (B) How long does it take  $v_G(t)$  to pass by  $V_{OL}$ ? This delay is the fall time of the inverter.
- (C) Assume that the MOSFET has been on for a very long time. At  $t = 0$ ,  $v_{IN}$  turns the MOSFET off. Determine  $v_G(t)$  for  $t \geq 0$ .
- (D) How long does it take  $v_G(t)$  to pass by  $V_{OH}$ ? This delay is the rise time of the inverter.
- (E) How can the fall and rise times be shortened via the design of  $R_{PU}$ ? What limits the extent to which this design path may be followed?



**Problem 6.2:** In the circuit shown below, a MOSFET and an external resistor having resistance  $R_X$  are used to control the current  $i_R$  in the winding of a relay. Here, the relay is modeled as a series inductor and resistor having inductance  $L_R$  and resistance  $R_R$ , respectively. The MOSFET may be modeled as an ideal switch.

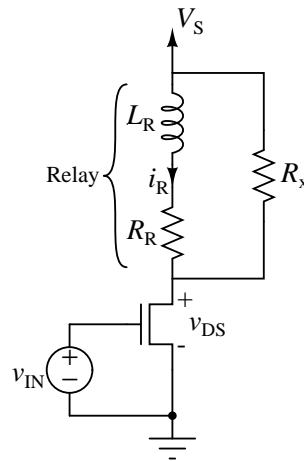- (A) At  $t = 0$ ,  $v_{IN}$  turns the MOSFET on so that  $v_{DS} = 0$ . Determine  $i_R(t)$  for  $t \geq 0$  given that  $i_R(t = 0) = 0$ .
- (B) Next, at  $t = T$ ,  $v_{IN}$  turns the MOSFET off. Determine both  $i_R(t)$  and  $v_{DS}(t)$  for  $t \geq T$ . Hint:  $i_R(t)$  is continuous at  $t = T$ .
- (C) Sketch and clearly label graphs of both  $i_R(t)$  and  $v_{DS}(t)$  for  $t \geq 0$  assuming that  $T \approx 5L_R/R_R$  and  $R_X = R_R$ .
- (D) The relay control circuit would be less expensive without the external resistor, which may be “removed” from the circuit by considering the limit  $R_X \rightarrow \infty$ . Why might such a cost reduction be unwise?



**Problem 6.3:** At  $t = 0^-$ , the networks shown below have zero initial state. That is, the capacitor voltage  $v(t)$  and the inductor current  $i(t)$  are both zero at  $t = 0^-$ . At  $t = 0$ , the voltage source produces an impulse of area  $\Lambda$ , and the current source produces an impulse of area  $Q$ .

- (A) Derive the differential equation that relates  $v(t)$  to  $I(t)$  and  $i(t)$  to  $V(t)$ . Hint: consider using Thevenin or Norton equivalent networks to simplify the work.
- (B) Find the capacitor voltage  $v(t)$  and the inductor current  $i(t)$  at both  $t = 0^+$  and  $t = \infty$ . One way to find the states at  $t = 0^+$  is to integrate the corresponding differential equations from  $t = 0^-$  to  $t = 0^+$  under the assumption that each state remains finite during that time; you should justify this assumption. Then, substitute the initial conditions at  $t = 0^-$  into the results to determine the states at  $t = 0^+$ . Try to determine the states at  $t = \infty$  through physical, rather than mathematical, reasoning.
- (C) Next, find the time constant by which each state goes from its initial value at  $t = 0^+$  to its final value at  $t = \infty$ .
- (D) Using the previous results, and without necessarily solving the differential equations directly, construct  $v(t)$  and  $i(t)$  for  $t \geq 0$ .
- (E) Verify that the solutions to Part (D) are correct by substituting them into the differential equation found in Part (A).

