

Massachusetts Institute of Technology
 Department of Electrical Engineering and Computer Science


6.002 – Circuits and Electronics
 Spring 2003

Handout S03-007 - Homework #1

Issued: Wed. Feb 5
 Due: Fri. Feb 14


In Problems 1.1 and 1.2 use the convention that a logical one corresponds to a high voltage level and a logical zero corresponds to a low voltage level. Assume that the high voltage level is much greater than the threshold voltage. When the voltage v_A associated with the Boolean variable A is high (3 volts), $A = 1$; when v_A is low (≈ 0 volts), $A = 0$. The same relationship holds with v_C and C .

Problem 1.1:

 

- 1) For each circuit above, generate a truth table which shows how the output depends on the input(s).
- 2) Assume that the “on” resistance of the MOSFETs is 100Ω . What is the value of the output voltage v_C for $C = 0$ and for $C = 1$?

 Problem 1.4: Consider the inverter below:




Assume that the FET has an “on” resistance of 200Ω and a threshold voltage of $2.5 \pm 0.1V$. The ± 0.1 deviation accounts for device-to-device variations. The static discipline for the chip in which this FET will be used is

$$\text{INPUT} \begin{cases} v_{IH} = 4V \\ v_{IL} = 2V \end{cases} \quad \text{OUTPUT} \begin{cases} v_{OH} = 5V \\ v_{OL} = 0.5V \end{cases}$$

- 1) If R is too small, the inverter will not satisfy the static discipline. What is the minimum permissible value of R ?
- 2) What are the noise margins for each logical state of the input?
- 3) What is the width of the forbidden region?
- 4) What part(s) of the static discipline would you change to make the 0 and 1 noise margins equal? How does this change the forbidden region?

Problem 1.5: Determine the voltage v_X in the circuit below. **Hint:** Define a reference node and write a pair of node equations.

 

Problem 1.6: For the circuit below, write a set of three KCL equations sufficient to solve for the node to reference voltages e_1, e_2 , and e_3 . Express your equations in the form:

$$\begin{aligned} [\dots]e_1 - [\dots]e_2 - [\dots]e_3 &= \text{source terms} \\ -[\dots]e_1 + [\dots]e_2 - [\dots]e_3 &= \text{source terms} \\ -[\dots]e_1 - [\dots]e_2 + [\dots]e_3 &= \text{source terms} \end{aligned}$$

where the brackets contain sums of conductances.

Do not solve these equations!

