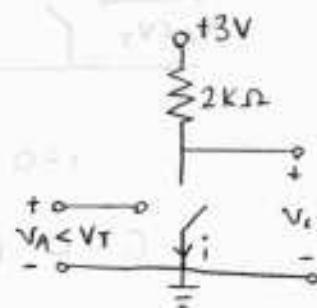


HW 1 Solutions


1.1 (i) inverter

A	C
0	1
1	0

2) $C = 1 \ (A=0)$: $C=0 \ (A=1)$:



$$i = 0 \\ \Rightarrow V_c = 3V$$

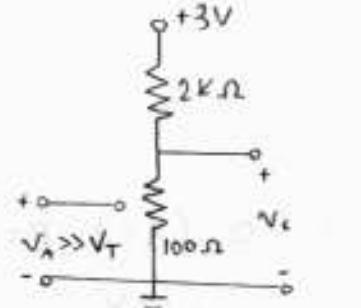


$$V_c = 3V \frac{100\Omega}{2100\Omega} \\ = 17V$$

(ii) nand gate

A	B	C
0	0	1
0	1	1
1	0	1


2) $C = 1 \ (A=B=0)$:

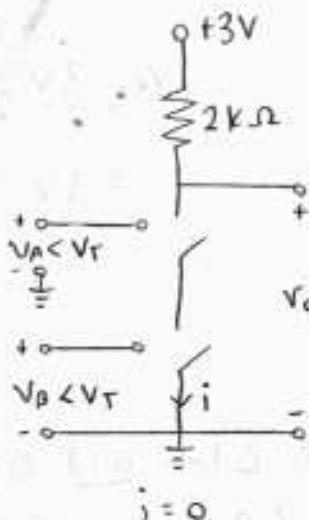

$$i = 0 \\ \Rightarrow V_c = 3V$$

Some situation
with $A=1$ or $B=1$
(but not both)

$C=0 \ (A=B=1)$:

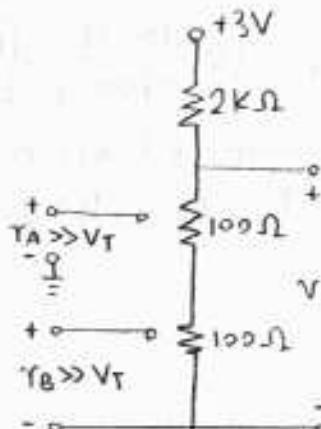


$$V_c = 3V \frac{200\Omega}{2200\Omega} \\ = 3/11V$$


(iii) nor gate

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

2) $C = 1 \quad (A = B = 0)$:

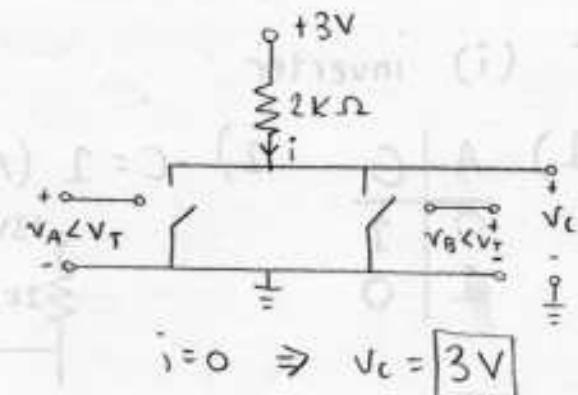


$C = 0 \quad (A = 1, B = 0)$:

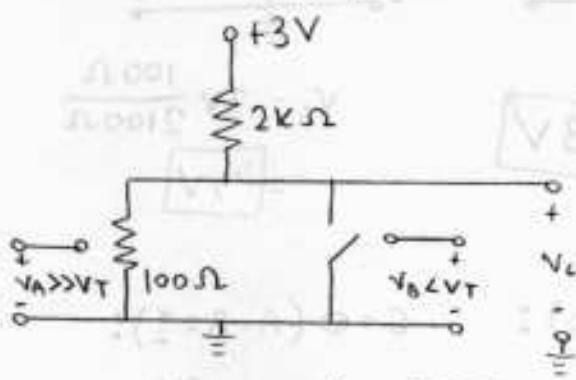

$$V_C = 3V \frac{100\Omega}{2100\Omega} = \boxed{\frac{1}{7}V}$$

Same situation
for $A = 0, B = 1$

$C = 0 \quad (A = B = 1)$:

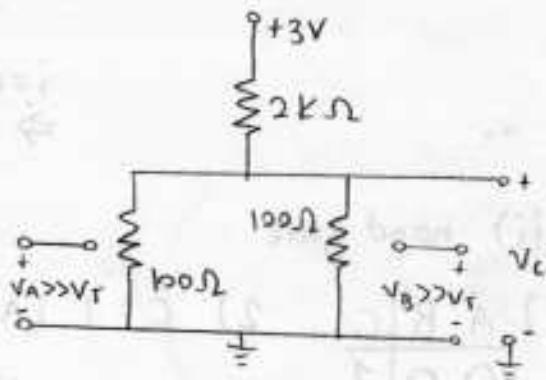

$$V_C = 3V \frac{100 \parallel 100\Omega}{2k\Omega + 100 \parallel 100\Omega} = 3V \frac{50\Omega}{2050\Omega} = \boxed{\frac{3}{41}V}$$

1.2

1) Logic: X is high if C low and D high and
(A low or B high):


$$X = \overline{C} \wedge D \wedge (\overline{A} \vee B)$$

$$= \overline{C \vee D} \wedge \overline{A \wedge \overline{B}}$$

A	0 0 0 0	0 0 0 0	1 1 1 1	1 1 1 1
B	0 0 0 0	1 1 1 1	0 0 0 0	1 1 1 1
C	0 0 1 1	0 0 1 1	0 0 1 1	0 0 1 1
D	0 1 0 1	0 1 0 1	0 1 0 1	0 1 0 1
$\bar{A} \vee B$	1 1 1 1	1 1 1 1	0 0 0 0	1 1 1 1
$\bar{C} \wedge D$	0 1 0 0	0 1 0 0	0 1 0 0	0 1 0 0
X	0 1 0 0	0 1 0 0	0 0 0 0	0 1 0 0

2) Lowest value:

$$A = \bar{B} = C = \bar{D} = 1$$

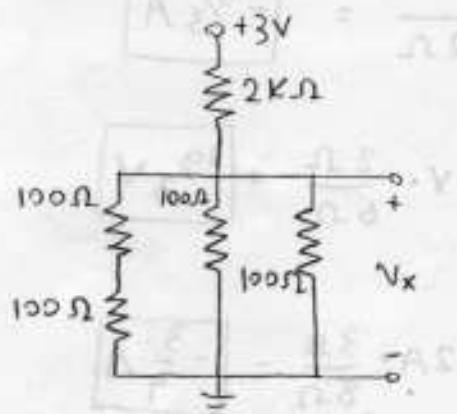


$$\begin{aligned} V_x &= \frac{200 \parallel 100 \parallel 100 \Omega}{2k\Omega + 200 \parallel 100 \parallel 100 \Omega} \cdot 3V \\ &= \frac{200 \parallel 50 \Omega}{2k\Omega + 200 \parallel 50 \Omega} \cdot 3V \\ &= \frac{40 \Omega}{2040 \Omega} \cdot 3V = 17V \end{aligned}$$

Highest value:

$$A = \bar{B} = 1$$

$$C = \bar{D} = 0$$

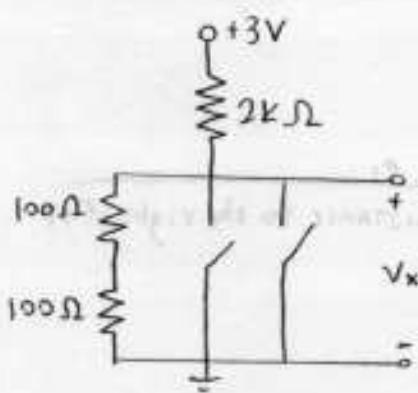

$$\begin{aligned} V_x &= \frac{200 \Omega}{2200 \Omega} \cdot 3V \\ &= 11V \end{aligned}$$

$$17V \leq V_x \leq 11V$$

3) Power: $P = IV = \frac{V^2}{R}$

V: voltage across circuit
 I: total current thru circuit
 R: total resistance of circuit

$V = +3V$

\Rightarrow minimum R produces max. power
 from (2) minimum R is 2040Ω . ($A=B=C=D=1$)

$$\Rightarrow P = \frac{(3V)^2}{2040\Omega} = \boxed{\frac{3}{680}W} \approx 4.4 \text{ mW}$$


1.3

(i) $i_Y = -\frac{10V}{4\Omega + 3116\Omega} = \frac{-10V}{4\Omega + 2\Omega} = \boxed{-\frac{5}{3}A}$

$$v_X = 10V \cdot \frac{3116\Omega}{4\Omega + 3116\Omega} = 10V \cdot \frac{2\Omega}{6\Omega} = \boxed{\frac{10}{3}V}$$

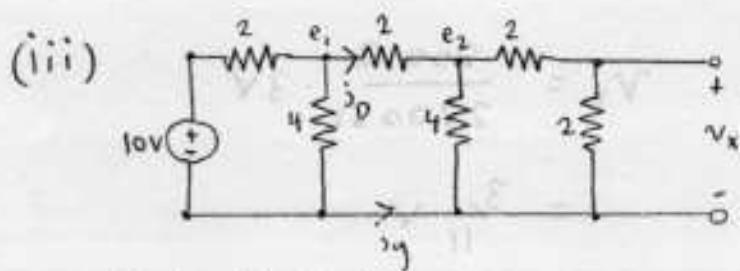(ii) $i_Y = -2A \cdot \frac{1\Omega + 2\Omega}{5\Omega + 1\Omega + 2\Omega} = -2A \cdot \frac{3\Omega}{8\Omega} = \boxed{-\frac{3}{4}A}$

$$v_X = 2\Omega \cdot (-2A - i_Y) = (2\Omega)(-\frac{5}{4}A) = \boxed{-\frac{5}{2}V}$$



Note that $i_Y = -i_D$. $i_D = \frac{e_1}{\text{resistance to the right of } e_1}$

$e_1 = 10V$ resistance to the right of e_1 / total resistance

$$\begin{aligned}
 \text{Total resistance } R_{\text{TOT}} &= 2 + (4 \parallel (2 + (4 \parallel (2+2)))) \\
 &= 2 + (4 \parallel (2 + (4 \parallel 4))) \\
 &= 2 + (4 \parallel (2+2)) \\
 &= 2 + 2 = 4 \Omega
 \end{aligned}$$

(branch current)

resistance right
of e_1


$$R_{e_1} = 2 + 4 \parallel (2+2) = 2+2 = 4 \Omega$$

$$e_1 = 10V \frac{R_{e_1}}{R_{\text{TOT}}} = 10V \frac{2\Omega}{4\Omega} = 5V$$

$$i_y = -i_0 = -\frac{e_1}{R_{e_1}} = -\frac{5V}{4\Omega} = -1.25A$$

$$v_x = e_2 \frac{2\Omega}{4\Omega} = \frac{1}{2} e_2, \quad e_2 = e_1 \frac{4 \parallel (2+2)\Omega}{2+4 \parallel (2+2)\Omega} = e_1 \frac{2\Omega}{4\Omega} = \frac{1}{2} e_1$$
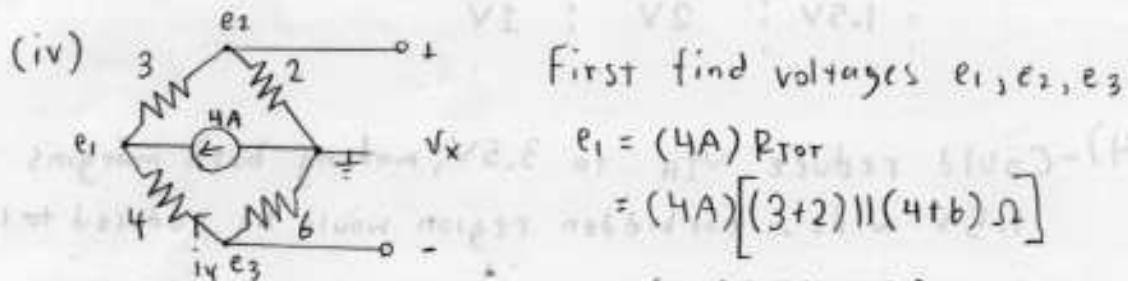
$$v_x = \frac{1}{2} e_2 = \frac{1}{4} e_1 = \frac{5}{4} V$$



$$\begin{aligned}
 e_1 &= (4A) R_{\text{TOT}} \\
 &= (4A) [(3+2) \parallel (4+6) \Omega]
 \end{aligned}$$

$$= (4A)(5 \parallel 10 \Omega) = 4A \cdot \frac{5}{15} \Omega = \frac{40}{3} V$$

$$e_2 = e_1 \cdot \frac{2\Omega}{(2+3)\Omega} = \frac{2}{5} \cdot \frac{40}{3} V = \frac{16}{3} V$$

$$e_3 = e_1 \cdot \frac{6\Omega}{(4+6)\Omega} = \frac{6}{10} \cdot \frac{40}{3} V = 8V \quad v_x = e_2 - e_3 = \frac{16}{3} V - 8V = -\frac{8}{3} V$$

$$i_y = -\frac{e_1}{(4+6)\Omega} = -\frac{40}{30} A = -\frac{4}{3} A$$

1.4 1) If $V_I < V_{IL}$, $V_o = +6V$ (switch open)
no dependence on R

If $V_I > V_{IH}$, $V_o = +6V \cdot \frac{R_{ON}}{R_{ON}+R}$ (switch closed)

need $V_o < V_{OL}$: $6V \cdot \frac{200}{200+R} < 0.5V$


$$1200 < 0.5(200+R)$$

$$1100 < 0.5R$$

$$R > 2200$$


2)

3)

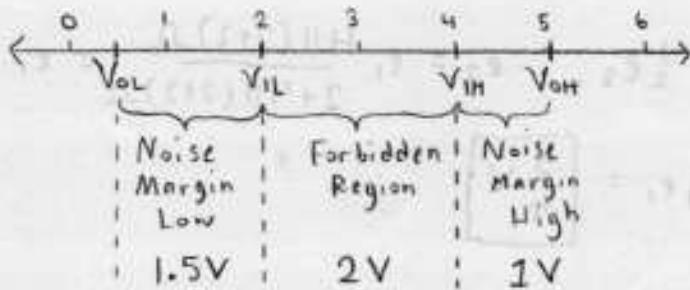

- 4) - Could reduce V_{IH} to 3.5V, making both margins 1.5V wide. Forbidden region would be reduced to 1.5V
- Could reduce V_{IL} to 1.5V, making both margins 1V wide. Forbidden region would be enlarged to 2.5V
- Could raise V_{OH} to 5.5V, making both margins 1.5V wide. Forbidden region would be unchanged
- Could raise V_{OL} to 1V, making both margins 1V wide. Forbidden region unchanged.
- Other possibilities as well

1.5

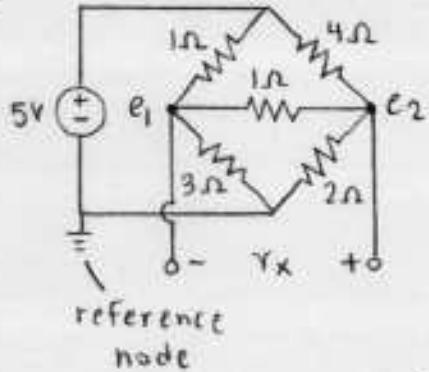Nodes e_1, e_2 KCL at e_1 :

$$\frac{5V - e_1}{1\Omega} + \frac{e_2 - e_1}{1\Omega} + \frac{-e_1}{3\Omega} = 0$$

KCL at e_2 :

$$\frac{5V - e_2}{4\Omega} + \frac{e_1 - e_2}{1\Omega} + \frac{-e_2}{2\Omega} = 0$$

$$5 - e_1 + e_2 - e_1 - \frac{e_1}{3} = 0$$

$$5 - \frac{7}{3}e_1 + e_2 = 0$$

$$e_2 = \frac{7}{3}e_1 - 5$$

$$\frac{5}{4} - \frac{e_2}{4} + e_1 - e_2 - \frac{e_2}{2} = 0$$

$$\frac{5}{4} - \frac{7}{4}e_2 + e_1 = 0$$

$$\text{substitute } \rightarrow \frac{5}{4} - \frac{49}{12}e_1 + \frac{35}{4} + e_1 = 0$$

$$10 = \frac{37}{12}e_1 \quad e_1 = \frac{120}{37}V$$

$$e_2 = \frac{7}{3} \cdot \frac{120}{37} - 5 = \frac{95}{37}V$$

1.6 KCL at e_1 : $I_1 + (-G_1 e_1) + G_2 (e_2 - e_1) = 0$

$$e_1 (-G_1 - G_2) + e_2 G_2 = -I_1 \quad ①$$

KCL at e_2 : $G_2 (e_1 - e_2) + G_3 (V_1 - e_2) + G_2 (e_3 - e_2) = 0$

$$e_1 G_2 + e_2 (-G_3 - 2G_2) + e_3 G_2 = -G_3 V_1 \quad ②$$

KCL at e_3 : $-I_2 + (-G_4 e_3) + G_2 (e_2 - e_3) = 0$

$$e_2 G_2 + e_3 (-G_2 - G_4) = I_2 \quad ③$$

$$\begin{aligned} ① & \left\{ \begin{array}{l} (-G_1 - G_2)e_1 + (G_2)e_2 + \\ (G_2)e_1 + (-G_3 - 2G_2)e_2 + (G_2)e_3 = -G_3 V_1 \end{array} \right. \\ ② & \left. \begin{array}{l} (G_2)e_2 + (-G_2 - G_4)e_3 = I_2 \end{array} \right. \end{aligned}$$