


NOTES FOR 6.002 LECTURE #4 FEBRUARY 13, 2003

P.E. GRAY'S OFFICE HOURS: EVERY WEDNESDAY 3-5 PM IN 38-344 OR BY ARRANGEMENT (3-4665)


READINGS THIS WEEK: SECTIONS 3.1-3.3, 3.5

NOW, FOLLOWING TOOLS FOR ANALYSIS OF LUMPED ELECTRIC CIRCUITS, TAKE UP TWO THEOREMS APPLICABLE TO NETWORKS COMPRISED OF LINEAR ELEMENTS.


STRICT DEFINITION OF LINEARITY:

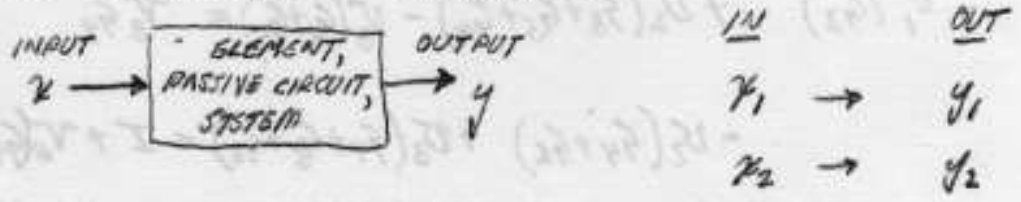

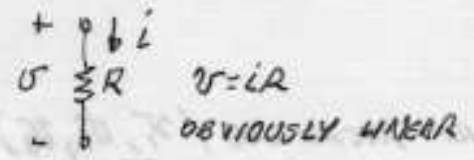THE BOX IS LINEAR IF:  $ax_1 + bx_2 \rightarrow ay_1 + by_2$



UNLESS a, b ARE CONSTANTS

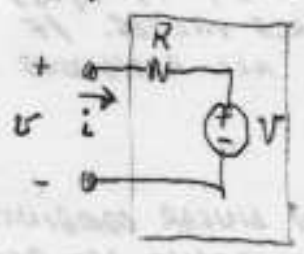


PASSIVE - AN INDEPENDENT SOURCE IS PRESENT

WE WILL SOON INTRODUCE OTHER LINEAR ELEMENTS: INDUCTORS, CAPACITORS, DEPENDENT SOURCES.

DEVELOP THE SUPERPOSITION PRINCIPLE, FORMALLY A THEOREM

WHAT FOLLOWS IS A PLAUSIBILITY ARGUMENT

CONSIDER CIRCUIT OF LECTURE #3:

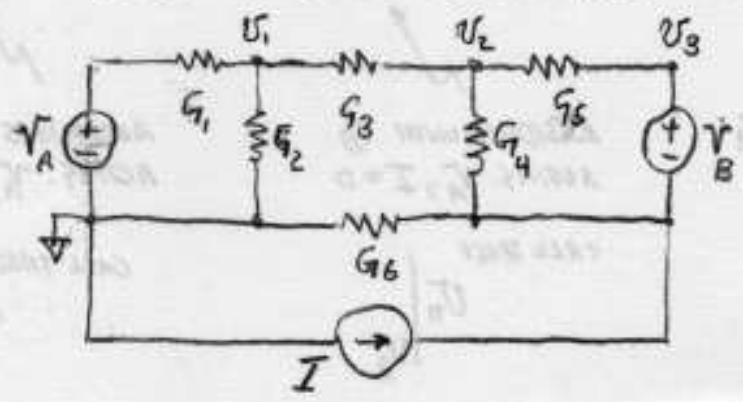

THE 3 KCL EQUATIONS ARE:

$$(V_1 - V_A) g_1 + V_1 g_2 + (V_1 - V_2) g_3 = 0$$

$$(V_2 - V_1) g_3 + (V_2 - V_3) g_5 + [V_2 - (V_3 - V_B)] g_4 = 0$$

$$(V_3 - V_2) g_5 + (V_3 - V_B) g_6 - I + [(V_3 - V_B) - V_2] g_4 = 0$$

REWRITTEN, COLLECTING TERMS:

$$V_1 (g_1 + g_2 + g_3) - V_2 (g_3) = V_A g_1$$

$$-V_1 (g_3) + V_2 (g_3 + g_5 + g_4) - V_3 (g_4 + g_5) = V_B g_4$$

$$-V_2 (g_4 + g_5) + V_3 (g_4 + g_5 + g_6) = I + V_B (g_4 + g_6)$$

NOTE SYMMETRY ACROSS THE DIAGONAL AND NATURE OF COEFFICIENTS.

NOTE ALSO THAT THE NETWORK RESPONSES ( $V_1, V_2, V_3$ ) ARE LINEARLY RELATED TO THE THREE SOURCE VALUES. IF ALL SOURCE VALUES ARE MULTIPLIED BY  $k$ , ALL RESPONSES ARE  $k$  TIME AS WELL.

BECAUSE THE SOURCES APPEAR ONLY IN LINEAR COMBINATIONS (AT MOST) THE RESPONSES FOR EACH SOURCE ACTING ALONE ARE READILY DETERMINED. THREE SINGLE-SOURCE EQUATION SETS:

①

②

③

$$\begin{bmatrix} \text{CONDUCTANCE} \\ \text{MATRIX} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} V_A g_1 \\ 0 \\ 0 \end{bmatrix} \quad \begin{bmatrix} \text{DITTO} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ V_B g_4 \\ V_B (g_4 + g_6) \end{bmatrix} \quad \begin{bmatrix} \text{DITTO} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ I \end{bmatrix}$$

RESPONSES WITH  $V_A$  ACTING,  $V_B, I = 0$

CALL THESE

$$V_m \Big|_{V_A}$$

RESPONSES WITH  $V_B$  ACTING,  $V_A, I = 0$


CALL THESE

$$V_m \Big|_{V_B}$$

RESPONSES WITH  $I$  ACTING,  $V_A, V_B = 0$

CALL THESE

$$V_m \Big|_I$$

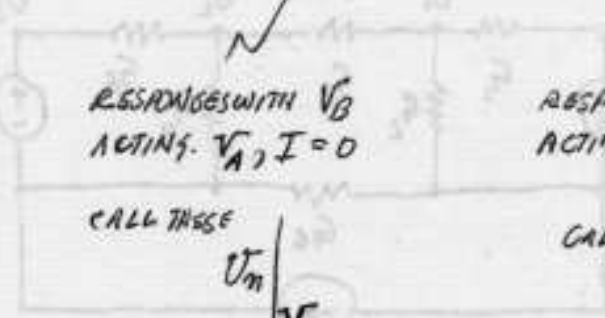


Clearly the complete responses are:  $V_n = V_n|_{V_A} + V_n|_{V_B} + V_n|_I$   
 I.E. THE SUM OF THE COMPONENT RESPONSES

SUPERPOSITION PRINCIPLE:

THE RESPONSE OF A NETWORK COMPRISED OF LINEAR ELEMENTS WHICH CONTAINS  $n$  INDEPENDENT SOURCES IS EQUAL TO THE RESPONSE OF  $n$  DIFFERENT NETWORKS EACH OF WHICH HAS ONLY ONE SOURCE ACTING, WITH THE OTHER SOURCES SHUT OFF.

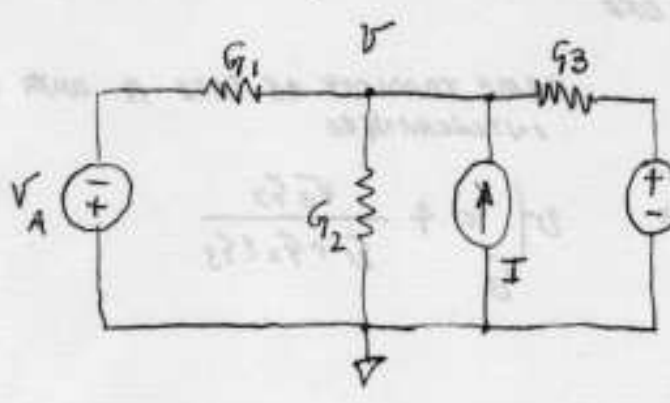CONSIDER AN ALGEBRAICALLY-SIMPLER EXAMPLE:



KCL AT V:  $(V+V_A)G_1 + VG_2 + (V-V_B)G_3 - I = 0$

$(G_1 + G_2 + G_3)V = -V_A G_1 + V_B G_3 + I$

$V = \frac{-V_A G_1 + V_B G_3 + I}{G_1 + G_2 + G_3}$



THE NETWORK RESPONSE

NOW CONSIDER THE NETWORK UNDER THREE CONDITIONS, EACH WITH ONE SOURCE ACTING, THE OTHER TWO TURNED OFF.

WHAT DOES IT MEAN TO TURN A SOURCE OFF?


VOLTAGE SOURCE

CURRENT SOURCE

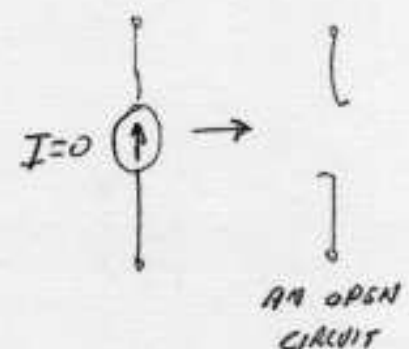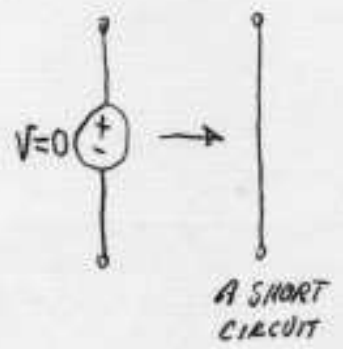

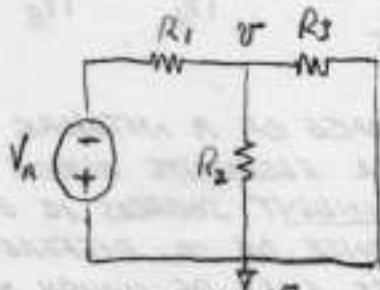(4)

CASE A:  $V_A$  ACTIVE,  $V_B, I$  OFF ( $R_2 = 1/g_2$ )




$I$  REMOVED,  $V_B$  REPLACED BY A SHORT

BY INSPECTION: 
$$V = -V_A \frac{R_2 // R_3}{R_1 + R_2 // R_3} = -V_A \frac{\frac{R_2 R_3}{R_2 + R_3}}{\frac{R_2 R_3}{R_2 + R_3} + R_1}$$

$$V \Big|_{V_A} = -V_A \frac{R_2 R_3}{R_2 R_3 + R_1 R_2 + R_1 R_3} = \frac{-V_A g_1}{g_1 + g_3 + g_2}$$

MULTIPLY NUMERATOR AND DENOMINATOR BY  $g_1 g_2 g_3$

CASE B:  $V_B$  ACTIVE,  $V_A, I$  OFF

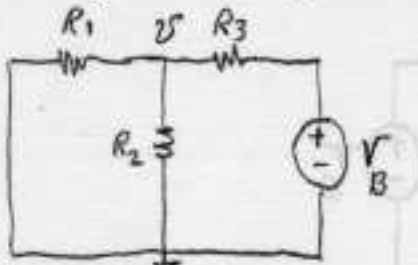


$V_A$  REPLACED BY A SHORT  
 $I$  REMOVED

SAME TOPOLOGY AS CASE A WITH  $R_1, R_3$  INTERCHANGED


$$V \Big|_{V_B} = + \frac{V_B g_3}{g_1 + g_2 + g_3}$$

CASE C:  $I$  ACTIVE,  $V_A, V_B$  OFF

THREE CONDUCTANCES IN PARALLEL

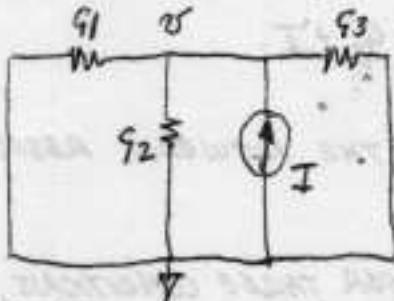

$V_A, V_B$  REPLACED BY SHORTS

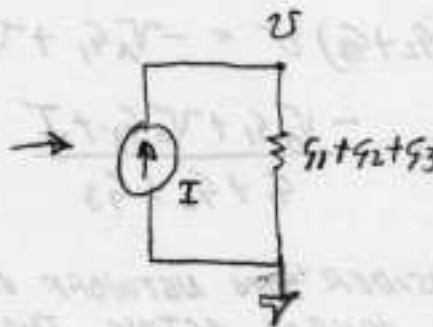

$$V \Big|_I = \frac{I}{g_1 + g_2 + g_3}$$

THE THREE COMPONENTS ADDED TOGETHER GIVE THE COMPLETE RESPONSE