

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science


6.002 – Circuits and Electronics
Spring 2003

Handout S03-021 - Homework #4


Issued: Wed. Feb 26
Due: Fri. Mar 7

Problem 4.1: The nonlinear element in the circuit below has the i - v characteristics shown in the graph.

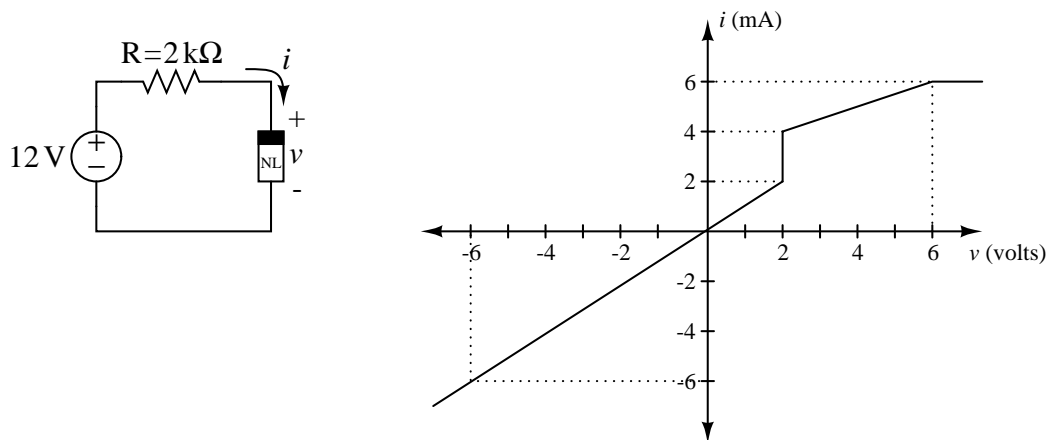
(A) Estimate values of the voltage v across and the current i through the element.



(B) Assume the nonlinear device is connected upside down as shown below. What are the values of v and i in this case?

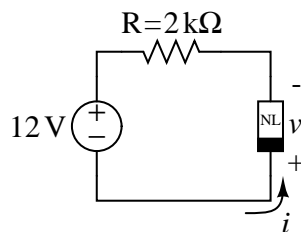

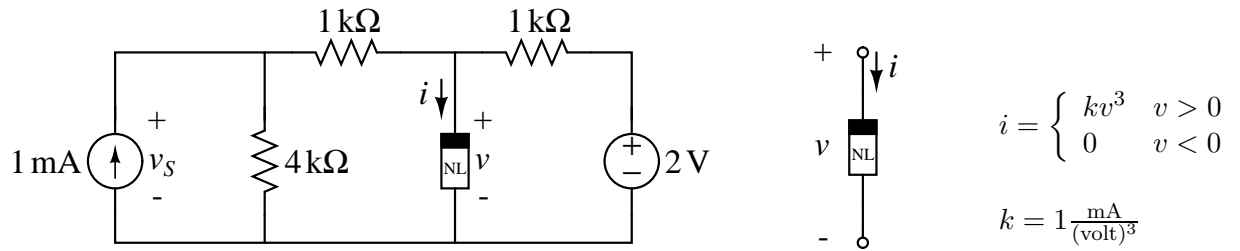Problem 4.2: The circuit below contains a single nonlinear element whose i - v characteristic is indicated.



- (A) Determine the voltage v and the current i .
- (B) Determine the voltage v_S across the current source.

Hint: Think about Thevenin and/or Norton equivalent circuits.