

(S03-030)

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits and Electronics
Spring 2003

Handout S03-025 - Quiz # 1

Wednesday March 5, 2003

WITH SOLUTIONS

Name: _____

Recitation Instructor (circle one):

Baldo

Hutchinson

Kolodziejski

Schindall

Wilson

Recitation Hour (circle one):

9

10

11

12

1

2


ALL PROBLEMS CARRY THE SAME WEIGHT

Problem	Points	Score	Grader
1	25		
2	25		
3	25		
4	25		
Total	100		

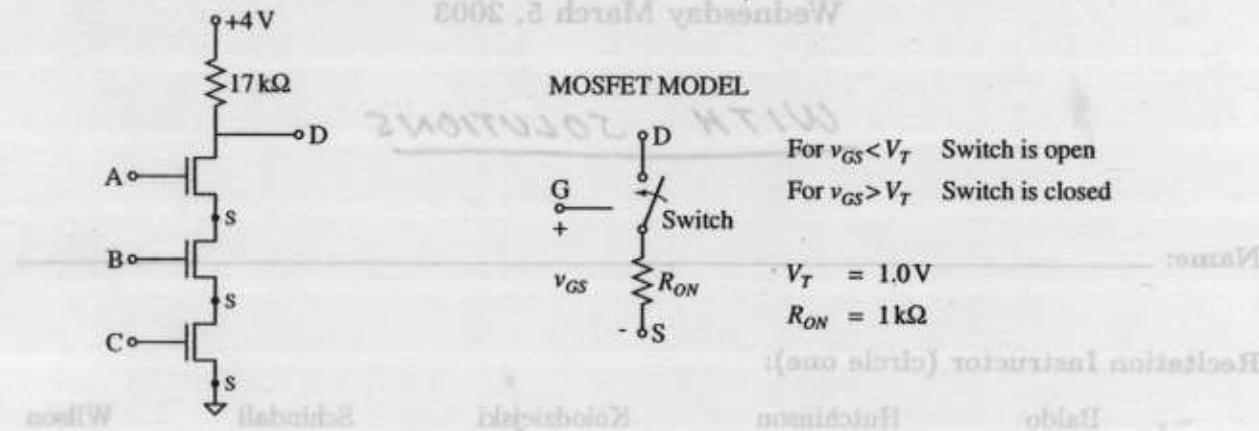PROBLEM 1

E003 - Circuits and Electronics

Assume the convention that a high voltage level denotes a Boolean 1, and a low voltage level denotes a Boolean 0.



- (A) What is the logical function of this circuit? Express your answer as a boolean function or as a truth table.

This is a THREE-INPUT NOR GATE $D = \overline{ABC}$

TRUTH TABLE:

ALL PROBLEMS CARRY THE SAME WEIGHT


A	B	C	D
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Problem	Points	Score	Grade
1	25		
2	25		
3	25		
4	25		
Total	100		

Name: _____

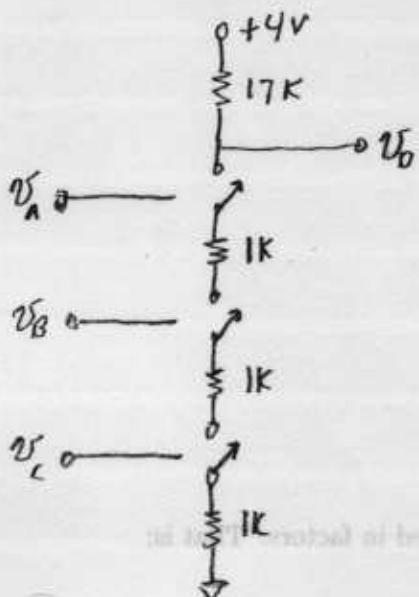- (B) What minimum value of 1-state voltage at the inputs will ensure proper operation of the circuit?

THE CIRCUIT WITH THE SR MODEL INSERTED IS:



WITH ALL INPUTS HIGH (ALL SWITCHES CLOSED)

$$\text{THE CURRENT DOWN THE FETS IS } I_D = \frac{4}{17 + 3 \times 1} = 0.2 \text{ mA}$$

THUS THERE IS A 0.2 VOLT DROP ACROSS EACH FET ($V_{DS} = 0.2V$)

THE SOURCE TERMINAL OF THE TOP FET IS $0.2 \times 2 = 0.4V$ ABOVE GROUND. THE MINIMUM ONE-STATE INPUT VOLTAGE IS SET BY THE TOP FET AND IS $0.4V + V_T = 1.4$ VOLTS


- (C) What is the value of the 0-state output voltage?

THE ZERO-STATE OUTPUT VOLTAGE IS AT THE DRAIN OF THE TOP FET WHEN ALL SWITCHES ARE CLOSED. IT IS $0.2 \times 3 = 0.6$ VOLTS

Name: _____

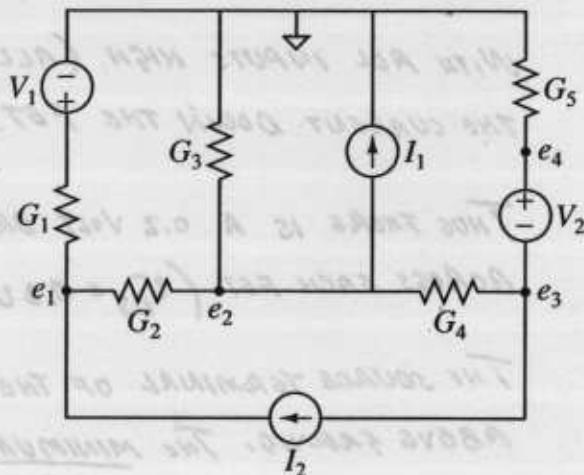PROBLEM 2

Use the node-to-reference voltages indicated on the circuit below to write a set of independent node equations (KCL statements) sufficient to solve for the unknown voltages. Do not solve them.



Please put your equations in a form in which all conductances are collected in factors. That is:

$$[\text{conductances}] \cdot e_1 \pm [\text{conductances}] \cdot e_2 \pm \dots \text{ ETC.}$$

NOTE THAT e_3 AND e_4 ARE NOT INDEPENDENT BUT ARE CONSTRAINED BY V_2
 $e_4 = e_3 + V_2$

KCL AT e_1, e_2, e_3 YIELDS (ADDITION CURRENTS OUT)

$$(e_1 - V_1)g_1 + (e_1 - e_2)g_2 - I_2 = 0$$

$$e_2 g_3 + (e_2 - e_1)g_2 + (e_2 - e_3)g_4 + I_1 = 0$$

$$(e_3 - e_2)g_4 + (e_3 + V_2)g_5 + I_2 = 0$$

$\underbrace{}_{= e_4}$

COLLECTING TERMS:

$$(g_1 + g_2)e_1 - (g_2)e_2 = I_2 + g_1 V_1$$


$$-(g_2)e_1 + (g_3 + g_2 + g_4)e_2 - (g_4)e_3 = -I_1$$

$$-(g_4)e_2 + (g_4 + g_5)e_3 = -I_2 - g_5 V_2$$

Name: _____

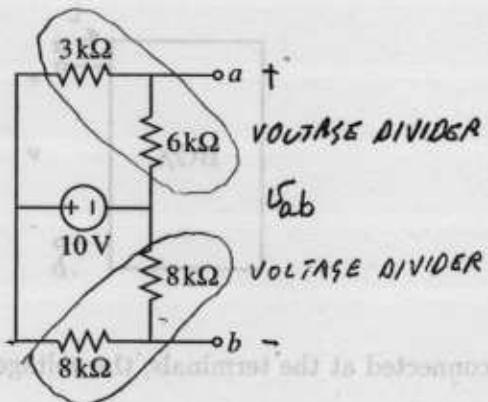PROBLEM 3

Devise Thevenin And Norton equivalent circuits at terminals *a*, *b* for the circuit below. Be sure to specify units and polarities.




$$\text{DETERMINING } V_{OC} = V_{ab}$$

$$V_{ab} = +10 \times \frac{6}{3+6} - 10 \times \frac{8}{8+8} = +\frac{20}{3} - 5$$

$$= +\underline{\underline{\frac{5}{3} \text{ VOLTS}}}$$

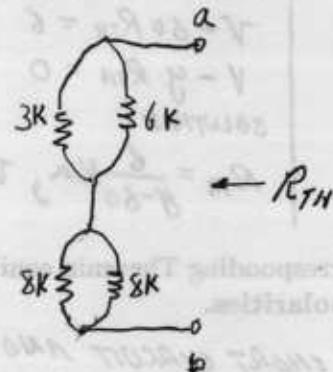
WITH THE 10V SOURCE REPLACED BY A SHORT-CIRCUIT, THE CIRCUIT REDUCES TO:




$$\text{BY INSPECTION, } R_{TH} = 3//6 + 8//8 = 2+4 = \underline{\underline{6 \text{ K}\Omega}}$$

$$I_{SC} = \frac{V_{OC}}{R_{TH}} = \frac{\frac{5}{3}}{6 \text{ K}\Omega} = \underline{\underline{\frac{5}{18} \text{ mA}}}$$

THEVENIN EQUIVALENT

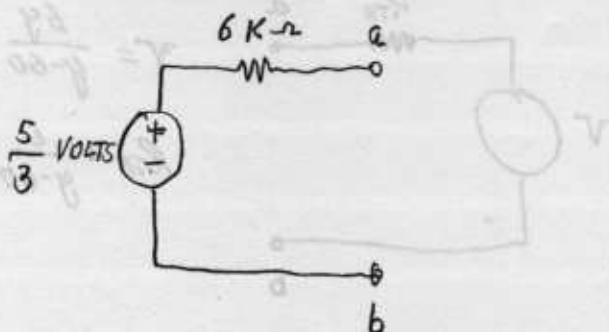


NORTON EQUIVALENT

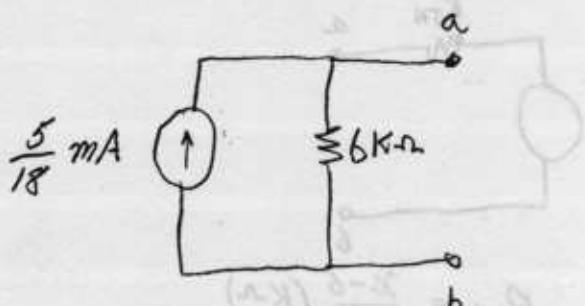

Name: _____

PROBLEM 4

The box in the circuit below contains linear elements (resistances) and independent sources.

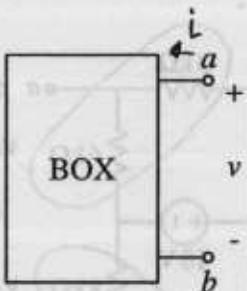

PROBLEM 4

With a 100Ω resistor connected at the terminals, the voltage is $v = 6$ Volts.

$$i = \frac{-6}{100} = -60 \text{ mA}$$

One other measurement suffices to determine the Thevenin equivalent circuit of the box.

- (A) Decide what circuit element, if any, you would connect, and describe the one measurement you would make.

ANY RESISTANCE NOT 100Ω , A SHORT-CIRCUIT, AN OPEN-CIRCUIT OR
A SOURCE OF KNOWN VOLTAGE OR CURRENT WILL DO.

EQUATIONS FOR SHORT-CIRCUIT CASE

$$V - 60R_{TH} = 6 \quad R_{TH} \text{ IN } K\Omega$$


$$V - 60R_{TH} = 0$$

SOLUTION:

$$R_{TH} = \frac{6}{60} K\Omega, \quad V = \frac{6}{60} \text{ VOLTS}$$

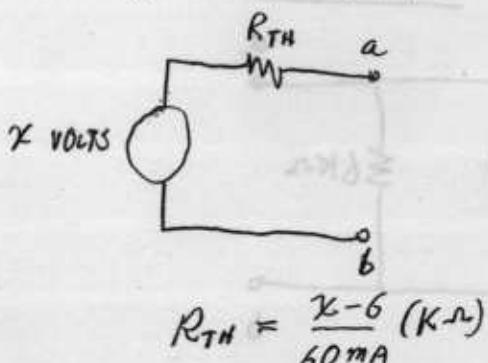
- (B) Assume a numerical value for that measurement and draw the corresponding Thevenin equivalent circuit with element values attached. Specify units and polarities.

FOR AN OPEN CIRCUIT AND V
ASSUMED TO BE 12 VOLTS,
THEVENIN EQUIVALENT IS



$$R_{TH} = \frac{12 - 6}{60 \text{ mA}} (K\Omega)$$

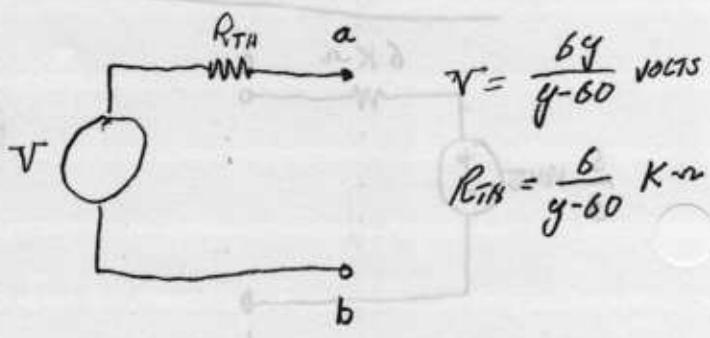FOR A SHORT CIRCUIT AND I_{SC}
ASSUMED TO BE 60 mA , THE
THEVENIN EQUIVALENT IS:



$$R_{TH} = \frac{6}{60 \text{ mA}} K\Omega$$

NOTE: IF $V < 6$ VOLTS OR $I_{SC} < 60 \text{ mA}$, R_{TH} WILL BE NEGATIVE. OK UNTIL YOU ASK FOR ONE
AT THE INSTRUMENT ROOM