


Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.002 – Circuits and Electronics  
Spring 2003

Handout S03-032 - Homework #6

Issued: Wed. Mar 12  
Due: Fri. Mar 21

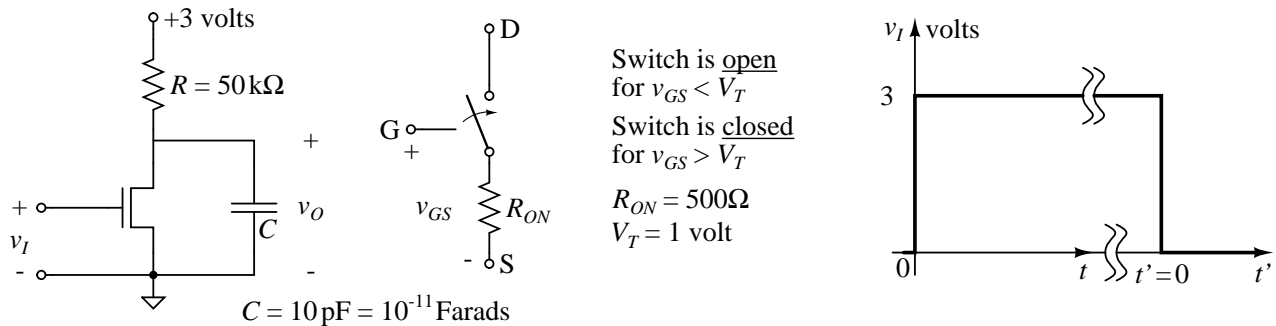**Problem 6.1:** The FET in the circuit below can be modeled with the switch-resistor (SR) model shown.




For  $t < 0$  the input voltage  $v_I$  is zero. At  $t = 0$   $v_I$  changes instantly to  $v_I = 3\text{V}$ . A long time later at a time  $t' = 0$ , the input voltage changes instantly to zero, as shown in the sketch above.

- (A) What is  $v_O$  for  $t < 0$ ?
- (B) Draw a circuit diagram which incorporates the SR model and applies for  $t > 0$  (in the interval of time for  $t' < 0$ ).
- (C) Write a differential equation which describes  $v_O(t)$ .

**Hint:** Think node equation.

- (D) Solve this equation for  $t > 0$ . Sketch and dimension your result and label initial and final (asymptotic) values of  $v_O(t)$  and mark the numerical value of the time constant on the time axis.
- (E) Repeat Parts (B) (C) and (D) for the second interval of time starting at  $t' = 0$ . Note that the differential equation changes.
- (F) Explain why the two time constants differ by more than an order of magnitude.

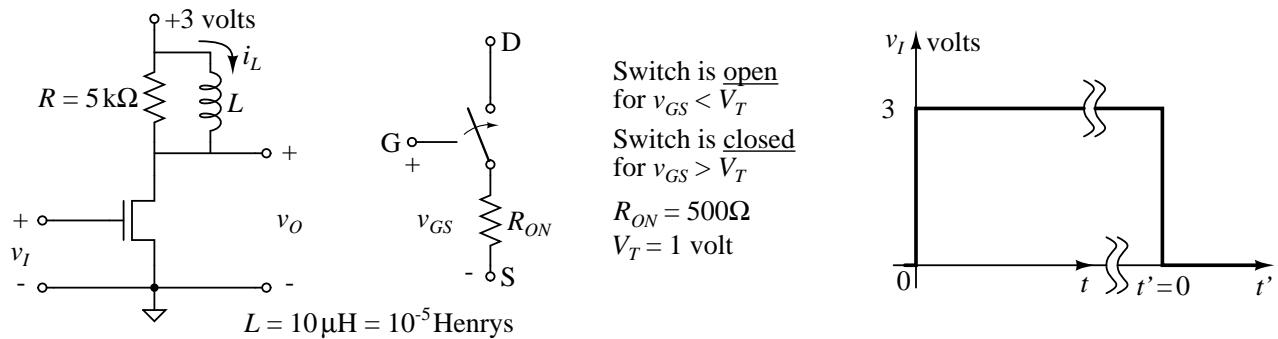**Problem 6.2:** The FET in this circuit is the same as that in problem 6.1 and can be describe by the same SR model. The waveform for  $v_I$  is the same as in Problem 6.1.




- (A) What are the values of  $v_O(t)$  and  $i_L(t)$  for  $t < 0$ ?
- (B) Write a differential equation for  $i_L(t)$  which applies in the first interval of time where  $t > 0$ .

**Hint:** To avoid getting tangled up in this write a node equation at the drain terminal of the FET in terms of  $v_O$  and  $i_L$ . Then use the defining constituent relation for the inductor to replace  $v_O$ .

- (C) Solve this equation for  $i_L(t)$  for  $t > 0$ . From this result derive an expression for  $v_O(t)$ . Sketch and dimension both curves, labeling initial and final values and the numerical value of the time constant.
- (D) Repeat parts (A), (B), and (C) for the second interval of time starting at  $t' = 0$ . Note that the differential equation changes.
- (E) Explain why the value of  $v_O$  at  $t' = 0+$  is so large.

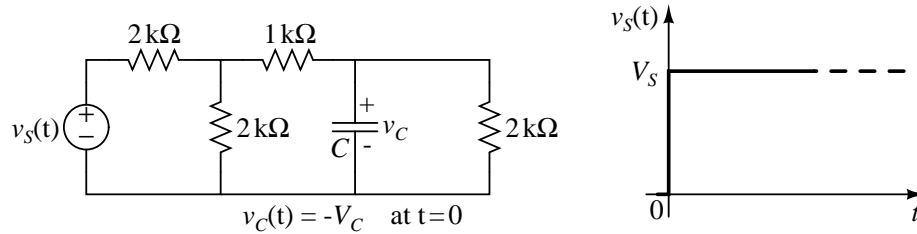**Problem 6.3:** In the circuit below  $v_I(t)$  is a step of magnitude  $V_S$  at  $t = 0$ . That is,  $v_S(t) = V_S u_{-1}(t)$ . At  $t = 0$  the voltage  $v_C(t)$  across the capacitor is  $-V_C$  volts as a result of some previous excitation.



(A) Write a differential equation for  $v_C(t)$  for  $t > 0$ .

**Hint:** Recall problem 4.2 and make use of a Thevenin or Norton equivalent before forming the differential equation.

(B) Let  $C = 1\mu\text{F} = 10^{-6}\text{F}$  and determine the value of the time constant which governs the transient response of this circuit.

(C) Solve the differential equation from Part A) for  $v_C(t)$  for  $t > 0$ . Sketch and dimension your result and label initial and final values.

(D) There is a value of  $v_C(0)$  for which there is no transient. What is it?