


NOTES FOR 6.002 LECTURE # 12, TUESDAY, MARCH 12, 2003

LABORATORY #2 THIS WEEK!

- CIRCUITS NO MORE COMPLEX THAN IN THE FIRST LAB.
- BUILD AND CHANGE CIRCUIT WITH THE POWER OFF.
- IF YOUR CIRCUIT DOESN'T WORK, CHECK WIRING FIRST, IF THAT DOESN'T FIX IT, CHANGE THE FET.

READ 12.1-12.3

 FURTHER ILLUSTRATION OF THE HANDLING OF IMPULSE EXCITATIONS AND OTHER SINGULARITY FUNCTIONS.



AT $t=0^-$, $V(0^-) = V_1$
(INITIAL CHARGE ON C)

$$\text{THUS } \frac{Q}{C} = V(0^+) - V(0^-)$$

$$\text{OR } \underline{V(0^+) = Q/C + V_1}$$

IF THE CURRENT IMPULSE WERE TO GO INTO R, V WOULD BE A VOLTAGE IMPULSE - NOT POSSIBLE GIVEN THE PARALLEL CAPACITOR. THUS IT FLOWS INTO C, CHANGING THE VOLTAGE BY Q/C .


MORE FORMALLY, DE AT $t=0$ IS:

$$Q\delta(t) = \frac{V}{R} + C \frac{dV}{dt} \quad \text{INTEGRATE THROUGH } t=0$$



$$\int_{0^-}^{0^+} Q\delta(t) dt = \frac{1}{R} \int_{0^-}^{0^+} V dt + C V \Big|_{0^-}^{0^+}$$

0 BECAUSE THE INTEGRAND IS FINITE AND THE INTERVAL IS INFINITESIMAL.

 FOR $t > 0$ THE CURRENT SOURCE IS ZERO. CIRCUIT IS:



  THE INITIAL VOLTAGE $V(0^+)$ DECAYS EXPONENTIALLY WITH A TIME CONSTANT RC .



DE. AT $t=0$

$$\lambda\delta(t) = RI + L \frac{dI}{dt} \quad \text{INTEGRATE THROUGH } t=0$$



$$\lambda = R \int_{0^-}^{0^+} I dt + L I \Big|_{0^-}^{0^+} \quad \text{THUS } [I(0^+) - I(0^-)] = \frac{\lambda}{L}$$

$$\text{OR } \underline{I(0^+) = \lambda/L + I_1}$$

THE CURRENT DECAYS EXPONENTIALLY WITH A TIME CONSTANT L/R :


$$I(t) = \left(\frac{\lambda}{L} + I_1 \right) e^{-\frac{tR}{L}} \quad t > 0$$

  THE VOLTAGE $v(t)$ IS $v = L \frac{di}{dt} = -(\frac{\lambda}{L} - I_1) \frac{R}{L} e^{-tR/L} = -(\frac{\lambda}{L} - I_1) R e^{-\frac{tR}{L}}$



FOR $t > 0$, THE INDUCTOR CURRENT DECAYS THROUGH THE RESISTOR

 NOTE THAT IF $\frac{\lambda}{L} = I_1$, THE INITIAL FLUX LINKAGE AND ENERGY IN L IS EXACTLY REMOVED BY THE IMPULSE AND THERE IS NO TRANSIENT.



O.E. $\lambda u_0(t) = L \frac{di}{dt} + \frac{1}{C} \int i dt$ ASAIN INTEGRATE THROUGH $t=0$

$$\lambda \int_{0^-}^{0^+} u_0(t) dt = L [i(0^+) - i(0^-)] + \frac{1}{C} \int_{0^-}^{0^+} i dt dt$$


$\underbrace{\hspace{10em}}_{L i(0^+)} \quad \underbrace{\hspace{10em}}_0$

$$i(0^+) = \frac{\lambda}{L} \quad v(0^+) = 0$$


BEHAVIOR FOR $t > 0$ IS THE SUBJECT OF LECTURE 13

A GENERALIZATION: OBSERVE THE DIFFERENTIAL EQUATION WITH A IMPULSE AS THE DRIVE. THE IMPULSE IS ABSORBED BY THE HIGHEST ORDER TERM ON THE RIGHT. THAT IS: IN 1), BY $C \frac{dv}{dt}$ RATHER THAN v/R . IN 2), BY $L \frac{di}{dt}$ RATHER THAN Ri . IN 3) BY $L \frac{di}{dt}$ RATHER THAN $\int i dt$.

 DIFFERENT SUBJECT: ENERGY STORAGE IN DIGITAL SWITCHES



 MODEL THE LEFT FET WITH THE SR MODEL, THE RIGHT WITH THE GATE-TO-SOURCE CAPACITANCE 'C'



SW IS CLOSED WHEN v_I IS HIGH

SW IS OPEN WHEN v_I IS LOW

CONSIDER A FULL CYCLE $v_I = 0 \rightarrow v_I = V \rightarrow v_I = 0$

WHAT IS THE POWER DISSIPATION OVER A CYCLE?

WITH SW OPEN THERE IS NO CURRENT IN R, $V = V$ AND THE ENERGY STORED IN C IS $E_A = \frac{1}{2} CV^2$

WHEN SW CLOSES THIS STORED ENERGY IS DISSIPATED GRADUALLY IN THE FET, THAT IS IN R_{ON} . IN THIS STATE THERE IS POWER DISSIPATED IN R:

$$P_B = \frac{V^2}{R} \text{ ASSUMING } R_{ON} \ll R$$

WHEN SW OPENS AGAIN THE ENERGY PROVIDED BY THE POWER SOURCE IS:

$E_T = \int_0^{\infty} V i dt$ WHERE i IS THE CURRENT CHARGING C. BY INSPECTION,

THE CHARGING CURRENT IS: $i(t) = \frac{V}{R} e^{-t/RC}$ ASSUMING SW OPENS AT $t=0$

THUS
$$E_T = \frac{V^2}{R} \int_0^{\infty} e^{-t/RC} dt = -\left(\frac{V^2}{R}\right)(RC) e^{-t/RC} \Big|_0^{\infty} = CV^2 \quad E_B = CV^2$$

AFTER SEVERAL TIME CONSTANTS THE CAPACITOR VOLTAGE IS $V e^{-1} V$ AND THE STORED ENERGY IS $\frac{1}{2} CV^2$. THE DIFFERENCE BETWEEN E_B AND $CV^2/2$ IS ENERGY DISSIPATED IN R DURING CHARGING.

THE AVERAGE POWER DISSIPATION OVER A CYCLE IS:


$$P_{AVG} = \frac{CV^2}{T} + \frac{P_B}{2} \text{ WHERE } T \text{ IS THE PERIOD AND BY ASSUMPTION THE SWITCH IS CLOSED FOR HALF THE PERIOD.}$$

THE TERM CV^2/T IS UNAVOIDABLE DISSIPATION IN STATE OPERATION.


HALF OF IT IS DISSIPATED IN R WHEN C IS CHARGING, AND IT IS INDEPENDENT OF R. THE OTHER HALF IS DISSIPATED IN R_{ON} WHEN C IS DISCHARGED THROUGH R_{ON} .

NOTE THAT THIS UNAVOIDABLE DYNAMIC LOSS VARIES AS V^2 - THUS THE DRIVE TO LOWER OPERATING VOLTAGES AND IS PROPORTIONAL TO THE FREQUENCY OF THE CYCLE $f = 1/T$.

 THE STATIC LOSS P_B IS ALWAYS PRESENT IN CIRCUITS USING ONLY N-CHANNEL FETS (NMOS LOGIC). IT CAN BE COMPLETELY ELIMINATED IN CMOS LOGIC IN WHICH THE PULL UP RESISTOR IS REPLACED BY A P-CHANNEL FET.




 CONDUCTS WHEN $V_{GS} > V_T$ (POSITIVE QUANTITY)




CONDUCTS WHEN $V_{GS} < V_T$ (NEGATIVE QUANTITY)

CMOS LOGIC

 


UPPER FET IS P-CHANNEL. LOWER IS N-CHANNEL
 V_O IS LOW
 WHEN V_I IS HIGH UPPER IS OFF, LOWER IS ON, BUT
 THERE IS NO STEADY CURRENT DOWN THE GATE.
 WHEN V_I IS LOW, LOWER IS OFF, BUT UPPER IS
 ON SO THAT V_O IS HIGH. AGAIN THERE IS NO
 STATIC CURRENT. $P_B \approx 0$. THE ONLY DISSIPATION
 IS DYNAMIC (DURING SWITCHING) AND IS $CV^2 f$

 
DIGITAL MEMORY - RELIES ON THE ENERGY STORED IN A CAPACITOR.



POSSIBLE CIRCUITS:

 

 WHEN SW CLOSSES THE HIGH OR LOW VOLTAGE
 AT IN IS STORED ON C. THE SWITCH CAN BE
 A FET OPERATED IN THE SWITCHING MODE
 PROBLEMS: V_{OUT} DECAYS BECAUSE OF LEAKAGE
 CURRENTS AND ENERGY LOST WHEN V_{OUT}
 IS SAMPLED.



AS ABOVE EXCEPT SW2 CLOSSES
 PERIODICALLY WHEN V_{OUT} IS HIGH
 TO RENEW CHARGE ON C, WHICH
 CAN BE THE GATE-TO-SOURCE
 CAPACITANCE OF THE FIRST
 INVERTER.