






Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits and Electronics
Spring 2003

Handout S03-037 - Homework #7

Issued: Wed. Mar 19
Due: Fri. Apr 4

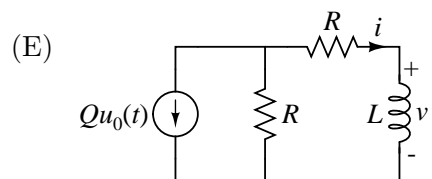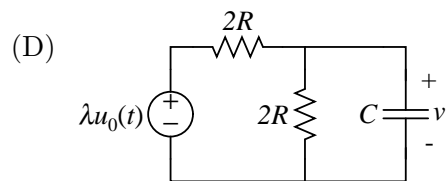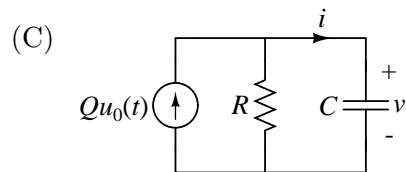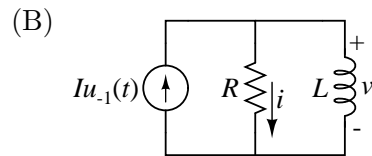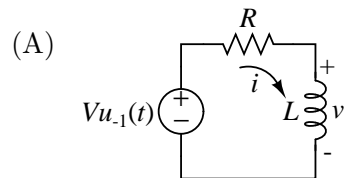
Problem 7.1: The circuits below are driven by either step functions or impulse functions. In each case determine the initial ($t = 0^+$) and final (asymptotic) values of the designated voltages and/or currents. Label your answers clearly.




Problem 7.2: Pick any three of the five circuits shown in Problem 7.1. For each of your choices, sketch and dimension the indicated voltages and currents for $t > 0$. Evaluate time constants in terms of circuit elements. Label your drawings clearly, including the designation (A), (B) \dots (E) of your choices.

Endeavor to do this problem without formally solving the differential equations.

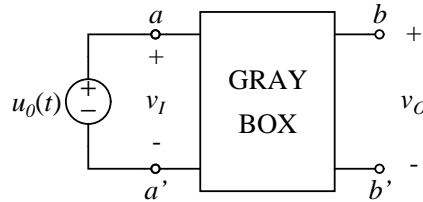Problem 7.3: The gray box shown below contains only linear circuit elements and satisfies the strict definition of linearity.



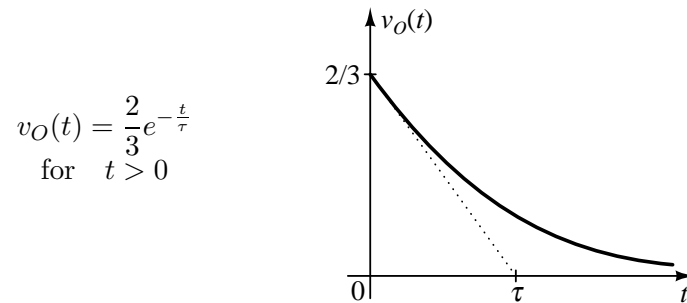When the box is initially without stored energy and is driven by a unit voltage impulse at the terminals aa' as shown, the response of the voltage v_O for $t > 0$ is




$$v_O(t) = \frac{2}{3}e^{-\frac{t}{\tau}}$$

for $t > 0$

(A) Determine the response $v_O(t)$ when the input v_I at aa' is a step of amplitude V .

$$v_I = Vu_{-1}(t)$$

(B) The input to the box is shown below.

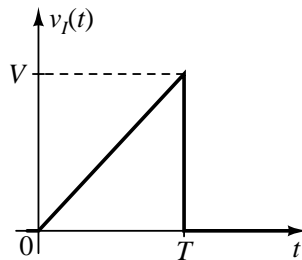

Determine the output voltage $v_O(t)$ for $t > 0$.


Note that a response to a delayed input can be written as

$$v(t) = u_{-1}(t - T)f(t - T)$$

where $f(t)$ is the response to an excitation at $t = 0$ and T is the time the input is delayed. The multiplier $u_{-1}(t - T)$ ensures that there is no response for $t < T$.

Hint: Resolve the input into the sum of three inputs, each of which is a scaled singularity function.

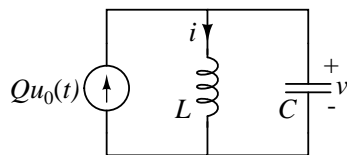
Problem 7.4: The LC circuit below is driven by an impulse:



(A) Determine $v(0^+)$ and $i(0^+)$.

(B) At $t = 0^+$: What is the sign of the first derivative of v ?
What is the sign of the first derivative of i ?

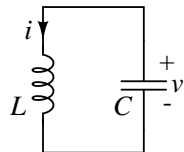(C) Note that for $t > 0$ the circuit is:



Write a differential equation for $v(t)$ or $i(t)$ and solve it. Express both $v(t)$ and $i(t)$ as functions of time.