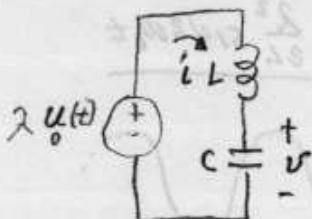


NOTES FOR 6.002 LECTURE #13, MARCH 20, 2003

READ 13.1-13.3, 13.5


REPRISÉ ON DIGITAL MEMORY (NOTES OF LECTURE #12)

SECOND ORDER RESPONSES:

FOR $t < 0$

$$i = v = 0$$

(NO STORED ENERGY)

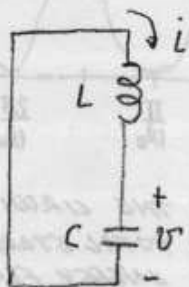

WHERE $\omega_0^2 = 1/LC$

AND ω_0 IS THE NATURAL FREQUENCY OF THE OSCILLATOR,THE INITIAL CONDITION REQUIRES $i(0^+) = 2/L$. THUS $B = 2/L$ AND A IS NOT DETERMINED YET:

$$t > 0 \quad i(t) = \frac{2}{L} \cos \omega_0 t + B \sin \omega_0 t$$

WHAT ABOUT THE VOLTAGE v ? $v = \frac{1}{C} \int i dt$

$$v(t) = \frac{2}{\omega_0 LC} \sin \omega_0 t - \frac{B}{\omega_0 C} \cos \omega_0 t + C \quad \text{A CONSTANT OF INTEGRATION}$$

 $v(0^+) = 0$ THUS $B = C = 0$ AND THE COMPLETE SOLUTION IS

$$\left. \begin{aligned} i(t) &= \frac{2}{L} \cos \omega_0 t \\ v(t) &= 2\omega_0 \sin \omega_0 t \end{aligned} \right\} \text{ORTHOGONAL SINE WAVES}$$

KVL AROUND LOOP: $2u_0(t) = L \frac{di}{dt} + \frac{1}{C} \int i dt$

THE IMPULSE IS ABSORBED BY $L \frac{di}{dt}$ (HIGHEST-ORDER TERM) THUS $i(0^+) = 2/L$ AND ENERGY HAS BEEN PUT IN THE INDUCTOR BY THE IMPULSE.FOR $t > 0$, AFTER THE IMPULSE HAS PASSED, THE CIRCUIT IS:


AND THE D.E. IS: $L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$

EQUIVALENTLY: $LC \frac{d^2 i}{dt^2} + i = 0$

THIS IS THE D.E. OF A HARMONIC OSCILLATOR

SOLUTIONS ARE OF THE FORM:
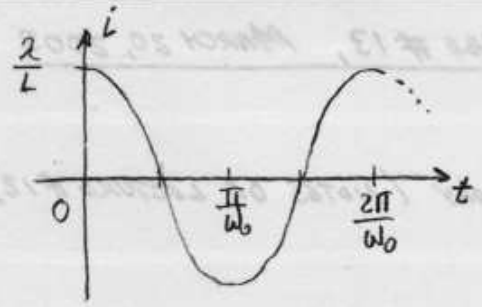
$$i(t) = A \sin \omega_0 t + B \cos \omega_0 t$$



WHAT ABOUT STORED ENERGIES?




$$E_L = \frac{1}{2} L i^2 = \frac{\lambda^2}{2L} \cos^2 \omega_0 t$$

$$E_C = \frac{1}{2} C v^2 = \frac{C \lambda^2 \omega_0^2}{2} \sin^2 \omega_0 t$$

OR

$$E_C = \frac{\lambda^2}{2L} \sin^2 \omega_0 t$$

ETC.

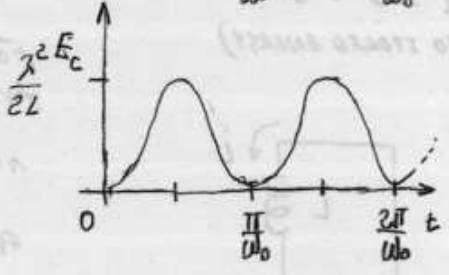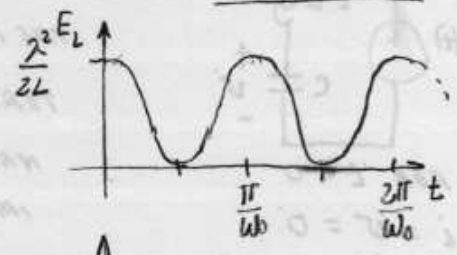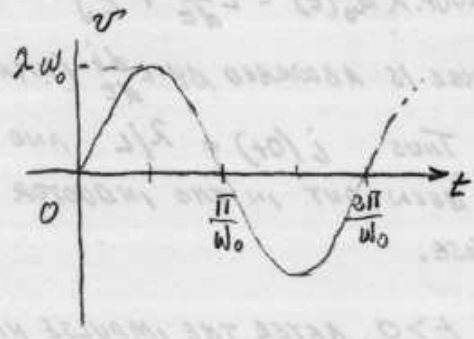


THE TOTAL STORED ENERGY IS

$$E_{TOTAL} = \frac{\lambda^2}{2L} (\cos^2 \omega_0 t + \sin^2 \omega_0 t)$$

$$E_{TOTAL} = \frac{\lambda^2}{2L}$$

WITH NO LOSS MECHANISM THE CIRCUIT OSCILLATES AT ω_0 INDEFINITELY WITH TOTAL STORED ENERGY CONSTANT AND WITH THE ENERGY FLOPPING BACK AND FORTH BETWEEN THE INDUCTOR AND THE CAPACITOR.

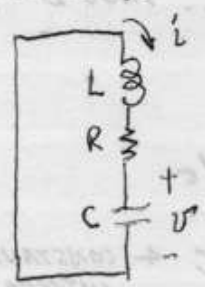INTRODUCE A LOSS MECHANISM WHICH ABSORBS A SMALL FRACTION OF THE STORED ENERGY EACH CYCLE: RESISTANCE IN THE INDUCTOR WINDING.



ASSUME THE CURRENT AND VOLTAGE WAVEFORMS DON'T CHANGE MUCH OVER A CYCLE.

AVERAGE LOSS = $\frac{1}{T} \int_0^T i^2 R dt$ WHERE T IS THE PERIOD $\frac{2\pi}{\omega_0}$

$$AVS. LOSS = \frac{\lambda^2 R}{T L^2} \int_0^{2\pi/\omega_0} \cos^2 \omega_0 t dt = \frac{\lambda^2 R}{T L^2} \left(\frac{\pi}{\omega_0} \right)$$


OR AVS LOSS = $\frac{R \lambda^2}{2L^2} \approx \frac{R}{L} \left(\frac{\lambda^2}{2L} \right) \leftarrow E_{TOTAL}$

THE D.E. WHICH DESCRIBES ENERGY DECAY IS: $\frac{dE}{dt} = -AVS LOSS$
(DROPPING TOTAL FROM E)

OR $\frac{dE}{dt} + \frac{R}{L} E = 0$ THE SOLUTION IS $E(t) = E(0) e^{-t/\tau}$ $\tau = \frac{L}{R}$

THE CURRENT i AND THE VOLTAGE v ARE PROPORTIONAL TO \sqrt{E}

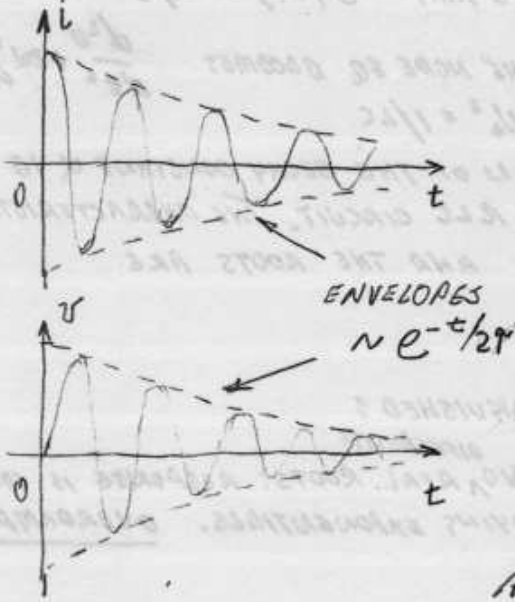THUS THEIR AMPLITUDES DECAY WITH A TIME CONSTANT $\frac{L}{2R}$



AN EXACT SOLUTION CAN BE FOUND AS ALWAYS BY GOING BACK TO THE D.E. WITH R PRESENT: FOR $t > 0$

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = 0 \text{ KVL}$$

OR

$$\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \omega_0^2 i = 0$$

WHERE $\omega_0^2 = \frac{1}{LC}$, $\alpha = \frac{R}{2L}$

ASSUME Ae^{st} AS A SOLUTION.

THE CHARACTERISTIC EQUATION IS $s^2 + 2\alpha s + \omega_0^2 = 0$

FOR THE OSCILLATORY CASE $\alpha < \omega_0$ AND THE ROOTS ARE:

$$s_1, s_2 = -\alpha \pm j \sqrt{\omega_0^2 - \alpha^2} \text{ COMPLEX ROOTS}$$

(NOTE THAT IN EECs, TO AVOID CONFUSION WITH CURRENT, $\sqrt{-1} = j$ NOT i)

AFTER A MODEST AMOUNT OF ALGEBRA AND TRIGONOMETRY AND THE

ASSUMPTION THAT R IS SMALL (MORE PRECISELY $\alpha \ll \omega_0$):

$$\left. \begin{aligned} i(t) &\approx \frac{\lambda}{L} e^{-\alpha t} \cos \omega_0 t \\ v(t) &\approx \lambda \omega_0 e^{-\alpha t} \sin \omega_0 t \end{aligned} \right\} \text{ WHICH CORRESPONDS TO THE DRAWINGS ABOVE.}$$

THIS SLIGHTLY-DAMPED OSCILLATOR IS AN IMPORTANT CONCEPT

AS A SECOND EXAMPLE CONSIDER A PARALLEL RLC CIRCUIT EXCITED BY A CURRENT IMPULSE

ADDENDUM TO (503-039), NOTES FOR LECTURE #13, 3/20/03

I) THE ANALYSIS AT THE BOTTOM OF p1 IS INCORRECT. THE EXPRESSION FOR $i(t)$ SHOULD READ:

$$t > 0: i(t) = \frac{\lambda}{2} \cos \omega_0 t + A \sin \omega_0 t. \text{ THE CORRECT EXPRESSION FOR } v(t) \text{ IS:}$$

$$t > 0: v(t) = \frac{\lambda}{\omega_0 L} \sin \omega_0 t - \frac{A}{\omega_0 C} \cos \omega_0 t + K \quad (K \text{ IS CONST. OF INTEG.})$$

BECAUSE $v(0+) = 0$, $\frac{di}{dt}(0+)$ MUST BE ZERO, AS REQUIRED BY THE DIFFERENTIAL EQUATION; AT $t=0+$, $\int i(t) dt = 0$ BECAUSE $i(t)$ IS FINITE

$$\frac{di}{dt} = -\frac{\lambda \omega_0}{L} \sin \omega_0 t + A \omega_0 \cos \omega_0 t \text{ BY DIFFERENTIATION.}$$

THUS $A = 0$ AND $K = 0$ TO SATISFY $v(0+) = 0$

MY ^{ORIGINAL} ALGEBRA REQUIRED: $-\frac{A}{\omega_0 C} + K = 0$, WHICH IS INSUFFICIENT.

(COURTESY OF PROF. HUTCHINSON)

II) THE ARGUMENT AT THE END OF THE HOUR, NOT INCLUDED IN THE NOTES, WENT LIKE THIS:

$$\text{ENERGY LOSS PER PERIOD} = \frac{\lambda^2 R}{L^2} \left(\frac{\pi}{\omega_0} \right) \left[\text{FROM } \int_0^{\pi} i(t)^2 R dt \right]$$

$$\text{ENERGY LOSS PER RADIAN} = \frac{\lambda^2 R}{L^2} \left(\frac{\pi}{\omega_0} \right) \frac{L}{2\pi} = \frac{\lambda^2}{2L} \left(\frac{R}{L\omega_0} \right)$$

$$\text{AVERAGE STORED ENERGY IN A PERIOD} = \frac{\lambda^2}{2L} \left[\text{FROM MIDDLE OF } \rho_2 \right]$$

$$\text{THUS } \frac{\text{AVG. STORED ENERGY}}{\text{ENERGY LOSS/RADIAN}} = \frac{L\omega_0}{R} = Q, \text{ THE QUALITY FACTOR}$$

$$\text{FROM } \rho_3 \text{ MIDDLE WHERE } \frac{R}{\omega_0 L} = \alpha, \quad Q = \frac{\omega_0}{2\alpha}$$

HIGH Q MEANS LONGER LASTING OSCILLATION.

HOW GREAT IS THE DECAY IN Q PERIODS? I.E. LET $\omega_0 t = Q(2\pi)$

$$e^{-\alpha t} = e^{-\left[\alpha \frac{Q(2\pi)}{\omega_0} \right] t} = e^{-\pi} \approx \frac{1}{23} \text{ OR ABOUT 4\% OF INITIAL VALUE}$$

A ROUGH MEASURE OF Q CAN BE OBTAINED BY COUNTING THE NUMBER OF CYCLES TO BE DOWN TO 4% OF THE INITIAL AMPLITUDE

N.B. THIS ENERGY-BASED ANALYSIS WORKS ONLY FOR HIGH Q . I.E., $Q > 5$.