
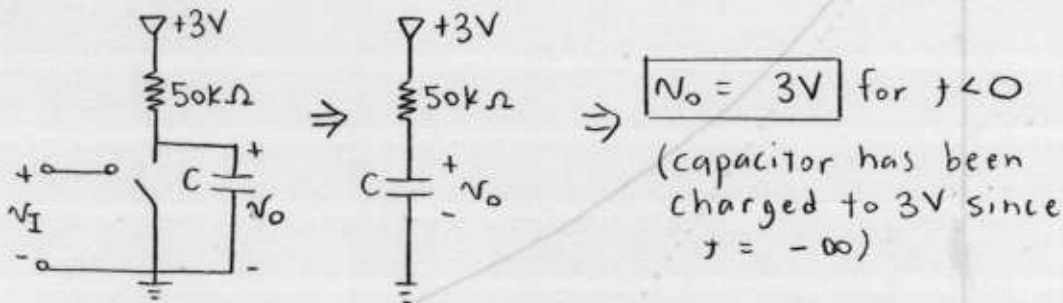


S03-S041 HW 6 Solutions

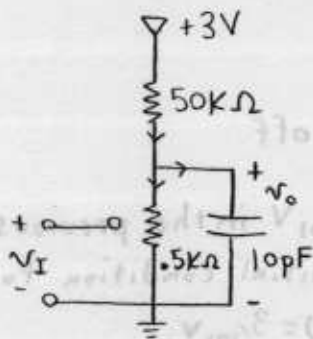6.1 (A) since $v_I = 0$ for all $t < 0$, circuit is (for $t < 0$):



(B) $v_I = 3V > V_T$ for $t > 0$, $t' < 0$
 \Rightarrow MOSFET is on:



(C) KCL:

$$\frac{3V - v_o}{50k\Omega} = \frac{v_o}{.5k\Omega} + \frac{dv_o}{dt} (10pF)$$

↑ current thru R_{pu} ↑ current thru R_{on} ↑ current thru cap

Note that v_o is the node voltage.

(D) Rearranging + dropping units: $\frac{dv_o}{dt} + (2.02 \times 10^8)v_o = 6 \times 10^6$

Homogenous v_{oH}

$$\frac{dv_o}{dt} + (2.02 \times 10^8)v_o = 0$$

$$v_{oH} = Ae^{-(2.02 \times 10^8)t}$$

Particular v_{oP}

Guess $v_{oP} = c$, then

$$0 + (2.02 \times 10^8)c = 6 \times 10^6$$

$$c = \frac{6 \times 10^6}{2.02 \times 10^8} = \frac{3}{101} V$$

$$v_o(t) = v_{oH} + v_{oP}$$

$$= Ae^{-(2.02 \times 10^8)t} + \frac{3}{101} V$$


Initial Condition $v(0^-) = 3V$

$$Ae^0 + \frac{3}{101} V = 3V$$


$$A = \frac{300}{101} V$$

$$v_o(t) = \frac{300}{101} e^{-(2.02 \times 10^8)t} + \frac{3}{101} V$$

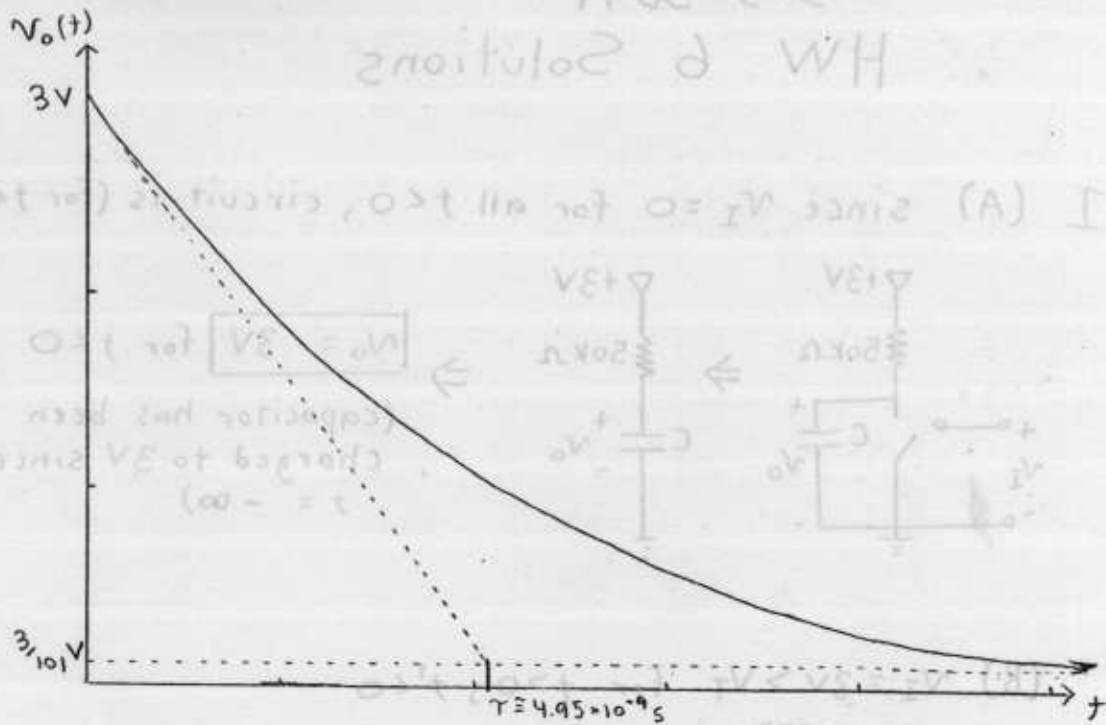Note that $\tau = \frac{1}{2.02 \times 10^8} \approx 4.95 \times 10^{-9} s$



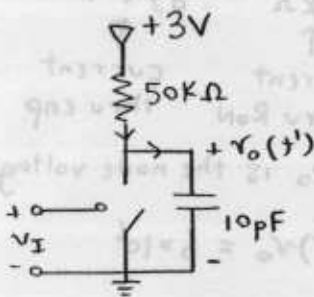(E) $v_1 = 0V < V_T$ for $t' > 0 \Rightarrow$ MOSFET is off



Remember that $v_o \rightarrow 3/101V$ in the previous problem; thus the initial condition for this part is $v_o(0^-) = 3/101V$

$$\text{KCL: } \frac{3V - v_o}{50k\Omega} = (10pF) \frac{dv_o}{dt}$$

$$\text{Rearranging: } \frac{dv_o}{dt} + (2 \times 10^6) v_o = 6 \times 10^6$$

Homogenous v_{oH}

$$\frac{dv_o}{dt} + (2 \times 10^6) v_o = 0$$

$$v_{oH} = A e^{-(2 \times 10^6)t}$$

Particular v_{oP}

guess $v_{oP} = c$

$$0 + (2 \times 10^6)c = 6 \times 10^6$$

$$c = 6/2 = 3V$$

Initial Condition $v_o(0^-) = 3/101V$

$$v_{oH}(0) + v_{oP}(0) = 3/101V$$

$$A e^0 + 3V = 3/101V$$


$$A = -\frac{300}{101}V$$

So,

$$v_o(t) = -\frac{300}{101} e^{-(2 \times 10^6)t} + 3V$$

Note that

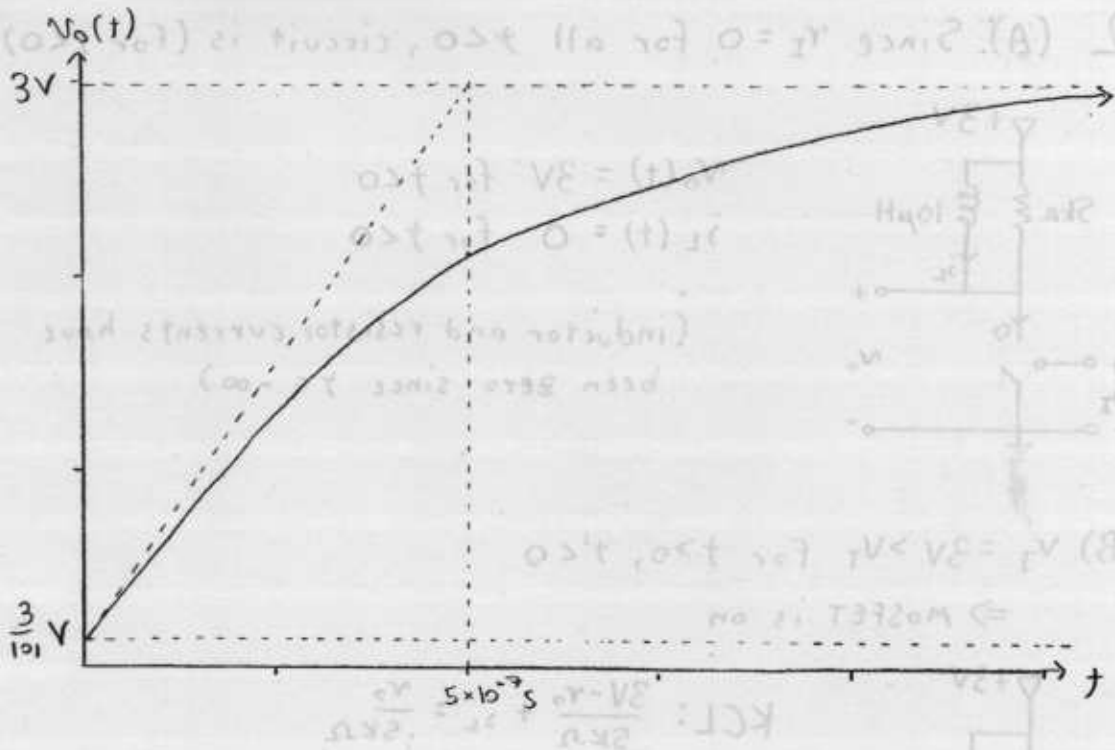
$$\tau = \frac{1}{2 \times 10^6} = 5 \times 10^{-7} s$$



(F) The time constant in part (E) is much larger than the one in part (D) because in the circuit of part (E) the capacitor charges through a resistor of $50\text{K}\Omega$ while in part (D) the capacitor discharges through the 500Ω on resistance and the $50\text{K}\Omega$ resistor in parallel. (to see this, note that $\tau = 2.02 \times 10^{-8} = (10\text{pF})(500\Omega \parallel 50\text{K}\Omega)$)

The size of the resistor affects the amount of charge that can flow into/out of the capacitor per unit time. Note that the two time constants differ by about a factor of 100 and so do the two resistors.

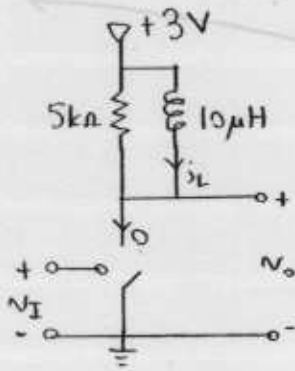6.2 (A) Since $v_I = 0$ for all $t < 0$, circuit is (for $t < 0$):




$$v_o(t) = 3V \text{ for } t < 0$$

$$i_L(t) = 0 \text{ for } t < 0$$

(inductor and resistor currents have been zero since $t = -\infty$)

(B) $v_I = 3V > V_T$ for $t > 0$, $t' < 0$

\Rightarrow MOSFET is on

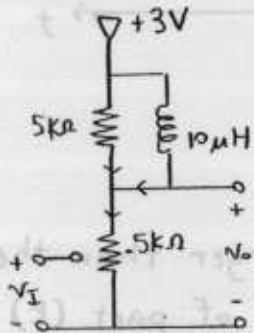

$$\text{KCL: } \frac{3V - v_o}{5k\Omega} + i_L = \frac{v_o}{.5k\Omega}$$

$$6 \times 10^{-4} \text{ A} = v_o \left(\frac{1}{5k\Omega} + \frac{1}{500\Omega} \right) - i_L$$

$$6 \times 10^{-4} \text{ A} = \left(3V - 10\mu\text{H} \frac{di_L}{dt} \right) \left(\frac{1}{5k\Omega} + \frac{1}{500\Omega} \right) - i_L$$

$$-6 \times 10^{-3} = -2.2 \times 10^{-8} \frac{di_L}{dt} - i_L$$

$$\boxed{\frac{di_L}{dt} + \frac{i_L}{2.2 \times 10^{-8}} = \frac{30}{11} \times 10^5}$$

(C) Homogenous i_{LH} Initial Condition $i_L(0^-) = 0$

$$\frac{di_L}{dt} + \frac{i_L}{2.2 \times 10^{-8}} = 0$$

$$i_{LH}(t) = A e^{-t/2.2 \times 10^{-8}}$$

$$A e^{-t/2.2 \times 10^{-8}} \Big|_{t=0} + 6 \times 10^{-3} = 0$$

$$A e^0 + 6 \times 10^{-3} = 0$$

$$A = -6 \times 10^{-3}$$

Particular i_{LP}

$$\text{guess } i_{LP}(t) = C$$

$$0 + \frac{C}{2.2 \times 10^{-8}} = \frac{30}{11} \times 10^5$$

$$C = (2.2 \times 10^{-8}) \left(\frac{30}{11} \times 10^5 \right)$$




$$= 6 \times 10^{-3}$$

$$i_L(t) = (-6 \times 10^{-3}) e^{-t/2.2 \times 10^{-8}} + 6 \times 10^{-3} \text{ A}$$


$$= (6 \times 10^{-3} \text{ A}) (1 - e^{-t/2.2 \times 10^{-8}})$$

$$v_o(t) = 3V - 10\mu\text{H} \frac{di_L(t)}{dt}$$
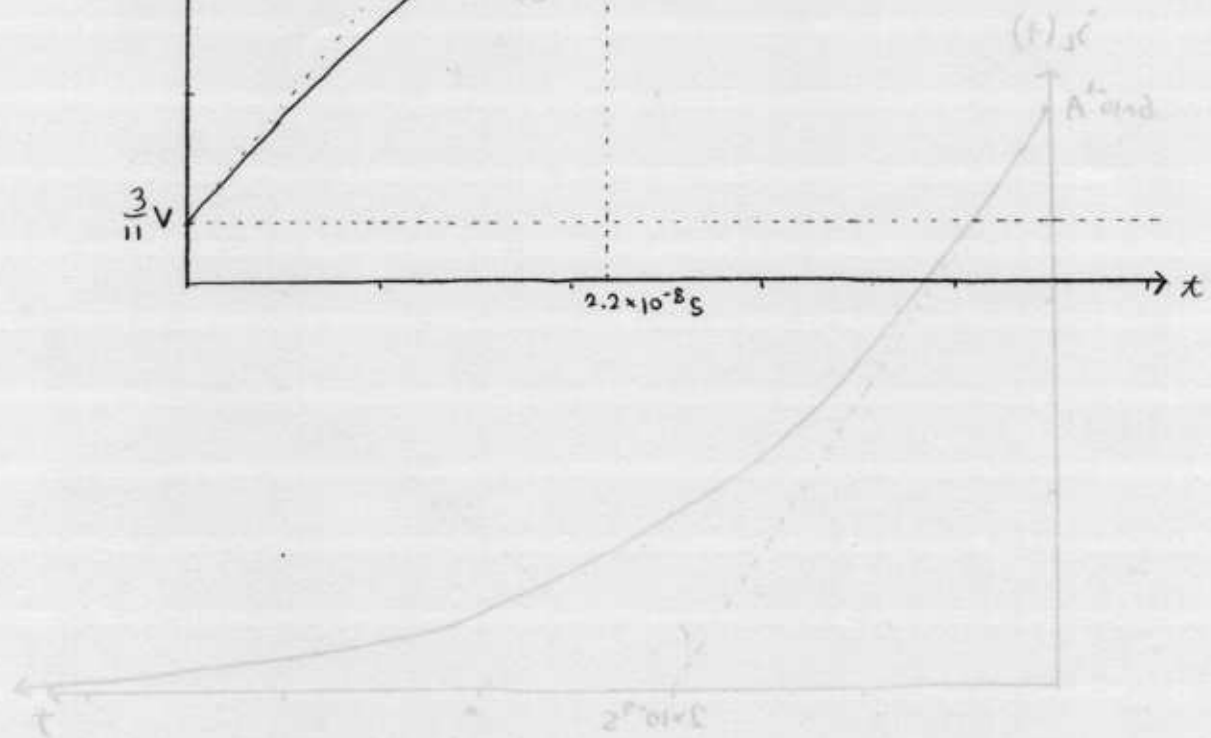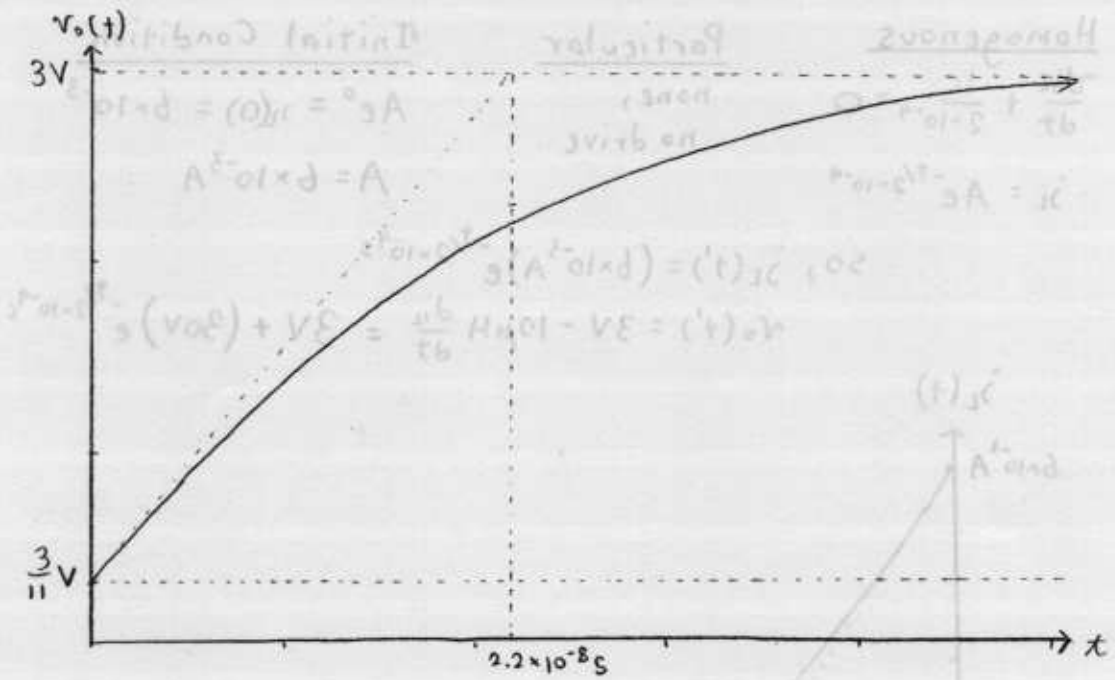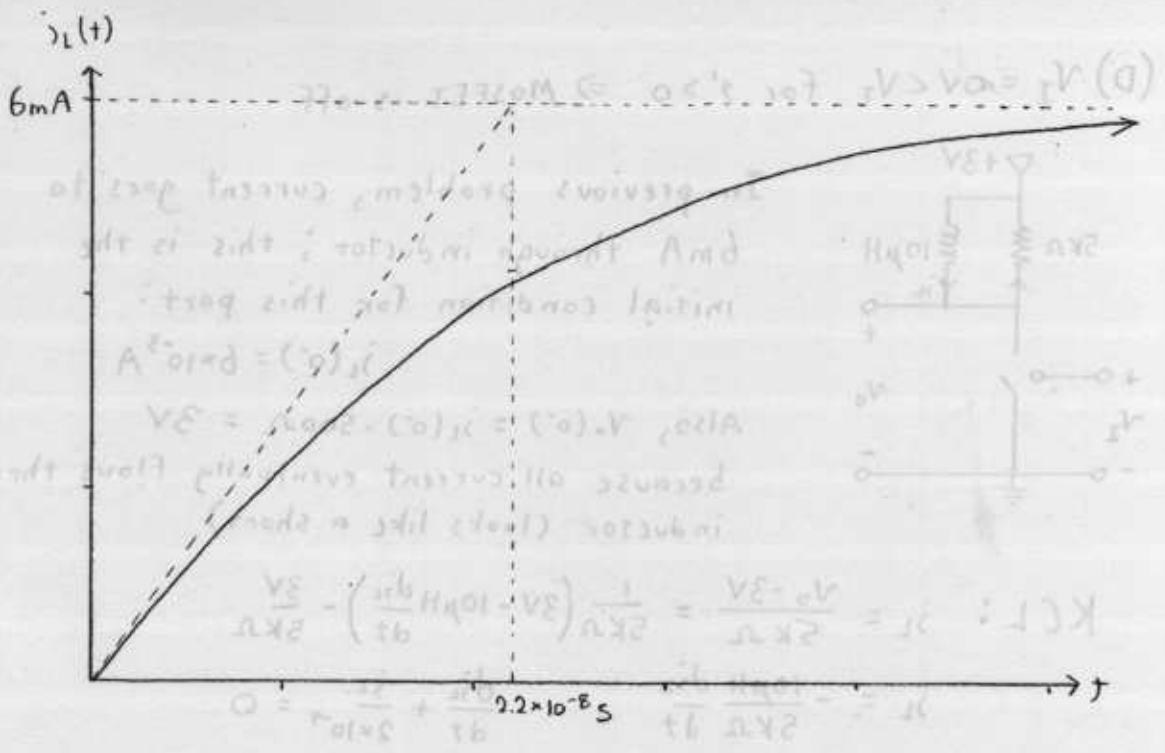
$$= 3V - \frac{30}{11} e^{-t/2.2 \times 10^{-8}} \text{ V}$$



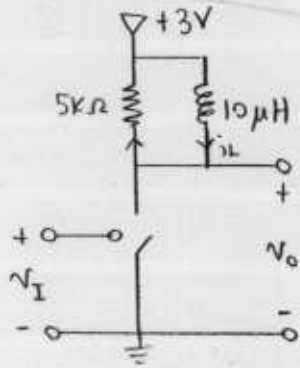(D) $V_I = 0V < V_T$ for $t' > 0 \Rightarrow$ MOSFET is off



In previous problem, current goes to 6mA through inductor; this is the initial condition for this part:

$$i_L(0^-) = 6 \times 10^{-3} \text{ A}$$

$$\text{Also, } V_o(0^-) = i_L(0^-) \cdot 500\Omega = 3V$$

because all current eventually flows thru inductor (looks like a short)

$$\text{KCL: } i_L = \frac{V_o - 3V}{5k\Omega} = \frac{1}{5k\Omega} \left(3V - 10\mu H \frac{di_L}{dt} \right) - \frac{3V}{5k\Omega}$$

$$i_L = -\frac{10\mu H}{5k\Omega} \frac{di_L}{dt} \quad \frac{di_L}{dt} + \frac{i_L}{2 \times 10^{-9}} = 0$$

Homogenous

$$\frac{di_L}{dt} + \frac{i_L}{2 \times 10^{-9}} = 0$$

$$i_L = A e^{-t/2 \times 10^{-9}}$$

Particular

none,
no drive


Initial Condition


$$A e^0 = i_L(0) = 6 \times 10^{-3}$$

$$A = 6 \times 10^{-3} \text{ A}$$

$$\text{So, } i_L(t') = (6 \times 10^{-3} \text{ A}) e^{-t'/2 \times 10^{-9} \text{ s}}$$
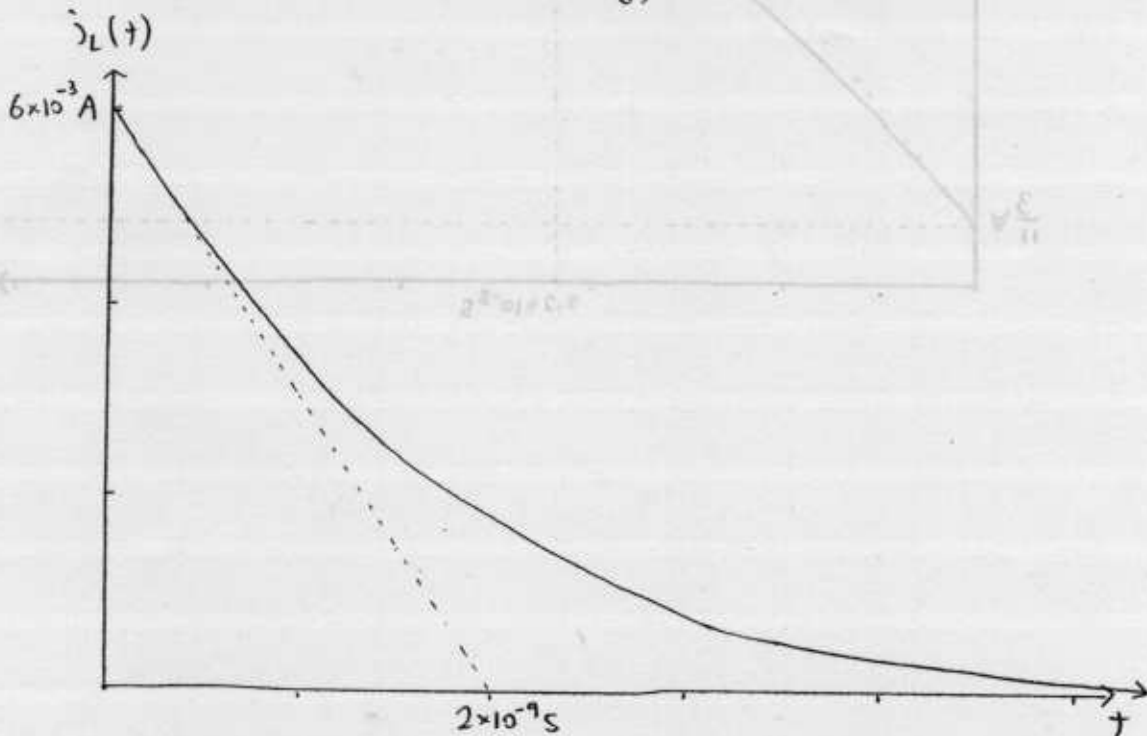
$$V_o(t') = 3V - 10\mu H \frac{di_L}{dt} = 3V + (30V) e^{-t'/2 \times 10^{-9} \text{ s}}$$



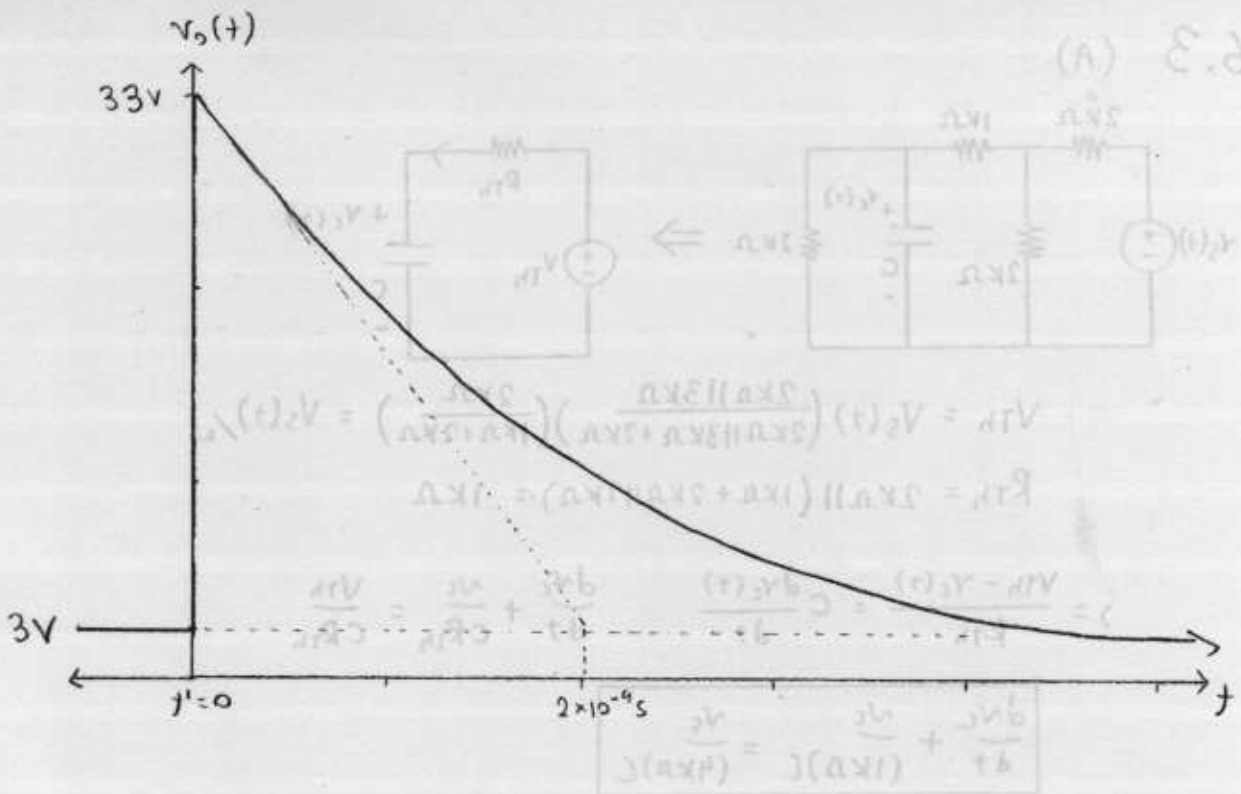

(E) At time $t'=0$, the 500Ω resistance is removed from the circuit. The current through the inductor at $t'=0$ is 6mA and since this value cannot change instantly (without an infinite voltage drive), the inductor must force the current through the $5\text{k}\Omega$ resistor, generating a voltage of $(5\text{k}\Omega)(6\text{mA}) = 30\text{V}$ which is added to the 3V source voltage.

$$v_c(t) = -\left(V_c + \frac{V_c}{\tau} t \right) e^{-t/\tau} + V_c$$

for $t > 0$

Particular $v_p(t)$


$$v_c(t) = v_p(t) + v_h(t)$$

$$0 + 3e^{-t/\tau} = 3e^{-t/\tau} + 0$$

$$0 = v_h(t)$$

$$v_c(t) = \frac{V_c}{\tau} t e^{-t/\tau}$$

6.3 (A)

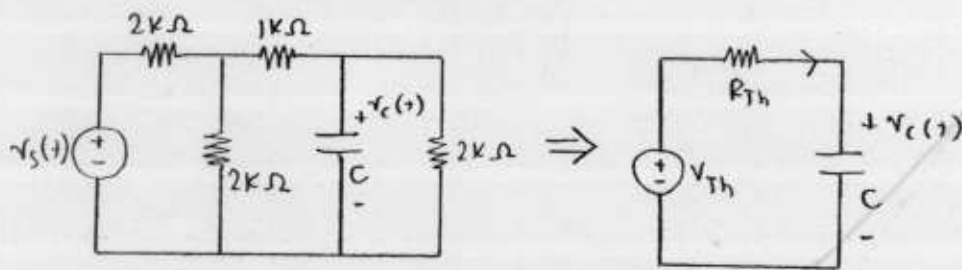

$$V_{Th} = V_s(t) \left(\frac{2k\Omega \parallel 3k\Omega}{2k\Omega \parallel 3k\Omega + 2k\Omega} \right) \left(\frac{2k\Omega}{1k\Omega + 2k\Omega} \right) = V_s(t)/4$$

$$R_{Th} = 2k\Omega \parallel (1k\Omega + 2k\Omega \parallel 2k\Omega) = 1k\Omega$$

$$i = \frac{V_{Th} - v_c(t)}{R_{Th}} = C \frac{dv_c(t)}{dt} \quad \frac{dv_c}{dt} + \frac{v_c}{CR_{Th}} = \frac{V_{Th}}{CR_{Th}}$$

$$\boxed{\frac{dv_c}{dt} + \frac{v_c}{(1k\Omega)C} = \frac{v_s}{(4k\Omega)C}}$$

(B) $\tau = CR_{Th} = (10^{-6}F)(1k\Omega) = 10^{-3}s = \boxed{1ms}$

(C) Homogenous $v_{cH}(t)$

$$\frac{dv_c}{dt} + \frac{v_c}{1ms} = 0$$

$$v_{cH}(t) = A e^{-t/1ms}$$

Initial Condition

$$\begin{aligned} v_c(0^+) &= -V_c \\ &= A e^{-0/1ms} + \frac{V_s}{4} \mu_1(0) \\ &= A + \frac{V_s}{4} \\ &\rightarrow A = -V_c - \frac{V_s}{4} \end{aligned}$$

Particular $v_{cP}(t)$

guess $v_{cP}(t) = C \mu_1(t)$


$$0 + \frac{C \mu_1(t)}{1ms} = \frac{V_s \mu_1(t)}{4ms}$$

$$C = \frac{V_s}{4}$$

$$v_{cP}(t) = \frac{V_s}{4} \mu_1(t)$$

So,
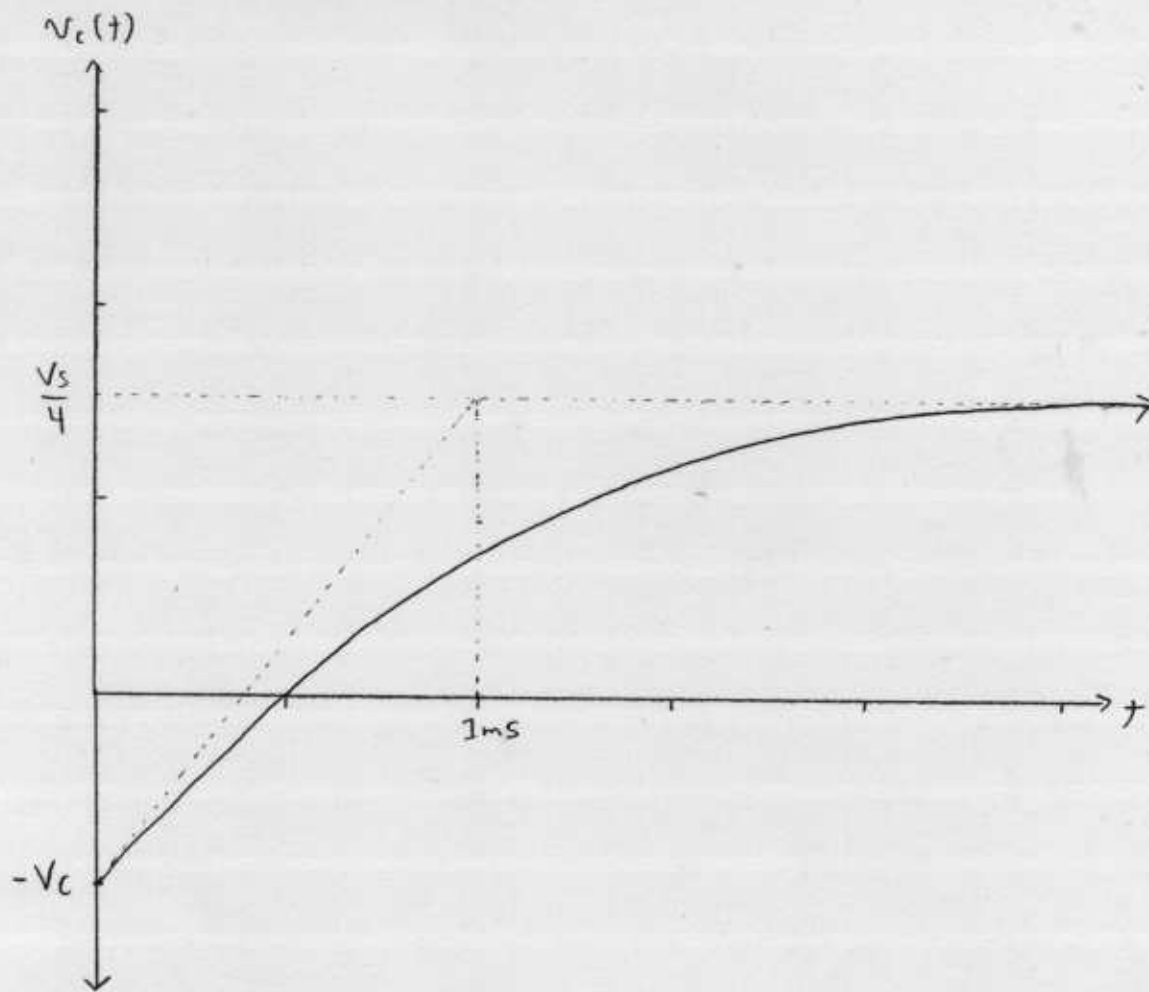
$$\boxed{v_c(t) = -\left(V_c + \frac{V_s}{4}\right) e^{-t/1ms} + \frac{V_s}{4} \text{ for } t > 0}$$



(D) No transient \rightarrow no dying exponential

$$v_c(t) = -\left(v_c + \frac{v_s}{4}\right) e^{-t/2ms} + \frac{v_s}{4}$$

$$\text{need } v_c + \frac{v_s}{4} = 0$$

$$-v_c = \boxed{+\frac{v_s}{4} = v_c(0)}$$