
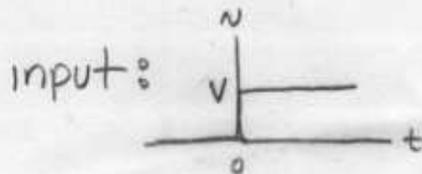


6.002 HOMEWORK #7 SOLUTIONS

PROBLEM 7.1

(A)

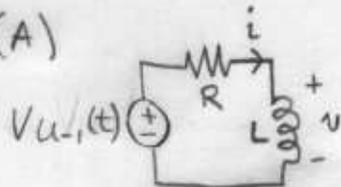

output: at $t=0^+$ the inductor looks like



an open circuit, so $L = \infty$



$t=0^+$	$i=0$	$v=V$
---------	-------	-------



at $t \rightarrow \infty$ the inductor looks like a short circuit, so


$t \rightarrow \infty$	$i = \frac{V}{R}$	$v=0$
------------------------	-------------------	-------

(B)

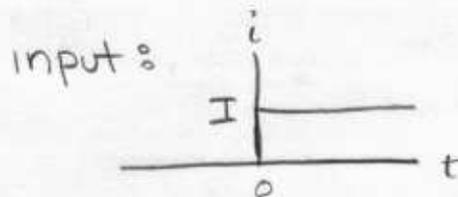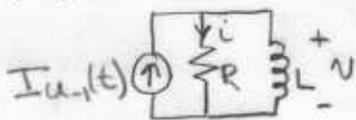


output:



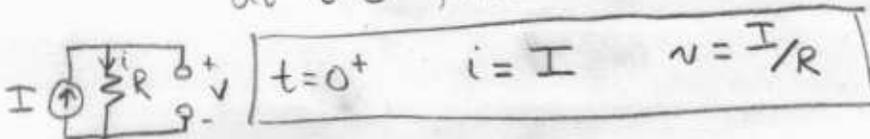
at $t=0^+$, the inductor is open, all current goes through R.



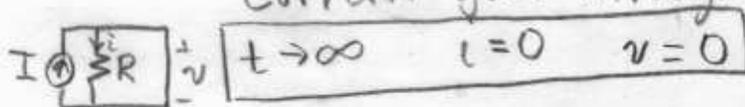at $t \rightarrow \infty$, the inductor is a short, all current goes through the short.




HW 7 SOLUTIONS p. 2



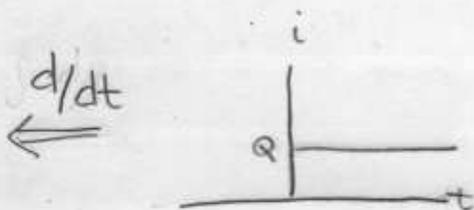
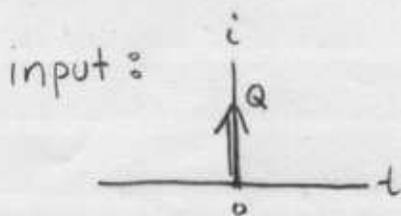
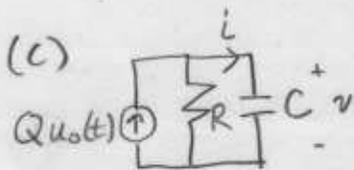


Output of step:

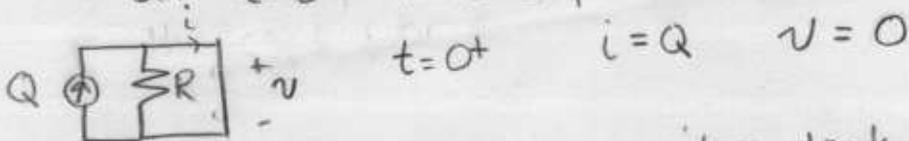at $t=0^+$ the capacitor looks like a short



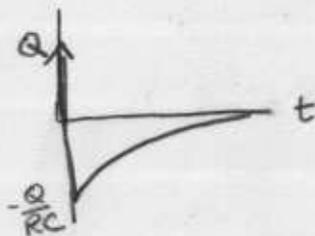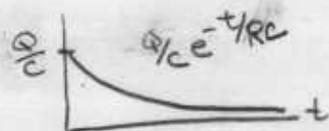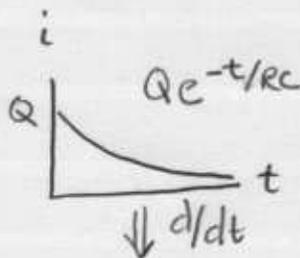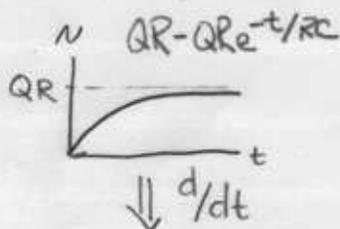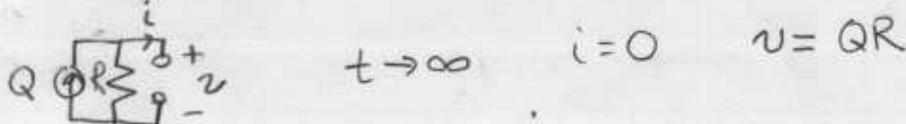at $t \rightarrow \infty$ the capacitor looks like an open





IMPULSE RESPONSE
= $\frac{d}{dt}$ STEP RESPONSE


Impulse Response: $Q = CV$, the impulse dumps charge on the capacitor, so $v = Q/C$, which then decays to 0. An impulse of Q passes through the cap at $t=0$ (because it acts like a short), the induced voltage then decays as current through R in the negative direction.

$t=0^+$	$i = -Q/RC$	$v = Q/C$
$t \rightarrow \infty$	$i = 0$	$v = 0$

HW 7 SOLUTIONS p.3

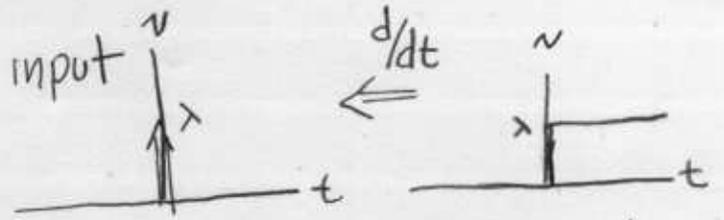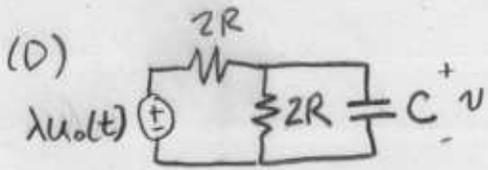


Thévenin Equivalent:


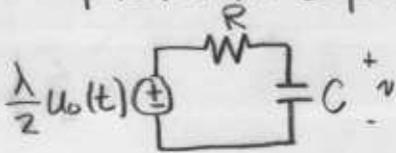


Step response:

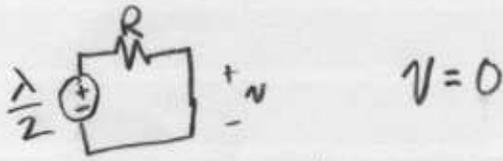
$t=0^+$ the capacitor looks like a short.



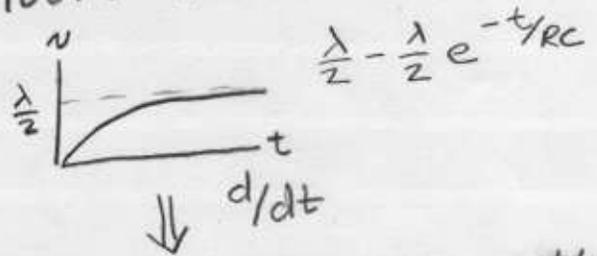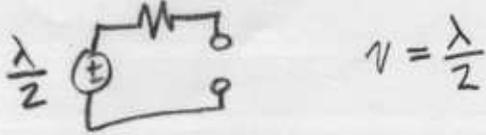
$t \rightarrow \infty$ the capacitor looks like an open.



Impulse Response:

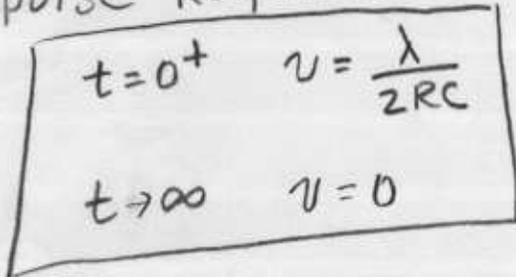

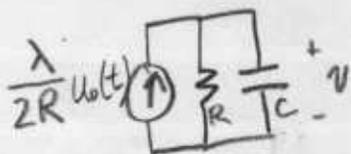This is easy to see if we change the Thévenin equivalent to a Norton equivalent.





at $t=0^+$ an impulse of charge is dumped on the capacitor.

$$Q = CV$$

$$V = \frac{Q}{C} = \frac{\lambda}{2RC}$$


HW 7 SOLUTIONS P.4

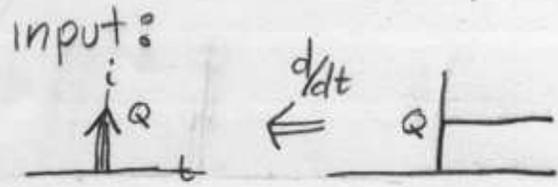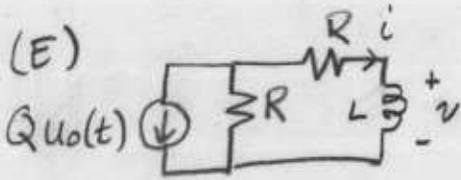

Norton Equivalent:





Step Response:


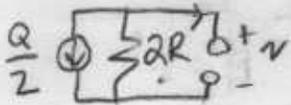


$t=0^+$: the inductor looks like an open circuit, all current flows through the resistor.
 $i=0$ $v = -\frac{Q}{2} \cdot 2R = -QR$

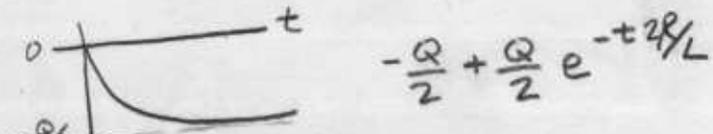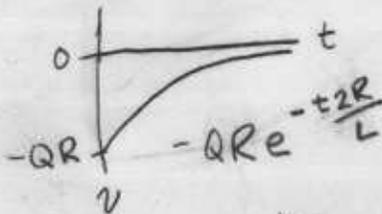$t \rightarrow \infty$: the inductor looks like a short, all current flows through the inductor.
 $i = -\frac{Q}{2}$ $v = 0$




IMPULSE RESPONSE:

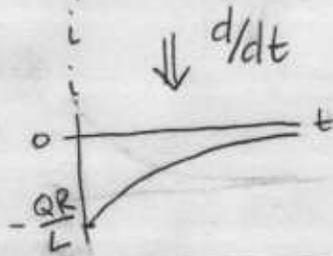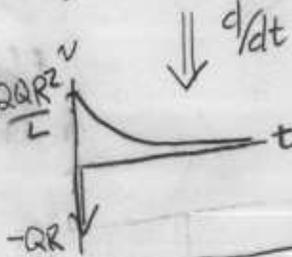

$t=0^+$	$v = \frac{2QR^2}{L}$	$i = -\frac{QR}{L}$
$t \rightarrow \infty$	$i = 0$	$v = 0$

let's look at the Thévenin EQUIVALENT:

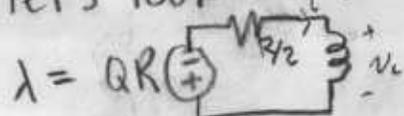

$\lambda = Li$



$t=0$ flux linkage through $L: -QR = \lambda$
 this induces a current $= -\frac{QR}{L}$
 this current induces a voltage across R and decays.

HW 7 SOLUTIONS p. 5



PROBLEM 7.2

FOR EXPLANATIONS SEE SOLUTION FOR PROBLEM 7.1



(A) $\tau = L/R$

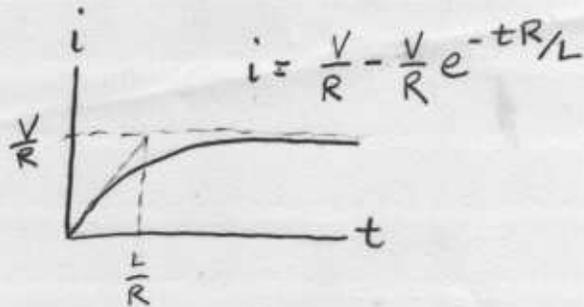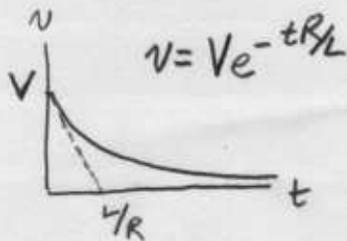


(B) $\tau = L/R$

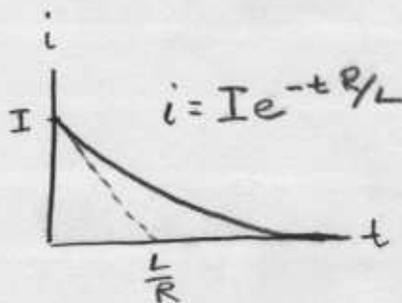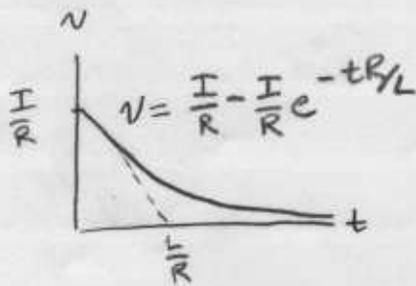

(C) $\tau = RC$

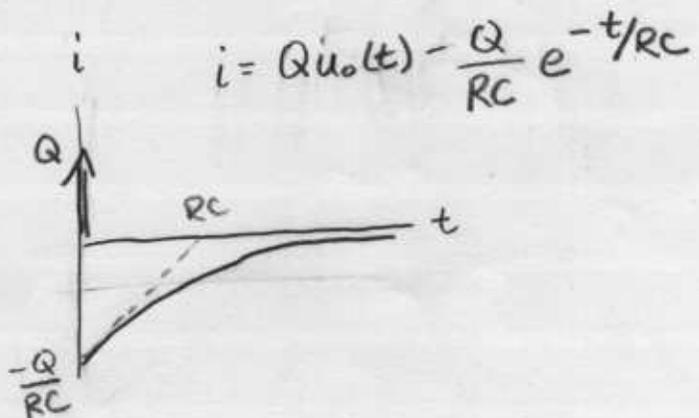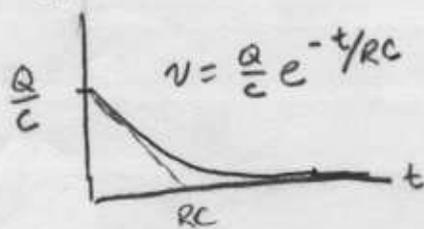


(D) $\tau = RC$

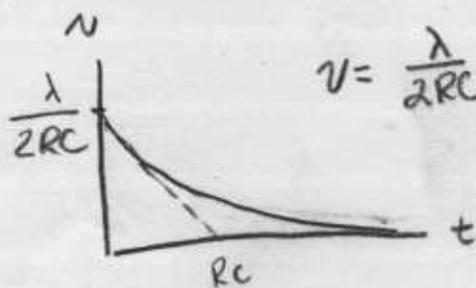

HW 7 SOLUTIONS p. 6

$$(E) \tau = \frac{L}{2R}$$

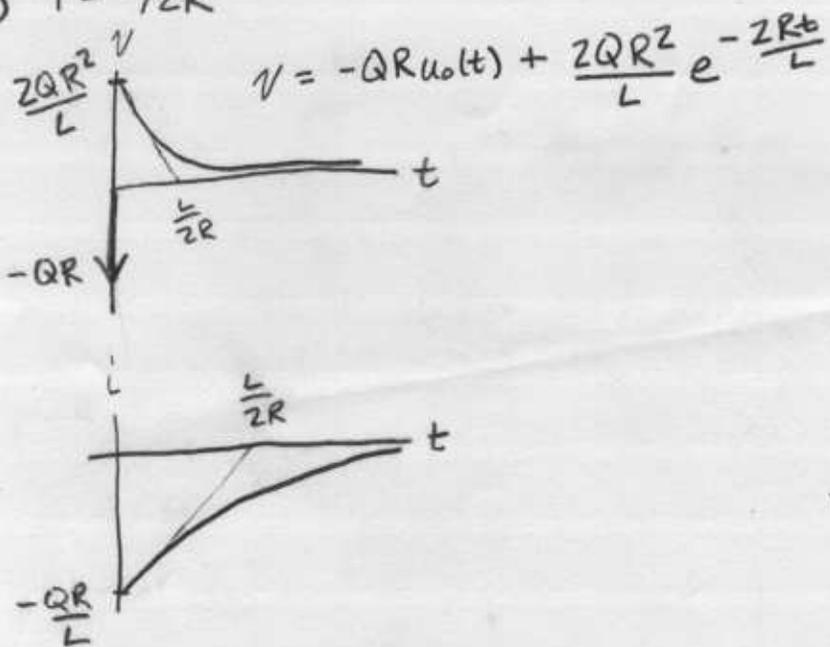

PROBLEM 7.3


(A) The graph shown is the output of a unit impulse excitation. The integral of this graph is the output of a unit step excitation.

$$v_0(t) = \int \frac{2}{3} e^{-t/\tau} dt \quad \text{for } t > 0$$


$$v_0(t) = -\frac{2V\tau}{3} e^{-t/\tau} + C$$

There is no impulse in the output of the impulse response, therefore we can assume that the voltage starts at $v(0) = 0$
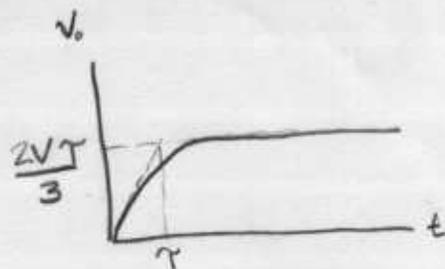
$$v_0(t) = \frac{2V\tau}{3} - \frac{2V\tau}{3} e^{-t/\tau}$$



HW 7 SOLUTIONS P. 7

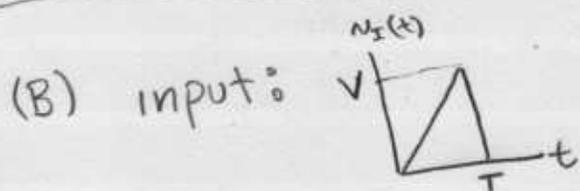

$$v_I(t) = \frac{v}{T}u_{-2}(t) - \frac{v}{T}u_{-2}(t-T) - vu_{-1}(t-T)$$

the input is the sum of 3 inputs,

- ① a ramp of slope v/T that starts at $t=0$
- ② a ramp of slope $-v/T$ that starts at $t=T$
- ③ a down step $\frac{v}{T}$ at $t=T$.

output: sum of 3 individual responses.

① a ramp is the integral of the step.

$$v_o = \int \left[\frac{2vT}{T^3} - \frac{2vT}{T^3} e^{-t/\tau} \right] dt = \frac{2vT}{T^3}t + \frac{2vT^2}{T^3} e^{-t/\tau} + C$$


$$v_o(0) = 0 \quad C = -\frac{2vT^2}{3T}$$

$$\Rightarrow v_o = \frac{2vT^2}{T^3} e^{-t/\tau} + \frac{2vT}{T^3}t - \frac{2vT^2}{3T}$$




② this is a negative scaled ramp
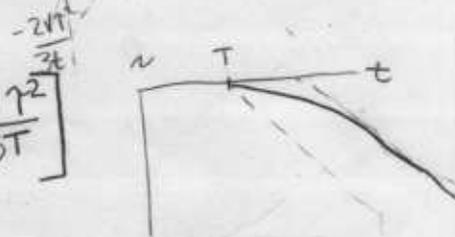
$$\Rightarrow v_o = u_{-1}(t-T) \left[-\frac{2vT^2}{3T} e^{-\frac{t-T}{\tau}} - \frac{2vT}{3T}(t-T) + \frac{2vT^2}{3T} \right]$$



③ this is a negative step
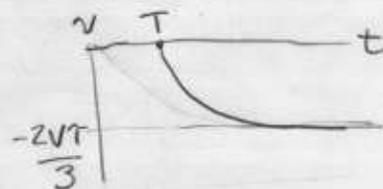
$$\Rightarrow v_o = u_{-1}(t-T) \left[\frac{2vT}{3} e^{-\frac{t-T}{\tau}} - \frac{2vT}{3} \right]$$



Total:

$$v_o(t) = \begin{cases} \frac{2vT^2}{3T} e^{-t/\tau} + \frac{2vT}{3T}t - \frac{2vT^2}{3T}, & 0 < t < T \\ \frac{2vT}{3} e^{-t/\tau} \left[\frac{\tau}{T} + (1 - \frac{\tau}{T}) e^{T/\tau} \right] u_{-1}(t-T), & T < t \end{cases}$$

See next page for calc. of

HW 7 SOLUTIONS P. 8

$$\begin{aligned} \frac{1}{3}(t-T) &= \frac{2V\gamma^2}{3T} e^{t/T} + \frac{2V\gamma}{3T} t - \frac{2V\gamma^2}{3T} + \\ & - \frac{2V\gamma^2}{3T} e^{-\frac{(t-T)}{\gamma}} - \frac{2V\gamma}{3T} t + \frac{2V\gamma}{3} + \frac{2V\gamma^2}{3T} + \\ & \frac{2V\gamma}{3} e^{-\frac{(t-T)}{\gamma}} - \frac{2V\gamma}{3} \end{aligned}$$


$$= \frac{2V\gamma^2}{3T} e^{-t/T} - \frac{2V\gamma^2}{3T} e^{-t/T} e^{T/T} + \frac{2V\gamma}{3} e^{-t/T} e^{T/T}$$

$$= \frac{2V\gamma}{3} e^{-t/T} \left[\frac{\gamma}{T} - \frac{\gamma}{T} e^{T/T} + e^{T/T} \right]$$

$$= \frac{2V\gamma}{3} e^{-t/T} \left[\frac{\gamma}{T} + \left(1 - \frac{\gamma}{T}\right) e^{T/T} \right]$$

↗ this is the response after $T=t$
it decays to 0 as $t \rightarrow \infty$

PROBLEM 7.4

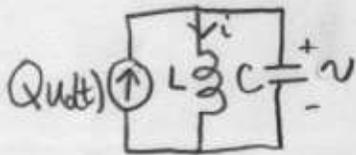

(A) The impulse places charge across the capacitor.

$$Q = CV, \text{ so } v(0^+) = Q/C$$

This voltage begins to change the current through the inductor, but cannot change it immediately $v = L \frac{di}{dt}$, so $i(0^+) = 0$

HW 7 SOLUTIONS P. 9

(B) at $t=0^+$ the current through the inductor increases because we have placed a positive voltage across it.

$$\boxed{\frac{di_L}{dt} \Rightarrow (+)}$$

The current induced through the inductor is negative through the capacitor.

$$i = C \frac{dv}{dt}$$


Because the current is negative, the voltage must be decreasing.

$$\boxed{\frac{dv_C}{dt} \Rightarrow (-)}$$

(c) differential equation for $v(t)$:

$$i = -C \frac{dv}{dt} \quad i = \frac{1}{L} \int v dt$$

$$\frac{1}{L} \int v dt + C \frac{dv}{dt} = 0$$

$$C \frac{d^2 v}{dt^2} + \frac{1}{L} v = 0$$

$$v'' + \frac{1}{LC} v = 0$$

choose $v = A \cos(\omega t)$ ← cosine because $v(0) \neq 0$

$$v' = -A \omega \sin(\omega t)$$

$$v'' = -A \omega^2 \cos(\omega t)$$

$$\rightarrow -A \omega^2 \cos(\omega t) + \frac{A}{LC} \cos(\omega t) = 0$$

$$\omega = \frac{1}{\sqrt{LC}}$$

HW 7 SOLUTIONS p.10

$$v_o(t) = A \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$v_o(0) = Q/C$$

$$v_o(t) = \frac{Q}{C} \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_o(t) = -C \frac{dv}{dt} = \frac{Q}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

EQUIVALENTLY, YOU COULD WRITE A DIFFERENTIAL EQN. FOR $i(t)$:

$$v = -\frac{1}{C} \int i dt \quad v = L \frac{di}{dt}$$

$$L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$i'' + \frac{1}{LC} i = 0$$

choose $i = A \sin(\omega t)$ ← sine because $i(0) = 0$

$$i' = A\omega \cos(\omega t)$$

$$i'' = -A\omega^2 \sin(\omega t)$$

$$\rightarrow -A\omega^2 \sin(\omega t) + \frac{1}{LC} \sin(\omega t) = 0 \quad \omega = \frac{1}{\sqrt{LC}}$$

$$i(t) = A \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$i(0) = 0$ ← this doesn't help us

$$v(t) = L \frac{di}{dt} = \frac{LA}{\sqrt{LC}} \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$v(0) = Q/C = LA/\sqrt{LC} \quad A = \frac{Q\sqrt{LC}}{LC} = \frac{Q}{\sqrt{LC}}$$

$$i(t) = \frac{Q}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$v(t) = \frac{Q}{C} \cos\left(\frac{t}{\sqrt{LC}}\right)$$