

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits and Electronics
Spring 2003

Handout S03-048 - Quiz # 2

Thursday April 9, 2003

Name: _____

Recitation Instructor (circle one):

Baldo Hutchinson Kolodziejewski Schindall Wilson

Recitation Hour (circle one):

9 10 11 12 1 2


ALL PROBLEMS CARRY THE SAME WEIGHT

Problem	Points	Score	Grader
1	25		
2	25		
3	25		
4	25		
Total	100		

Name: _____

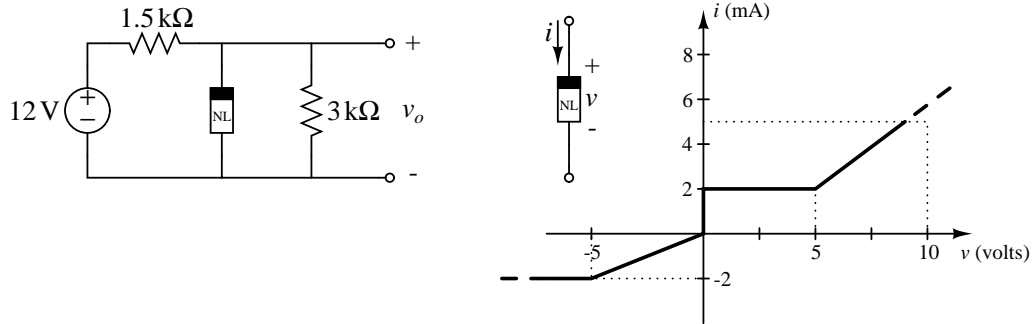PROBLEM 1

The circuit below contains a nonlinear element whose i v characteristics are shown.




(A) Determine the voltage v_o graphically - show your construction.

(B) Can this circuit be described by a Thevenin equivalent circuit at the terminals? Explain!


Name: _____

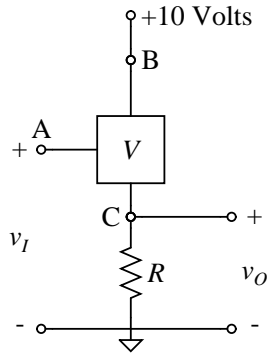PROBLEM 2

This circuit uses a control valve V which has the small-signal model shown.



Small-Signal Model of V

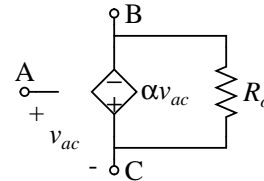

Assume that the static component of v_I establishes a suitable operating point at which the small-signal model applies.

- (A) Sketch and label a small-signal model of the circuit which can be used to calculate the small-signal voltage gain $A_v = \frac{v_o}{v_i}$ where v_o and v_i are the small-signal components of v_O and v_I .

Name: _____

(B) Express v_{ac} in terms of v_i and v_o .

For Extra Credit: (one-third the value of a problem)


(C) Derive an expression for $A_v = \frac{v_o}{v_i}$, the incremental voltage gain.

Name: _____

PROBLEM 3


For each of the circuits below, determine the initial and final (asymptotic) values of the indicated variables.

(A)

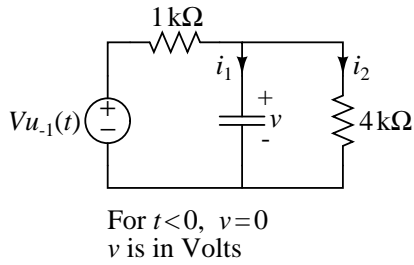

VARIABLE	$t = 0^+$	$t \rightarrow \infty$	UNITS
v			
i_1			
i_2			

(B)


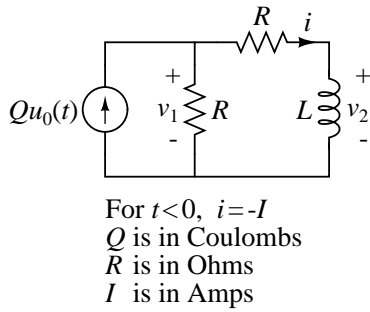


VARIABLE	$t = 0^+$	$t \rightarrow \infty$
i		
v_1		
v_2		

Name: _____

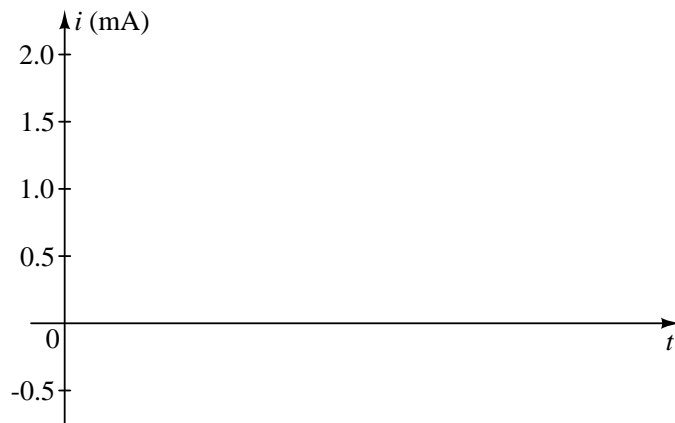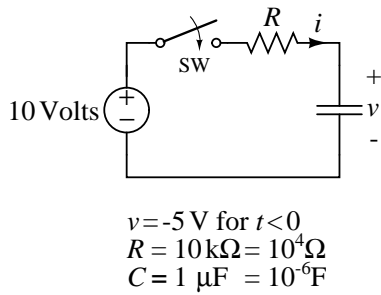PROBLEM 4

The capacitor in the circuit below is initially charged to the voltage $v = -5$ Volts. At $t = 0$ the switch closes.



- (A) Without detailed analysis of the circuit, sketch $v(t)$ and $i(t)$ for $t > 0$. Label initial values and asymptotes.
- (B) Determine the time constant with which the circuit responds.
- (C) Express either $v(t)$ or $i(t)$ as a function of time. If you can do this without first developing an analytical solution, fine.

Name: _____

THIS PAGE INTENTIONALLY LEFT BLANK FOR WORK ON PROBLEM 4