

1

(503-055) PAUL E. GARY

# NOTES FOR 6002 LECTURE # 19, APRIL 17, 2003

READ: 16.1 - 16.5

A NEW TOPIC: OPERATIONAL AMPLIFIERS.

FIRST A FEW WORDS ABOUT NEGATIVE FEEDBACK (ERROR CORRECTING FEEDBACK)

EXAMPLES: A THERMOSTAT IN AN OVEN (ON-OFF IN NATURE)

DRIVING ON A ROAD WITH CURVES


AUTOMATIC CONTROL OF A SHIP'S HEADING

IN EACH CASE A COMPARATOR (THERMOSTAT BISTABLE ELEMENT, EYES AND BRAIN, AN ANGLE SENSOR ON A GYROCOMPASS), DETECTS AN ERROR AND INSTRUCTS AN OUTPUT DEVICE (HEATING ELEMENT, STEERING WHEEL, RUDDER POSITION SETTING MECHANISM) TO RESPOND TO REDUCE THE ERROR.

AN OPERATIONAL AMPLIFIER COMBINES A COMPARATOR AND AN AMPLIFIER WHICH PRODUCES THE ELECTRICAL RESPONSE.

CIRCUIT DIAGRAM - TWO INPUTS (741 USED IN LAB 4)

SYMBOL

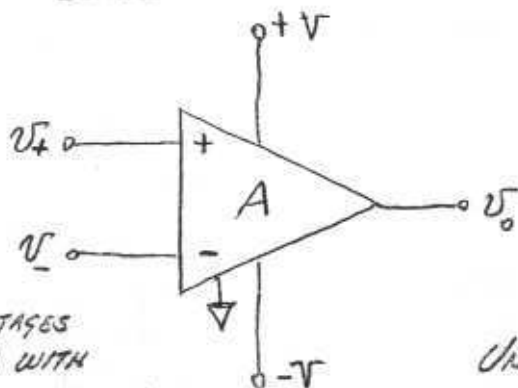

ALL VOLTAGES  
DEFINED WITH  
RESPECT TO GROUND

$\pm V$  COMMONLY  $\pm 5-12$  VOLTS

A IS THE VOLTAGE TRANSFER  
RATIO (A CONSTANT)

$V_+$ ,  $V_-$  ARE INPUT VOLTAGES

$V_0$  IS THE OUTPUT VOLTAGE

UNDER APPROPRIATE CONDITIONS:


$$\underline{V_0 = A(V_+ - V_-)}$$

THIS IS A DIFFERENCE AMPLIFIER. IT RESPONDS NOT TO  $V_+$  OR  $V_-$  BUT TO THEIR DIFFERENCE ( $V_+ - V_-$ )

A IS COMMONLY QUITE LARGE  $A \sim 10^5$  TO  $10^6$   $\frac{\text{VOLTS}}{\text{VOLT}}$

IT REQUIRES NEGLECTIBLE CURRENT AT THE INPUTS. WE ASSUME ZERO INPUT CURRENT

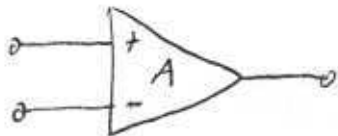USUALLY THE CIRCUIT SYMBOL IS SIMPLIFIED TO:




BUT REMEMBER THAT THIS CONTROL VALVE GETS ITS ENERGY FROM  $\pm V$ .

THE OP-AMP HAS DEFECTS: ITS GAIN  $A$  VARIES CONSIDERABLY FROM UNIT TO UNIT.  
IT IS EXTRAORDINARILY TEMPERATURE SENSITIVE.

THE DEFECTS ARE DEALT WITH BY PUTTING NEGATIVE FEEDBACK AROUND THE OP-AMP.

DEMO

SIMPLEST NON-INVERTING CIRCUIT:

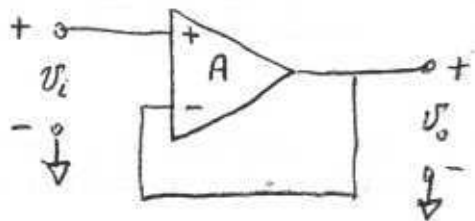

CONSIDER QUALITATIVE ACTION

ANALYSIS:


$$V_o = A(V_+ - V_-)$$

$\uparrow$   $V_i$        $\downarrow$   $V_o$

$$V_o = AV_i - AV_o$$

$$V_o(1+A) = AV_i \quad \frac{V_o}{V_i} = \frac{A}{1+A} \approx 1$$

A MORE USEFUL NON-INVERTING CIRCUIT:

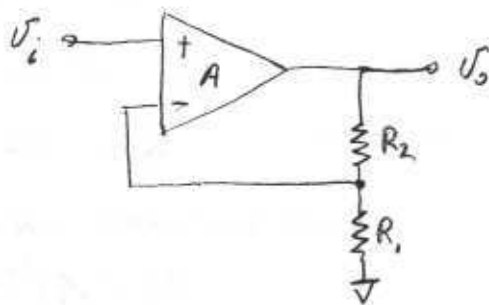

ANALYSIS:

$$V_o = A(V_+ - V_-)$$

$$V_+ = V_i$$

$$V_- = \frac{R_1}{R_1 + R_2} V_o$$

$$V_o + A \frac{R_1}{R_1 + R_2} (V_o) = AV_i$$


$$\text{IF } A \frac{R_1}{R_1 + R_2} \gg 1 \quad \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_1}$$

$$\frac{V_o}{V_i} = \frac{A}{1 + A \frac{R_1}{R_1 + R_2}}$$

THIS APPROXIMATION IF THE OPEN LOOP GAIN  $A$  IS MUCH GREATER THAN THE GAIN WITH FEEDBACK  $\frac{R_1 + R_2}{R_1}$ , WHICH CAN EASILY BE SET (VIA  $R_1$ ) TO BE AS LARGE AS  $10^3$  OR SO.

DEMO

THERE IS ALSO AN INVERTING VERSION:

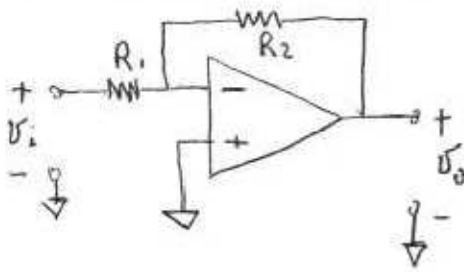

ANALYSIS:

$$V_o = A(V_+ - V_-)$$

$$V_- = V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2}$$

SUBSTITUTE AND SOLVE

$$\frac{V_o}{V_i} = - \frac{A \frac{R_2}{R_1 + R_2}}{1 + A \frac{R_1}{R_1 + R_2}} \approx - \frac{R_2}{R_1}$$

CONSIDER QUALITATIVE ACTION

THE APPROXIMATION IS VALID

$$\text{IF } \frac{AR_2}{R_1 + R_2} \gg 1$$

THE AMPLIFYING RANGE AT THE OUTPUT IS LIMITED BY  $\pm V$


USEFUL SIMPLIFYING APPROXIMATIONS:

THE IDEAL OP-AMP  $A \rightarrow \infty$  WHICH MEANS ANY

FINITE OUTPUT  $V_o$  CAN BE DEVELOPED WITH AN INFINITESIMAL

VOLTAGE DIFFERENCE AT THE INPUT I.E.  $V_+ \approx V_-$

CONSIDER

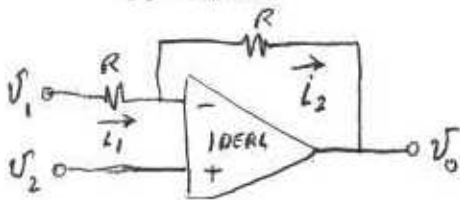

ANALYSIS:  $V_+ = V_-$   
 $I_1 = I_2$  (NO OP-AMP INPUT CURRENT)

THUS

$$\frac{V_1 - V_2}{R} = \frac{-V_o}{R} \text{ OR } \underline{V_o = V_1 - V_2}$$

WHICH ILLUSTRATES ANOTHER USEFUL CONCEPT IN THE

INVERTING CONNECTION: THE "CURRENT MIRROR"  $I_1 = I_2$

NOTE THAT ALL THIS ANALYSIS EMBODIES A CIRCUIT MODEL FOR THE OP AMP:

