

WITH SOLUTIONS
(S03-054)

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits and Electronics
Spring 2003

Handout S03-048 - Quiz # 2

Thursday April 9, 2003

Name: _____

Recitation Instructor (circle one):

Baldo Hutchinson Kolodziejksi Schindall Wilson

Recitation Hour (circle one):

9 10 11 12 1 2



ALL PROBLEMS CARRY THE SAME WEIGHT

Problem	Points	Score	Grader
1	25		
2	25		
3	25		
4	25		
Total	100		

Name: _____

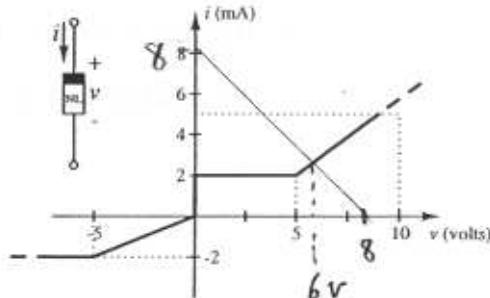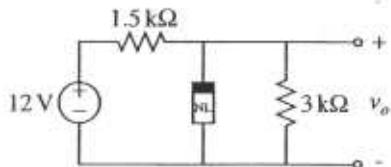PROBLEM 1

The circuit below contains a nonlinear element whose *iv* characteristics are shown.



- (A) Determine the voltage v_O graphically - show your construction.

REDUCE THE LINEAR PORTION OF THE CIRCUIT TO A THEVENIN EQUIVALENT:

$$V_{OC} = 12 \cdot \frac{3k}{4.5k} = 8V$$

Use a load-line construction:

$$R_{TH} = 1.5k \parallel 3k = 1k$$

$$\text{INTERCEPTS: } i=0 \quad v_o = 8V$$

$$v_o = 0 \quad i = \frac{8V}{1k} = 8mA$$

$$\text{ZERO INTERSECTION: } v_o \approx 6V$$


- (B) Can this circuit be described by a Thevenin equivalent circuit at the terminals? Explain!

No The concept of Thevenin equivalents is built on the superposition principle which demands linear elements

Name: _____

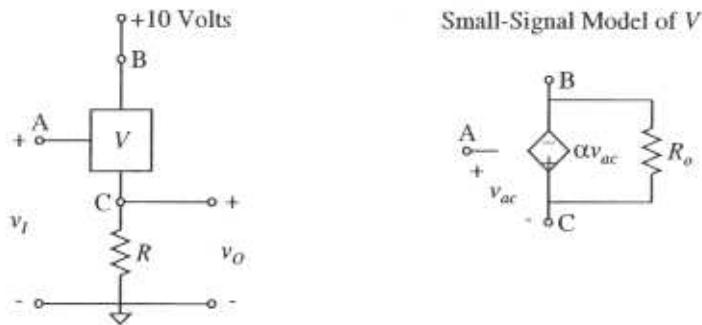
PROBLEM 2

This circuit uses a control valve V which has the small-signal model shown.



Assume that the static component of v_I establishes a suitable operating point at which the small-signal model applies.

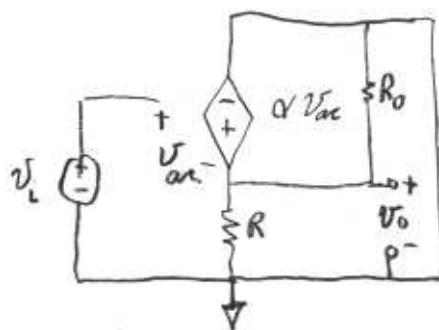- (A) Sketch and label a small-signal model of the circuit which can be used to calculate the small-signal voltage gain $A_v = \frac{v_o}{v_i}$ where v_o and v_i are the small-signal components of v_O and v_I .



Name: _____

(B) Express v_{ac} in terms of v_i and v_o .

$$V_{ac} = V_i - V_o$$

For Extra Credit: (one-third the value of a problem)

(C) Derive an expression for $A_v = \frac{v_o}{v_i}$, the incremental voltage gain.

$$V_o = \alpha V_{ac} = \alpha(V_i - V_o)$$

$$V_o(1+\alpha) = \alpha V_i$$

$$\frac{V_o}{V_i} = A_v = \frac{\alpha}{1+\alpha}$$


NOTE THAT R AND R_o ARE IN PARALLEL AND THE VOLTAGE ACROSS THEM IS V_o

Name: _____

PROBLEM 3


For each of the circuits below, determine the initial and final (asymptotic) values of the indicated variables.

(A)

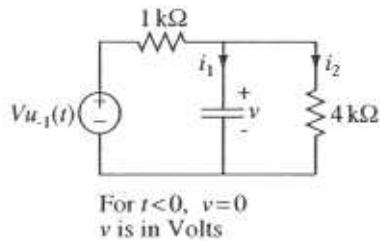


VARIABLE	$t = 0^+$	$t \rightarrow \infty$	UNITS
v	0	0.8	V
i_1	1	0	mA
i_2	0	0.2	mA

THEVENIN EQUIVALENT SEEN BY C:

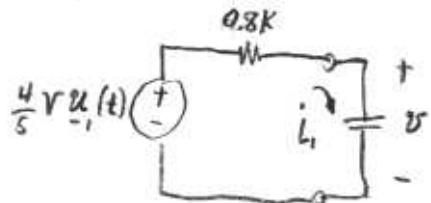


THE CAPACITOR VOLTAGE STARTS AT ZERO, RISE TO 0.8V
 i_1 STARTS AT $\frac{0.8V}{0.8k} = 1\text{ mA}$ AND FALLS TO ZERO
 $i_2 = \frac{v}{4k}$, STARTS AT ZERO, RISES TO $\frac{0.8V}{4k} = 0.2\text{ mA}$

(B)

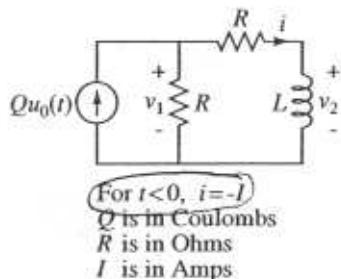

VARIABLE	$t = 0^+$	$t \rightarrow \infty$
i	$\frac{QR}{L} - I$	0
v_1	$-R(\frac{QR}{L} - I)$	0
v_2	$-2R(\frac{QR}{L} - I)$	0

NORTON EQUIVALENT SEEN BY L:

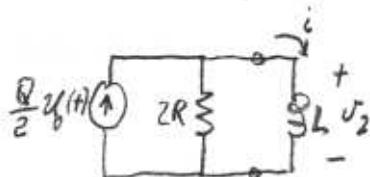

THE CURRENT IMPULSE PRODUCES A VOLTAGE IMPULSE $\frac{Q}{2} \times 2R = QR$ ACROSS L AND 2R. THIS ESTABLISHES AN INDUCTOR CURRENT $i(0+) = 1 \frac{QR}{L} - I$. THIS CURRENT DECAYS TO ZERO THROUGH 2R ESTABLISHING A VOLTAGE


$$U_2(0+) = -2R \left(\frac{QR}{L} - I \right)$$

OBVIOUSLY IN ORIGINAL CIRCUIT $v_1 = U_2/2 = -R \left(\frac{QR}{L} - I \right)$

Name: _____

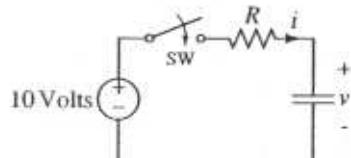PROBLEM 4

The capacitor in the circuit below is initially charged to the voltage $v = -5$ Volts. At $t = 0$ the switch closes.



$$v = -5 \text{ V for } t < 0$$

$$R = 10 \text{ k}\Omega = 10^4 \Omega$$

$$C = 1 \mu\text{F} = 10^{-6} \text{ F}$$

$$\text{INITIAL VOLTAGE} = -5 \text{ V}$$


$$\text{INITIAL CURRENT:}$$

$$i = \frac{10 - (-5)}{10k} = 1.5 \text{ mA}$$

DECAYS TO ZERO

FINAL CURRENT = 0

FINAL VOLTAGE = +10

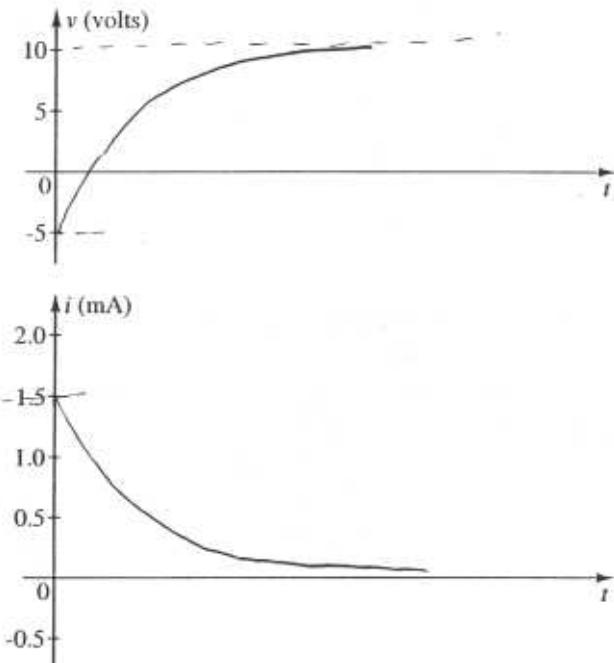

- (A) Without detailed analysis of the circuit, sketch $v(t)$ and $i(t)$ for $t > 0$. Label initial values and asymptotes.

- (B) Determine the time constant with which the circuit responds.

$$\tau = RC = 10^4 \times 10^{-6} = 10^{-2} \text{ sec}$$

$$\underline{\underline{\tau = 10 \text{ msec}}}$$

- (C) Express either $v(t)$ or $i(t)$ as a function of time. If you can do this without first developing an analytical solution, fine.

$$i(t) = 1.5 e^{-t/\tau} \text{ mA}$$

$$v(t) = -5 + 15(1 - e^{-t/\tau}) \text{ V} \approx 10 - 15e^{-t/\tau} \text{ V}$$