

First, a few general thoughts regarding this unit on operational amplifiers (op-amps).

How do engineers (and others) deal with design and analysis of large, complex systems?

- Break large systems into [relatively] independent subsystems
- Sometimes called "modules," or "blocks," or "layers."

This happens all the time.

- Divide automobile into engine, transmission, power steering, braking, electrical
- Different cross-sections depending on questions asked
- Electrical contains elements from engine, transmission, etc.
- Reference is "Zen and the Art of Motorcycle Maintenance"  
By Robert Persig.

- In software design, divide software into layers
- e.g. BIOS, then DOS or Windows (op sys), then word processor (app)
- In hardware design, divide circuit into blocks (block diagram)
- Radio has antenna, RF, LO, mixer, IF, detector, amp, PA.


Many mechanical designs use high gain amplifier plus negative feedback

- Power steering
- Cruise control
- Control of many biological processes
- PEOPLE (you and me)
- Catching a baseball
- Wheelchair tennis
- Lifting your arm to a set position (we'll try this in class!)


Development of integrated circuits led to design of integrated op-amps

- Credited to Bob Pease, MIT '61, in late '60's
- Devices were 702, 709, 741 (still used!)
- Pease still at National Semiconductor, still writes informative columns
- Excellent example of compartmentalization
- Could achieve result with fewer transistors but
- Gain block is easy to design with
- Transistors are "cheap" to incorporate on IC
- Mass production is efficient
- Feedback allows consistent transfer function despite op-amp inaccuracies  
(see homework problem 10.1)

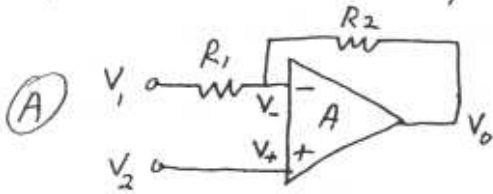Quick review of simple op-amp configurations



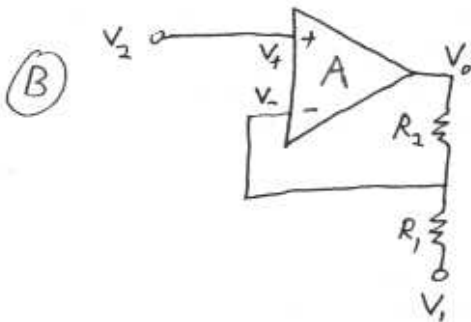With  $V_2 = 0$ , this is an inverting amplifier  
 For  $A \gg \frac{R_2}{R_1}$ ,  $V_- \approx V_+$  and  $V_0 = -\frac{R_2}{R_1} V_1$



With  $V_1 = 0$ , this is a non-inverting amplifier

For  $A \gg \frac{R_1 + R_2}{R_1}$ ,  $V_- \approx V_+$  and  $V_0 =$

$$V_0 = \left(1 + \frac{R_2}{R_1}\right) V_2$$

$\uparrow$  from voltage across  $R_1$        $\uparrow$  from voltage across  $R_2$

What if we use (A) with  $V_1 = 0$  and input is  $V_2$ ?

Then it's the identical circuit to (B),  
 just drawn differently

What if we use (B) with  $V_2 = 0$  and input is  $V_1$ ?

Then it's the identical circuit to (A),  
 just drawn differently

By superposition

$$V_0 = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_2$$

Actual op-amp circuits have output resistance

[Show 741 schematic diagram]

But the negative feedback causes op-amp to do


"whatever it takes" to achieve  $-\frac{R_2}{R_1} V_{IN}$  (inverting case)

This significantly reduces the effective output resistance

[but not under all conditions, as we shall demonstrate]

Let's examine op-amp with negative feedback

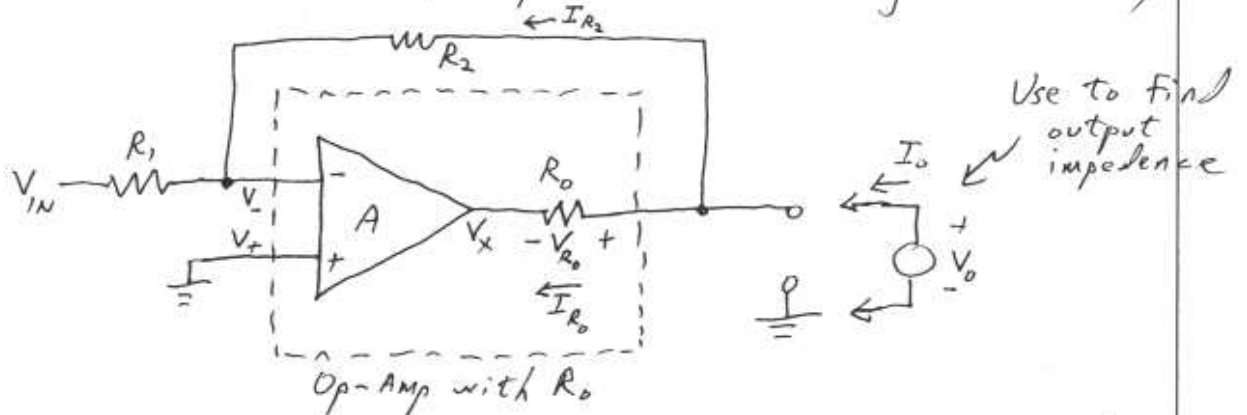Will use external output resistor to gain visibility



Can make Thevenin equivalent

With  $V_{IN} = 0$ , connect  $V_0$  to output and calculate  $I_0$

$$V_0 \text{ at output} \rightarrow \frac{R_1}{R_1 + R_2} V_0 \text{ at } V_-$$

$$\text{Which produces } -A \frac{R_1}{R_1 + R_2} V_0 \text{ at } V_x$$

$$\text{So } V_{R_0} = V_0 - \left[ -A \frac{R_1}{R_1 + R_2} V_0 \right] = V_0 \left[ 1 + A \frac{R_1}{R_1 + R_2} \right]$$

$$\text{and } I_{R_0} = \frac{V_0}{R_0} \left[ 1 + A \frac{R_1}{R_1 + R_2} \right]$$

$$I_0 = I_{R_0} + I_{R_2} = \frac{V_0}{R_0} \left[ \underbrace{1 + A \frac{R_1}{R_1 + R_2}}_{\approx A \frac{R_1}{R_2}} \right] + \frac{V_0}{R_2} \text{ small}$$

$$\text{So } \frac{V_0}{I_0} \approx \frac{R_0}{A \left[ \frac{R_1}{R_2} \right]} \text{ inverse gain}$$

What is going on?

$V_o$  at output pulls right end of  $R_o$  "up" by  $V_o$  volts  
 But this pulls  $V_-$  up by  $\frac{R_1}{R_1+R_2}$  volts, which

is approx the inverse gain of the amplifier

This ~~part~~ is amplified by the op-amp, pulling the left side of  $R_o$  down by  $A \times [\text{inverse gain}]$

IF gain = 100 and  $A = 10^5$


left side of  $R_o$  goes down by 1000  $V_o$

So  $R_o$  pulls 1001 times the current that it would pull if connected to ground


Feedback makes  $R_o$  act like  $\frac{R_o}{1001}$

$30\Omega \rightarrow 30 \text{ milliohms}$


Thevenin equivalent is approx

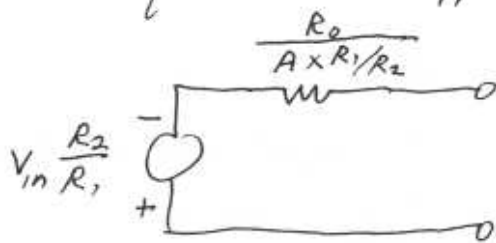

DEMO #1

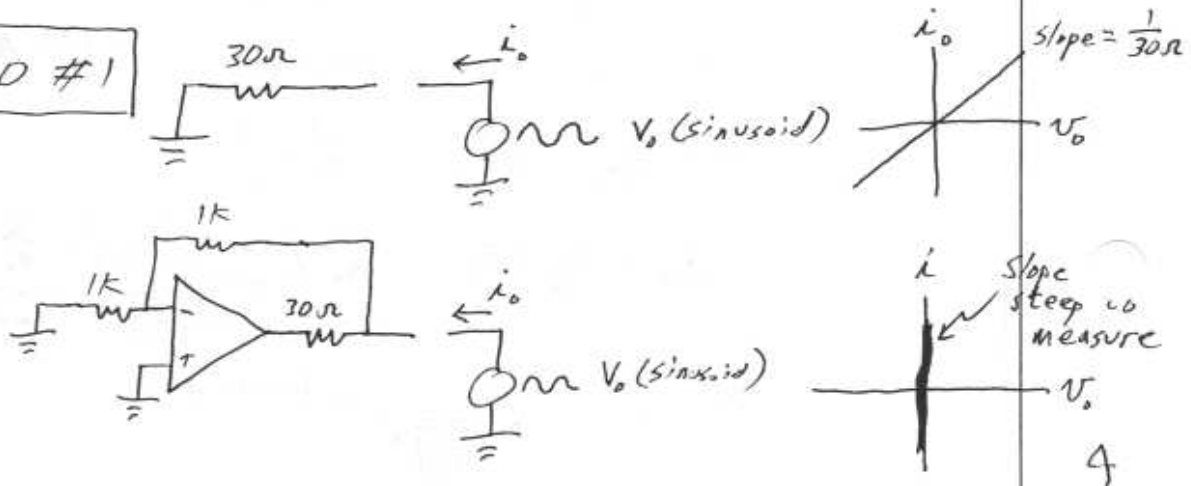

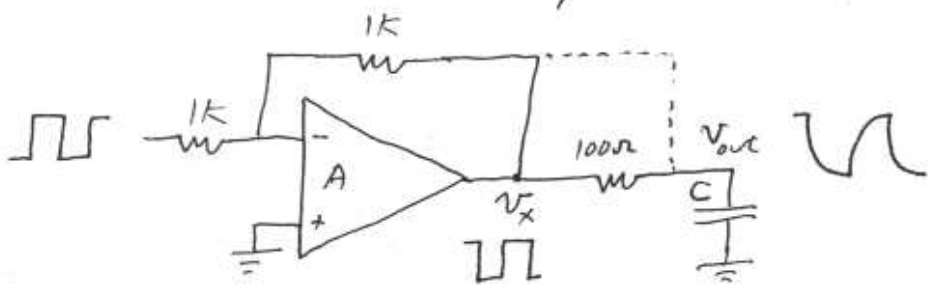What if we use an op-amp with square wave  $V_{in}$  to drive a capacitor? Start with  $100\Omega$  "output resistance" outside the feedback loop



Now connect the feedback directly to the capacitor, as shown by the dotted line

If  $A = 10^6$ , should reduce output impedance ~~to~~ from  $100\Omega$  to  $200\mu\Omega$

Would expect this to force square wave at capacitor, right?


Wrong!

[Student Fill in waveform here] →

Why is this?

[Discussion in class]

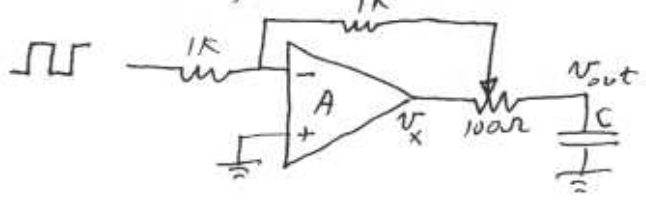What if we gradually move feedback from  $V_x$  to  $V_{out}$



$V_{out}$  starts as  $\sim$  and improves to  $\sim$

$V_x$  starts as  $\square$  and moves to  $\sim$  to provide additional charging current to C

But eventually the  $V_x$  peaks hit the op-amp voltage limits 5

Op-Amp ~~and~~ circuit analysis

Start with what you know


(input voltage, etc.)

Move where circuit constraints "help" you

$$V_+ = V_- \quad i_{in} = 0 \quad \text{at op-amp} \\ \text{(in active region with feedback)}$$

It's like the game of minesweeper

[describe]

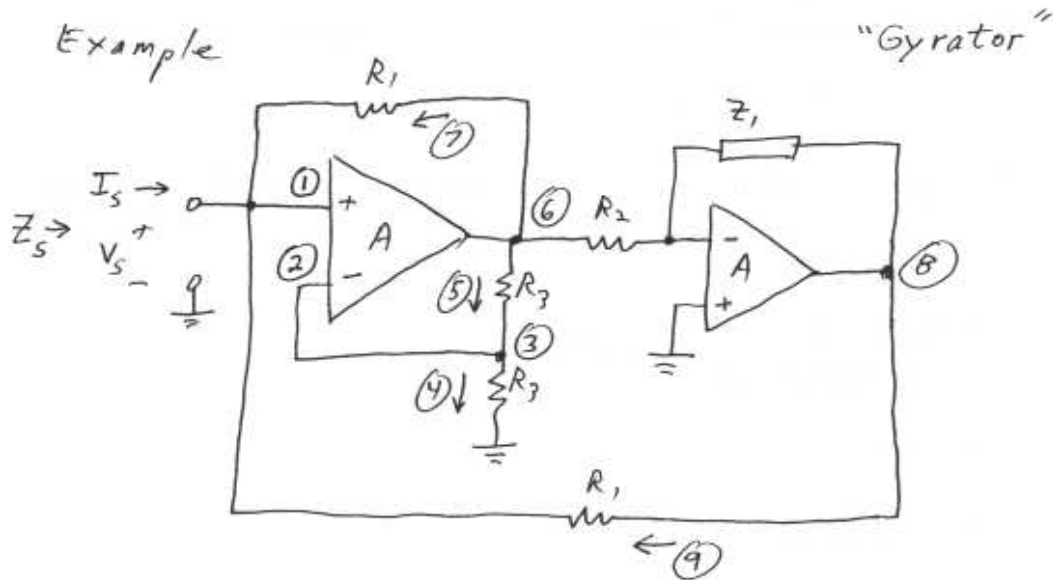

Flow is from ① to ② to ... to ⑨

Every step is easy