

(503-0602)

PROBLEM 10.1

A) First, we convert to a system of 3 equations:

$$y = A\delta \quad \delta = x - y' \quad y' = \beta y$$

Next, simplify to a single equation:

$$y = A[x - y'] = A[x - \beta y]$$

$$y = Ax - A\beta y$$

Solving for  $y$  we get:

$$y = \frac{Ax}{1+A\beta} \Rightarrow \boxed{\frac{y}{x} = T = \frac{A}{1+A\beta}}$$

B)  $T = \frac{A}{1+A\beta} \Rightarrow$  (in table form)  $\Rightarrow$

| A               | T     |
|-----------------|-------|
| $10^5$          | 99.90 |
| $5 \times 10^5$ | 99.98 |
| $10^6$          | 99.99 |

from the table,

$$\boxed{\Delta T = 0.09}$$

assuming  $A = 500,000$  (the midrange value)

$$\boxed{\frac{\Delta T}{T} = \frac{0.09}{99.98} \approx 9 \times 10^{-4}}$$


$$dT = \frac{dA(1+A\beta) - A(\beta dA)}{(1+A\beta)^2} \Rightarrow \boxed{\frac{dT}{dA} = \frac{1}{(1+A\beta)^2}}$$

$$\frac{dT}{T} = \left[ \frac{1}{(1+A\beta)^2} \right] \left[ \frac{1+A\beta}{A} \right] dA = \left[ \frac{1}{1+A\beta} \right] \frac{dA}{A} = f(A) \frac{dA}{A}$$

$$\boxed{f(A) = \frac{1}{1+A\beta}}$$

$$\frac{dT}{T} = f(A) \frac{dA}{A} = \left( \frac{1}{1+A\beta} \right) \left( \frac{dA}{A} \right) \Big|_{A=5 \times 10^5} = \boxed{(1.9996 \times 10^{-4}) \left( \frac{dA}{A} \right)}$$

c) First, we draw a system diagram:

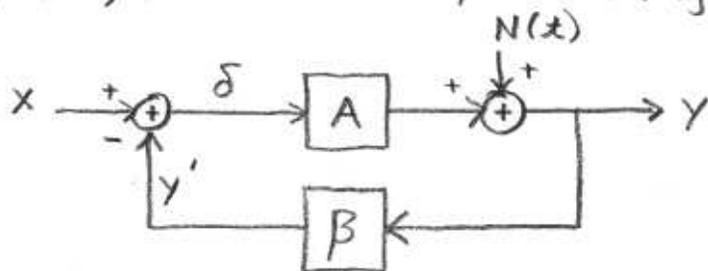

Then we write a system of equations and solve for  $y$  as a function of  $N(x)$ .

Because we are only interested in  $y$  as a function of  $N(x)$ , we can ignore the  $x$  input (superposition):  $x = 0$

$$\delta = 0 - y' = -y'$$

$$y' = \beta y$$

$$y = A\delta + N(x)$$

$$y = A(-y') + N(x) = A(-\beta y) + N(x)$$

$$y[1 + A\beta] = N(x)$$

$$\boxed{y = \frac{N(x)}{1 + A\beta}} \quad \text{or} \quad \boxed{\frac{y}{N(x)} = \frac{1}{1 + A\beta}}$$

from Part B:  $A = 5 \times 10^5$ ,  $\beta = .01$

$$\boxed{y = \frac{5V}{1 + A\beta} = 9.998 \times 10^{-4}}$$

D) We can substitute  $A(s) = \frac{A_0 s_1}{s + s_1}$  directly into the expression for  $T$  from Part A:

$$T = \frac{A(s)}{1 + A(s)\beta} = \frac{A_0 s_1}{s + s_1} \cdot \frac{1}{1 + \frac{\beta A_0 s_1}{s + s_1}} = \frac{A_0 s_1}{s + s_1} \cdot \frac{s + s_1}{s + s_1 + \beta A_0 s_1} = \frac{A_0 s_1}{s + (1 + A_0 \beta) s_1}$$

$$\boxed{T \approx \frac{A_0 s_1}{s + A_0 \beta s_1}}$$

This is the transfer function of a lowpass filter with a single pole at  $\omega = A_0 \beta s_1$ .

### PROBLEM 10.2

These are all ideal opamps, therefore we make the following assumptions:

- $i_{IN+} = i_{IN-} = 0$
- $v_+ = v_-$
- $v_o$  is whatever it has to be to guarantee the other assumptions

A)  $v_+ = 0$  implies that  $v_- = 0$

All of the current,  $I$ , flowing through  $R_1$  must flow through  $R_2$  ... the input current,  $i_{IN-}$ , is zero.

$$\text{Therefore: } I = \frac{v_1 - v_-}{R_1} = \frac{v_- - v_o}{R_2} \quad (v_- = 0)$$

$$\frac{v_1}{R_1} = -\frac{v_o}{R_2}$$

$$\boxed{v_o = \left(-\frac{R_2}{R_1}\right)v_1}$$

B) We can find  $v_+$  using the voltage divider relationship:

$$v_+ = v_2 \left[ \frac{R_2}{R_1 + R_2} \right] \quad (\text{and we know that } v_- = v_+)$$

Now we use the relationship from Part A:

$$\frac{v_1 - v_-}{R_1} = \frac{v_- - v_o}{R_2}$$

solving for  $v_o$  and collecting terms gives

$$v_o = \left[ \frac{R_1 + R_2}{R_1} \right] v_- - \frac{R_2}{R_1} v_1$$

substituting for  $v_-$ , we get

$$v_o = \left[ \frac{R_1 + R_2}{R_1} \right] \left[ \frac{R_2}{R_1 + R_2} \right] v_2 - \frac{R_2}{R_1} v_1 \quad \text{or} \quad \boxed{v_o = \frac{R_2}{R_1} [v_2 - v_1]}$$

c) Again, we can solve directly for  $v_+$  (and therefore  $v_-$ ),  
 $v_+$  is halfway between  $v_1$  and  $v_2$ :

$$v_+ = \frac{v_1 + v_2}{2} = v_-$$

To find  $v_o$ , we write

$$\frac{v_3 - v_-}{R} = \frac{v_- - v_o}{R} \Rightarrow v_o = -(v_3 - 2v_-) \\ = 2v_- - v_3$$

substituting for  $v_-$  gives

$$v_o = 2\left(\frac{v_1 + v_2}{2}\right) - v_3 \Rightarrow \boxed{v_o = v_1 + v_2 - v_3}$$

### PROBLEM 10.3

For all of these opamp problems, we first solve directly for  $v_+$  or  $v_-$  and assume the other one is the same.

Then we use the fact that the input currents are zero to write an expression relating  $v_o$  to the input voltages and  $v_+$  and  $v_-$ .

Finally we substitute for  $v_+$  and  $v_-$  and solve for  $v_o$ .

$$v_+ = 0 = v_-$$

$$i_D = \frac{K}{2} (v_{GS} - V_T)^2 = \frac{K}{2} (v_1 - v_- - V_T)^2 = \frac{v_1 - v_o}{R}$$

$$v_o = -\frac{KR}{2} [v_1 - V_T]^2 = -.25 [v_1 - 1]^2$$

$$v_o = -\left(\frac{v_1 - 1}{2}\right)^2$$

This expression is only valid if  $v_1 > 1V$ . If  $v_1 < 1V$ , there is no current flowing and  $v_o$  must be zero.

$$\boxed{v_o = \begin{cases} -\left(\frac{v_1 - 1}{2}\right)^2 & v_1 > 1V \\ 0 & v_1 < 1V \end{cases}}$$

### PROBLEM 10.4

A) This is an inverting amplifier, similar to problem 10.2 part A. The only difference is that  $R_2$  has been replaced by a complex impedance,  $\frac{1}{Cs}$ .

Therefore,  $\frac{V_o}{V_i} = \bar{A}(s) = -\frac{1/Cs}{R}$


$\bar{A}(s) = -\frac{1}{RCs}$

which is an integrator. (think of Laplace)


Because the opamp is ideal, this expression holds for all frequencies:

$0 \leq \omega \leq \infty$

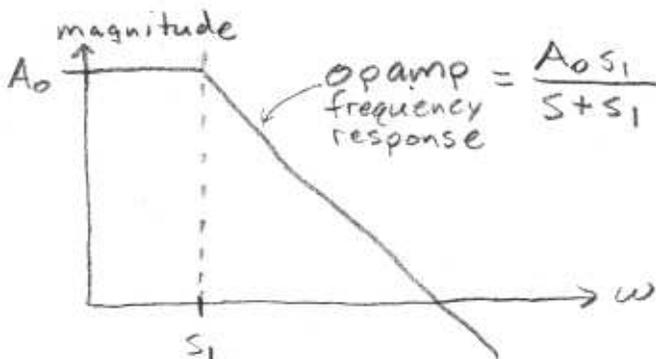But in the real world, the opamp has a finite gain,  $A_o$ , at low frequencies as shown below:



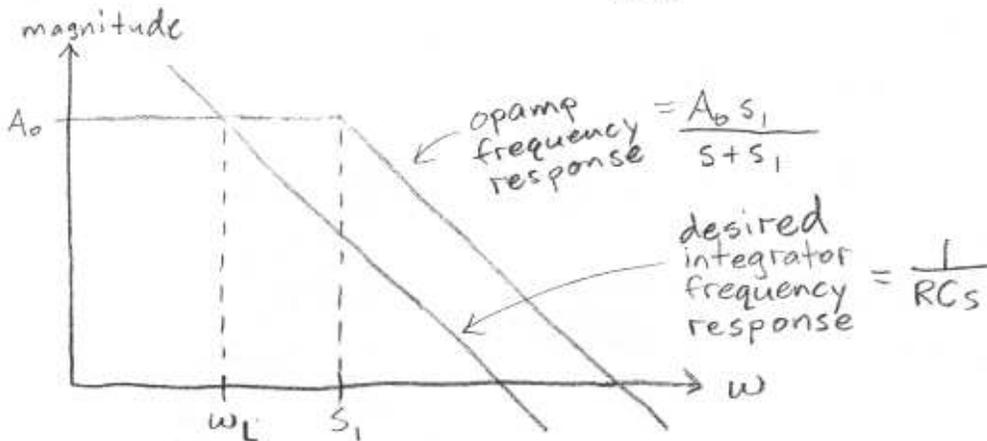At some frequency  $\omega = \omega_L$ , the integrator runs out of "headroom". It needs more gain than the opamp can provide. So the  $\bar{A}(s) = \frac{1}{RCs}$  is only valid for  $s \gg \omega_L$ .



50 SHEETS  
100 SHEETS  
200 SHEETS  
22-141  
22-142  
22-144  
AMPAC

B) This is a non-inverting amplifier topology. We can write  $\bar{A}(s)$  directly, in a way similar to Part A:

$$\bar{A}(s) = \frac{\bar{v}_o}{\bar{v}_i} = 1 + \frac{R}{Ls \parallel \frac{1}{Cs}}, \text{ where } Ls \parallel \frac{1}{Cs} = \frac{L/C}{Ls + \frac{1}{Cs}} = \frac{Ls}{LCs^2 + 1}$$

$$\bar{A}(s) = 1 + \frac{R}{\frac{Ls}{LCs^2 + 1}} = 1 + \frac{RLCs^2 + R}{Ls} = \frac{Ls + RLCs^2 + R}{Ls}$$

$$\bar{A}(s) = \frac{s^2 + \frac{1}{RC}s + \frac{1}{LC}}{\frac{1}{RC}s}$$

assuming R is large enough,  $A(s) \approx RC \left( \frac{s^2 + LC}{s} \right)$   
see attached Bode Plot.

PROBLEM 10.5

We know that the leftmost opamp subcircuit is an inverter with a gain of 1. Therefore, its output is just  $-v_1$ . This is the input to the second subcircuit.

We know that this signal must be negative, because it's given that  $v_1 > 0$ .

The second subcircuit is an inverter with a non-linear element in the feedback path.  $i_D$  must flow through  $R_2$ , therefore we can write:

$$i_D = \frac{K}{2} (v_{GS} - V_T)^2 = \frac{v_- - (-v_1)}{R_2}$$

substituting ( $v_2 = v_{GS}$ ) and ( $V_T = 0$ ) and ( $v_- = 0$ ) we get

$$\frac{K}{2} (v_2)^2 = \frac{v_1}{R_2}$$

solving for  $v_2$  and substituting, we get

$$v_2 = \sqrt{\left(\frac{2}{KR_2}\right)v_1} = \sqrt{\frac{2v_1}{(0.0001)(1000)}} = \sqrt{20v_1} = v_2$$

### PROBLEM 10.6

For Parts A and B, we solve in similar fashion to Problems 10.5 and 10.3...

A) we can write

$$\frac{v_i - v_o}{R} = i \approx I_s (e^{-v_o/V_{TH}}); \quad V_{TH} = \frac{KT}{q}$$

$$\ln\left(\frac{v_i}{RI_s}\right) = -\frac{v_o}{V_{TH}} \Rightarrow \boxed{v_o = -\frac{KT}{q} \ln\left(\frac{v_i}{RI_s}\right)}$$

current can only flow through the diode if

$$\boxed{v_o \text{ is negative}}$$

B)  $i \approx I_s e^{-v_i/V_{TH}} = \frac{v_o}{R}; \quad V_{TH} = \frac{KT}{q}$

$$\boxed{v_o = RI_s e^{-v_i, q/KT}}$$

$$\boxed{v_o \text{ is positive}}$$


c) Here is a straightforward circuit, using the ideas that

- $\ln(AB) = \ln A + \ln B$
- $e^{\ln x} = x$

The detailed analysis is left to the reader.

(see the next page)

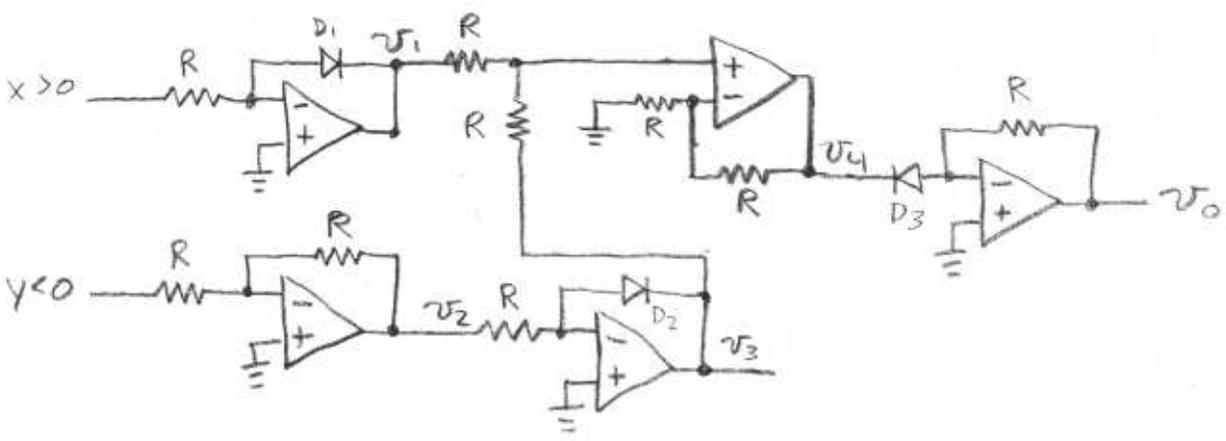22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS  
ANAPRO



$$v_1 = -\frac{kT}{q} \ln\left(\frac{x}{RI_s}\right)$$

$$v_2 = -y = |y|$$


$$v_3 = -\frac{kT}{q} \ln\left(\frac{|y|}{RI_s}\right)$$

$$v_4 = v_1 + v_3 = -\frac{kT}{q} \left[ \ln\left(\frac{x}{RI_s}\right) + \ln\left(\frac{|y|}{RI_s}\right) \right] = -\frac{kT}{q} \ln\left(\frac{x|y|}{(RI_s)^2}\right)$$


$$v_0 = RI_s e^{-\frac{q}{kT} v_4} = RI_s e^{\ln\left(\frac{x|y|}{(RI_s)^2}\right)} = \frac{RI_s x|y|}{(RI_s)^2}$$

$$v_0 = \left(\frac{1}{RI_s}\right) (x)(|y|)$$

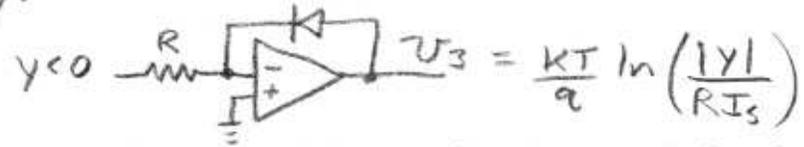By reversing the direction of diode  $D_2$ , the inverter can be omitted and  $(y < 0)$  can be connected directly:



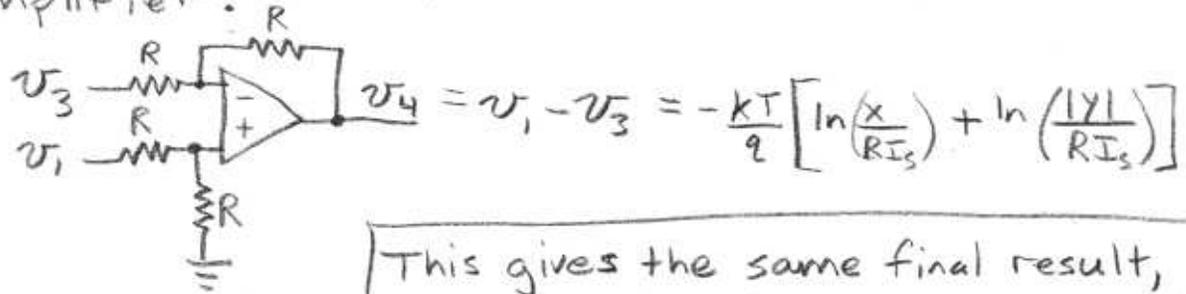Then  $v_4$  can be computed using a difference amplifier:



This gives the same final result,  $v_0 = \left(\frac{1}{RI_s}\right) (x)(|y|)$  but with only 4 opamps.

Problem 10.4, Part B ( $L=1, C=1, R=10^{12}$ )

