


Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.002 – Circuits & Electronics  
Spring 2004

Problem Set #8

Issued 3/31/04 – Due 4/7/04

**Exercise 8.1:** Using one 1-nF capacitor and two resistors, construct a two-port network that has the following response to a 1-V step input; assume that the capacitor voltage is zero prior to the step. Provide a diagram of the network, and specify the values of the two resistors.

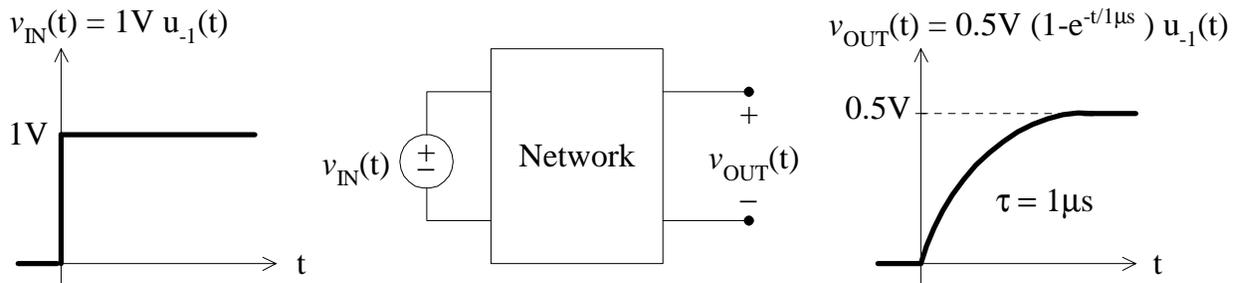


**Exercise 8.2:** Repeat Exercise 8.1 given that the allowable components are now one 1-mH inductor and two resistors; assume that the inductor current is zero prior to the step.

**Problem 8.1:** The network shown below includes a switch with three positions: A, B and C. Prior to  $t = 0$ , the switch is in Position B, and the inductor current  $i(t)$  and capacitor voltage  $v(t)$  are both zero.

- (A) At  $t = 0$  the switch moves to Position A, and it remains there until  $t = T_1$ . Find  $i(t)$  and  $v(t)$  for  $0 \leq t \leq T_1$ .
- (B) At  $t = T_1$  the switch moves to Position C, and it remains there until  $i(t)$  goes to zero, at which time the switch moves back to Position B. Define the time at which  $i(t)$  goes to zero as  $t = T_2$ . Determine  $T_2$ , and find both  $i(t)$  and  $v(t)$  for  $T_1 \leq t \leq T_2$ .
- (C) The switch remains in Position B until  $t = T_3$ . Find both  $i(t)$  and  $v(t)$  for  $T_2 \leq t \leq T_3$ .
- (D) At  $t = T_3$  the switch moves again to Position A, and it remains there until  $t = T_4$ . Find  $i(t)$  and  $v(t)$  for  $T_3 \leq t \leq T_4$ .

- (E) Finally, at  $t = T_4$  the switch moves to Position C, and it remains there until  $i(t)$  again goes to zero, at which time the switch moves back to Position B. Define the time at which  $i(t)$  again goes to zero as  $T_5$ . Determine  $T_5$ , and find both  $i(t)$  and  $v(t)$  for  $T_4 \leq t \leq T_5$ .
- (F) Sketch and clearly label  $i(t)$  and  $v(t)$  for  $0 \leq t \leq T_5$ .

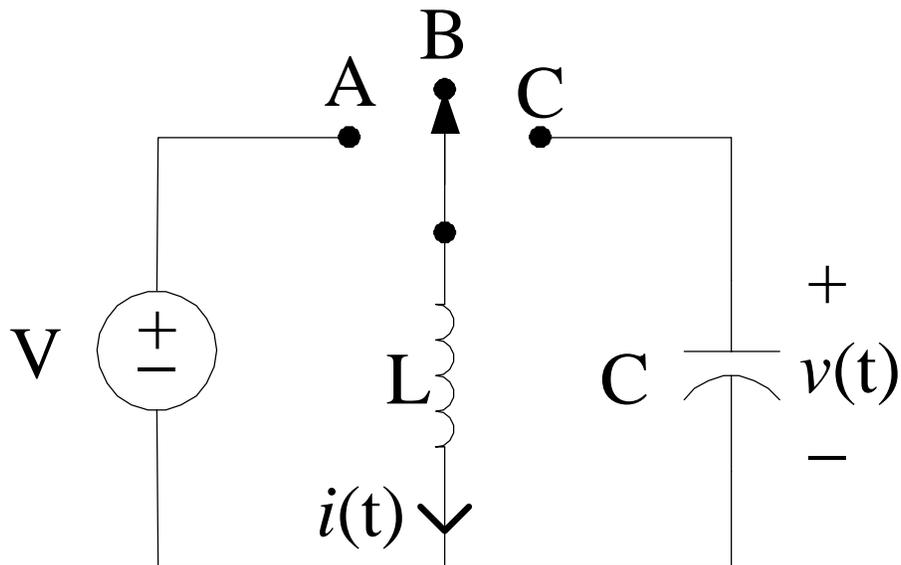

**Problem 8.2:** This problem is a continuation of Problem 8.1. It explores the use of energy conservation to analyze the operation of the network described therein.

- (A) Determine the energy stored in the inductor at  $t = T_1$ .
- (B) The energy stored in the inductor at  $t = T_1$  is fully transferred to the capacitor at  $t = T_2$ . Use this fact to determine  $v(T_2)$ . This answer should match your answer to Part B of Problem 8.1 when the latter is evaluated at  $t = T_2$ .
- (C) Determine the energy stored in the inductor at  $t = T_4$ .
- (D) Use energy conservation to determine the energy stored in the capacitor at  $t = T_5$ , and then determine  $v(T_5)$ . This answer should match your answer to Part E of Problem 8.1 when the latter is evaluated at  $t = T_5$ .
- (E) Now let the switch move repetitively through the cycle of Positions B to A to C to B. Assume that in each cycle the switch remains in Position A for the duration  $T$ . Further, assume that switch always moves from Position C to Position B when  $i(t)$  reaches zero. Assuming that  $v$  and  $i$  are initially zero, determine  $i$  at the end of the  $n$ th switching cycle in terms of  $n$ ,  $C$ ,  $L$ ,  $T$  and  $V$ .

**Problem 8.3:** In the network shown below, the inductor and capacitor have zero current and voltage, respectively, prior to  $t = 0$ . At  $t = 0$ , a step in voltage from 0 to  $V_0$  is applied by the voltage source as shown.

- (A) Find  $v_C$ ,  $v_L$ ,  $v_R$ ,  $i$  and  $\frac{di}{dt}$  just after the step at  $t = 0$ .
- (B) Argue that  $i = 0$  at  $t = \infty$  so that  $i(t)$  has no constant component.
- (C) Find a second-order differential equation which describes the behavior of  $i(t)$  for  $t \geq 0$ .
- (D) Following (B) the current  $i(t)$  takes the form  $i(t) = I \sin(\omega t + \phi)e^{-\alpha t}$ . Find  $I$ ,  $\omega$ ,  $\phi$  and  $\alpha$ .  
Hint: first find  $\omega$  and  $\alpha$  from the differential equation, and then find  $I$  and  $\phi$  from the initial conditions; alternatively, solve this problem by any method you wish.
- (E) Suppose that the input is a voltage impulse with area  $\Lambda_0$  where  $\Lambda_0 = \tau V_0$ ,  $V_0$  is the amplitude of the voltage step shown below, and  $\tau$  is a given time constant. Find the response of the network shown below to the impulse. Hint: before solving this problem directly, consider the relation between step and impulse responses.

Save a copy of your answers to this problem. They will be useful during the pre-lab exercises for Lab #3.

