

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits & Electronics
Spring 2004

Lab #4: Audio Playback System

Introduction

In this lab, you will construct, test and demonstrate the audio playback system that you designed in Problem Set #11. The lab consists of two parts: pre-lab exercises and in-lab exercises; there are no post-lab exercises. You should complete the pre-lab exercises in your lab notebook before coming to lab. Then, carry out the in-lab exercises on your assigned lab day between May 3 and May 7. After completing the in-lab exercises, have a TA or LA check your work and sign your lab notebook. You may hand in your lab notebook to *your* TA for grading at that time, or any other time before the week of final exams.

During the in-lab exercises, you are welcome to work with a partner. In this case, it is best if one person constructs the clock and digital-to-analog converter, while the other person constructs the low-pass filter and power amplifier. These blocks can be constructed on separate protoboards. Signal and ground connections may then be made between protoboards to complete the construction of the audio playback system. The point of working with a partner is to speed up construction, but not to miss out on testing all four blocks. If you do work with a partner, make sure to participate in testing the two blocks constructed by your partner so that you see how they work.

Pre-Lab Exercises

- (4-1) Copy into your lab notebook your design for the clock from Problem 1 of Problem Set #11. Label all resistor and capacitor names and values.
- (4-2) Next to your design for the clock, copy into your lab notebook the graph from Part (E) of Problem 1 of Problem Set #11. You will use this information to determine whether the clock you construct during In-Lab Exercise 4-2 works correctly.
- (4-3) Copy into your lab notebook your design for the digital-to-analog converter from Problem 2 of Problem Set #11. Label all resistor names and values.
- (4-4) Next to your design for the digital-to-analog converter, make a table showing the expected converter output v_{DAC} when each of the data-bit input voltages is 5 V and the others are all 0 V. Base the table on the actual resistor values used in your design. Also, note the expected value of the offset voltage v_{OFF} required to center the converter. You will use this information to determine whether the converter you construct during In-Lab Exercise 4-4 works correctly.
- (4-5) Copy into your lab notebook your design for the low-pass filter from Problem 3 of Problem Set #11. Label all resistor and capacitor names and values.
- (4-6) Next to your design for the low-pass filter, copy into your lab notebook the graph from

Part (F) of Problem 3 of Problem Set #11. Also, make a table showing the expected magnitude and phase of the filter output v_{LPF} given a 2-V peak-to-peak sinusoidal input with a frequency of 4 kHz, 8 kHz and 16 kHz. Base the table on the actual resistor and capacitor values used in your design. You will use this information to determine whether the filter you construct during In-Lab Exercise 4-6 works correctly.

- (4-7) Copy into your lab notebook your design for the power amplifier from Problem 4 of Problem Set #11. Label all resistor and capacitor names and values.
- (4-8) Next to your design for the power amplifier, make a table showing the expected magnitude and phase of the power amplifier output v_{OUT} given a 2-V peak-to-peak sinusoidal input with a frequency of 10 Hz, 100 Hz and 1 kHz. Base the table on the actual resistor and capacitor values used in your design. You will use this information to determine whether the amplifier you construct during In-Lab Exercise 4-8 works correctly.

In-lab Exercises

The in-lab exercises involve constructing and testing the individual functional blocks of the audio playback system, and then demonstrating the operation of the system as a whole. Before you begin to work on the in-lab exercises, you must obtain from the Instrument Desk in the Lab a plug-in board with the counter and memory, a piezo-electric speaker, and a 74HC14 CMOS inverter chip for constructing the clock. You may keep the inverter chip and the speaker, but you must return the plug-in board.

The in-lab exercises are organized so that you will construct and test one functional block at a time. As each block is found to work properly, you will connect it to those which already work. Consequently, you will alternately construct and test various parts of the audio playback system. *As you develop the system in this manner, it is essential that you turn off the power to the protoboard before you make modifications to your system, or begin any new construction. Also, check your wiring carefully before turning the power back on.* This will avoid damaging the components in the system, and save you considerable debugging time.

Finally, construct the functional blocks as compactly and neatly as possible. In this spirit, you should find it easiest to use the components to wire themselves together, rather than using extra wires. This will save you considerable construction time, as well as considerable debugging time.

- (4-1) To minimize wiring in this lab, the counter and memory have already been assembled on a printed-circuit board. On the back of this board are pins that will plug into the protoboards in the Lab. Plug these pins into the protoboards so that each pin is inserted into a separate protoboard row. Further, locate the board so that there is considerable protoboard space on the side with the memory output data bits. This will make connection to the board easiest. For example, locating the board towards the lower left corner of the protoboard may prove best. The clock can then be constructed above the board, while the digital-to-analog converter, the low-pass filter and the power amplifier can be constructed to the right of the board.

Figure 1 shows the pin assignments for the printed circuit board. The pins for the eight memory output data bits are on the right hand side. The pins for power and ground, and the clock input to the counter are on the left hand side. You should connect the power pin to the 5-V power supply on the protoboard, and the ground pin to ground

on the protoboard. There are also four counter and memory control pins which must be connected to the 5-V power supply and ground as shown in Figure 1.

- (4-2) Following your design from Pre-Lab Exercise 4-1, construct the clock using the 74HC14 inverter chip obtained earlier. Figure 2 shows the pin assignments for the inverter chip. Use any two of the inverters in the chip, and leave the others unconnected. Do not yet connect the clock output v_{CLK} to the clock input of the counter. Rather, use one channel of the oscilloscope to observe the oscillator output v_{OSC} , and trigger the oscilloscope from that channel. Use the other channel to observe v_{CAP} and the clock output v_{CLK} . Compare what you observe with the oscilloscope to the graph prepared during Pre-Lab Exercise 4-2 to determine whether or not the clock is functioning properly. In particular, the clock output v_{CLK} should remain between 0 V and 5 V so as not to damage the counter which it drives.
- (4-3) Provided that the clock functions properly, and most importantly that the clock output v_{CLK} remains within the range of 0 V to 5 V, connect the clock output to the clock input of the counter. With the oscilloscope, verify that the eight data bits from the memory output are changing in time.
- (4-4) Following your design from Pre-Lab Exercise 4-3, construct the digital-to-analog converter using a 741 op-amp. Figure 3 shows the pin assignments for the 741 op-amp. Do not yet connect the converter data-bit inputs to the data-bit outputs from the memory. Rather, adjust the offset voltage v_{OFF} to 0 V, and connect each input individually to the 5-V power supply while leaving the other inputs grounded. Then, measure v_{DAC} with the multimeter, and compare the measurements to the data in the table prepared during Pre-Lab Exercise 4-4 to determine whether or not the converter is functioning properly.
- (4-5) Connect the eight data-bit inputs of the digital-to-analog converter to their corresponding data-bit outputs from the memory; refer to Figure 1 for the memory pin assignments. With the oscilloscope, observe the converter output v_{DAC} . You should see an audio signal reconstructed in a piecewise constant manner. Adjust the offset voltage v_{OFF} so that the audio signal is centered around 0 V.

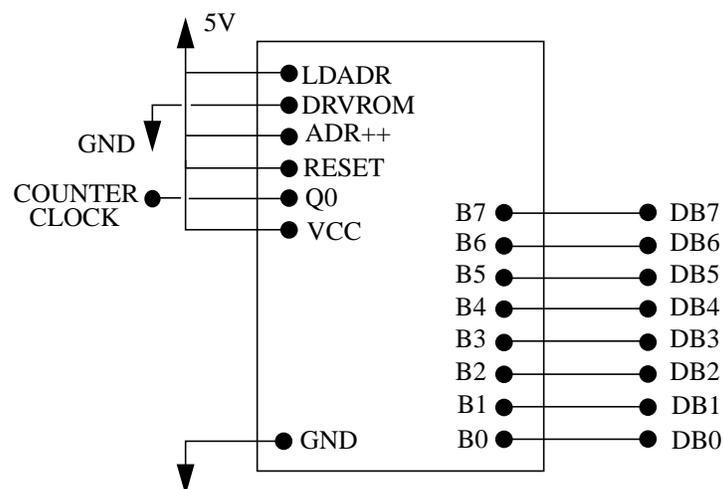


Figure 1: pin assignments for the printed circuit board that contains the counter and memory.

- (4-6) Following your design from Pre-Lab Exercise 4-5, construct the low-pass filter using a 741 op-amp. Set the function generator to produce an unbiased 1-kHz sinusoid with a 2-V peak-to-peak amplitude and connect it to the input of the filter. With one channel of the oscilloscope, observe the input to the filter, and trigger the oscilloscope from that channel. With the other channel, observe the filter output v_{LPP} . Vary the frequency of its input voltage and compare the frequency response of the filter to that predicted by the graph and table prepared during Pre-Lab Exercise 4-6 to determine whether or not the filter is functioning properly.
- (4-7) Connect the output from the digital-to-analog converter to the input of the low-pass filter. Using the oscilloscope, compare the output from the converter to the output from the filter. While the two outputs should look similar, the output from the filter should look considerably smoother upon detailed inspection. Adjust the offset voltage v_{OFF} in the converter again if the low-pass filter output v_{LPP} does not appear to be centered around 0 V.

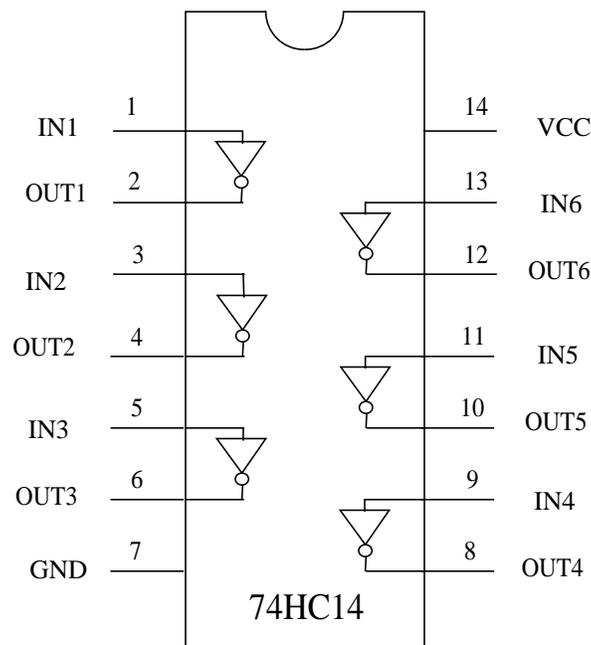


Figure 2: pin assignments for the 74HC14 inverter chip.

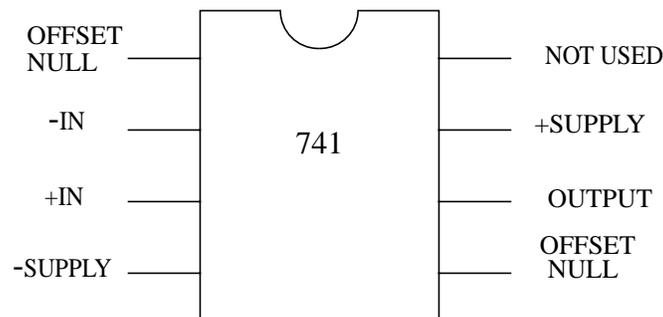


Figure 3: pin assignments for the 741 op-amp.

(4-8) Following your design from Pre-Lab Exercise 4-7, construct the power amplifier using a 741 op-amp, but do not yet connect it to the speaker. Set the function generator to produce an unbiased 1-kHz sinusoid with a 2-V peak-to-peak amplitude and connect it to the input of the power amplifier. With one channel of the oscilloscope, observe the input to the amplifier, and trigger the oscilloscope from that channel. With the other channel, observe the amplifier output v_{OUT} . With the gain of the power amplifier set to 10, vary the frequency of its input voltage and compare the frequency response of the amplifier to that predicted by the table prepared during Pre-Lab Exercise 4-8 to determine whether or not the amplifier is functioning properly. Also, vary the gain of the power amplifier by changing the potentiometer setting; verify that it ranges from 10 to 20, at least for frequencies between 1 kHz and 10 kHz.

(4-9) Next, connect the power amplifier to the piezoelectric speaker according to your design from Pre-Lab Exercise 4-7. Set the function generator to produce an unbiased 1-kHz sinusoid with a 2-V peak-to-peak amplitude and connect it to the input of the amplifier. You should now hear a single-harmonic tone. Sweep the frequency of the signal generator over the range of 10 Hz to 10 kHz and vary the gain of the power amplifier. As you do this, use the oscilloscope to again demonstrate that the power amplifier is working properly.

The piezoelectric speaker has an internal resonance at about 4 kHz. When this resonance is excited the speaker sounds as if it is rattling. In order to damp this resonance and produce a better sounding output, you might try covering the output port of the speaker slightly, or stuffing a very small amount of soft cotton into the speaker port.

(4-10) Complete the audio playback system by connecting the output of the low-pass filter directly to the input of the power amplifier, and set the gain of the power amplifier to 10. You should now hear the audio signal recorded in the memory as it is played back through the speaker or headphones. It is possible that the original audio signal was digitized and recorded in the memory at lower than full amplitude. In this case, the peak-to-peak voltage across the piezoelectric speaker will be much less than 25 V, and the audio signal will be weak. To compensate for this, increase the gain of the power amplifier.

(4-11) As a final in-lab exercise, experiment with the audio playback system. For example, remove the low-pass filter and see how your perception of the audio signal changes. Also, disconnect one or more of the least significant memory data bits from the digital-to-analog converter and see how your perception of the audio signal changes. Try this with and without the low-pass filter. How many data bits are necessary to make the audio signal intelligible?