

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits & Electronics
Spring 2004

Quiz #3

28 April 2004

Name: SOLUTIONS


Instructor: Kassakian Kassakian Wilson Berggren Berggren
Time: 10 11 12 1 2

- Please put your name in the space provided above, and circle the name of your recitation instructor together with the time of your recitation.
- Do your work for each question within the boundaries of the question. When finished, write your answer to each question in the corresponding answer box that follows the question.
- This is a closed-book quiz, but calculators are allowed.
- Graded quizzes will be returned in tutorial on Monday May 3, and also in Recitation on Wednesday May 5. If you do not attend tutorial and/or recitation on those days, then it is your responsibility to get your quiz from your recitation instructor. You will have until Monday May 17 to request a quiz grading review, regardless of whether or not you attend tutorial on Monday May 3 and take back your quiz. If you wish to have your quiz grade reviewed, you must return your quiz to your recitation instructor, within the two week period, together with a written explanation of why you think a grading mistake was made. This is the only way in which a quiz grade will be reviewed.
- Good luck!

Problem 1	Problem 2	Problem 3	Total Grade

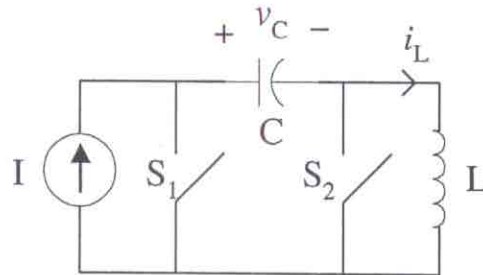Problem 1 – 20%

This problem focuses on the circuit shown below, which contains a constant current source, two switches, a capacitor and an inductor. Prior to $t = 0$, the two switches are closed, and the capacitor and inductor are both at rest.



- (1A) (5%) At $t = 0$, switch S_1 opens. Determine the capacitor voltage v_C and the inductor current i_L at $t = T$.

$v_C(T):$	$\frac{I T}{C}$	$i_L(T):$	\bigcirc
-----------	-----------------	-----------	------------

↑
Capacitor
charges.

↑
Inductor
remains
shorted.

$$v_C = \frac{Q}{C} = \frac{IT}{C}$$

- (1B) (5%) At $t = T$, switch S2 opens and then switch S1 closes immediately thereafter. Determine the time at which the capacitor voltage v_C next goes to zero.

$$t: \quad T + \frac{\pi \sqrt{LC}}{2}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\text{Period} = 2\pi \sqrt{LC}$$

$$\frac{1}{4} \text{ Period} = \frac{\pi}{2} \sqrt{LC}$$

- (1C) (5%) Determine the inductor current i_L when the capacitor voltage v_C goes to zero as described in Part B.

$$i_L: \quad - \frac{IT}{\sqrt{LC}}$$

Energy Conservation \Rightarrow $\underbrace{i_L}_{\text{Peak}} = \pm \sqrt{\frac{C}{L}} \underbrace{v_C}_{\text{Peak}}$

\uparrow
 $\frac{IT}{C}$


- (1D) (5%) When the capacitor voltage v_C goes to zero as described in Part B, switch S2 closes and then switch S1 opens immediately thereafter. After a further period of duration T , switch S2 opens and then switch S1 closes immediately thereafter. Determine the inductor current i_L when the capacitor voltage v_C next goes to zero.

$$i_L: \quad -\sqrt{2} \frac{IT}{\sqrt{LC}}$$

Two cycles \Rightarrow double energy storage.

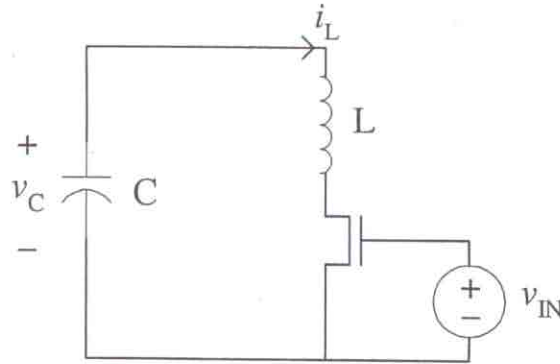Problem 2 – 35%

The circuit shown below contains a capacitor, an inductor and a MOSFET. Its purpose is to deliver a pulse of current to the inductor. Model the MOSFET as a switch having on-state resistance R_{ON} . Prior to $t = 0$, $v_C = V$, $i_L = 0$, and the MOSFET is held off by v_{IN} . For $t \geq 0$ the MOSFET is turned on by v_{IN} .



- (2A) (15%) Derive an expression for the inductor current i_L for $t \geq 0$. In doing so, assume that C satisfies $C < 4L/R_{ON}^2$.

$$i_L(t \geq 0): \frac{V}{L\omega} e^{-\alpha t} \sin(\omega t) \quad \alpha \equiv R_{ON}/2L$$

$$\omega \equiv \sqrt{1/LC - (R_{ON}/2L)^2}$$

$$R_{ON} i_L + L \frac{di_L}{dt} + \frac{1}{C} \int_{-\infty}^t i_L dt = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{R_{ON}}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

$$i_L \sim e^{st} \Rightarrow s = -\underbrace{\frac{R_{ON}}{2L}}_{\alpha} \pm j \underbrace{\sqrt{\frac{1}{LC} - \left(\frac{R_{ON}}{2L}\right)^2}}_{\omega}$$

$$\Rightarrow i_L = A_s e^{-\alpha t} \sin(\omega t) + A_c e^{-\alpha t} \cos(\omega t)$$

$$i_L(0) = 0 \Rightarrow A_c = 0$$

$$\frac{di_L(t)}{dt} = \frac{V}{L} \Rightarrow A_s = \frac{V}{L\omega}$$

} Initial
Conditions

- (2B) (10%) It is desired that the inductor current i_L be a single pulse of minimal time duration with no reversal in sign. Determine the value of C that achieves this objective; C need not satisfy $C < 4L/R_{ON}^2$.

$$C: \frac{4L}{R_{ON}^2}$$

No sign reversal \Rightarrow 2 real roots for s .

Minimal duration \Rightarrow Both real roots for s are equal, otherwise the slow one can be made faster

Requirement \Rightarrow Critical damping $\Rightarrow \omega = 0$

$$\Rightarrow C = \frac{4L}{R_{ON}^2}$$

- (2C) (10%) Determine the peak, or maximum positive value, of the inductor current i_L given the design of Part B.


$$\text{Peak } i_L: \quad \frac{2V}{e R_{ON}}$$

$$\lim_{\omega \rightarrow 0} \Rightarrow i_L(t) = \frac{Vt}{L} e^{-\alpha t} \quad \dots \text{From Part A.}$$

$$\frac{di_L}{dt} = 0 \Rightarrow t = 1/\alpha \Rightarrow \text{Peak } i_L = \frac{2V}{e R_{ON}}$$

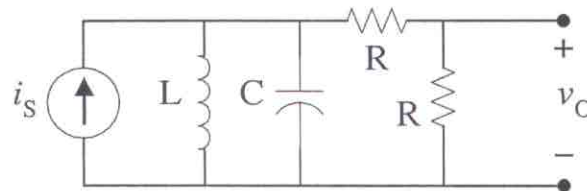Problem 3 – 45%

This problem focuses on the network shown below. It contains a current source, a capacitor, an inductor and two identical resistors. It also has a single port. Except for the last part of this problem, the network operates in the sinusoidal steady state with the sourced current taking the form $i_S(t) = I \cos(\omega t)$. For the last part of this problem, the network is at rest until the sourced current takes a step of the form $i_S(t) = I u_{-1}(t)$.




- (3A) (10%) The output voltage v_O at the port takes the form $v_O(t) = V \cos(\omega t + \phi)$ in sinusoidal steady state. Determine V and ϕ .

$$V: \frac{\omega L I / 2}{\sqrt{(1 - \omega^2 LC)^2 + (\omega L / 2R)^2}} \quad \phi: \tan^{-1} \left(\frac{1 - \omega^2 LC}{\omega L / 2R} \right)$$

$$\begin{aligned} \hat{V} &= \frac{1}{\frac{1}{j\omega L} + j\omega C + \frac{1}{2R}} \cdot I \cdot \frac{1}{2} \\ &= \frac{j\omega L / 2R}{1 - \omega^2 LC + j\omega L / 2R} \cdot R I \end{aligned}$$

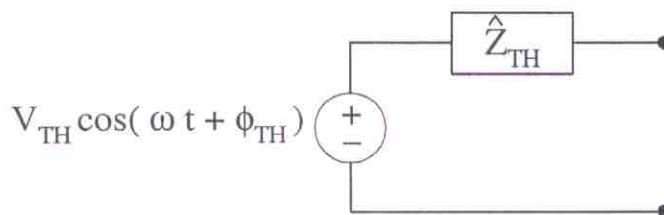
- (3B) (10%) The sinusoidal-steady-state Thevenin equivalent of the network, as viewed from its port is shown below. Determine the parameters V_{TH} , ϕ_{TH} and \hat{Z}_{TH} that define the equivalent. Note that \hat{Z}_{TH} is the complex Thevenin-equivalent impedance.



$$V_{TH}: \quad V \text{ From Part A}$$



$$\phi_{TH}: \quad \phi \text{ From Part A}$$
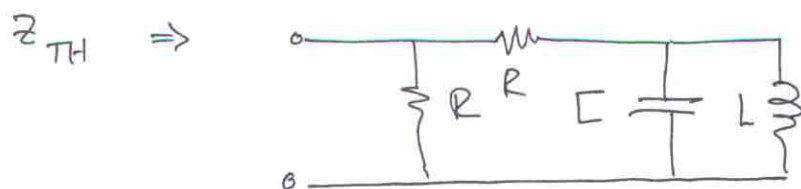
$$\hat{Z}_{TH}: \quad \frac{R \left(R + \frac{j\omega L}{1 - \omega^2 LC} \right)}{2R + \frac{j\omega L}{1 - \omega^2 LC}}$$



$$R \parallel \left(R + \frac{j\omega L}{1 - \omega^2 LC} \right)$$

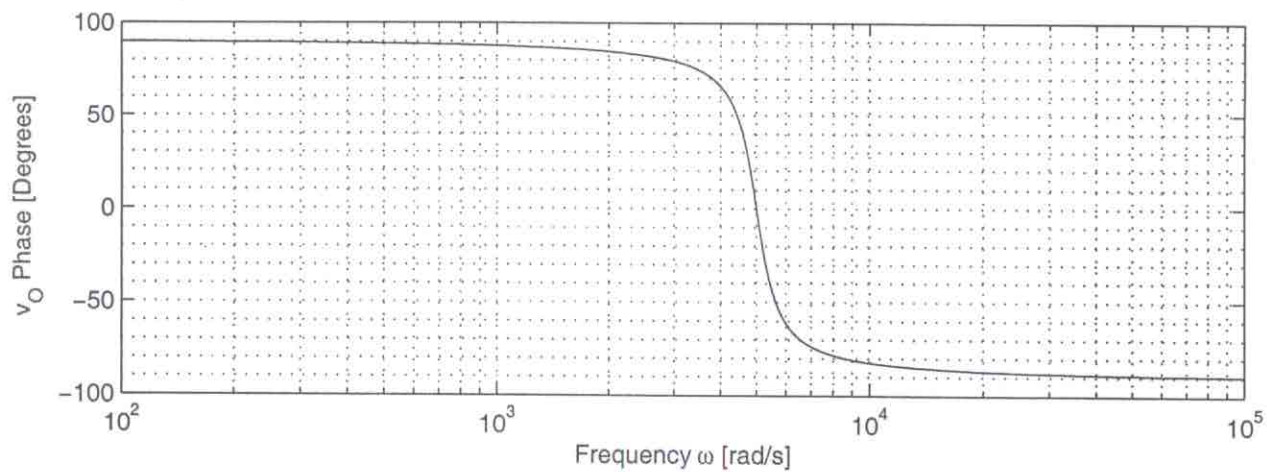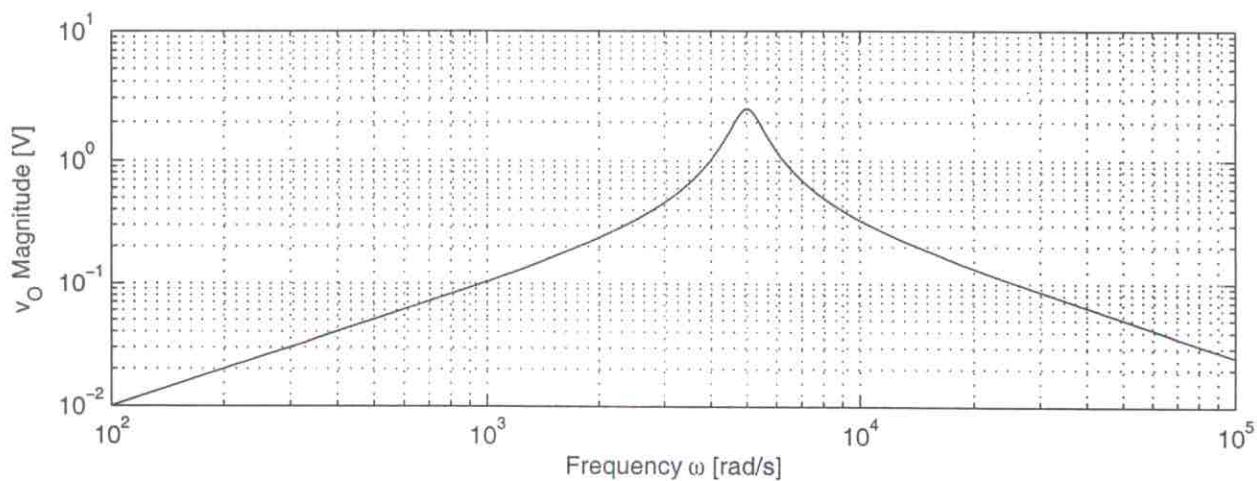The figures shown below present a numerical evaluation of the magnitude V and the phase ϕ of v_O as functions of frequency ω for the specific case of $I = 100$ mA. Use this numerical evaluation to answer Parts C and D of this problem.



(3C) (15%) Determine the numerical values of R , L and C . Remember to include units.

$$R: 25 \Omega \quad L: 2 \text{ mH} \quad C: 20 \mu\text{F}$$

Low Frequency Asymptote @ $\omega = 10^2 \frac{\text{rad}}{\text{s}}$

$$|V_o| \approx \frac{\omega L I}{2} \Rightarrow L = 2 \text{ mH}$$


High Frequency Asymptote @ $\omega = 5 \cdot 10^4 \frac{\text{rad}}{\text{s}}$

$$|V_o|^2 \approx \frac{I^2}{2\omega C} \Rightarrow C = 20 \mu\text{F}$$

Peak @ $\omega = 5 \cdot 10^3 \frac{\text{rad}}{\text{s}} = \frac{1}{\sqrt{LC}}$

$$|V_o| = R I \Rightarrow R = 25 \Omega$$

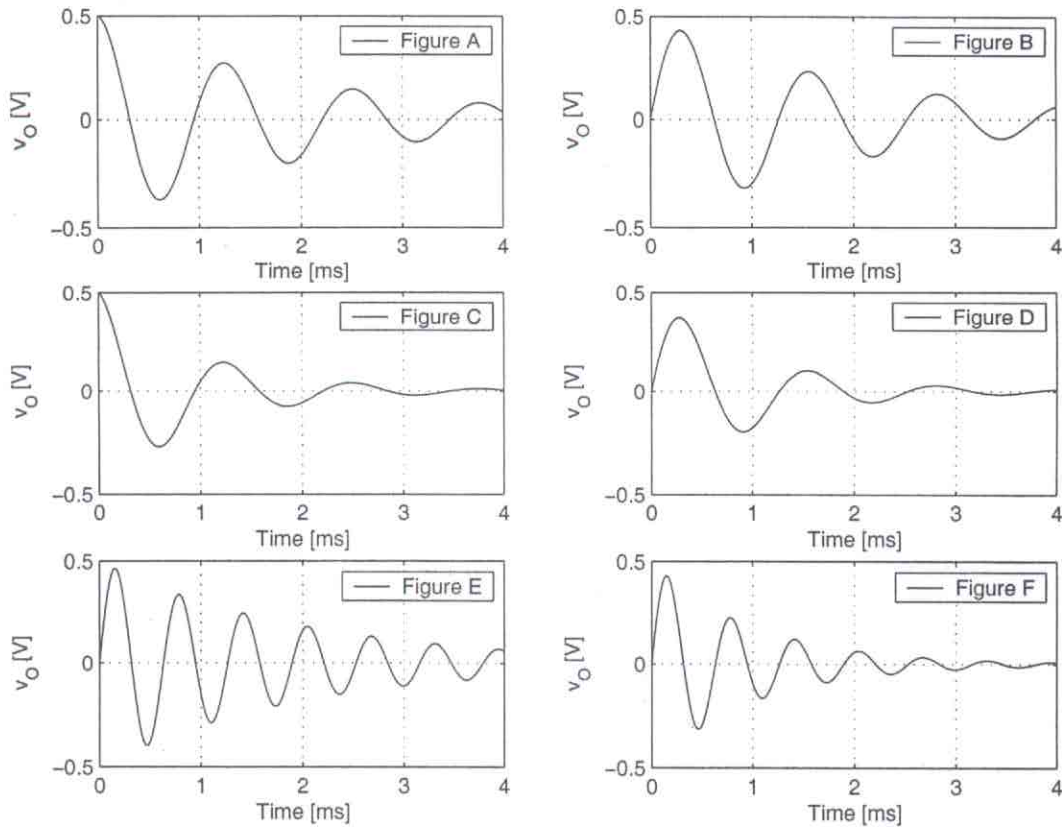- (3D) (10%) Assuming the network is at initially rest, which of the following figures corresponds to v_o for $t \geq 0$ given that $i_S(t) = 100 \text{ mA } u_{-1}(t)$?



Circle One:

A

B

C

D

E

F

Initial Voltage = 0 ... Rules out A & C.

Period = $\frac{2\pi}{5000} \text{ s} > 1 \text{ ms}$... Rules out E & F.

$\frac{1}{e}$ Decay Time = $4RC = 2 \text{ ms}$... Rules out C & D.

Elimination \Rightarrow B.