

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science

6.002 - Electronic Circuits  
 Spring 2000


Quiz #1 *solutions*  
 February 23, 2000  
 One Hour Closed Book

NOTE: Answer any 2 of the following 3 questions.

**Problem #1**


Find the current  $I$  in the circuit illustrated below:

*Superposition!*

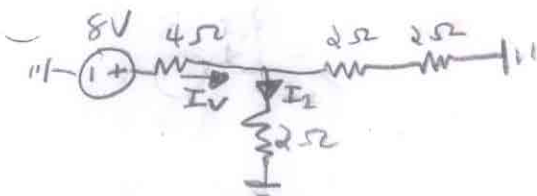


$$I_1 = \frac{8V}{4\Omega + 2\Omega \parallel 4\Omega} = 1.5A$$
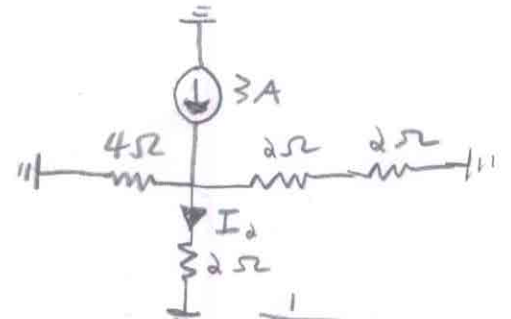
$$I_2 = \frac{\frac{1}{2\Omega}}{\frac{1}{2\Omega} + \frac{1}{4\Omega}} I_1 = 1A$$


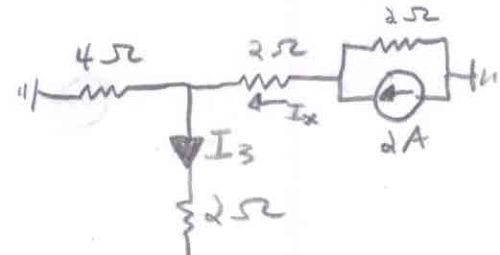
$$I_2 = \frac{\frac{1}{2\Omega}}{\frac{1}{4\Omega} + \frac{1}{4\Omega} + \frac{1}{2\Omega}} (3A) = 1.5A$$



$$I_3 = \frac{\frac{1}{2\Omega}}{\frac{1}{2\Omega + 4\Omega \parallel 2\Omega} + \frac{1}{2\Omega}} (2A) = 0.75A$$

$$I_3 = \frac{\frac{1}{2\Omega}}{\frac{1}{4\Omega} + \frac{1}{2\Omega}} I_x = 0.5A$$


$$I = I_2 + I_3 + I_1 = 1 + 1.5 + 0.5$$

$$I = 3A$$

# Solutions
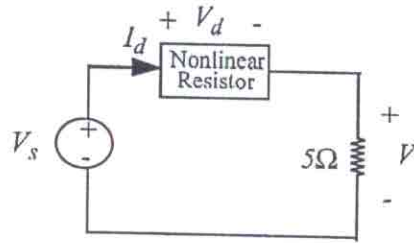
## Problem #2

Find the output voltage  $V$  in the circuit illustrated below:



Large signal:  $V_s = 20V$

$$V = I_d(5\Omega), \quad V + V_d = 20$$


$$I_d(5\Omega) + V_d = 20$$

$$I_d = 4A - \frac{V_d}{5\Omega} \Rightarrow \text{see graph}$$

(cross at  $I_d = 2A, V_d = 10V$ )

$$\text{so } V = 20 - 10 = 10V$$

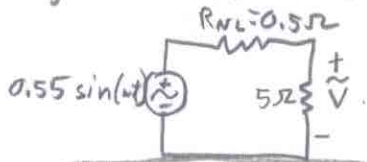small signal: Nonlin has slope  $\approx \frac{4A}{2V} = \frac{1}{0.5\Omega} = \frac{1}{R_{NL}}$




$$\tilde{V} = \frac{5\Omega}{0.5\Omega + 5\Omega} [0.55 \sin(\omega t)]$$

$$= 0.5 \sin(\omega t) V$$

$$V = V + \tilde{V} = 10V + 0.5V \sin(\omega t)$$

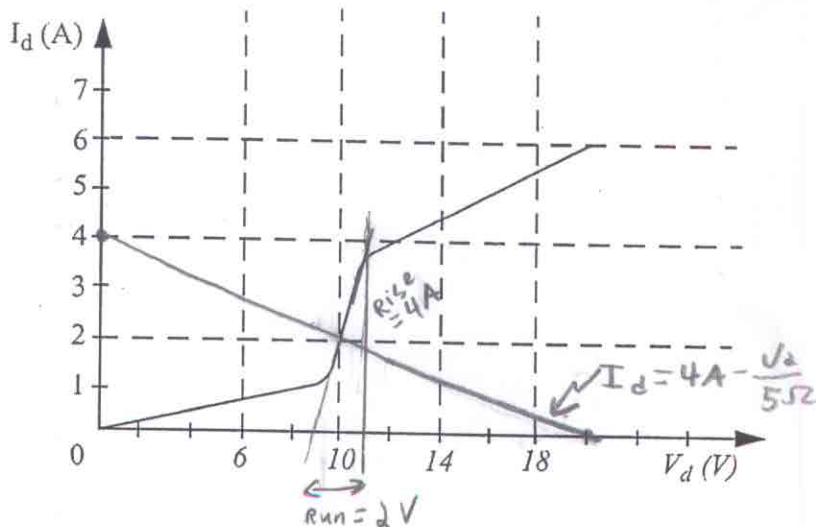Assume that  $V_s = 20V + 0.55V \sin(\omega t)$  and that the  $I_d - V_d$  characteristic of the nonlinear resistor is as shown below.




# Solutions

## Problem #3


Find an analytic expression for the  $V$ - $I$  relationship for the circuit illustrated below:

USE  
Thevenin / Norton  
Equivalents

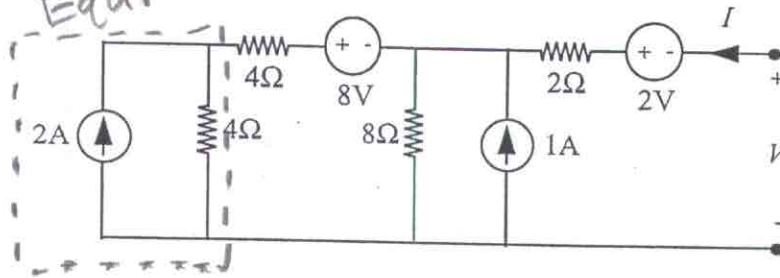


$$V_{oc} = I_{sc} R_{TH}$$

$$= (2A)(4\Omega) = 8V$$

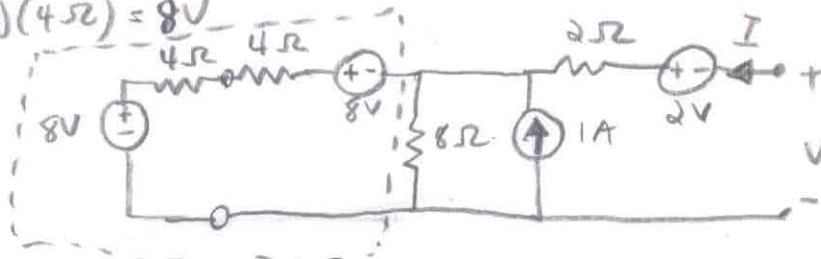


$$V_{oc} = 0V!$$

$$R_{TH} = 8\Omega$$

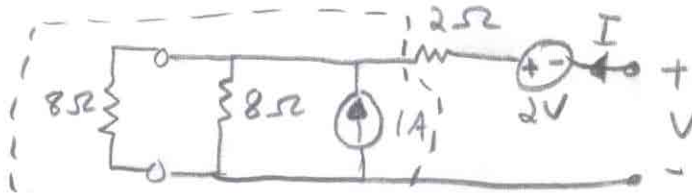

$$R_{TH} = 8\Omega // 8\Omega = 4\Omega$$
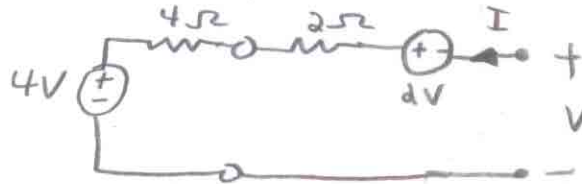
$$V_{oc} = I_{sc} R_{TH} = (1A)(4\Omega) = 4V$$



$$V_{oc} = 2V$$

$$R_{TH} = 6\Omega$$



$$V = 2V + I(6\Omega)$$