

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.002 --Electronic Circuits  
 Quiz #4  
 Closed Book

Friday (Cooke-Section), April 28, 2000

Name: \_\_\_\_\_

Section Hr: \_\_\_\_\_

**Problem 1** (5pts): The following RL network in Figure 1 is in the sinusoidal steady state. It is driven by an input voltage source,  $v_I$ , which results in an output voltage,  $v_O$ .


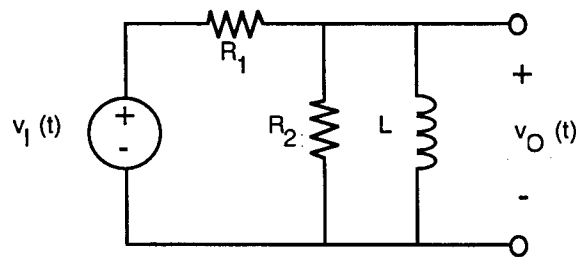


Figure 1

**Part 1A** Write an expression for the complex magnitude of the output  $V_O(j\omega)$  when  $v_I(t) = A \cos(\omega t)$ . Assume the circuit is in sinusoidal steady state.

$$V_O(j\omega) =$$

**Part 1B** Graph the magnitude of the output,  $|V_O(j\omega)|$  vs  $\omega$ , on log-log coordinates (the Bode diagram format) showing the asymptotes and any frequency values where the asymptotes intersect. Does the circuit exhibit high-pass or low-pass filter properties, if so which?

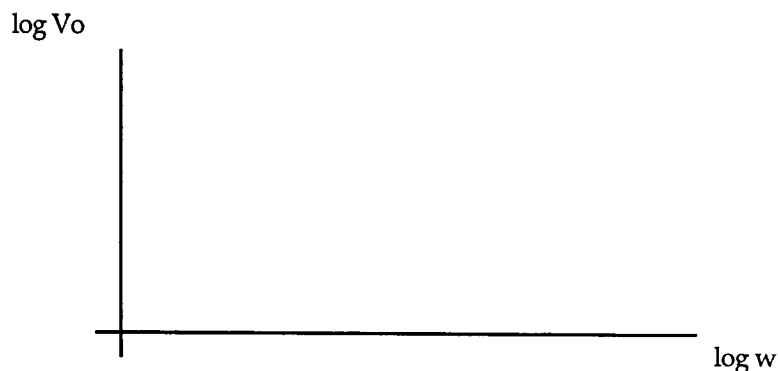

**Problem 2** (10pts): Consider the series connected RLC circuit, Figure 2.

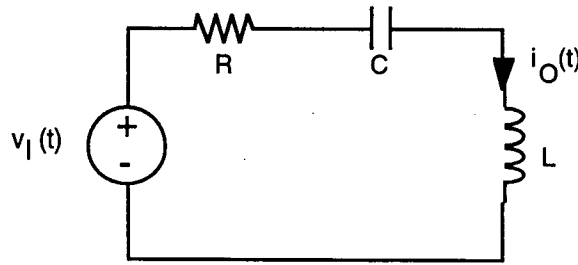


Figure 2

**Part 1A** Write the time-domain differential equation that relates for the output loop current,  $i_O(t)$ , in terms of the source voltage,  $v_1(t)$ , and the circuit elements  $R$ ,  $L$  and  $C$ .

**Part 1B** The circuit is now in the sinusoidal-steady-state, with the voltage source  $v_1(t) = V_1 \cos(\omega t)$ . Write an expression for the complex magnitude of the loop current,  $I_O$ , in terms of  $V_1$ ,  $R$ ,  $L$  and  $C$ .

**Part 1C** Write a complete expression with all numerical values for the time-domain output current,  $i_O(t)$ , in the sinusoidal steady state, when:  $v_1(t) = 5 \cos(10t)$ ; and  $R = 2$  ohms,  $C = 0.1$ F, and  $L = 0.3$  H.

$$i_O(t) =$$

**Problem 3** (5pts): Figure 3 shows the circuit for a resonant system. The voltage source is a step with magnitude  $K$  for  $t > 0$ , and 0 for  $t < 0$ . The circuit is at rest for  $t < 0$ , i.e.  $v_C(0^-) = 0$ , and  $i_L(0^-) = 0$

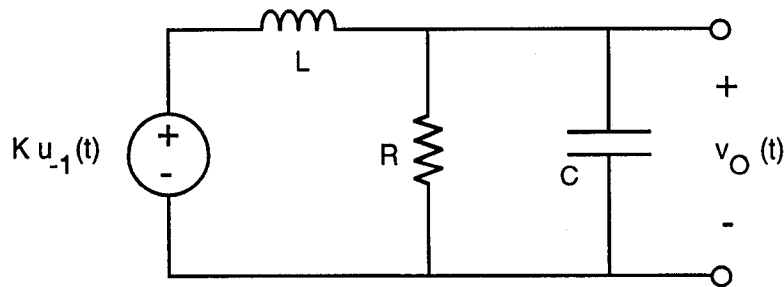


Figure 3

**Part 3A**


(i) What is the value of  $v_O(0^+)$  ?

(ii) What is the value of the derivative of the output,  $dv_O/dt$ , at  $t = 0^+$  ?

(iii) What is the final value of the output  $v_O(\infty)$  ?

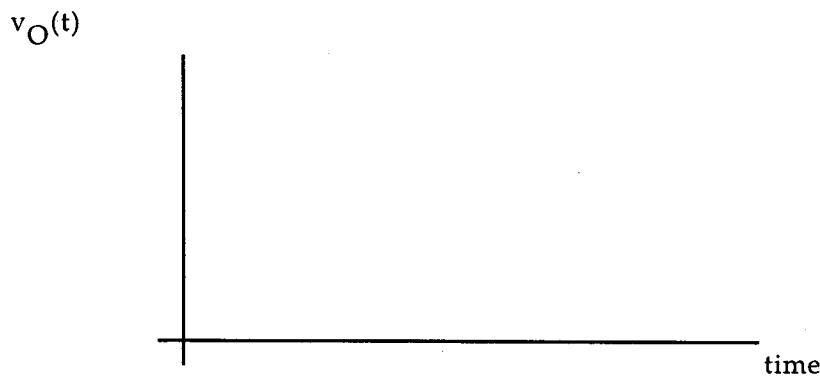**Part 3B**

Sketch and label (with approximate values) the form of the time response given that  $R$ ,  $L$  and  $C$  values yield an oscillatory characteristic, (i.e. damping is small).



OPTIONAL (no points, for 'fun' only)

**Part 3C**

Do you think this circuit is classified as a series or parallel resonant network, Provide a proof for your choice.

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.002 --Electronic Circuits  
 Quiz #4  
 Closed Book

Friday (Cooke-Section), April 28, 2000

Name: \_\_\_\_\_

Section Hr: \_\_\_\_\_

**Problem 1** (5pts): The following RL network in Figure 1 is in the sinusoidal steady state. It is driven by an input voltage source,  $v_I$ , which results in an output voltage,  $v_O$ .


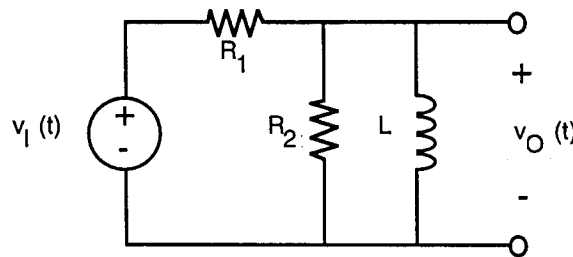


Figure 1

**Part 1A** Write an expression for the complex magnitude of the output  $V_O(j\omega)$  when  $v_I(t) = A \cos(\omega t)$ . Assume the circuit is in sinusoidal steady state.

$$V_O(j\omega) = A \frac{R_2 \parallel j\omega L}{R_1 + R_2 \parallel j\omega L} = \frac{j\omega R_2 L A}{R_1 R_2 + j\omega(R_1 + R_2)L}$$

**Part 1B** Graph the magnitude of the output,  $|V_O(j\omega)|$  vs  $\omega$ , on log-log coordinates (the Bode diagram format) showing the asymptotes and any frequency values where the asymptotes intersect. Does the circuit exhibit high-pass or low-pass filter properties, if so which?

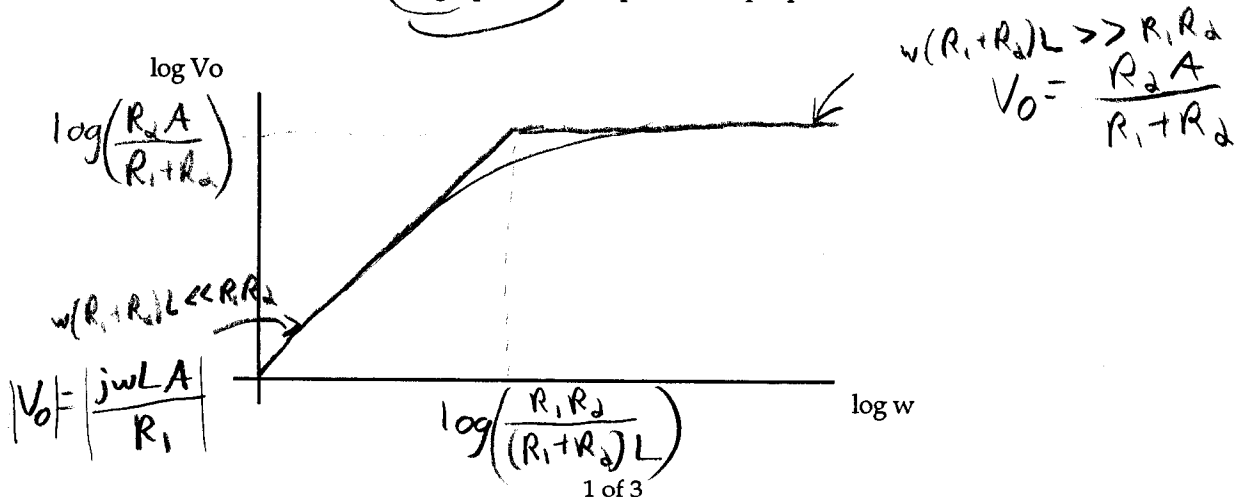

**Problem 2** (10pts): Consider the series connected RLC circuit, Figure 2.

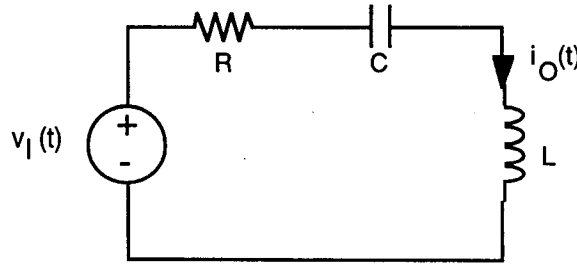


Figure 2

**Part 1A** Write the time-domain differential equation that relates for the output loop current,  $i_0(t)$ , in terms of the source voltage,  $v_1(t)$ , and the circuit elements  $R$ ,  $L$  and  $C$ .

$$v_I = i_0 R + L \frac{di_0}{dt} + \frac{1}{C} \int i_0 dt$$

$$\boxed{\frac{1}{L} \frac{dv_I}{dt} = \frac{d^2 i_0}{dt^2} + \frac{R}{L} \frac{di_0}{dt} + \frac{1}{LC} i_0}$$

**Part 1B** The circuit is now in the sinusoidal-steady-state, with the voltage source  $v_1(t) = V_i \cos(\omega t)$ . Write an expression for the complex magnitude of the loop current,  $I_0$ , in terms of  $V_i$ ,  $R$ ,  $L$  and  $C$ .

$$I_0 = \frac{V_i}{R + \frac{1}{j\omega C} + j\omega L} = \frac{V_i j\omega C}{j\omega R C + j^2 \omega^2 L C + 1}$$

$$\boxed{I_0 = \frac{j\omega V_i C}{1 - \omega^2 L C + j\omega R C}}$$

**Part 1C** Write a complete expression with all numerical values for the time-domain output current,  $i_0(t)$ , in the sinusoidal steady state, when:  $v_1(t) = 5\cos(10t)$ ; and  $R = 2$  ohms,  $C = 0.1F$ , and  $L = 0.3$  H.

$$\omega = 10$$

$$V_i = 5$$

$$|I_0| = \frac{(10)(5)(0.1F)}{\sqrt{[1 - (10^2)(0.3H)(0.1F)]^2 + [(10)(2\Omega)(0.1F)]^2}} = 1.768 \text{ A}$$

$$i_0(t) = 1.768 \text{ A} \cos\left(10t - \tan^{-1}\left(\frac{(10)(2\Omega)(0.1F)}{1 - (10^2)(0.3H)(0.1F)}\right)\right) = 135^\circ \left(\frac{3\pi}{4}\right)$$

$$\boxed{i_0(t) = (1.768 \text{ A}) \cos\left(10t + \frac{3\pi}{4}\right)}$$

**Problem 3** (5pts): Figure 3 shows the circuit for a resonant system. The voltage source is a step with magnitude  $K$  for  $t > 0$ , and 0 for  $t < 0$ . The circuit is at rest for  $t < 0$ , i.e.  $v_C(0^-) = 0$ , and  $i_L(0^-) = 0$

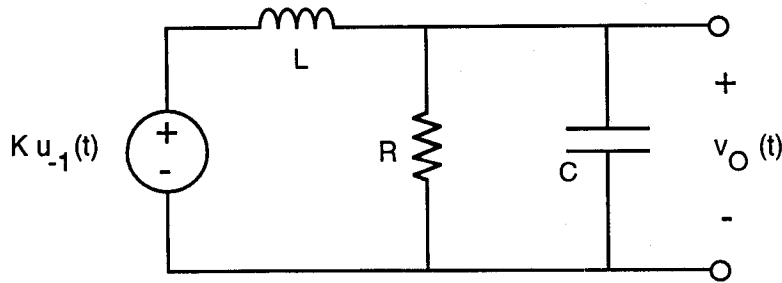


Figure 3

**Part 3A**


- (i) What is the value of  $v_O(0^+)$ ?  $= v_C(0^-) = \boxed{0}$ .  
*continuity requirement.*
- (ii) What is the value of the derivative of the output,  $dv_O/dt$ , at  $t = 0^+$ ?  
 $i_L(0^+) = 0$ , and  $v_R(0^+) = 0$ , so  $i_C(0^+) = 0$ .  $\frac{dv_O}{dt} = \frac{1}{C} i_C = \boxed{0}$
- (iii) What is the final value of the output  $v_O(\infty)$ ?

$L \Rightarrow$  short,  $C \Rightarrow$  open (assuming DC steady state)

$\boxed{v_O(\infty) = K}$

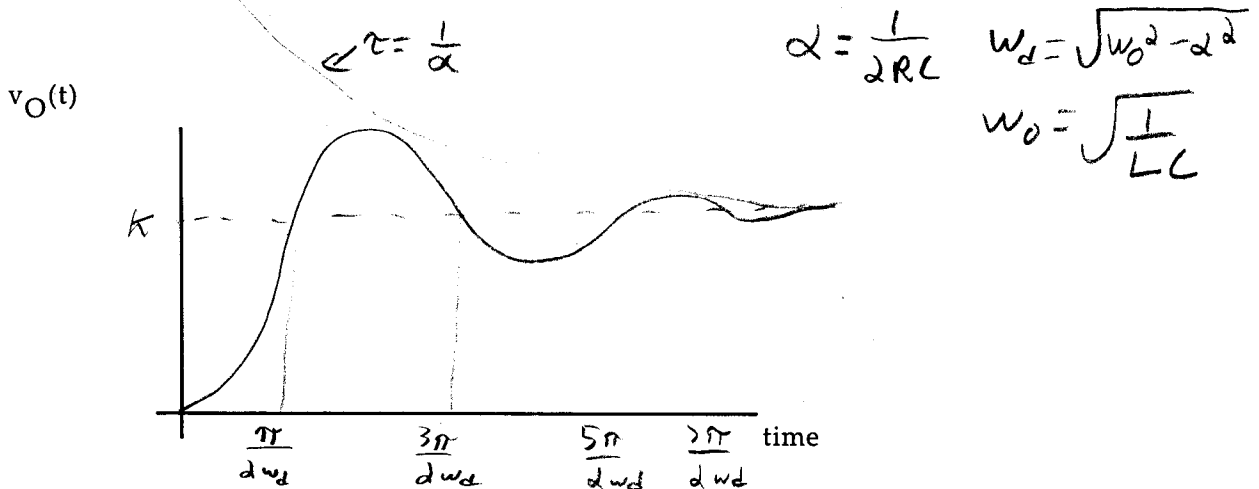**Part 3B**

Sketch and label (with approximate values) the form of the time response given that  $R$ ,  $L$  and  $C$  values yield an oscillatory characteristic, (i.e. damping is small).



OPTIONAL (no points, for 'fun' only)

**Part 3C**

Do you think this circuit is classified as a series or parallel resonant network, Provide a proof for your choice.

Parallel  $\Rightarrow$  set source = 0.  
(p root?)