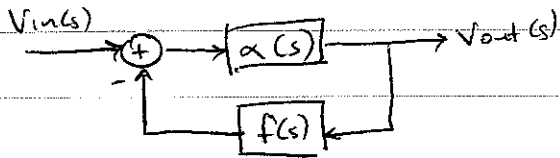


6.003 Recitation Friday March 19, Sections 3 & 4

- Today, ① Basic principles of negative feedback
 ② The seven benefits of negative feedback

"Squirrels do love running swiftly in snow"




$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{\alpha(s)}{1 + \alpha(s)f(s)} = \frac{1}{f(s)} \frac{L(s)}{1 + L(s)}, \text{ where } L(s) = \alpha(s)f(s)$$

If $L(s) \gg 1$, then $\left| \frac{L(s)}{1 + L(s)} \right| \approx 1$, independent of the exact value of $L(s)$,

thus $\frac{V_{out}(s)}{V_{in}(s)} \approx \frac{1}{f(s)}$, indep. of the exact value of $\alpha(s)$.

Simple example:

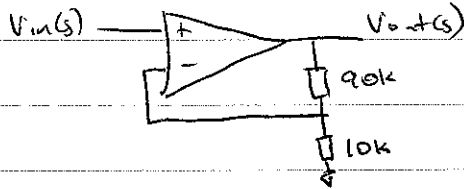


$$\frac{V_{out}}{V_{in}} = \frac{1}{0.1} \frac{10^4 \times 0.1}{10^4 \times 0.1 + 1} = 9.9999$$

where $f(s) = 0.1$, $\alpha(s) = 10^4$

Now, suppose $\alpha(s) = 10^5 \neq 10^4$, then $\frac{V_{out}}{V_{in}} = 9.9999$ [very similar because the loop transmission is large]

Benefit one: Sensitivity to $\alpha(s)$ is greatly reduced as long as $|\alpha(s)f(s)| \gg 1$.

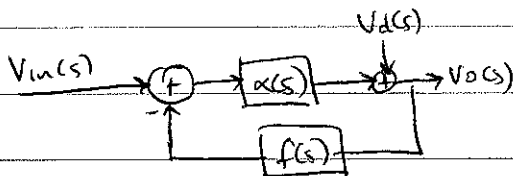Benefit two: Distortion and disturbance rejection at the output of the feedback loop.




$$\frac{V_{out}(s)}{V_d(s)} = \frac{1}{1 + \alpha(s)f(s)}$$

Benefit Three: Linearization of input-output transfer function with a linear $f(s)$ even if $x(s)$ is nonlinear as long as $x(s)f(s) \gg 1$.

eg) lecture example of a power amplifier driven by a preamp

Note: these nonlinearities can be viewed as disturbances from $x(s)$.

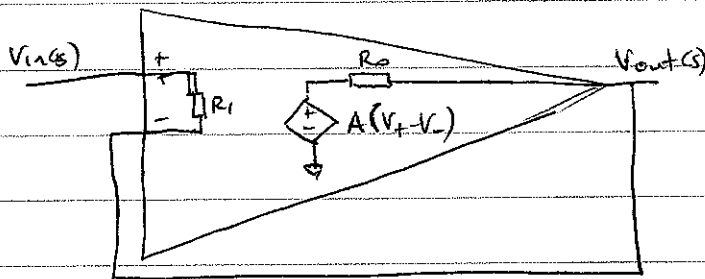
Benefit Four: Resistance or impedance transformations




Closed-loop input impedance is $R_i(1+A)$ ← increased

Closed-loop output impedance is $\frac{R_o}{1+A}$ ← decreased.

Benefit Five: Speed-up eg) in motors

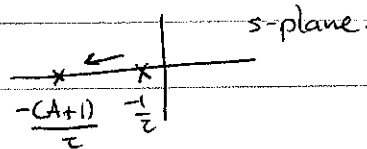

Benefit Six: Inverse transfer functions

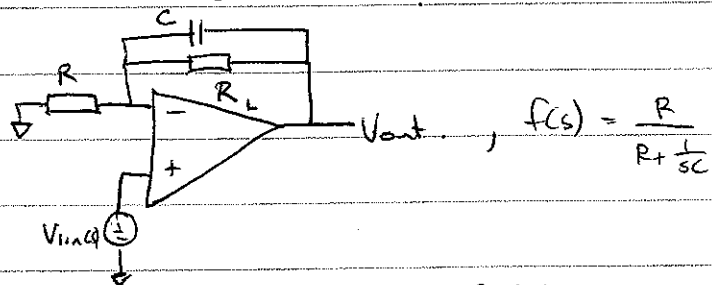

Implement $1/f(s)$ with $f(s)$ in feedback path. $f(V_{out}) = V_{in}$ [inputs almost equal].

Closed loop = $1 + \frac{1}{RCs}$

Benefit Seven: Stabilization of unstable systems eg) - inverted pendulum
- magnetic levitation.

