

Lecture 19

Transistor Amplifiers (II)

Common-Emitter Amplifier

Outline

- Common-source amplifier (summary)
- Common-emitter amplifier
- Common-emitter amplifier with current-source supply
- Common-emitter amplifier with emitter degeneration resistor

Reading Assignment:

Howe and Sodini; Chapter 8, Sections 8.4-8.6

Announcement:


Quiz #2: Wednesday, November 15, 7:30-9:30 PM at Walker Memorial. Lectures #10 - #17. Calculator Required. Open book & notes.

No Recitation on Wednesday: Instructors will be available in their offices during recitation times

Summary of Key Concepts

- Common-emitter amplifier with resistive supply
 - To maximize gain, large power supply required
 - High power consumption
- Performance improved by using common-emitter amplifier with current source supply.
- Two-port network computation of voltage gain, input resistance and output resistance of amplifier.

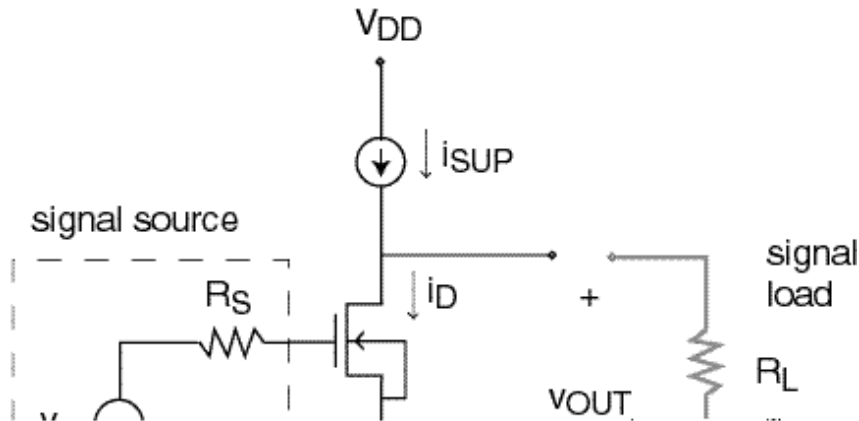1. Common Source Amplifier: with current source supply



Summary of small-signal results (unloaded):

- Voltage gain: $A_{vo} = -g_m (r_o // r_{oc})$.
- Input resistance: $R_{in} =$
- Output resistance: $R_{out} = r_o // r_{oc}$.

Relationship between circuit figures of merit and device parameters

Remember:

$$g_m = \sqrt{2 I_D \frac{W}{L} \mu_n C_{ox}}$$

$$r_o = \frac{1}{n I_D} \frac{L}{I_D}$$

Then:

Device* Parameters	Circuit Parameters		
	$ A_{vol} $	R_{in}	R_{out}
	$g_m(r_o // r_{oc})$		$r_o // r_{oc}$
I_{SUP}		-	
W		-	-
$\mu_n C_{ox}$		-	-
L		-	

* adjustments are made to V_{GG} so that none of the other parameters change

CS amplifier with current source supply is a good voltage amplifier (R_{in} high and $|A_{vol}|$ high), but R_{out} high too voltage gain degraded if $R_L \ll r_o // r_{oc}$.

2. Common-Emitter Amplifier:


Circuit Topology:

Consider it first unloaded by R_L . How does it work?


- V_{BIAS} , R_C and A_E of npn-BJT selected to bias transistor in forward active region (FAR) and obtain desired output bias point (i.e. $V_{OUT} = 0$).
- v_S v_{BE} i_B i_C v_{OUT}
- $A_v = v_{out} / v_s < 0$; output out of phase from input, but if amplifier is well designed, $|A_v| > 1$.

Watch notation: $v_{OUT}(t) = V_{OUT} + v_{out}(t)$

Load line of Common Emitter Amplifier:

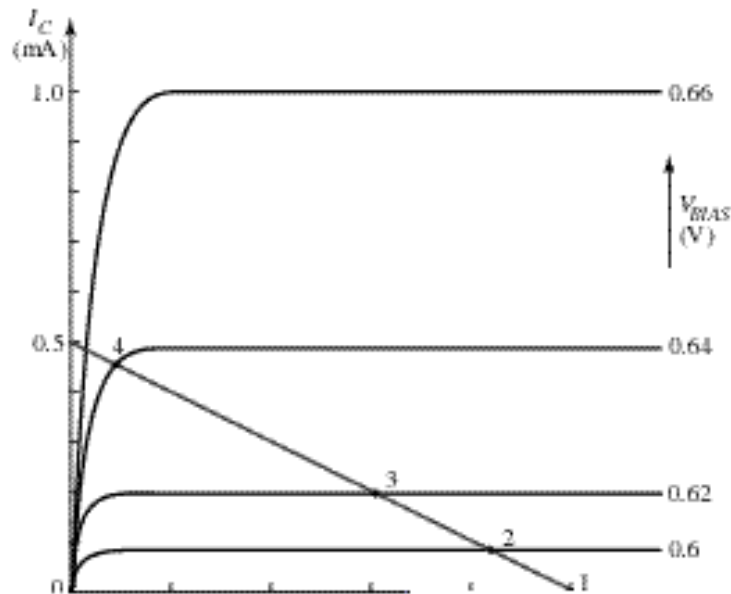


Transfer characteristics of amplifier:

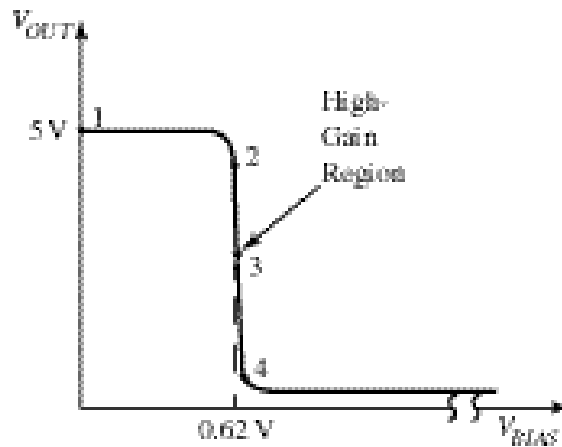

- Graphical approach
 - Plot I_C as a function of the DC base-emitter voltage V_{BIAS}
 - Note that normally we plot I_C vs. I_B , so we have to return to Ebers-Moll equations
- We can plot the forward active current for
 - $V_{CE} = V_{OUT} > V_{CE(sat)}$
 - Note that the range of V_{BIAS} is only 600-660 mV

Biasing the CE Amplifier

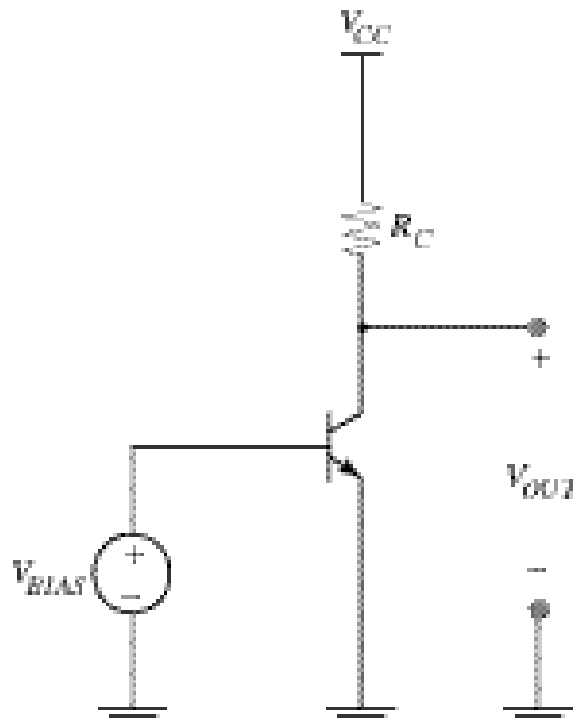

The collector current is given by the Ebers-Moll Equation:

$$I_C = I_S \exp \frac{V_{BE}}{V_{th}} - 1 - \frac{I_S}{R} \exp \frac{V_{BC}}{V_{th}} - 1$$

In Forward Active Region



$$I_C \approx I_S \cdot \exp \frac{V_{BE}}{V_{th}} = I_S \cdot \exp \frac{V_{BIAS}}{V_{th}}$$

Output Voltage

$$V_{OUT} = V_{CE} = V_{CC} - I_C R_C$$

Typically select $V_{OUT} = 1/2 V_{CC}$

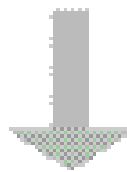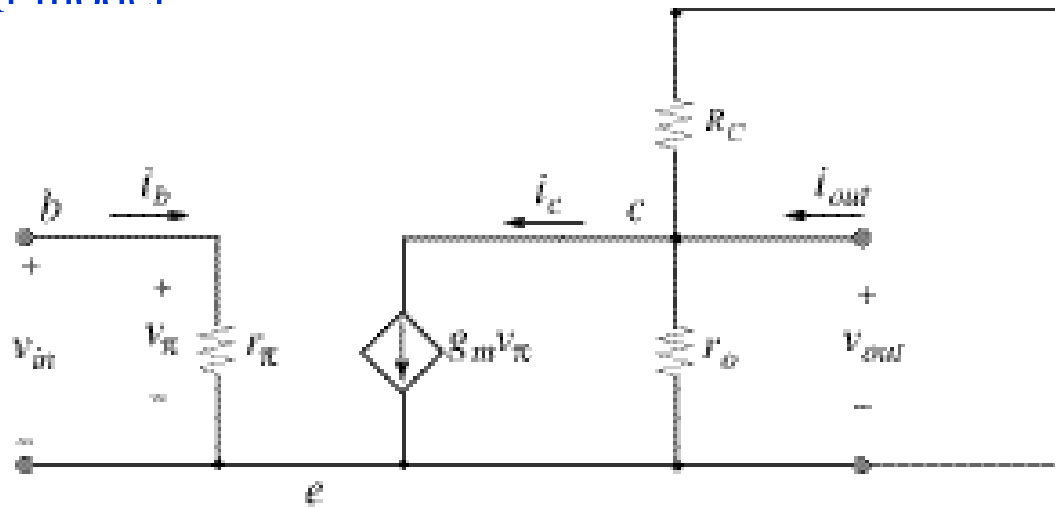Small-signal voltage gain: draw small-signal equivalent circuit model.




$$v_{out} = -g_m v_{in} (r_o // R_C)$$

$$g_m = \frac{qI_C}{kT}$$

Then unloaded voltage gain:

$$A_{vO} = \frac{v_{out}}{v_{in}} = -g_m (r_o // R_C)$$

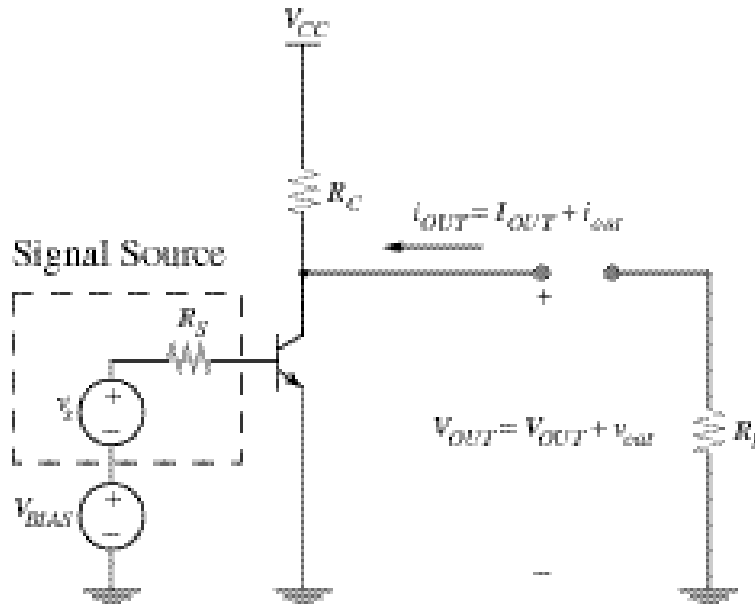Signal Swing and Effect of input/output loading:



- Upswing limited by resistive divider:

$$v_{OUT,max} = V_{CC} \frac{R_L}{R_L + R_C}$$

- Downswing not affected by loading $V_{OUT,min} = V_{CE,sat}$
- Voltage swing

$$v_{OUT} = v_{out} = V_{CC} \frac{R_L}{R_L + R_C} - V_{CE,sat}$$

- Voltage gain:
 - Input loading (R_S): R_S reduces voltage gain because it forms a resistor divider with r ;
 - Output loading (R_L): R_L reduces voltage gain because it draws current.

$$|A_v| = \frac{r}{r + R_S} g_m (r_o // R_C // R_L) < g_m (r_o // R_C)$$


Effect of loading on small-signal operation

Two-port network view of small-signal equivalent circuit model of amplifier:

R_{in} is *input resistance*

R_{out} is *output resistance*

A_{vo} is *unloaded voltage gain*

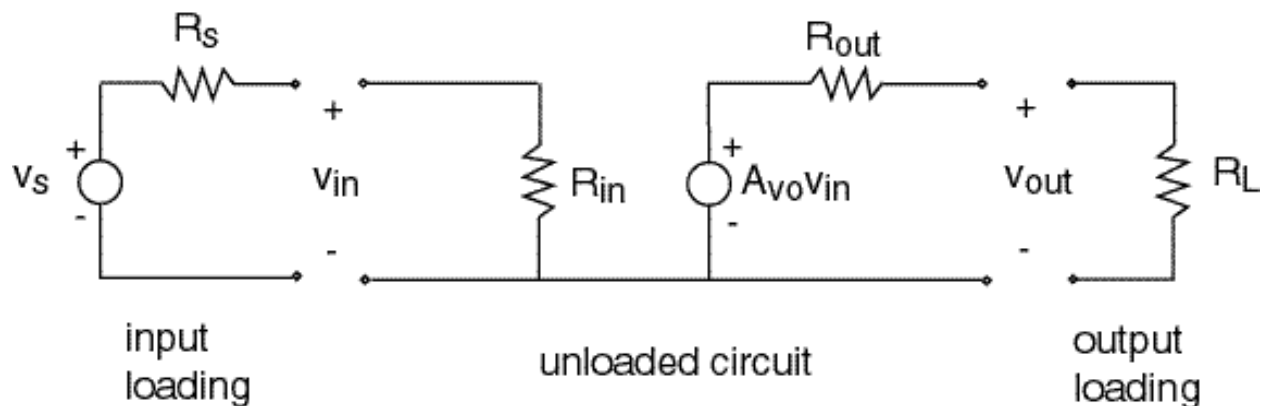

Voltage divider at input:
$$v_{in} = R_{in} \frac{v_s}{R_{in} + R_s}$$


Voltage divider at output:
$$v_{out} = R_L \frac{A_{vo} v_{in}}{R_{out} + R_L}$$

Loaded voltage gain:
$$\frac{v_{out}}{v_s} = \frac{R_{in}}{R_{in} + R_s} A_{vo} \frac{R_L}{R_L + R_{out}}$$

Input Resistance

- Calculation of input resistance, R_{in} :
 - Load amplifier with R_L
 - Apply test voltage (or current) at input, measure test current (or voltage).

For common-emitter amplifier:

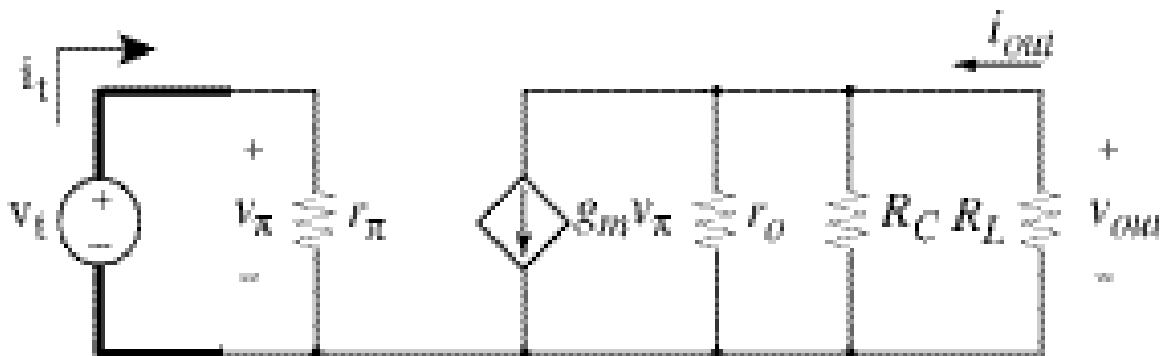


$$v_t = i_t r \quad R_{in} = \frac{v_t}{i_t} = r$$

No effect of loading at input.

Output Resistance

- Calculation of input resistance, R_{out} :
 - Load amplifier with R_S
 - Apply test voltage (or current) at output, measure test current (or voltage).


For common-emitter amplifier:

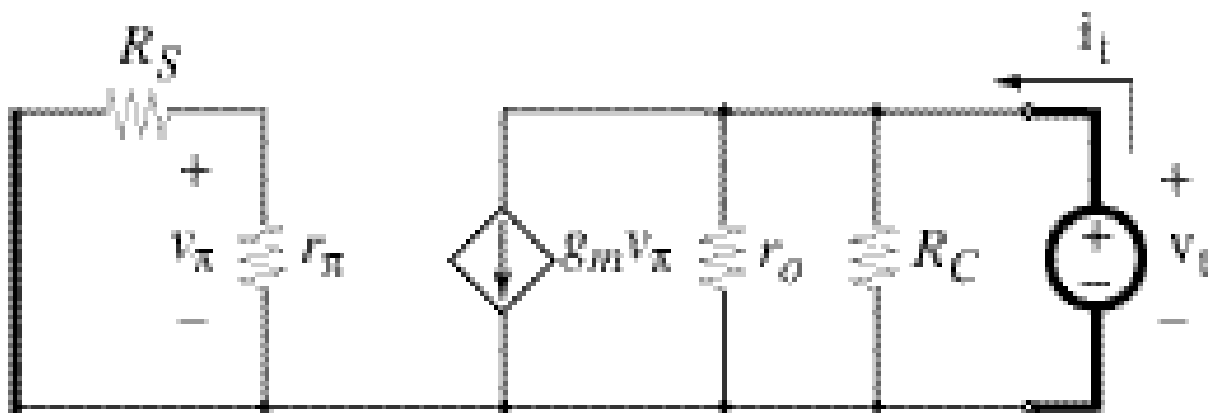

$$v = 0 \quad g_m v = 0 \quad v_t = i_t (r_o // R_C)$$

$$R_{out} = \frac{v_t}{i_t} = r_o // R_C$$

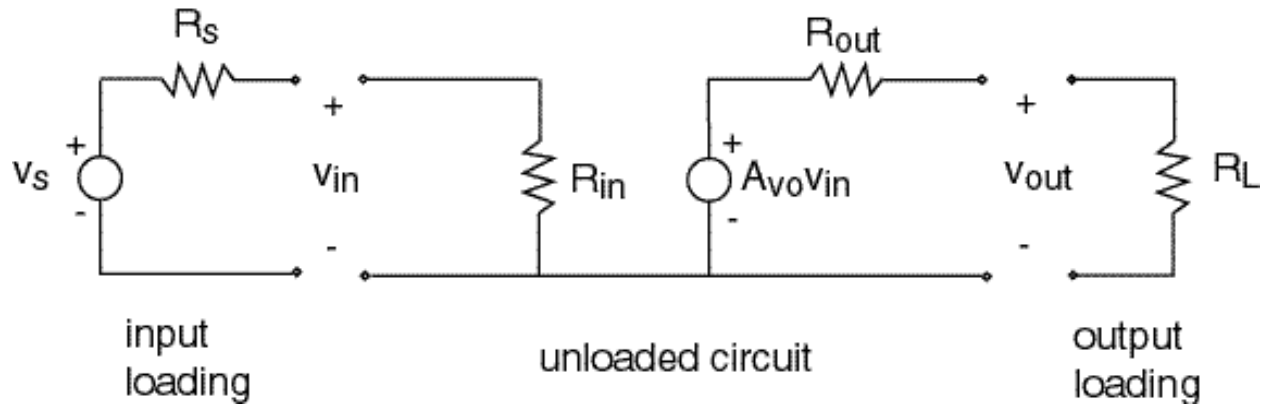Two-port network view of common-source amplifier



$$\begin{aligned} \frac{v_{out}}{v_s} &= \frac{R_{in}}{R_{in} + R_S} A_{vo} \frac{R_L}{R_L + R_{out}} \\ &= -\frac{r}{r + R_S} g_m (r_o // R_C) \frac{R_L}{R_L + r_o // R_C} \end{aligned}$$

Or:

$$\frac{V_{out}}{v_s} = -\frac{r}{r + R_S} g_m (r_o // R_C // R_L)$$

$$R_{out} = r_o // R_C$$

$$R_{in} = r$$

Design issues of common-emitter amplifier (unloaded)

- To maximize the output swing, set $V_{OUT} = V_{CC}/2$.
The load resistor value is coupled with the collector current through the load line equation

$$I_C = \frac{V_{CC} - V_{OUT}}{R_C} = \frac{V_{CC}}{2R_C}$$

- The transconductance is therefore

$$g_m = \frac{I_C}{V_{th}} = \frac{V_{CC}}{2R_C V_{th}}$$

- The small signal gain voltage gain (for $r_o \gg R_C$)


$$A_v = g_m R_C = \frac{-V_{CC}}{2 V_{th}}$$

Issue:


- To increase the voltage gain, the only option is to increase the supply voltage which wastes power

Solution: CE amplifier with current source supply

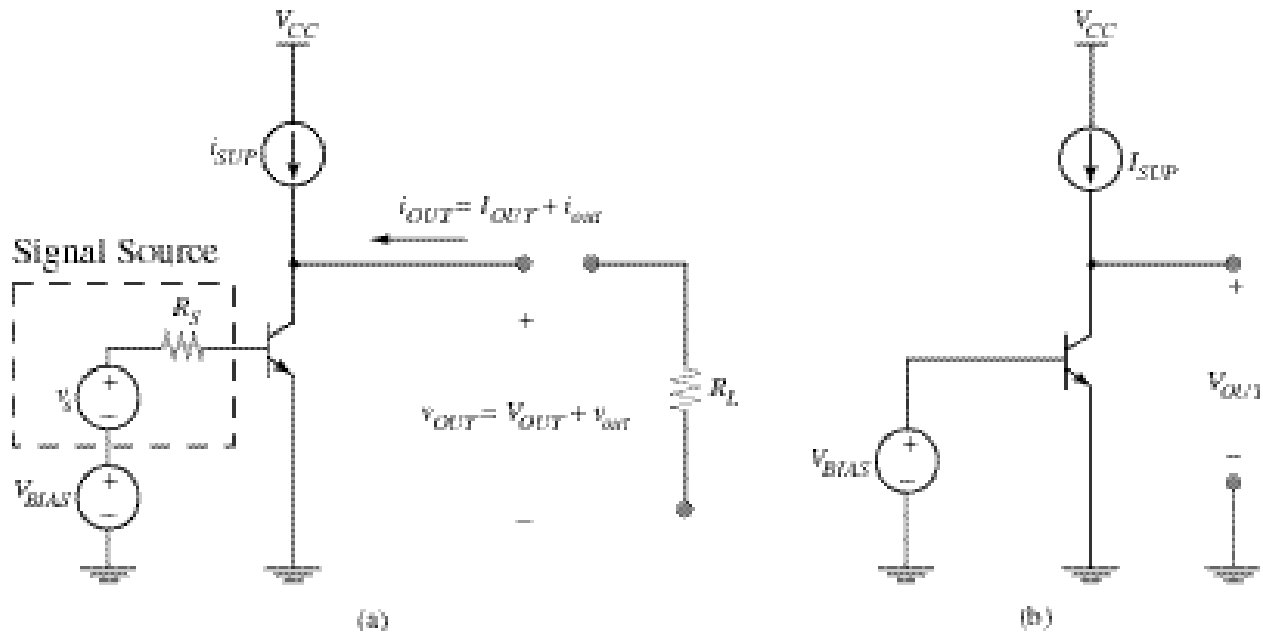
3. Common-source amplifier with current-source supply



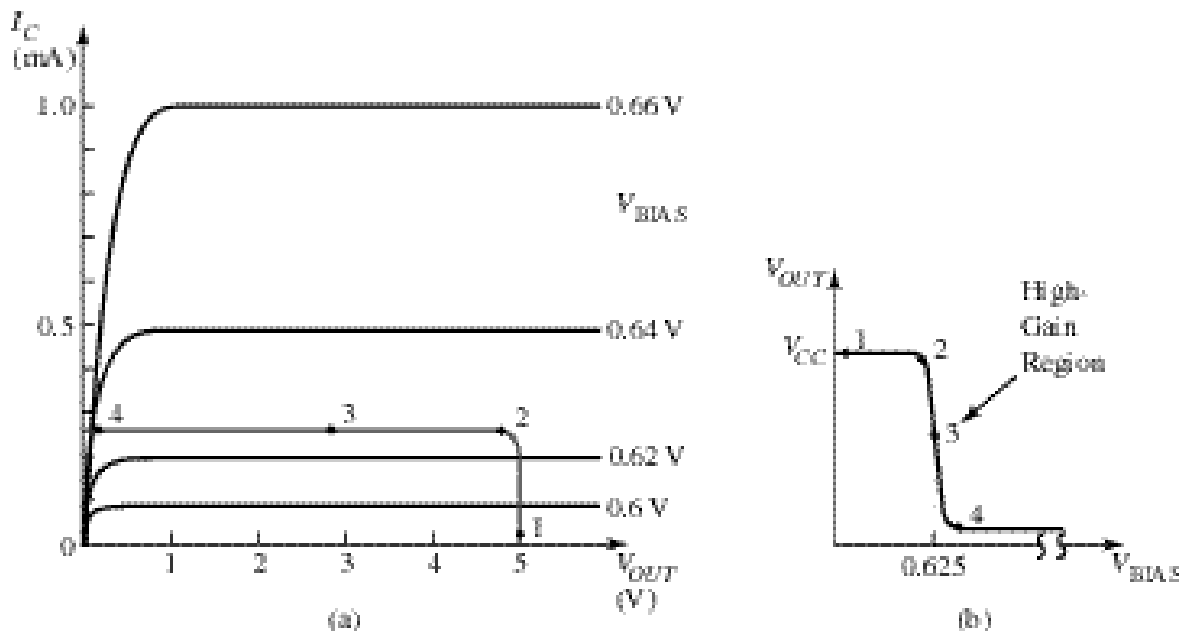CE Amplifier with Idealized Current Source Loadline :



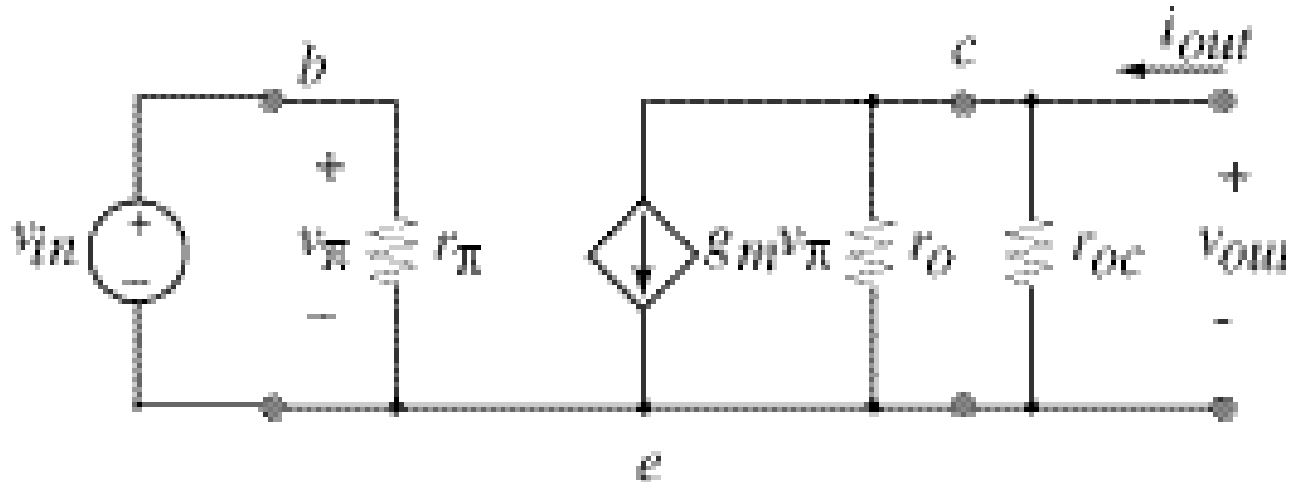Small-Signal Model for CE Amplifier with Current Source Supply



- Voltage Gain (unloaded)

$$\mathbf{A_{vo}} = \frac{\mathbf{V_{out}}}{\mathbf{V_{in}}} = -\mathbf{g_m}(\mathbf{r_o} // \mathbf{r_{oc}})$$

- For a well designed current source, $r_{oc} \gg r_o$, hence common emitter amplifier gain reduces to:

$$\mathbf{A_{vo}} \quad \mathbf{g_m r_o} = - \frac{\mathbf{I_C}}{\mathbf{V_{th}}} \quad \frac{\mathbf{V_A}}{\mathbf{I_C}} = - \frac{\mathbf{V_A}}{\mathbf{V_{th}}}$$

- Final expression depends on device dimensions and parameters
 - (e.g., base width and the ratio of base doping to collector doping)

Relationship between common emitter amplifier circuit figures of merit and device parameters

Remember:

$$g_m = \frac{I_C}{V_{th}}$$


$$r_o = \frac{V_A}{I_C}$$

Then:

Device Parameters	Circuit Parameters		
	$ A_{vo} $	R_{in}	R_{out}
	$g_m(r_o // r_{oc})$	r	$r_o // r_{oc}$
I_{SUP}	-		
r_o	-		-
V_A		-	

CE amplifier with current source supply is a good voltage amplifier (R_{in} medium and $|A_{vo}|$ high), but R_{out} high too voltage gain degraded if $R_L \ll r_o // r_{oc}$.

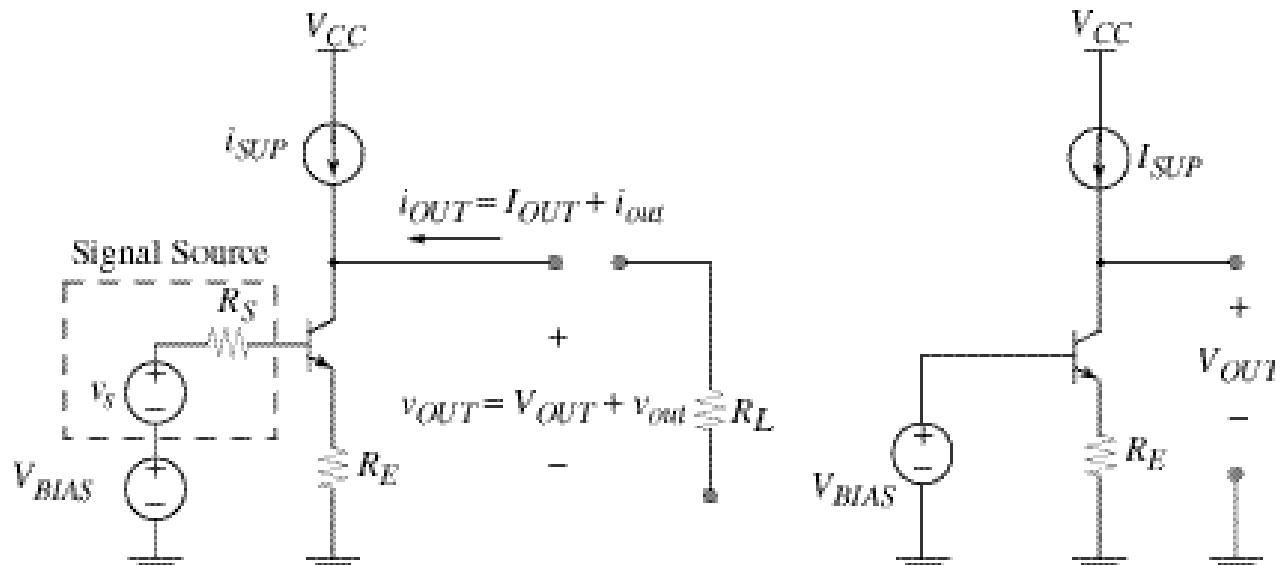Common Emitter Amplifier (with emitter degeneration resistor)



- Addition of emitter resistance leads to increase in input and output resistance
- Voltage gain depends predominantly on the emitter resistance resulting in a well controlled gain
 - Gain relatively independent of temperature and process variations


$$V_{BIAS} = V_{BE} + \frac{(F + 1)I_C}{F} R_E \quad V_{BE} + I_C R_E$$

$$V_{BE} = V_{th} \ln \frac{I_C}{I_S}$$

$$I_C = I_{SUP}$$

Small Signal Model

(CE Amplifier with R_E)

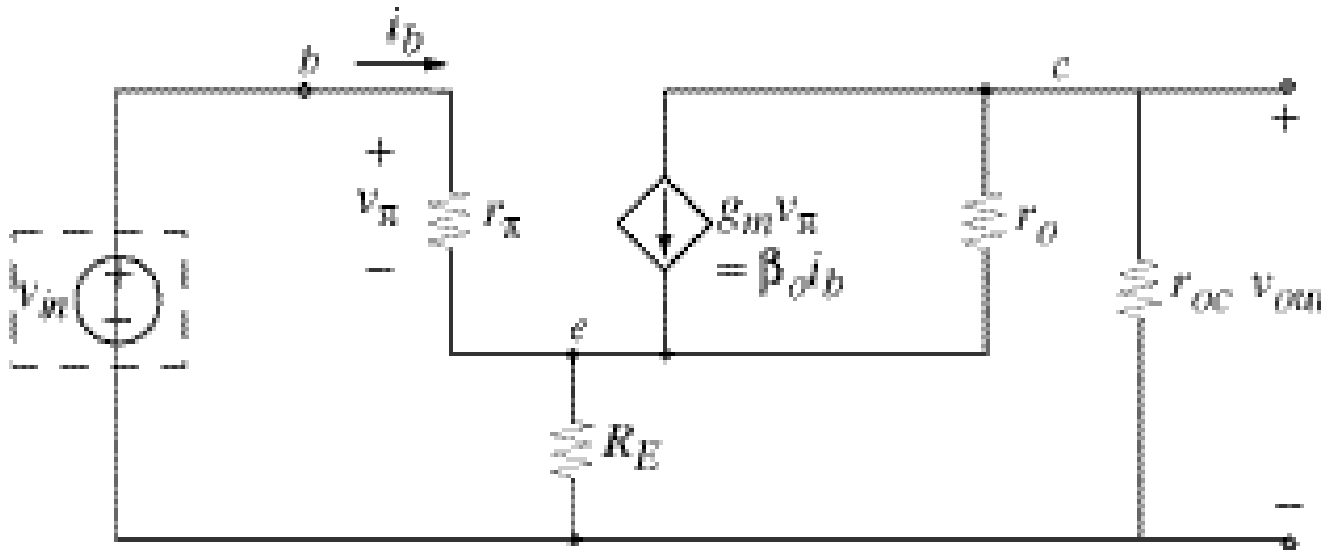

- Addition of emitter resistance leads to increase in input and output resistance by a factor $(1 + g_m R_E)$
- Voltage gain reduced by a factor $(1 + g_m R_E)$

$$A_v = \frac{g_m [r_{oc} // r_o (1 + g_m R_E)]}{1 + g_m R_E} = \frac{g_m r_{oc}}{1 + g_m R_E}$$

$$R_{in} = r (1 + g_m R_E)$$

$$R_{out} = r_{oc} // r_o (1 + g_m R_E)$$

What did we learn today?

Summary of Key Concepts

- Common-emitter amplifier with resistive supply
 - To maximize gain, large power supply required
 - High power consumption
- Performance improved by using common-emitter amplifier with current source supply.
- Two-port network computation of voltage gain, input resistance and output resistance of amplifier.