

April 14, 1999 - Quiz #2

Name: Solutions
Recitation: _____


problem	grade
1	
2	
3	
total	

General guidelines (please read carefully before starting):

- Make sure to write your name on the space designated above.
- Open book: you can use any material you wish.
- All answers should be given in the space provided. Please do not turn in any extra material. If you need more space, use the back page.
- You have 120 minutes to complete your quiz.
- Make reasonable approximations and state them, i.e. quasi-neutrality, depletion approximation, etc.
- Partial credit will be given for setting up problems without calculations. NO credit will be given for answers without reasons.
- Use the symbols utilized in class for the various physical parameters, i.e. μ_n , I_D , β_F , etc.
- Every numerical answer must have the proper units next to it. Points will be subtracted for answers without units or with wrong units.
- Use the following fundamental constants and physical parameters for silicon and silicon dioxide at room temperature:

$$\begin{aligned}n_i &= 1 \times 10^{10} \text{ cm}^{-3} \\kT/q &= 0.026 \text{ V} \\q &= 1.60 \times 10^{-19} \text{ C} \\ \epsilon_s &= 1.05 \times 10^{-12} \text{ F/cm} \\ \epsilon_{ox} &= 3.45 \times 10^{-13} \text{ F/cm}\end{aligned}$$

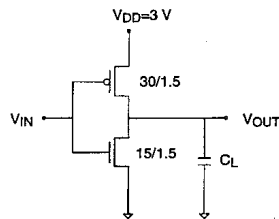1. (25 points) Below is a CMOS inverter with the following device data: $t_{ox} = 15 \text{ nm}$, $\mu_n = 300 \text{ cm}^2/\text{V}\cdot\text{s}$, $\mu_p = 100 \text{ cm}^2/\text{V}\cdot\text{s}$, $V_{Tp} = -1 \text{ V}$, $\lambda_n = \lambda_p = 0 \text{ V}^{-1}$. The device dimensions are $W_p = 30 \text{ }\mu\text{m}$, $L_p = 1.5 \text{ }\mu\text{m}$, $W_n = 15 \text{ }\mu\text{m}$, $L_n = 1.5 \text{ }\mu\text{m}$.



1a) (5 points) Calculate V_{TN} so that $V_{SI} = 1.5 \text{ V}$.

$$V_m = \frac{V_{TN} + \sqrt{\frac{K_p}{K_n}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{K_p}{K_n}}}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 2.3 \times 10^{-7} \text{ F/cm}^2$$

$$K_n = \left(\frac{W}{L}\right)_n \mu_n C_{ox} = 6.9 \times 10^{-4} \text{ F/V}\cdot\text{s}$$

$$K_p = \left(\frac{W}{L}\right)_p \mu_p C_{ox} = 4.6 \times 10^{-4} \text{ F/V}\cdot\text{s}$$

$$V_{TN} = V_m \left(1 + \sqrt{\frac{K_p}{K_n}}\right) - \sqrt{\frac{K_p}{K_n}} (V_{DD} + V_{Tp})$$

$$V_{TN} = 1.092 \text{ V}$$

$$S \frac{\text{F}}{\text{V}\cdot\text{s}} \frac{\text{V}^2}{\text{V}}$$

Assume $V_{TN} = 1V$ for parts 1b-1e.

1b) (5 points) What is the maximum value for C_L and still have both t_{PLH} and t_{PHL} less than $1 \mu s$? (Neglect C_{db} for this calculation.)

$$t_{PHL} = \frac{C_L \cdot V_{OH}/2}{\frac{K_n}{2} (V_{OH} - V_{TN})^2}$$

$$t_{PLH} = \frac{C_L \cdot V_{OH}/2}{K_p/2 (V_{OH} + V_{TP})^2}$$

$$V_{OH} = V_{DD}$$

$$C_L = \frac{t_{PHL} \frac{K_n}{2} (V_{DD} - V_{TN})^2}{V_{DD}/2} = 9.2 \times 10^{-13} \text{ F}$$

$$C_L = \frac{t_{PLH} \frac{K_p}{2} (V_{DD} + V_{TP})^2}{V_{DD}/2} = 6.133 \times 10^{-13} \text{ F}$$

$$C_{Lmax} = 6.133 \times 10^{-13} \text{ F} = 0.6133 \text{ pF}$$

1c) (5 points) A square wave signal from 0 to V_{DD} is applied to the input of this CMOS inverter with a frequency of 10 MHz. Calculate the power dissipated in the inverter. For this part, assume $C_L = 1 \text{ pF}$ and neglect any other parasitic capacitance.

$$P_D = C_L V_{DD}^2 f = 1 \times 10^{-12} (3)^2 (10 \times 10^6) \\ = 90 \mu\text{W}$$

1d) (5 points) What is the value of V_{DD} required to reduce the power dissipation in the inverter by a factor of 4?

$$\frac{P_D}{4} = C_L \left(\frac{V_{DD}}{2} \right)^2 f$$

$$V_{DD} = 1.5 \text{ V}$$

1e) (5 points) If V_{DD} is reduced to 1.5 V, sketch the voltage transfer characteristic, V_{out} vs. V_{in} , of the inverter.

$$- V_{OH} = V_{DD} \quad V_{OL} = 0$$

$$V_{IL} = V_m + \frac{V_{DD} - V_m}{A_v} \quad V_{IH} = V_m - \frac{V_m}{A_v}$$

$$V_m = \frac{V_{TN} + \sqrt{\frac{K_p}{K_n}} (V_{DD} + V_{TP})}{1 + \sqrt{\frac{K_p}{K_n}}}$$

$$= .775V$$


$$- A_v = -(g_{mn} + g_{mp})(r_{on} || r_{op})$$

$$r_{on} = \frac{1}{\lambda_n I_D} = \frac{1}{0} = \infty$$


$$r_{op} = \frac{1}{\lambda_p I_D} = \frac{1}{0} = \infty$$

$$A_v = \infty$$

$$V_{IL} = V_m \quad V_{IH} = V_m$$

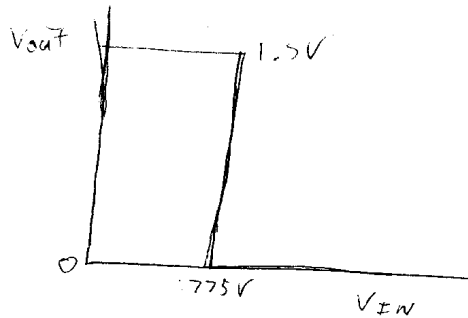

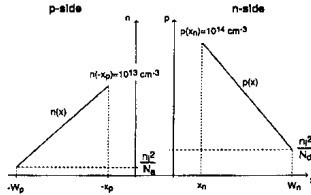2. (40 points) Below is a sketch not to scale of the minority carrier distribution across the quasi-neutral regions of a forward-biased p-n diode. For this diode, $W_p - x_p = 4 \mu\text{m}$, $W_n - x_n = 3 \mu\text{m}$, $D_n = 25 \text{ cm}^2/\text{V}\cdot\text{s}$, and $D_p = 10 \text{ cm}^2/\text{V}\cdot\text{s}$. The area of the junction is $10 \mu\text{m}^2$.



2a) (5 points) Calculate the hole current injected into the n-side of the diode.

$$I_p = A E J_{diff}^p \quad J_{diff}^p = -q D_p \frac{\partial p}{\partial x}$$

$$\frac{\partial p}{\partial x} = -\left(\frac{p(x_n) - 0}{W_n - x_n}\right) \quad \frac{n_0^2}{N_D} \ll p(x_n)$$

$$I_p = A E q D_p \left(\frac{p(x_n) - 0}{W_n - x_n}\right)$$

$$I_p = 10(10^{-4})^2 q (10) \left(\frac{10^{14}}{3 \times 10^{-4}}\right) = 53.3 \text{ nA}$$

2b) (5 points) Calculate the electron current injected into the p-side of the diode.

$$I_n = A E J_{diff}^n \quad J_{diff}^n = q D_n \frac{\partial n}{\partial x}$$

$$\frac{\partial n}{\partial x} = \frac{n(-x_p) - 0}{-x_p + W_p} \quad \frac{n_0^2}{N_A} \ll n(-x_p)$$

$$I_n = A E q D_n \left(\frac{n(-x_p) - 0}{W_p - x_p}\right)$$

$$I_n = 10(10^{-4})^2 q 25 \left(\frac{10^{13}}{4 \times 10^{-4}}\right) = 10 \text{ nA}$$

2c) (5 points) Calculate the diffusion capacitance associated with carrier storage on the n-side of the diode.

$$\begin{aligned} C_d &= \frac{q A E}{2 V_{th}} (W_n - x_n) \underbrace{p_{n0} e^{V_D/V_{th}}}_{p(x_n)} \\ &= \frac{q \cdot 10(10^{-4})^2}{2 \cdot 0.026} (3 \times 10^{-4}) (10^{14}) = 9.23 \text{ fF} \end{aligned}$$

2d) (5 points) Calculate the diffusion capacitance associated with carrier storage on the p-side of the diode.

$$\begin{aligned} C_d &= \frac{q A E}{2 V_{th}} (W_p - x_p) \underbrace{n_{p0} e^{V_D/V_{th}}}_{n(-x_p)} \\ &= \frac{q \cdot 10(10^{-4})^2}{2 \cdot 0.026} (4 \times 10^{-4}) (10^{13}) = 1.23 \text{ fF} \end{aligned}$$

2c) (5 points) How much should the voltage across the junction increase if we wish to double the total current through the diode?

$$I = I_0 e^{qV_0/KT}$$

$$I_{new} = I_0 e^{qV_{new}/KT}$$

$$I_{new} = 2I$$

$$\frac{I_{new}}{I} = \frac{I_0 e^{qV_{new}/KT}}{I_0 e^{qV_0/KT}}$$

$$\frac{I_{new}}{I} = e^{q(V_{new}-V_0)/KT}$$

$$V_{new}-V_0 = \frac{KT}{q} \ln\left(\frac{I_{new}}{I}\right)$$

$$V_{new}-V_0 = \frac{KT}{q} \ln(2) = 0.18V$$

2d) (5 points) If we increase the voltage in the manner suggested in the previous question, what happens to the total diffusion capacitance of the diode?

$$C_d = \frac{qA}{2V_{th}} \left((w_p-x_p) \frac{n_i^2}{N_A} + (w_n-x_n) \frac{n_i^2}{N_D} \right) e^{V_0/V_{th}}$$

$$C_{d,new} = \frac{qA}{2V_{th}} \left((w_p-x_p) \frac{n_i^2}{N_A} + (w_n-x_n) \frac{n_i^2}{N_D} \right) e^{V_{new}/V_{th}}$$

$$\frac{C_{d,new}}{C_d} = \frac{\frac{qA}{2V_{th}} \left((w_p-x_p) \frac{n_i^2}{N_A} + (w_n-x_n) \frac{n_i^2}{N_D} \right) e^{V_{new}/V_{th}}}{\frac{qA}{2V_{th}} \left((w_p-x_p) \frac{n_i^2}{N_A} + (w_n-x_n) \frac{n_i^2}{N_D} \right) e^{V_0/V_{th}}}$$


$$\frac{C_{d,new}}{C_d} = \frac{e^{V_{new}/V_{th}}}{e^{V_0/V_{th}}} = e^{(V_{new}-V_0)/V_{th}}$$

$$= e^{V_{th} \ln(2)/V_{th}} = e^{\ln(2)} = 2$$

$$\frac{C_{d,new}}{C_d} = 2 \quad C_{d,new} = C_d \times 2$$

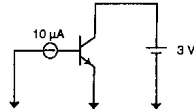3. (35 points) Consider a bipolar transistor with the following large-signal equivalent circuit model parameters $I_S = 10^{-16}$ A, $\beta_F = 100$, and $\beta_R = 1$. To answer some of the following questions, use the non-linear hybrid- π model of the transistor presented in class.

□ Answer the following questions when the device is biased as sketched in the diagram below:



3a) (5 points) In what regime is the device operating? Explain.

Fd, Active. $I_B > 0$ $V_{CE} = 3V$ $V_{BE} \approx .7V$
 $V_{BC} < 0$

3b) (5 points) Calculate the collector current, I_C .

$$I_C = \beta I_B = 100 \cdot 10 \mu A = 1 \text{ mA}$$

3c) (5 points) Calculate the base-emitter voltage V_{BE} .

$$I_C = I_S e^{\frac{V_{BE}}{V_{th}}}$$

$$V_{BE} = V_{th} \ln\left(\frac{I_C}{I_S}\right) = .026 \ln\left(\frac{10^{-3}}{10^{-16}}\right) = .778V$$

2a) (5 points) What is the ratio of the doping levels across the junction: N_a/N_d ?

$$\frac{p(x_n)}{n(-x_p)} = \frac{\frac{n_i^2}{n_d} e^{qV_0/KT}}{\frac{n_i^2}{N_a} e^{qV_0/KT}} = \frac{N_a}{N_d}$$

$$\frac{p(x_n)}{n(-x_p)} = \frac{10^{14}}{10^{13}} = 10 \quad \frac{N_a}{N_d} = 10$$

2b) (5 points) In what direction should N_a/N_d change if we wish to redesign the diode so as to get less diffusion capacitance at the same current level? (Assume that in redesigning the diode D_n , D_p , $W_n = x_n$, and $W_p = x_p$ do not change).

Choose one: N_a/N_d must increase (N_a/N_d must decrease) Explain (no explanation, no points).

$$C_d = \frac{qA}{2V_{th}} \left((W_p - x_p) \frac{n_i^2}{n_d} e^{V_0/V_{th}} + (W_n - x_n) \frac{n_i^2}{N_a} e^{V_0/V_{th}} \right)$$

$$C_d = \frac{qA}{2V_{th}} \left((W_p - x_p) n(-x_p) + (W_n - x_n) p(x_n) \right)$$

C_d is proportional to $n(-x_p)$ and $p(x_n)$. $I = I_p + I_n$

$$I_p = q D_p A E \frac{p(x_n) - 0}{W_n - x_n}$$

$$I_n = q D_n A E \frac{n(-x_p) - 0}{W_p - x_p}$$

We can increase I_n and decrease I_p and maintain I . Since $\frac{D_n}{W_p - x_p} > \frac{D_p}{W_n - x_n}$ we

can decrease ~~$p(x_n)$~~ $p(x_n)$ more than

we increase $n(-x_p)$. In this way

we get the same current with a

lower $n(-x_p) + p(x_n)$. Since $C_d \propto n(-x_p) + p(x_n)$


C_d will be lower too. $\frac{p(x_n)}{n(-x_p)} = \frac{N_a}{N_d}$.

We must lower $\frac{N_a}{N_d}$.

$$\text{for } \frac{N_a}{N_d} = 10 \quad C_d = 10.46 \text{ fF}$$

$$\text{for } \frac{N_a}{N_d} = .35 \quad C_d = 7.23 \text{ fF}$$

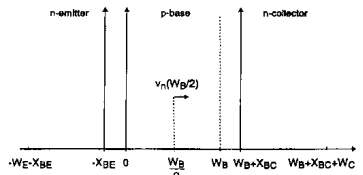3d) (5 points) If the doping level in the base is $N_{aB} = 10^{17} \text{ cm}^{-3}$ and the area of the base-emitter junction is $A_E = 40 \mu\text{m}^2$, calculate the electron velocity in the middle of the quasi-neutral base (see sketch below).



$$I_C = A_E J$$

$$J = q n_p v_n$$

$$v_n = \frac{I_C}{A_E q n_p (w_{B/2})}$$

$$n_p(x) = -\frac{n_i^2 e^{qV_{BE}/kT} - n_{p0}}{w_B} x + \frac{n_i^2 e^{qV_{BE}/kT}}{N_{aB}}$$

$$n_p\left(\frac{w_B}{2}\right) = \frac{1}{2} \frac{n_i^2}{N_{aB}} e^{qV_{BE}/kT} = 4.95 \times 10^{15} \text{ cm}^{-3}$$

$$v_n = \frac{I_C}{A_E q n_p (w_{B/2})} = \frac{10^{-3}}{10(10^{-4})^2 q (4.95 \times 10^{15})}$$

$$v_n = 1.26 \times 10^7 \text{ cm/s} \quad 1.26 \times 10^5 \text{ m/s}$$

3g) (5 points) Calculate the collector current, I_c .

$$I_c = I_s \left(e^{qV_{BE}/kT} - e^{qV_{BC}/kT} \right) - \frac{I_s}{\beta_R} \left(e^{qV_{BC}/kT} - 1 \right)$$

$$V_{BE} = V_{BC}$$

$$I_c = -\frac{I_s}{\beta_R} \left(e^{qV_{BC}/kT} - 1 \right)$$
$$-10^{-16} \left(e^{\frac{.7785}{.026}} - 1 \right) = -1.01 \text{ mA}$$

1.01 mA out of the collector