

Problem Set #9 - 6.012 - Solutions - December 5, 2000

Problem #1: Pg. 20

$$(a) \quad g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \Rightarrow \left(\frac{W}{L}\right)_1 = \frac{g_{m1}^2}{2\mu_n C_{ox} I_{D1}}$$

$$\left(\frac{W}{L}\right)_1 = \frac{(1 \times 10^{-3})^2}{2(50 \times 10^{-6})(100 \times 10^{-6})}$$

$$\boxed{\left(\frac{W}{L}\right)_1 = 100}$$

$$(b) \quad I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TN})^2 \quad \text{and} \quad V_{GS} = V_{Bias}$$

$$V_{Bias} = V_{TN} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \quad \text{for } I_{out} = 0, I_{D1} = 100 \mu A$$

$$= 0.7 + \sqrt{\frac{2(100 \times 10^{-6})}{(50 \times 10^{-6})(100)}}$$

$$\boxed{V_{Bias} = 0.9 \text{ V}}$$

(c) This is a cascode amplifier stage with cascode current supply.

$$\text{So } R_{out} = R_{outCS} \parallel R_{outCascode} \quad r_{o3} = r_{o4} = \frac{1}{\lambda_p I_{Dp}} = 200 \text{ k}\Omega$$

$$\text{Current source: } R_{outCS} = r_{o4} + r_{o3} + g_{m3} r_{o4} r_{o3} \quad \text{and} \quad g_{m3} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_3 I_{Dp}}$$

$$R_{outCS} = 15 \text{ M}\Omega \quad g_{m3} = 0.365 \text{ mS}$$

$$\text{Stage: } R_{outCascode} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} \quad \& \quad g_{m2} = \sqrt{2} g_{m3} = 0.516 \text{ mS}$$

$$R_{outCascode} = 10.8 \text{ M}\Omega \quad r_{o2} = r_{o1} = \frac{1}{\lambda_n I_{Dn}} = 142.9 \text{ k}\Omega$$

$$\boxed{R_{out} = 6.3 \text{ M}\Omega}$$

$$(d) \quad i_{out} = i_{sc} \frac{R_{out}}{R_L + R_{out}} \quad \text{where } i_{sc} \text{ is short circuit current.}$$

$$\frac{R_{out}}{R_L + R_{out}} = 0.8 \Rightarrow \boxed{R_L = 1 \text{ M}\Omega}$$


Problem # 2: Pg. 22

- (a) First leg (left most) $\Rightarrow I_{D1} = I_{REF} = 100 \mu A$
 Second leg \Rightarrow Current mirror with $(\frac{W}{L})_8 = (\frac{W}{L})_9 \Rightarrow I_9 = 100 \mu A$
 Third leg \Rightarrow Current mirror with $(\frac{W}{L})_{7B} = (\frac{W}{L})_7 \Rightarrow I_7 = 100 \mu A$
 Fourth leg \Rightarrow Current mirror with $(\frac{W}{L})_7 = (\frac{W}{L})_5 \Rightarrow I_5 = 100 \mu A$
 Fifth leg \Rightarrow Current mirror with $(\frac{W}{L})_9 = (\frac{W}{L})_{10} \Rightarrow I_{10} = 100 \mu A$

(b) $I_{D1} = \frac{1}{2} \mu_n C_{ox} (\frac{W}{L})_1 (V_{bias} - V_{Tn})^2 = I_7$

$$V_{bias} = V_{Tn} + \sqrt{\frac{I_7}{\frac{1}{2} \mu_n C_{ox} (\frac{W}{L})_1}} = \boxed{1.33 \text{ volts.}}$$

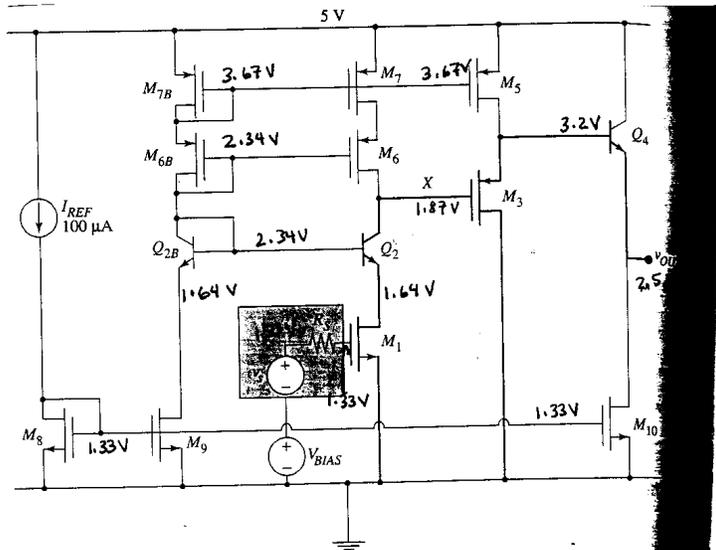(c) $V_{GS8} = V_{Tn} + \sqrt{\frac{I_9}{\frac{1}{2} \mu_n C_{ox} (\frac{W}{L})_8}} = \cancel{1.33} 1.33 \text{ volts}$
 $V_{SG7B} = -V_{Tp} + \sqrt{\frac{I_7}{\frac{1}{2} \mu_p C_{ox} (\frac{W}{L})_7}} = 1.33 \text{ volts}$



Problem # 2 : PG. 22 (cont.)

(d) Voltage on high side limited by Q_4 going from FBR to cutoff.

M_5 must have V_{TP} drop to stay in saturation. So, $V_{B_4}^{Max} = 4.3V$

and $V_{out}^{Max} = 3.6V$.

Voltage on low side limited by M_{10} going from saturation to linear.

$$V_{out}^{Min} > V_{GS} - V_{TN} = 1.33 - 0.7 = 0.67V$$

$$V_{swing} = V_{out}^{Max} - V_{out}^{Min} = 3.6 - 0.67 = \boxed{2.93V}$$

$$(e) R_{out\ cascode} = \beta_{o2} r_{o2} \parallel r_{oc} = 100 \left(\frac{20V}{100\mu A} \right) \parallel (r_{o6} + r_{o7} + g_{m6} r_{o6} r_{o7})$$

$$r_{o6} = r_{o7} = \frac{1}{(0.05)(100\mu A)} = \frac{1}{\lambda_p I_{Dp}} = 200k\Omega \quad \& \quad g_{m6} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{Dp}} = 0.316 \times 10^{-3}$$

$$R_{out\ cascode} = (20M\Omega \parallel 13M\Omega) = 7.9M\Omega$$

$$G_m = g_{m1} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{Dn}} = 0.316\ mS$$

$$\boxed{A_v^{Cas} = G_m R_{out\ cascode} = 2490}$$

(f) Next stage is a common drain: $A_{v2} \approx 1$


Next stage is a common collector: $A_{v3} \approx 1$

$$A_v = A_v^{Cas} A_{v2} A_{v3}$$

$$\boxed{A_v \approx 2490}$$

P10.24

Cascode voltage buffer
CS-CB-CD-CC

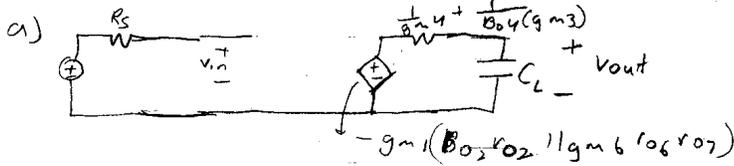

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_{m4} + B_{04}(g_{m3})} \quad (9.12)$$

$$A_{vOC} = -g_{m1}(B_{02} r_{02} \parallel g_{m6} r_{06} r_{07})$$

b) $A_{vOC} = -g_{m1}(B_{02} r_{02} \parallel g_{m6} r_{06} r_{07})$

$$g_{m1} = \frac{\sqrt{2 \frac{W}{L} \mu_n C_{ox} I_{D1}}}{1} \quad k_n = k_p \quad I_{D1} = I_{REF}$$

$$= \frac{\sqrt{2 \cdot 10 \cdot 50 \times 10^{-6} \cdot 50 \times 10^{-6}}}{1}$$

$$= 0.223 \text{ mS}$$

$$B_{02} = 100$$

$$r_{02} = \frac{V_A}{I_C} \quad I_C = I_{D1} \quad r_{02} = \frac{25}{50 \times 10^{-6}} = 500 \text{ k}\Omega$$

$$B_{02} r_{02} = 50 \text{ m}\Omega$$

$$g_{m6} = g_{m1} \quad \text{because } \left(\frac{W}{L}\right)_p = 2 \left(\frac{W}{L}\right)_n$$

$$r_{06} = r_{07} = \frac{1}{\lambda I_D} = \frac{1}{0.5 \cdot 50 \times 10^{-6}} = 400 \text{ k}\Omega$$

$$g_{m6} r_{06} r_{07} = 35.77 \text{ m}\Omega$$

$$A_{vOC} = 4662.7$$

c) $C_L = 0$
 the dominant pole is at the gate of M_3 because of the cascode's high output resistance

$$\omega_{3dB} = \frac{1}{(r_{o2} \parallel r_{oc}) [C_{\mu 2} + C_{gd6} + C_{gd3} + (1 + A_{vcas2}) C_{gs3}]} \quad (10.101)$$

$$r_{o2} \parallel r_{oc} = r_{o2} \parallel \frac{1}{g_m \beta_0 r_{o2}} = 50 \text{ M}\Omega \parallel 35.77 \text{ M}\Omega = 20.85 \text{ M}\Omega$$

$$\begin{aligned} C_{\mu 2} &= 10 \text{ fF} \\ C_{gd6} &= C_{ovp} W_6 = .35 \text{ fF}/\mu\text{m} \times 40 \mu\text{m} = 14 \text{ fF} \\ C_{gd3} &= C_{gd6} \\ C_{gs3} &= C_{ovn} W_3 + \frac{2}{3} W L C_{ox} = .5 \text{ fF}/\mu\text{m} \times 29 \mu\text{m} \\ &\quad + \frac{2}{3} (20)(2)(2.3) \\ &= 10 + 61.3 = 71.3 \text{ fF} \end{aligned}$$

$$A_{vcas2} = \frac{g_{m3}}{g_{m3} + g_{m6}} \quad g_{m6} \approx 0 \quad A_{vcas2} = 1$$

$$\omega_{3dB} = \frac{1}{20.85 \text{ M}\Omega [10 \text{ fF} + 14 + 71.3 \text{ fF} + 0]} = 503270 \text{ rad/sec}$$

$$f_{3dB} = 80.1 \text{ kHz}$$

d) $\omega_{3dB2} = \frac{1}{R_{C1} + R_{out} C_L} = .8 \left(\omega_{3dB1} = \frac{1}{R_{C1}} \right)$

$$\frac{1}{R_{C1} + R_{out} C_L} = \frac{.8}{R_{C1}} \quad \frac{1}{\omega_{3dB1} + R_{out} C_L} = .8 \omega_{3dB1}$$

$$C_L = \left(\frac{1}{.8} - 1 \right) \frac{1}{R_{out} \omega_{3dB1}} = \frac{1}{4} \left(\frac{1}{R_{out} \omega_{3dB1}} \right)$$

$$R_{out} = \frac{1}{g_{m4}} * \frac{1}{\beta_{04} g_{m3}}$$

$$\begin{aligned} g_{m3} &= g_{m1} \\ \beta_{04} &= 100 \end{aligned}$$

$$g_{m4} = \frac{I_{C4}}{V_{th}} \quad I_{C4} = I_{REF}$$

$$g_{m4} = \frac{50 \times 10^{-6}}{.026} = 1.92 \text{ mS}$$

$$R_{out} = \frac{1}{1.92 \times 10^{-3}} + \frac{1}{100.2236 \times 10^{-3}} = 565 \Omega$$

$$C_L = \frac{1}{4} \left(\frac{1}{565 (503270)} \right) = 878 \text{ pF}$$

P 11.12

a) $I_{BIAS} = I_{REF} = 100 \mu A$


$$I_1 = \frac{2.5 - V_{o1}}{R_D} \quad \text{set } V_{o1} = 0$$

$$I_1 = \frac{2.5}{R_D} \quad I_2 = \frac{2.5}{R_2}$$

$$I_{BIAS} = I_1 + I_2$$

$$I_1 = \frac{I_{BIAS}}{2}$$
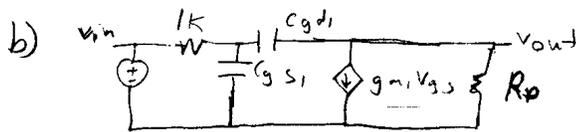
$$R_D = \frac{(2.5)(2)}{I_{BIAS}} = 50 \text{ k}\Omega$$



$$A_{VOC} = -g_{m1} R_D = a_{dm}$$

$$I_{D1} = \frac{I_{REF}}{2}$$

$$g_{m1} = \sqrt{\frac{W}{L} \mu_n C_{ox} I_{D1}} = \sqrt{50 (50 \times 10^{-6}) (2) (50 \times 10^{-9})}$$

$$= .5 \text{ mS}$$

$$a_{dm} = -25$$

$$\tau_1 = C_{gs} R_s$$

$$\tau_2 = C_{gd} (1 + g_m R_D) R_s$$

$$C_{gs} = C_{ovn} W_1 + \frac{2}{3} W_1 L, C_{ox} = (6.5)(100) + \frac{2}{3}(100)(2)(2.3)$$

$$= 357 \text{ fF}$$


$$\tau_1 = 3.57 \times 10^{-10}$$

$$C_{gd} = C_{ovn} W_1 = 50 \text{ fF}$$

$$\tau_2 = 50 \text{ fF} \cdot (1 + 25)(1 \times 10^3)$$

$$= 1.3 \times 10^{-9}$$
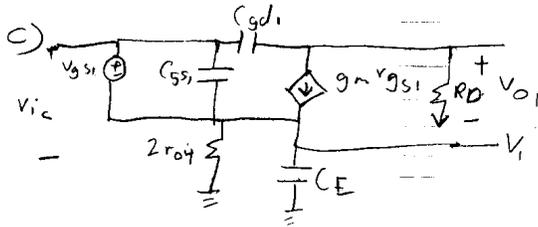
$$\omega_{3dB} = 769.2 \text{ M rad/sec} \quad 122.4 \text{ MHz}$$



$$V_{o1} = \frac{-g_m R_D}{1 + 2g_m r_{o4}} v_{i,c}$$


$$a_{cm} = - \frac{g_m R_D}{1 + 2g_m r_{o4}}$$

$$r_{o4} = \frac{1}{\lambda I_{D4}} = \frac{1}{.025 (100 \times 10^{-6})} = 400 \text{ k}\Omega$$

$$\lambda = \frac{.05 \times 2}{4}$$

$$a_{cm} = \frac{.5 \times 10^{-3} \cdot 50 \times 10^3}{1 + 2(.5 \times 10^{-3})(400 \text{ k})} = .062344$$

(look at example 11.3)

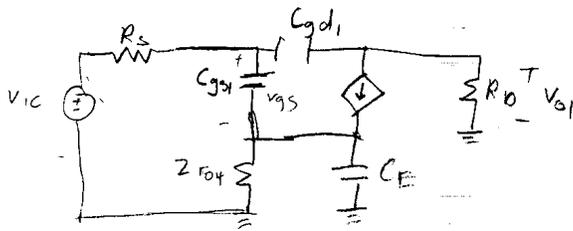

$$C_E = C_{d3} + C_{db3}$$

$$C_{gd3} = \omega_3 C_{ov} = 50 (.5) = 25 \text{ fF}$$

$$C_{db3} = \frac{\omega_3 L_{diff} C_{jn} + (2L_{diff} + \omega) C_{jsw}}{(50)(6)(.1) + (2(6) + 50)(.5)} = 61 \text{ fF}$$

$$C_E = 86 \text{ fF}$$

$$Z_e = z_{ro4} \parallel C_E = \frac{z_{ro4}}{1 + j\omega r_{o4} C_E}$$

$$a_{cm} = \frac{v_{oc}}{v_{ic}} = \frac{-g_m R_D}{1 + g_m Z_e}$$

$$|g_m Z_e| \gg 1$$

$$g_m z_e (\omega=0) = \frac{.5 \times 10^3 (2)(400 \times 10^3)}{1} = 400$$

$$a_{cm} = \frac{-R_D}{z_{ro4}} (1 + j\omega r_{o4} C_E)$$

$$\omega_{3dB} = \frac{1}{r_{o4} C_E} = \frac{1}{(2 \times 10^3)(86 \times 10^{-15})} = 29 \text{ Mrad/s} = 4.6 \text{ MHz}$$

$$c) CMRR = \frac{a_{dm}}{a_{cm}} = \frac{-25}{.062} = -403$$

