

# SINGLE-STAGE TRANSISTOR AMPLIFIERS

**COMMON EMITTER**

BIASING:  $I_C = I_{SUP}$

• GAIN STAGE  
• TRANSCONDUCTANCE AMP.

①  $A_m = \frac{I_C}{V_{IN}}$

•  $R_{IN} = r_{\pi}$  ← **LARGE**

•  $R_{OUT} = \begin{cases} r_{O1} || R_C \\ r_{O1} || R_L \end{cases}$  ← **LARGE**

②  $\beta_0 = \frac{V_A}{V_C}$

•  $\frac{I_{OUT}}{V_{IN}} = \left( \frac{R_{IN}}{R_{IN} + R_S} \right) g_m \left( \frac{R_{OUT}}{R_{OUT} + R_L} \right)$

•  $\frac{V_{OUT}}{V_{IN}} = -R_L \left( \frac{I_{OUT}}{V_{IN}} \right)$

**COMMON SOURCE**

BIASING:  $I_D = I_{SUP}$

• GAIN STAGE  
• TRANSCONDUCTANCE AMP.

①  $g_m = \sqrt{2 I_D \mu_n C_{OX}}$

•  $R_{IN} = \infty$  ← **LARGE**

•  $R_{OUT} = \begin{cases} r_{O1} || R_D \\ r_{O1} || R_L \end{cases}$  ← **LARGE**

②  $\beta_0 = \frac{V_A}{V_D}$

•  $\frac{I_{OUT}}{V_{IN}} = g_m \left( \frac{R_{OUT}}{R_{OUT} + R_L} \right)$

•  $\frac{V_{OUT}}{V_{IN}} = -R_L \left( \frac{I_{OUT}}{V_{IN}} \right)$

**COMMON COLLECTOR (EMITTER FOLLOWER)**

BIASING:  $I_C = I_{SUP}$

• VOLTAGE BUFFER  
• VOLTAGE AMPLIFIER

•  $A_V = \frac{1}{1 + \frac{r_{\pi}}{(C_{O1} || C_{O2}) (\beta_0 + 1)}}$   $\approx 1$

•  $R_{IN} = r_{\pi} + \beta_0 (C_{O1} || C_{O2} || R_L)$  ← **LARGE**

•  $R_{OUT} = \frac{1}{g_m} + \frac{R_S}{\beta_0}$  ← **SMALL**

•  $\frac{V_{OUT}}{V_{IN}} = \left( \frac{R_{IN}}{R_{IN} + R_S} \right) A_V \left( \frac{R_L}{R_L + R_{OUT}} \right)$

**COMMON DRAIN (SOURCE FOLLOWER)**

BIASING:  $I_D = I_{SUP}$

• VOLTAGE BUFFER  
• VOLTAGE AMPLIFIER

•  $A_V = \frac{g_m}{g_m + g_{mb}}$

•  $R_{IN} = \infty$  ← **LARGE**

•  $R_{OUT} = \frac{1}{g_m + g_{mb}}$  ← **SMALL**

•  $\frac{V_{OUT}}{V_{IN}} = A_V \left( \frac{R_L}{R_L + R_{OUT}} \right)$

$R_L' = R_L || C_{O2} || C_{O1}$

**COMMON BASE**

BIASING:  $I_{SUP} = I_{BIAS}$

• CURRENT BUFFER  
• CURRENT AMPLIFIER

•  $A_i = \frac{-\beta_0}{1 + \beta_0} \approx -1$  **SMALL**

•  $R_{IN} = \frac{1}{\frac{1}{r_{\pi}} + g_m + \frac{1 - g_m (C_{O1} || R_L)}{r_{\pi} + (C_{O1} || R_L)}}$  **LARGE**

•  $R_{OUT} \approx r_{O1} || \left[ r_{O1} \left( 1 + g_m (r_{\pi} || R_S) \right) \right]$  **LARGE**

•  $i_{in} = \left( \frac{R_S}{R_S + R_{IN}} \right) A_i \left( \frac{R_{OUT}}{R_{OUT} + R_L} \right)$

**COMMON GATE**

BIASING:  $I_{SUP} = I_{BIAS}$

• CURRENT BUFFER  
• CURRENT AMPLIFIER

•  $A_i = -1$

•  $R_{IN} \approx \frac{1}{g_m + g_{mb}}$  ← **SMALL**

•  $R_{OUT} \approx r_{O1} || \left[ r_{O1} (1 + g_m R_S) \right]$  **LARGE**

•  $i_{in} = \left( \frac{R_S}{R_S + R_{IN}} \right) A_i \left( \frac{R_{OUT}}{R_{OUT} + R_L} \right)$