

Lecture 13 - Digital Circuits (II)

MOS INVERTER CIRCUITS

March 22, 2001

Contents:

1. NMOS inverter with resistor pull-up (cont.)
2. NMOS inverter with current-source pull-up
3. Complementary MOS (CMOS) Inverter

Reading assignment:

Howe and Sodini, Ch. 5, §5.3



Key questions

- What are the key design trade-offs of the NMOS inverter with resistor pull-up?
- How can one improve upon these trade-offs?
- What is special about a CMOS inverter?

  1. NMOS inverter with resistor pull-up (*cont.*)

□ Dynamics

- C_L *pull-down* limited by current through transistor [will study in detail with CMOS]
- C_L *pull-up* limited by resistor ($t_{PLH} \sim RC_L$)
- pull-up slowest



□ Inverter design issues:

noise margins $\uparrow \Rightarrow |A_v| \uparrow \Rightarrow$

- $R \uparrow \Rightarrow RC_L \uparrow \Rightarrow$ slow switching
- $g_m \uparrow \Rightarrow W \uparrow \Rightarrow$ big transistor
(slow switching at input)

Trade-off between speed and noise margin.


During pull-up, need:

- high current for fast switching,
- but also high resistance for high noise margin.


\Rightarrow use *current source* as pull-up.

2. NMOS inverter with current-source pull-up


I-V characteristics of current source:

 

Equivalent circuit models:

 


large-signal model

 


small-signal model

- high current throughout voltage range: $i_{SUP} \simeq I_{SUP}$
- high small-signal resistance, r_{oc} .

 NMOS inverter with current-source pull-up:




Transfer characteristics:

 

High $r_{oc} \Rightarrow$ high noise margin


Dynamics:

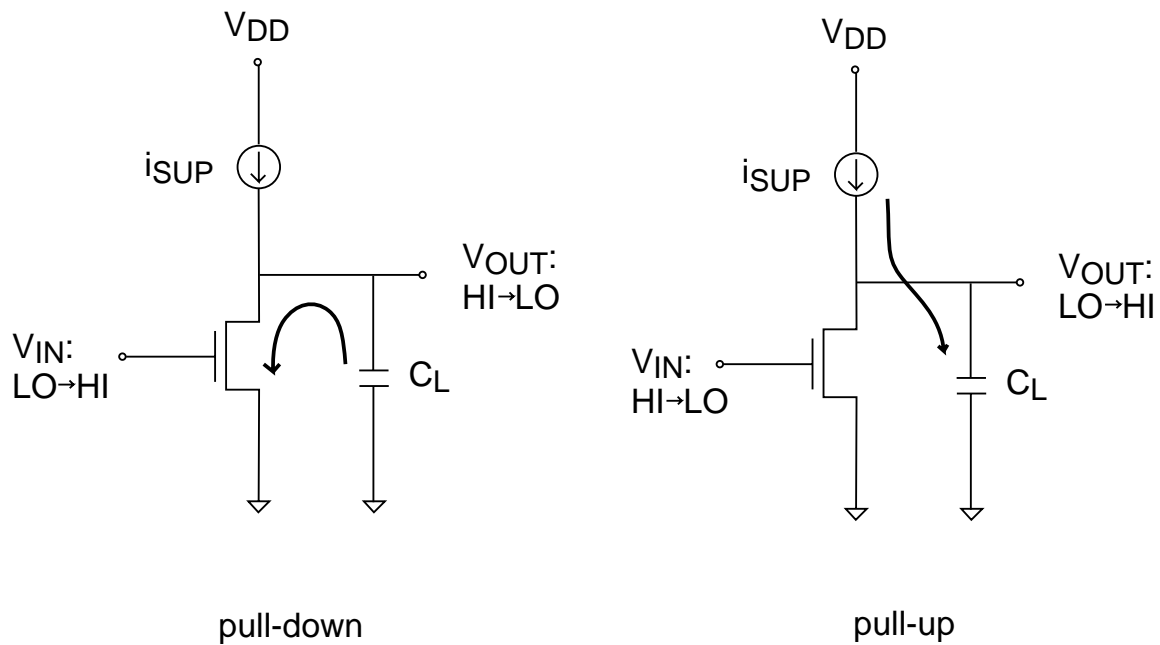

Faster pull-up because capacitor charged at constant current.

□ PMOS as current-source pull-up

I-V characteristics of PMOS:

 


Note: enhancement-mode PMOS has $V_{Tp} < 0$.


In saturation:

$$-I_{Dp} \propto (V_{SG} + V_{Tp})^2$$

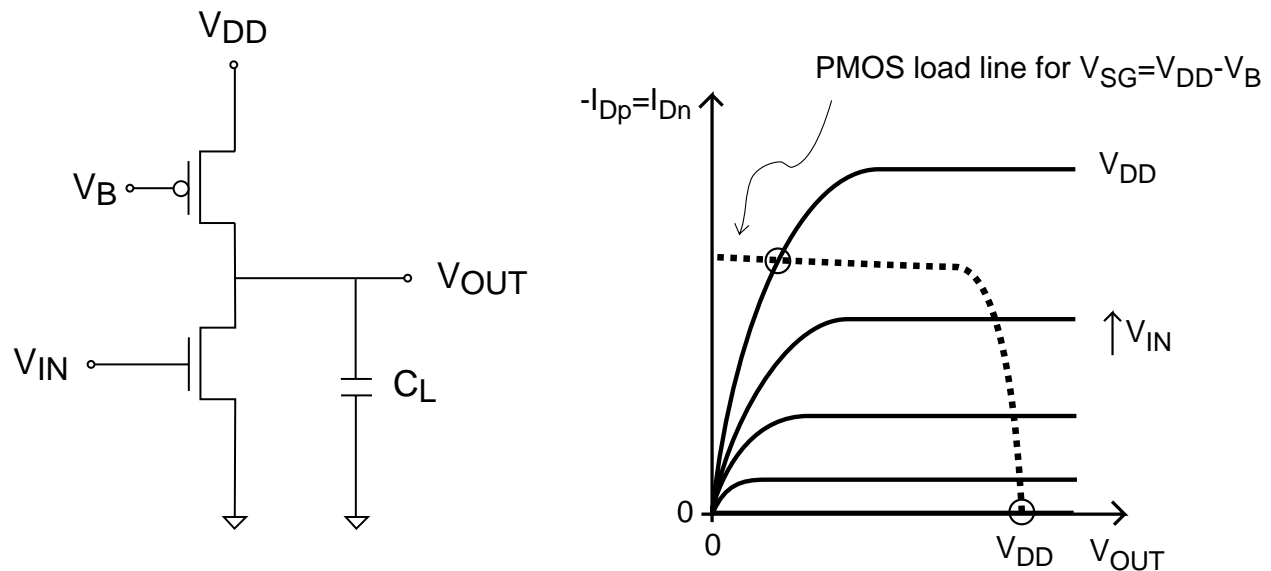Circuit and load-line diagram of inverter with PMOS current source pull-up:



Transfer function:

 

Noise margin:

- compute $V_M = V_{IN} = V_{OUT}$
- compute $|A_v(V_M)|$

At V_M both transistors saturated:

$$I_{Dn} = \frac{W_n}{2L_n} \mu_n C_{ox} (V_M - V_{Tn})^2$$

$$-I_{Dp} = \frac{W_p}{2L_p} \mu_p C_{ox} (V_{DD} - V_B + V_{Tp})^2$$



And:

$$I_{Dn} = -I_{Dp}$$

Then:

$$V_M = V_{Tn} + \sqrt{\frac{\mu_p \frac{W_p}{L_p}}{\mu_n \frac{W_n}{L_n}}} (V_{DD} - V_B + V_{Tp})$$

 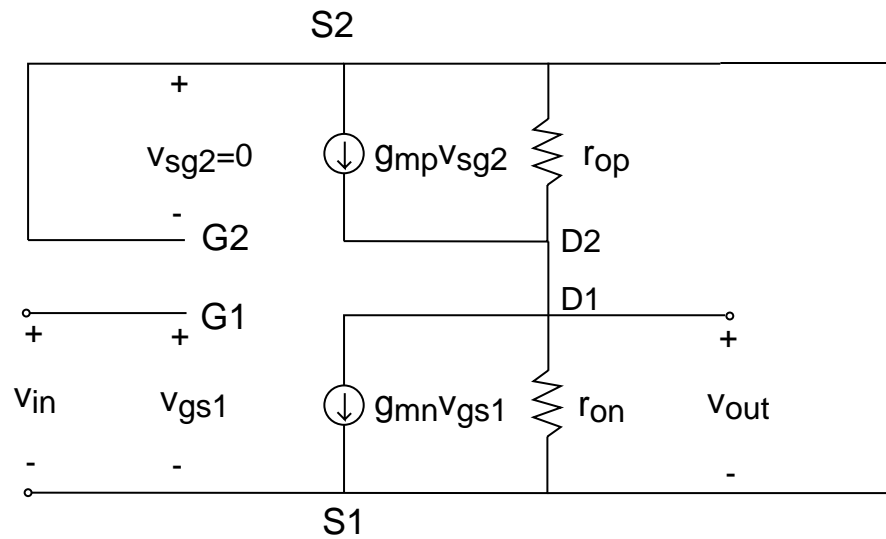
Small-signal equivalent circuit model at V_M :



$$A_v = -g_{mn}(r_{on} // r_{op})$$

NMOS inverter with current-source pull-up allows fast switching with high noise margins.

 
But... when $V_{IN} = V_{DD}$, there is a direct current path between supply and ground \Rightarrow power consumption even if inverter is idling.



Would like to have current source that is *itself* switchable, *i.e.*, it shuts off when input is high \Rightarrow CMOS!

3. Complementary MOS (CMOS) Inverter

Circuit schematic:

 

Basic operation:

- $V_{IN} = 0 \Rightarrow V_{OUT} = V_{DD}$

$$V_{GSn} = 0 < V_{Tn} \Rightarrow \text{NMOS OFF}$$

$$V_{SGp} = V_{DD} > -V_{Tp} \Rightarrow \text{PMOS ON}$$

- $V_{IN} = V_{DD} \Rightarrow V_{OUT} = 0$

$$V_{GSn} = V_{DD} > V_{Tn} \Rightarrow \text{NMOS ON}$$

$$V_{SGp} = 0 < -V_{Tp} \Rightarrow \text{PMOS OFF}$$

No power consumption while idling in any logic state.

Key conclusions

- In NMOS inverter with resistor pull-up: trade-off between noise margin and speed.
- Trade-off resolved using current-source pull-up: use PMOS as current source.
- In NMOS inverter with current-source pull-up: if $V_{IN} = HI$, power consumption even if inverter is idling.
- Complementary MOS: NMOS and PMOS switch alternatively \Rightarrow no power consumption while idling.