

Lecture 18 - The Bipolar Junction Transistor (II)

REGIMES OF OPERATION

April 19, 2001

Contents:

1. Regimes of operation.
2. Large-signal equivalent circuit model.
3. Output characteristics.


Reading assignment:

Howe and Sodini, Ch. 7, §§7.3, 7.4

Key questions


- What other regimes of operation are there for the BJT?
- What is unique about each regime?
- How do equivalent circuit models for the BJT look like?

1. Regimes of operation

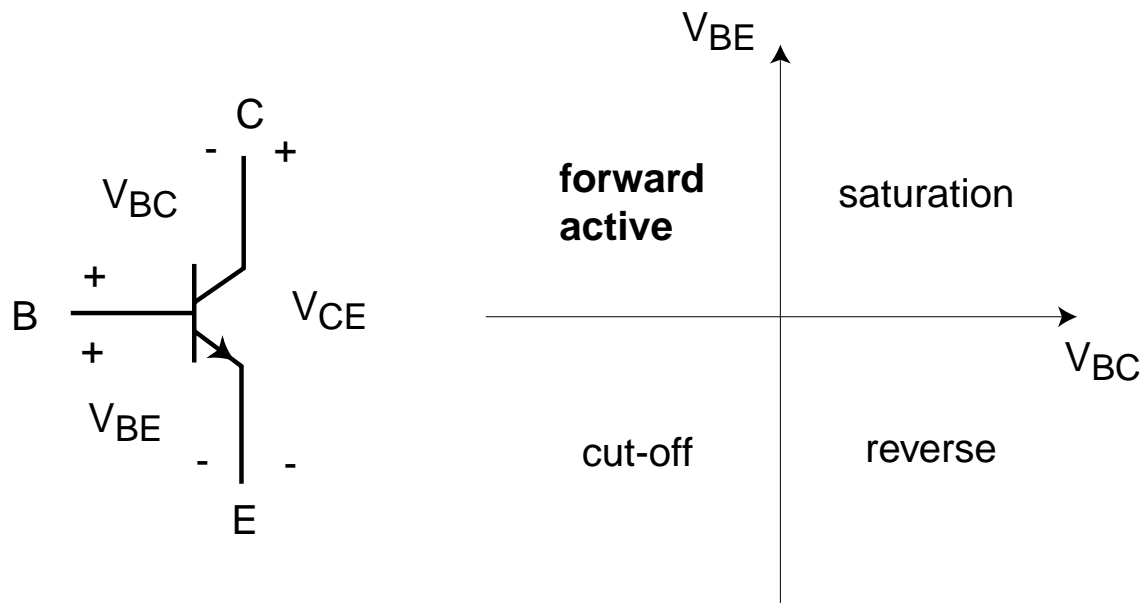


- *forward active*: device has good isolation and high gain; most useful regime;
- *saturation*: device has no isolation and is flooded with minority carriers \Rightarrow takes time to get out of saturation; avoid
- *reverse*: poor gain; not useful;
- *cut-off*: negligible current: nearly an open circuit; useful.

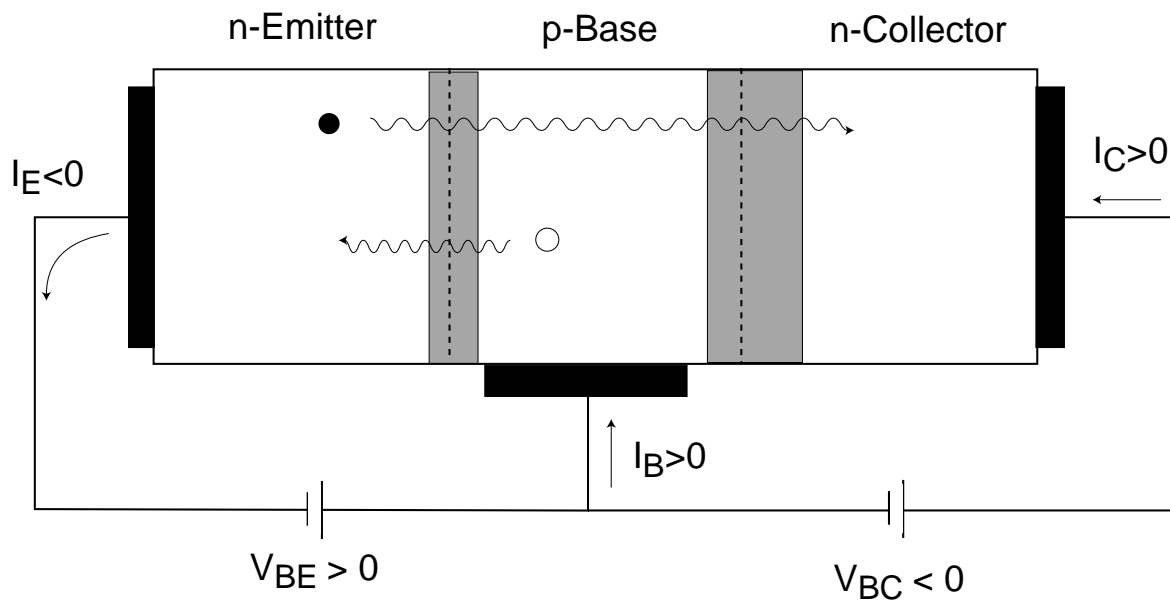□ FORWARD-ACTIVE REGIME: $V_{BE} > 0$, $V_{BC} < 0$



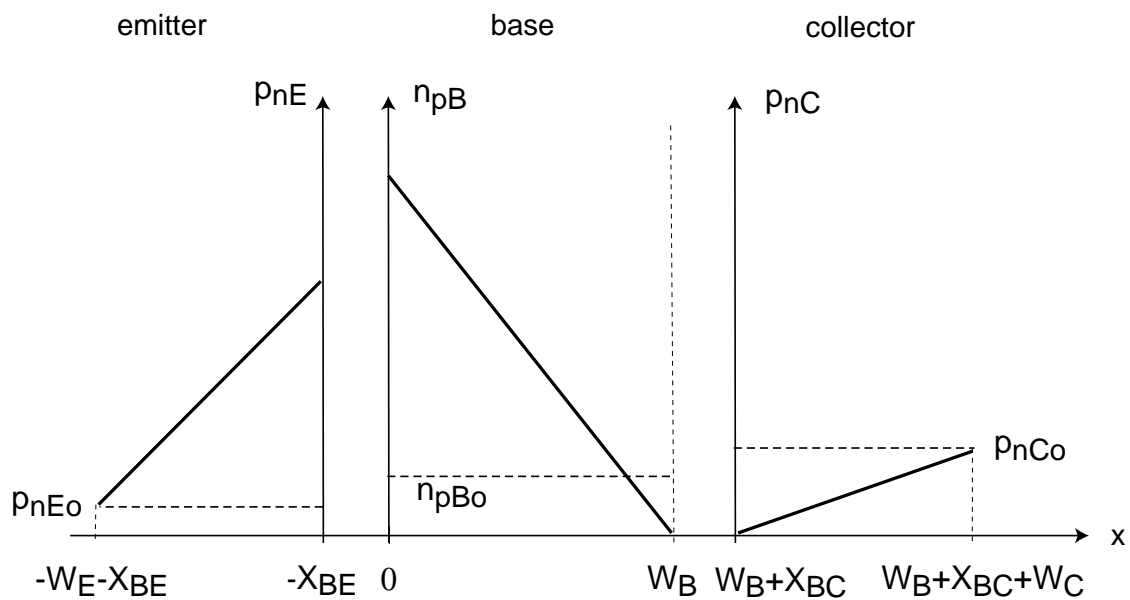Minority carrier profiles (*not to scale*):



- Emitter injects electrons into base, collector collects electrons from base:

$$I_C = I_S \exp \frac{qV_{BE}}{kT}$$

- Base injects holes into emitter, recombine at emitter contact:


$$I_B = \frac{I_S}{\beta_F} \left(\exp \frac{qV_{BE}}{kT} - 1 \right)$$

- Emitter current:


$$I_E = -I_C - I_B = -I_S \exp \frac{qV_{BE}}{kT} - \frac{I_S}{\beta_F} \left(\exp \frac{qV_{BE}}{kT} - 1 \right)$$

- State-of-the-art IC BJT's today: $I_C \sim 0.1 - 1 \text{ mA}$, $\beta_F \simeq 50 - 300$.
- β_F hard to control tightly \Rightarrow circuit design techniques required to be insensitive to variations in β_F .

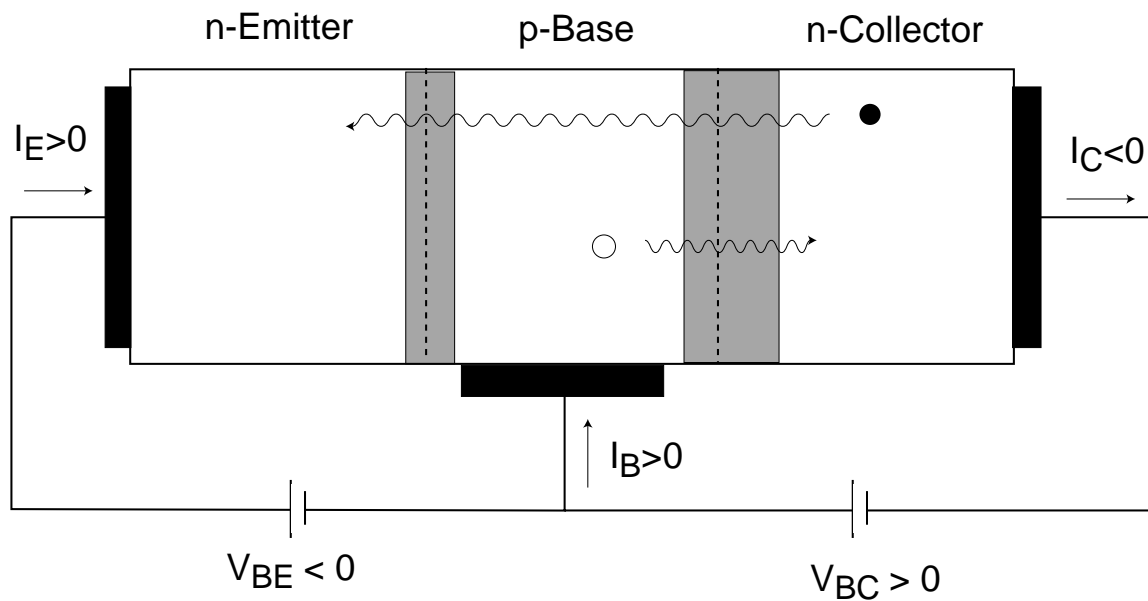□ REVERSE REGIME: $V_{BE} < 0$, $V_{BC} > 0$



Minority carrier profiles:

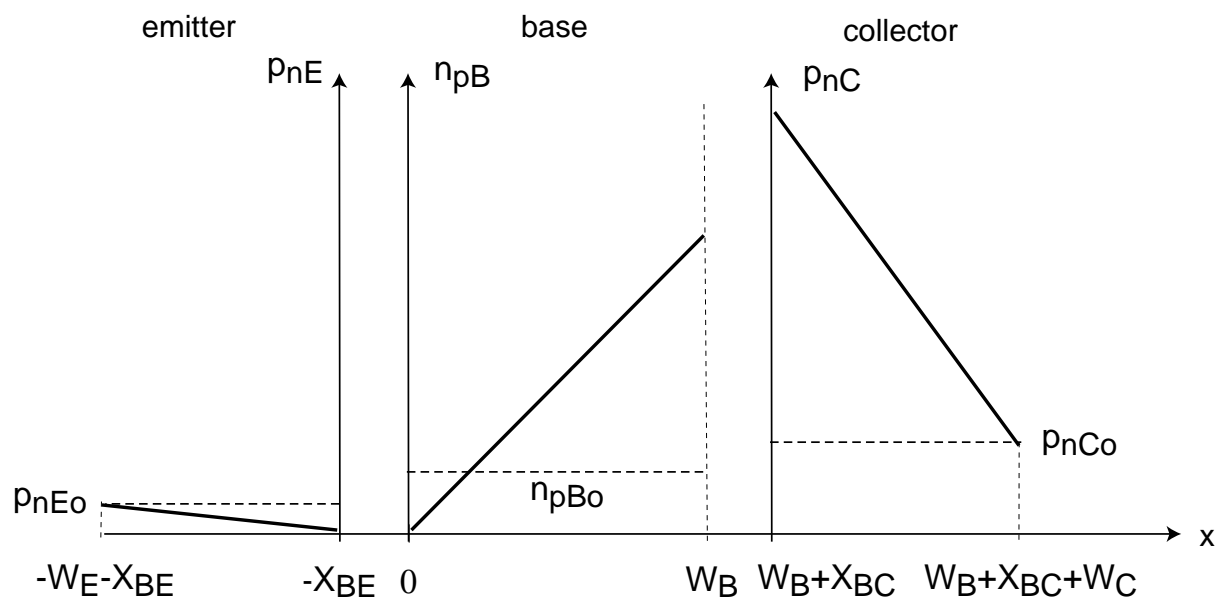

- Collector injects electrons into base, emitter collects electrons from base:

$$I_E = I_S \exp \frac{qV_{BC}}{kT}$$



- Base injects holes into collector, recombine at collector contact and buried layer:

$$I_B = \frac{I_S}{\beta_R} \left(\exp \frac{qV_{BC}}{kT} - 1 \right)$$


- Collector current:

$$I_C = -I_E - I_B = -I_S \exp \frac{qV_{BC}}{kT} - \frac{I_S}{\beta_R} \left(\exp \frac{qV_{BC}}{kT} - 1 \right)$$

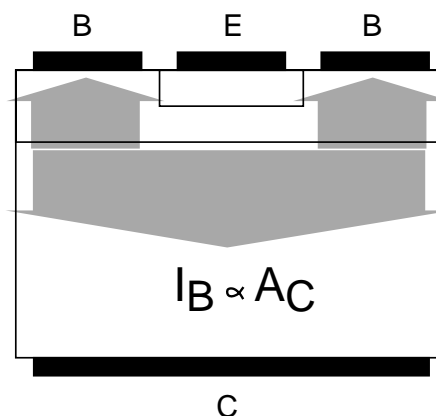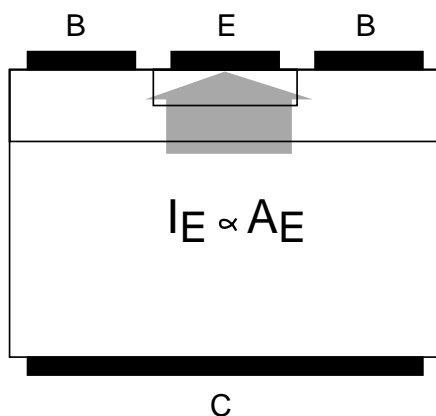
- Typically, $\beta_R \simeq 0.1 - 5 \ll \beta_F$.



□ CUT-OFF: $V_{BE} < 0$, $V_{BC} < 0$

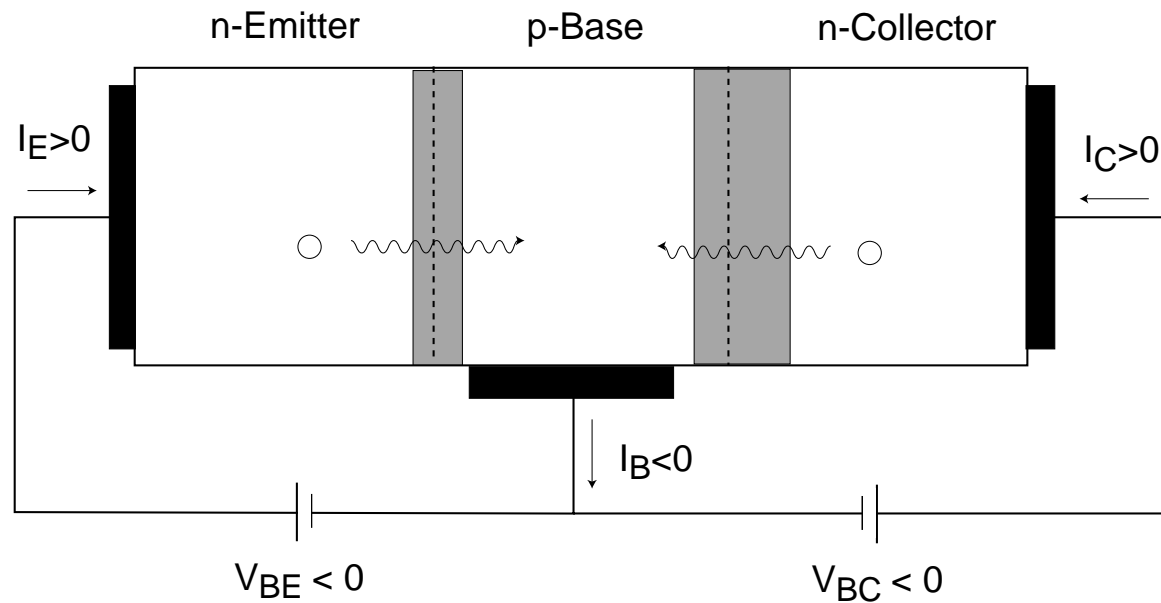

Minority carrier profiles:

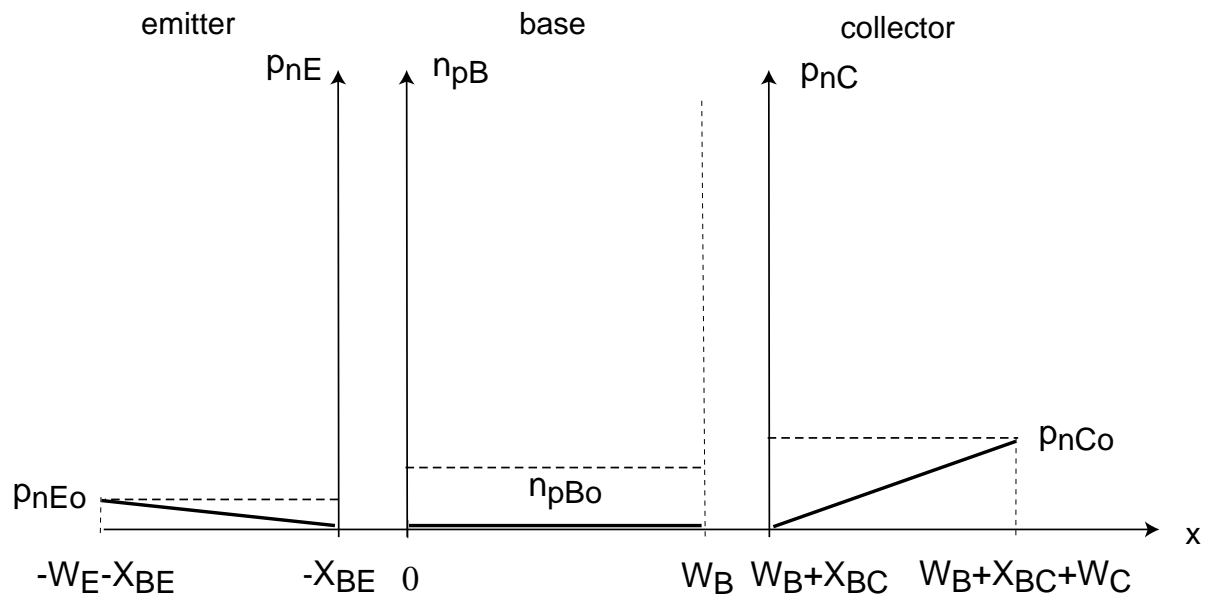

- Base extracts holes from emitter:


$$I_{B1} = -\frac{I_S}{\beta_F} = -I_E$$

- Base extracts holes from collector:


$$I_{B2} = -\frac{I_S}{\beta_R} = -I_C$$

- These are tiny leakage currents ($\sim 10^{-12}$ A).

□ SATURATION: $V_{BE} > 0$, $V_{BC} > 0$

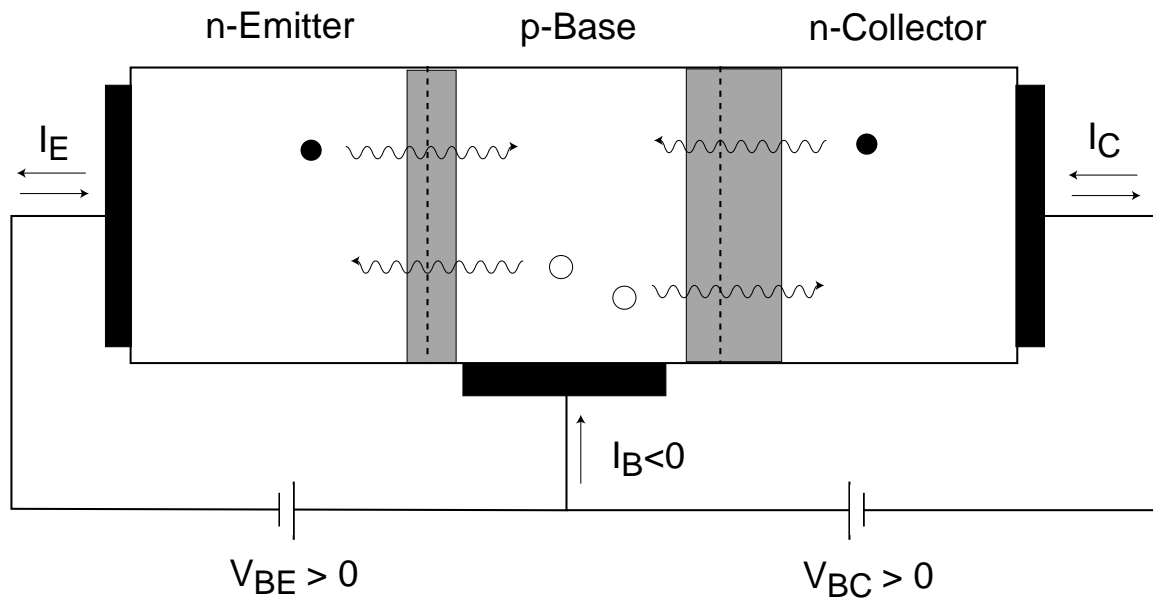

Minority carrier profiles:

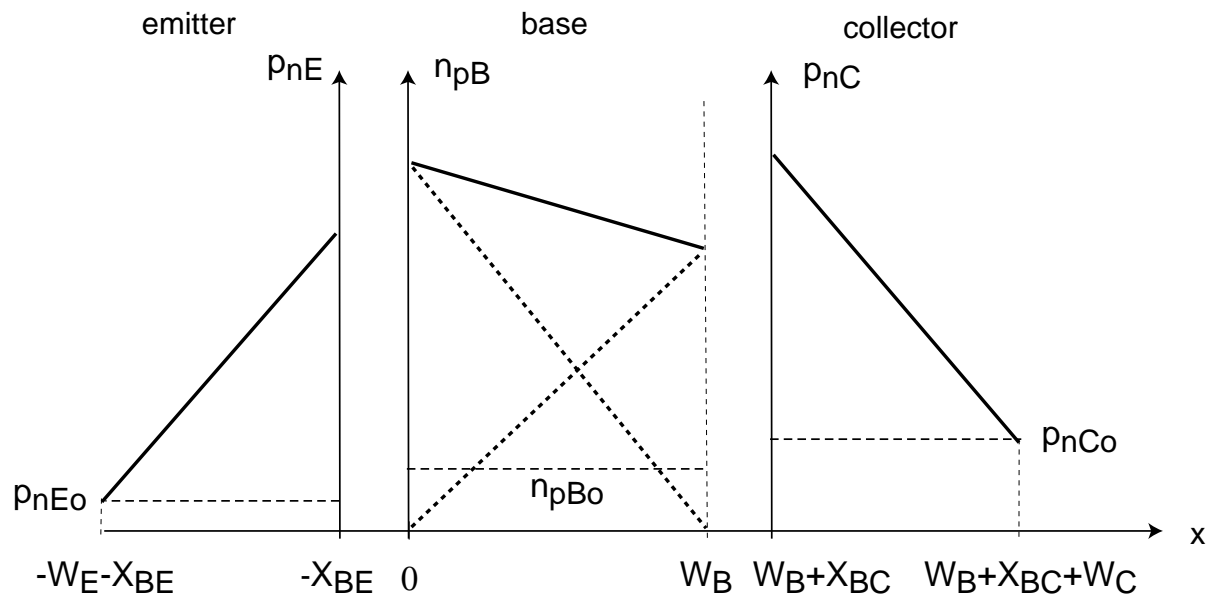


Saturation is superposition of forward active + reverse:

$$I_C = I_S \left(\exp \frac{qV_{BE}}{kT} - \exp \frac{qV_{BC}}{kT} \right) - \frac{I_S}{\beta_R} \left(\exp \frac{qV_{BC}}{kT} - 1 \right)$$

$$I_B = \frac{I_S}{\beta_F} \left(\exp \frac{qV_{BE}}{kT} - 1 \right) + \frac{I_S}{\beta_R} \left(\exp \frac{qV_{BC}}{kT} - 1 \right)$$

$$I_E = -\frac{I_S}{\beta_F} \left(\exp \frac{qV_{BE}}{kT} - 1 \right) - I_S \left(\exp \frac{qV_{BE}}{kT} - \exp \frac{qV_{BC}}{kT} \right)$$

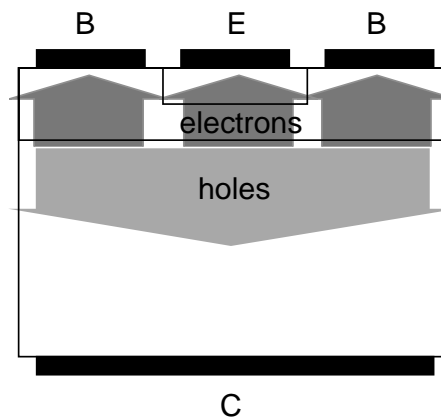- I_C and I_E can have either sign, depending on relative magnitude of V_{BE} and V_{BC} , and β_F and β_R .
- In saturation, collector and base flooded with excess minority carriers \Rightarrow takes lots of time to get transistor out of saturation.



2. Large-signal equivalent circuit model

System of equations that describes BJT operation:


$$I_C = I_S \left(\exp \frac{qV_{BE}}{kT} - \exp \frac{qV_{BC}}{kT} \right) - \frac{I_S}{\beta_R} \left(\exp \frac{qV_{BC}}{kT} - 1 \right)$$

$$I_B = \frac{I_S}{\beta_F} \left(\exp \frac{qV_{BE}}{kT} - 1 \right) + \frac{I_S}{\beta_R} \left(\exp \frac{qV_{BC}}{kT} - 1 \right)$$

$$I_E = -\frac{I_S}{\beta_F} \left(\exp \frac{qV_{BE}}{kT} - 1 \right) - I_S \left(\exp \frac{qV_{BE}}{kT} - \exp \frac{qV_{BC}}{kT} \right)$$

Equivalent-circuit model representation:

Non-Linear Hybrid- π Model

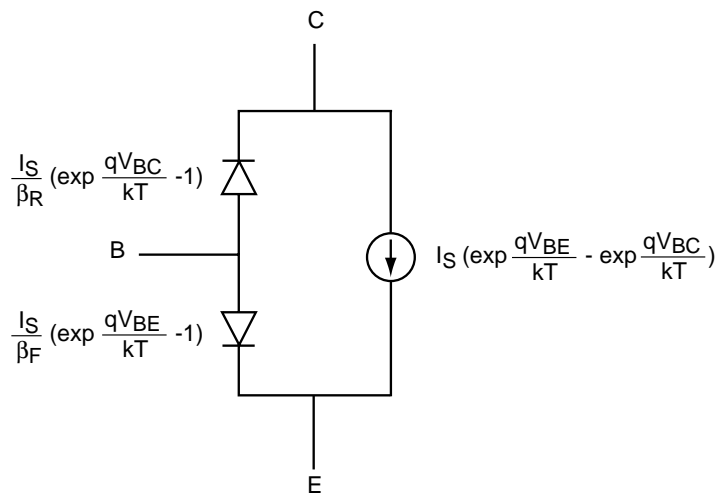


Three parameters in this model: I_S , β_F , and β_R .

Model equivalent to Ebers-Moll model in text.

Simplifications of equivalent-circuit model:

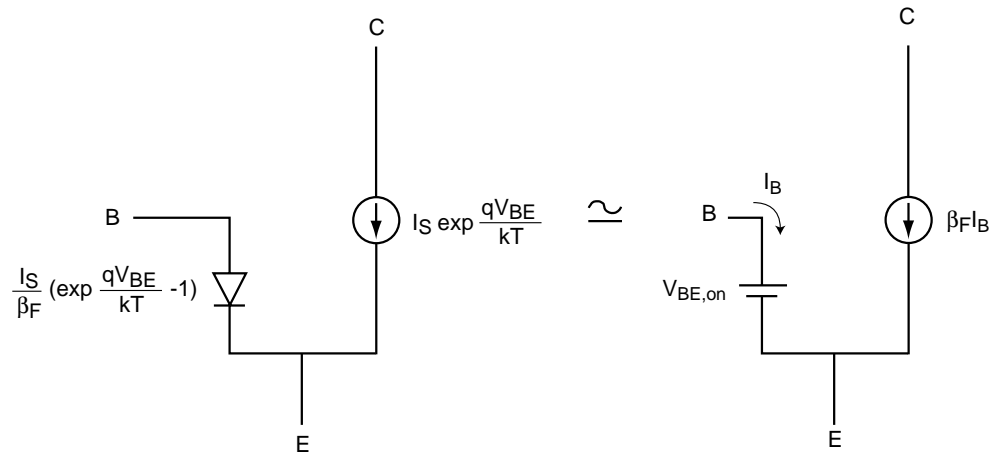
- Forward-active regime: $V_{BE} > 0$, $V_{BC} < 0$



For today's technology: $V_{BE,on} \simeq 0.7 \text{ V}$.

I_B depends on outside circuit.


- Reverse: $V_{BE} < 0$, $V_{BC} > 0$

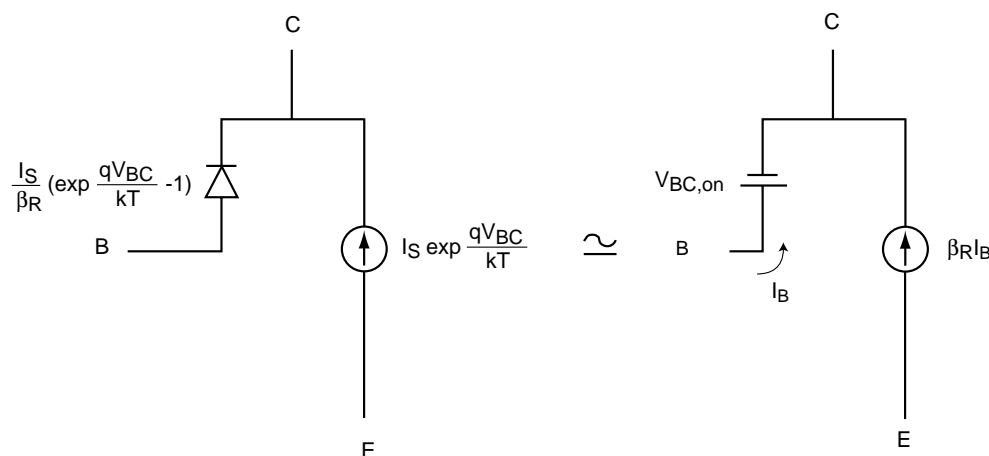


For today's technology: $V_{BC,on} \simeq 0.5 \text{ V}$.

I_B also depends on outside circuit.

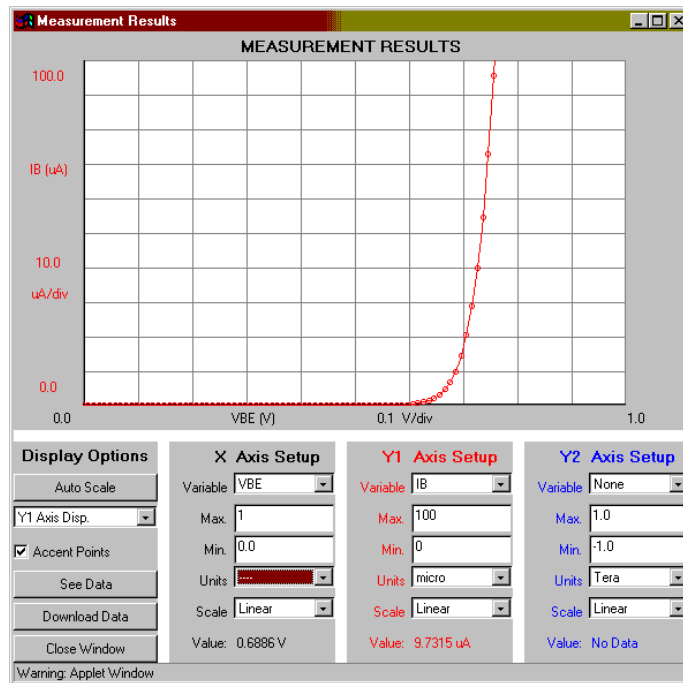
I_B vs. V_{BE} for $V_{CE} = 2.5\text{ V}$:



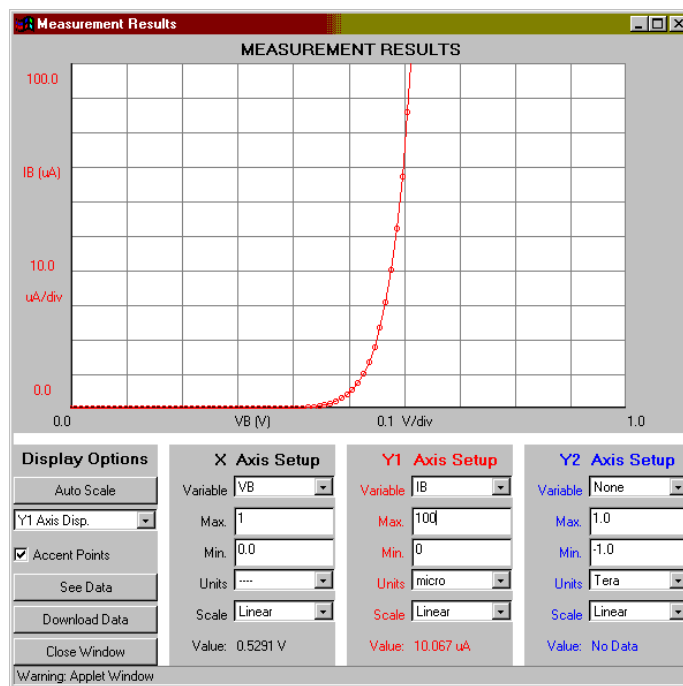I_B vs. V_{BC} for $V_{EC} = 2.5\text{ V}$:




- Saturation: $V_{BE} > 0$, $V_{BC} > 0$

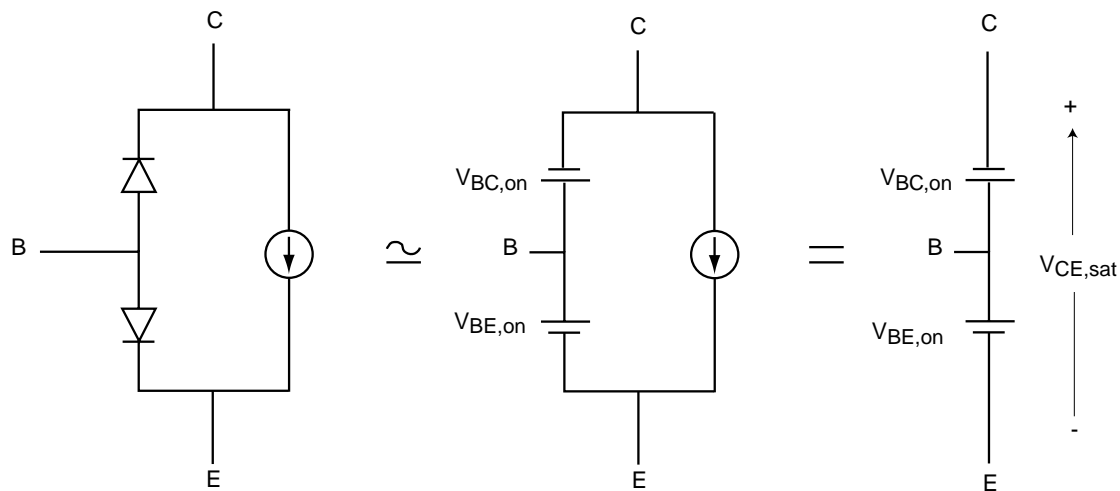

Today's technology: $V_{CE,sat} = V_{BE,on} - V_{BC,on} \simeq 0.2 \text{ V}$.
 I_B and I_C depend on outside circuit.


- Cut-off: $V_{BE} < 0$, $V_{BC} < 0$

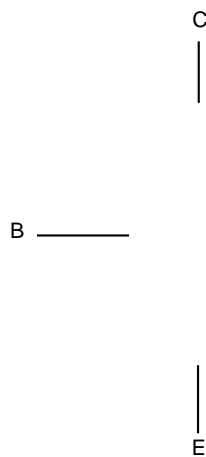


Only negligible leakage currents.

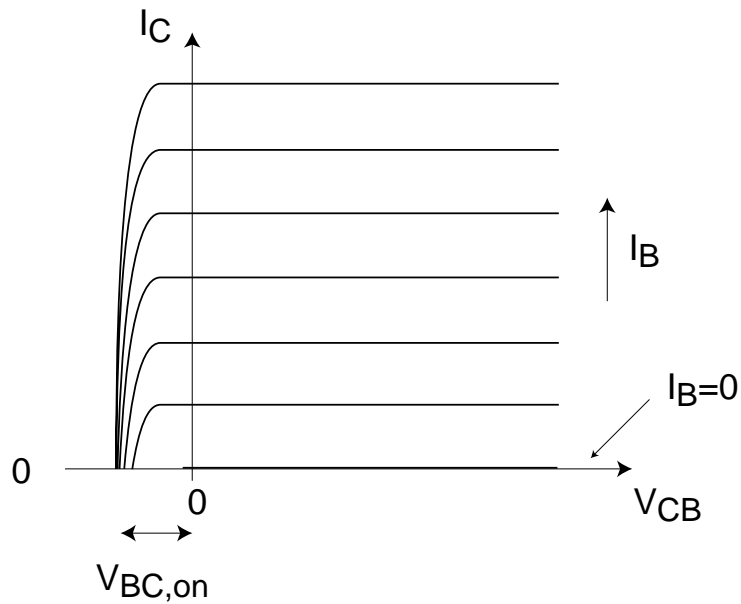3. Output characteristics


First, *common-base output characteristics*:



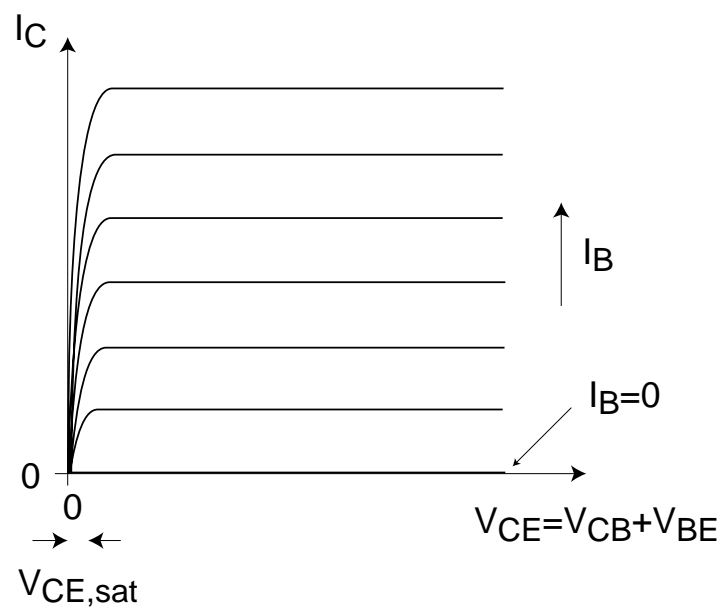
Next, *common-emitter output characteristics*:



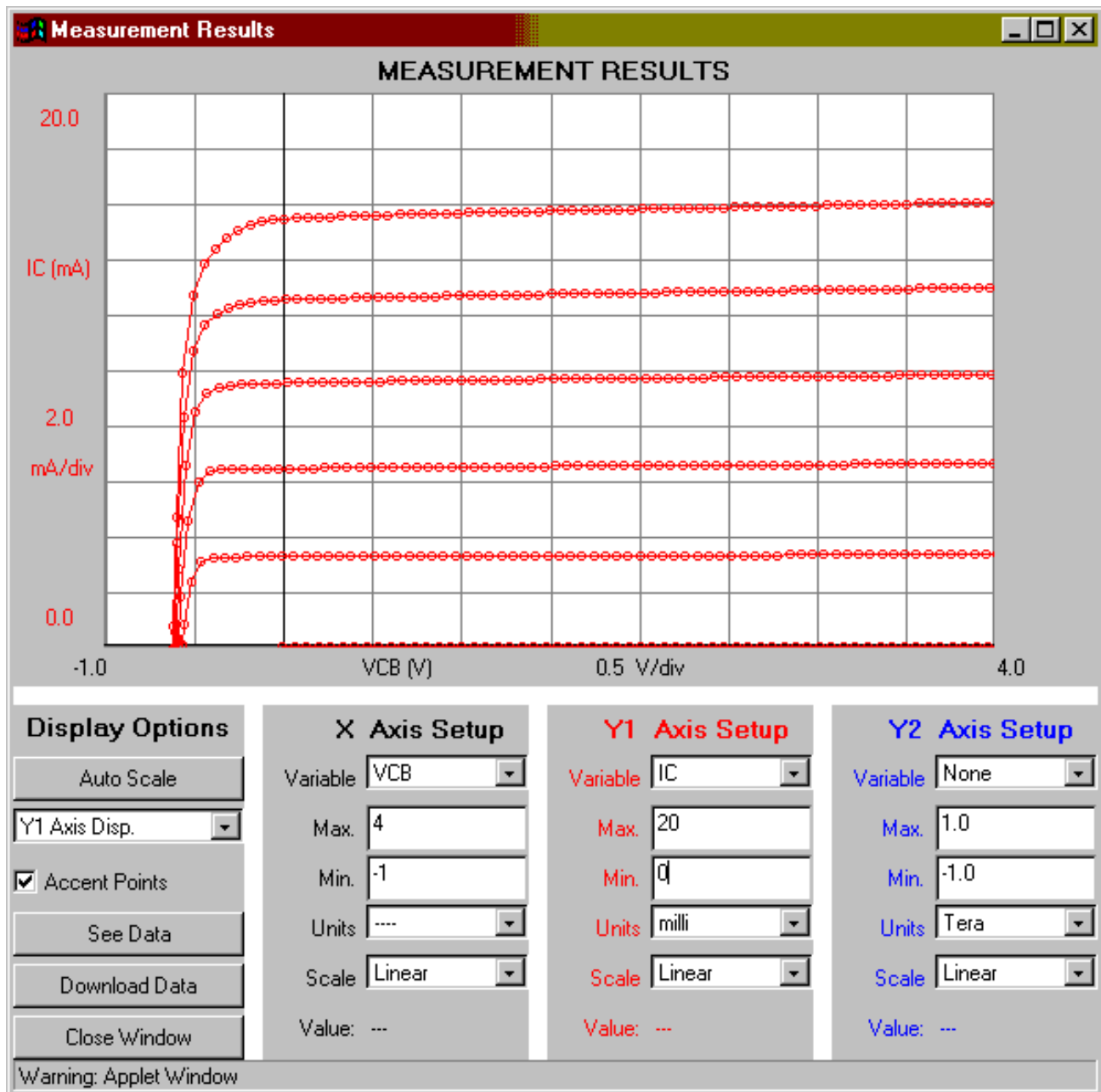
I_C vs. V_{CB} for $0 \leq I_B \leq 100 \mu A$:



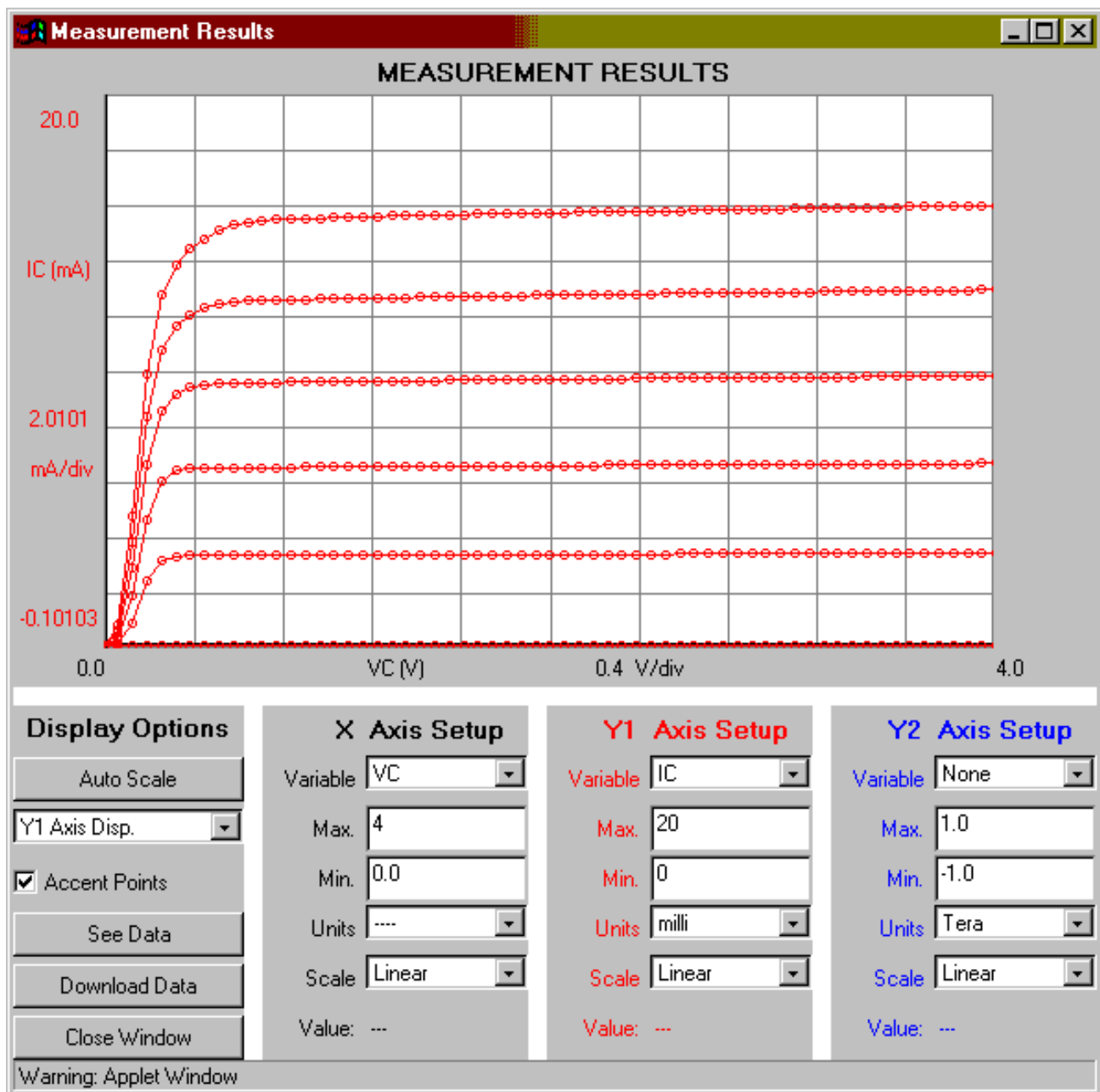I_C vs. V_{CE} for $0 \leq I_B \leq 100 \mu A$:




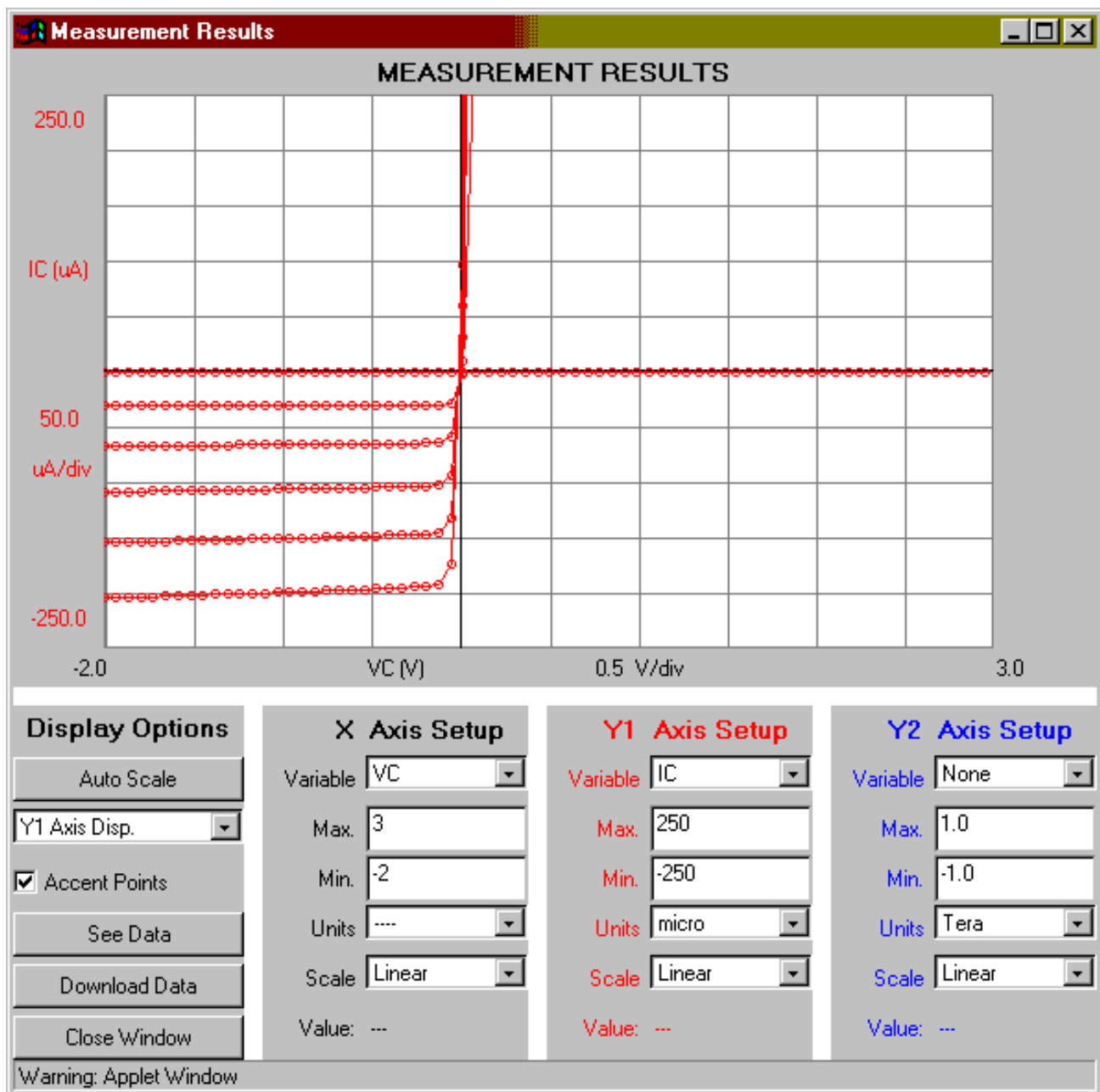I_C vs. V_{CE} for $0 \leq I_B \leq 100 \mu A$:




Key conclusions

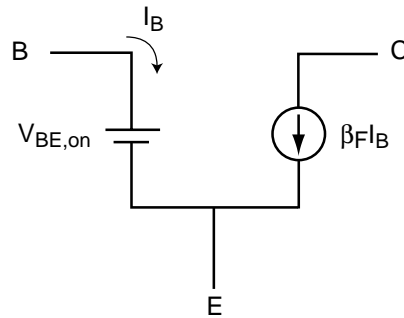- Forward-active regime: most useful, device has gain and isolation. For bias calculations:



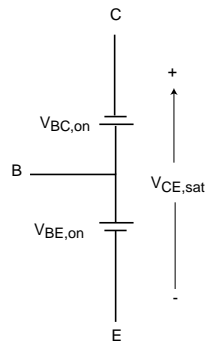- Saturation: device flooded with minority carriers. Not useful. For bias calculations:



- Cut-off: device open. Useful. For bias calculations:

