

# **Lecture 26 - Differential Amplifiers (II)**

**and**

## **6.012 Wrap-up**

May 17, 2001

### **Contents:**

1. Large-signal differential response of differential amplifier
2. Wrap-up of 6.012

### **Reading assignment:**

Howe and Sodini, Ch. 11, §§11.6


### **Announcement:**

Final exam: May 24, 9 AM-12 noon, Walker; open book, calculator required; entire subject under examination but emphasis on lectures #18-26.

## Key questions

- Is it possible to use the differential amplifier concept to do logic?
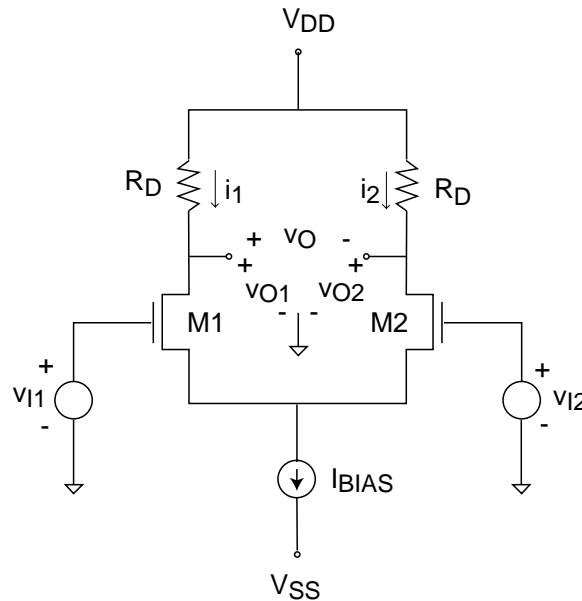
# 1. Large-signal differential response of differential amplifier



Examine large-signal transfer function:


- if  $v_{I1} = v_{I2} \Rightarrow v_{O1} = v_{O2} \Rightarrow v_O = 0$
- if  $v_{I1} > v_{I2} \Rightarrow$  M1 more *ON* than M2  $\Rightarrow i_1 > i_2 \Rightarrow v_{O1} < v_{O2} \Rightarrow v_O < 0$
- if  $v_{I1} \gg v_{I2} \Rightarrow$  M1 strongly *ON*, M2 goes *OFF*  $\Rightarrow i_1 \simeq I_{BIAS}, i_2 \simeq 0 \Rightarrow$

$$v_{O1} = v_{O1,min} = V_{DD} - I_{BIAS}R_D, \quad v_{O2} = v_{O1,max} = V_{DD}$$

$$v_{OD,min} = -I_{BIAS}R_D$$

- symmetric behavior for  $v_{I1} < v_{I2}$  and  $v_{I1} \ll v_{I2}$

 Saturating behavior for large differential input signals:



$v_{ID}$  that leads to amplifier saturation ( $v_{I1} \gg v_{I2}$ ):

$$v_{ID,sat} = v_{GS1} - v_{GS2}$$


With:

$$v_{GS1} = V_T + \sqrt{\frac{I_{BIAS}}{\frac{W}{2L}\mu C_{ox}}}$$

$$v_{GS2} = V_T$$

Then:
 
$$v_{ID,sat} = \sqrt{\frac{I_{BIAS}}{\frac{W}{2L}\mu C_{ox}}}$$




- For small  $v_{ID}$ ,  $v_O$  is *linear* in  $v_I \Rightarrow$  differential amplifier
- For large  $v_{ID}$ ,  $v_O$  *saturates*: once  $v_{ID}$  is large enough,  $v_O$  independent of  $v_{ID} \Rightarrow$  logic inverter!


Can do logic with this:

- Logic 0  $\leq -V_{ID,sat}$ , logic 1  $\geq V_{ID,sat}$
- regenerative if  $V_O(\text{swing}) > V_{ID,sat}$
- not used with MOSFETs
- but, used with Si BJT's: *Emitter-Coupled Logic* (ECL)
- and GaAs FETs: *Source-Coupled FET Logic* (SCFL).

□ Common-emitter differential pair:

 

Large-signal characteristics:

 

Differential input voltage to saturate amplifier:

$$v_{ID,sat} = v_{BE1} - v_{BE2} = \frac{kT}{q} \ln \frac{i_{C1}}{I_{S1}} - \frac{kT}{q} \ln \frac{i_{C2}}{I_{S2}}$$

If transistors are well matched:  $I_{S1} = I_{S2}$ , and:

$$v_{ID,sat} = \frac{kT}{q} \ln \frac{i_{C1}}{i_{C2}}$$

If we consider amplifier saturated when  $i_{C1} \simeq 100 i_{C2}$ , then:

$$v_{ID,sat} \simeq 120 \text{ mV}$$

For MOSFET,  $v_{ID,sat} \simeq 0.5 - 1 \text{ V}$ .

Since  $g_m$  of BJT is high and  $v_{ID,sat}$  is small, ECL is very fast logic!

At any one moment in time  $\tau_P(ECL) < \tau_P(CMOS)$ .  
But two trade-offs:

- power dissipation penalty:  $P_{dis}(ECL) \gg P_{dis}(CMOS)$   
(there is large DC power consumption in ECL),
- area and density penalty: BJT size  $\gg$  MOSFET size.

## 2. Wrap up of 6.012

### □ *The amazing properties of Si*

- two types of carriers: electrons and holes [although can make good electronic devices with just one, *i.e.* MESFET; but can't do CMOS without two]
- carrier concentrations can be controlled over many orders of magnitude and in short length scales by addition of dopants
- carrier concentrations can be controlled electrostatically
- carriers are fast:

– electrons can cross  $L = 0.1 \mu m$  in about:

$$\tau = \frac{L}{v_e} = \frac{0.1 \mu m}{10^7 cm/s} = 1 ps$$

– high current density:

$$\begin{aligned} J_e &= qnv_e = 1.6 \times 10^{-19} C \times 10^{17} cm^{-3} \times 10^7 cm/s \\ &= 1.6 \times 10^5 A/cm^2 \end{aligned}$$

$\Rightarrow$  high current drivability to capacitance ratio

- extraordinary physical and chemical properties



□ *The amazing properties of Si MOSFET*

- ideal properties of Si/SiO<sub>2</sub> interface: can drive surface all the way from accumulation to inversion [not possible in GaAs, for example]
- performance improves as MOSFET scales down in size; as  $L, W \downarrow$ :

– current:

$$I_D = \frac{W}{2L} \mu C_{ox} (V_{GS} - V_T)^2 \text{ unchanged}$$

– capacitance:

$$C_{gs} = WLC_{ox} \downarrow\downarrow$$

– figure of merit for device switching delay:

$$\frac{C_{gs}V_{DD}}{I_D} = L^2 \frac{2V_{DD}}{\mu(V_{GS} - V_T)^2} \downarrow\downarrow$$

- No gate current.
- $V_T$  can be engineered.
- MOSFETs come in two types: NMOS and PMOS.
- Easy to integrate.

□ *The amazing properties of Si CMOS*

- Rail-to-rail logic: logic levels are 0 and  $V_{DD}$ .
- No power consumption while idling in any logic state.
- Scales well.

As  $L, W \downarrow$ :

- Power consumption (all dynamic):

$$P_{diss} = fC_L V_{DD}^2 \propto fWL C_{ox} V_{DD}^2 \downarrow\downarrow$$

- Propagation delay:

$$t_P \propto \frac{C_L V_{DD}}{\frac{W}{L} \mu C_{ox} (V_{DD} - V_T)^2} \downarrow\downarrow$$

- Logic density:

$$Density \propto \frac{1}{A} = \frac{1}{WL} \uparrow\uparrow$$

□ All this is enabling the *electronics revolution*:

- *exponential growth* in complexity and functionality of integrated circuits [Moore's Law]
- *exponential decrease* in power per function and cost per function of integrated circuits
- profound penetration of IC technology into all aspects of human society


# □ Circuit design lessons from 6.012:

## 1. Importance of optimum level of abstraction:


- device physics equations, *i.e.*:

$$I_D = \frac{W}{2L} \mu C_{ox} (V_{GS} - V_T)^2, \text{ etc.}$$

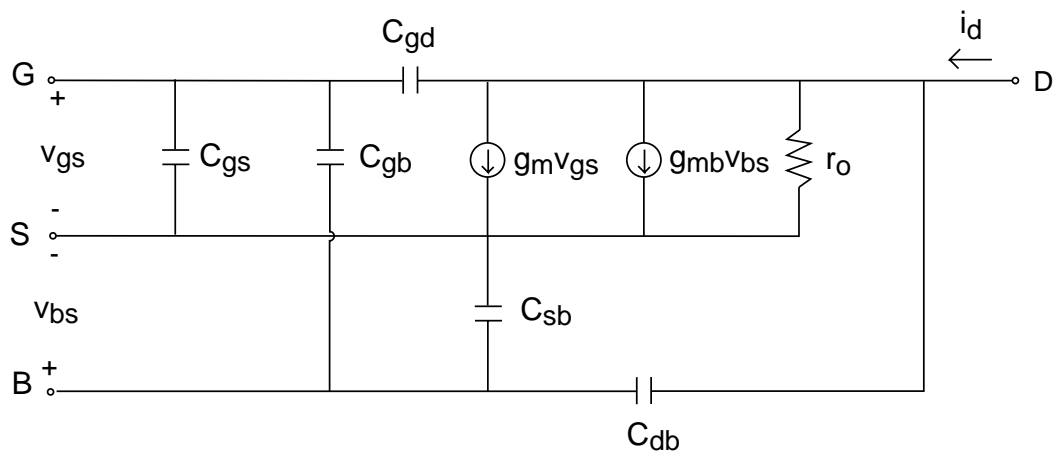- device equivalent circuit models, *i.e.*:



- device SPICE models, *i.e.*:

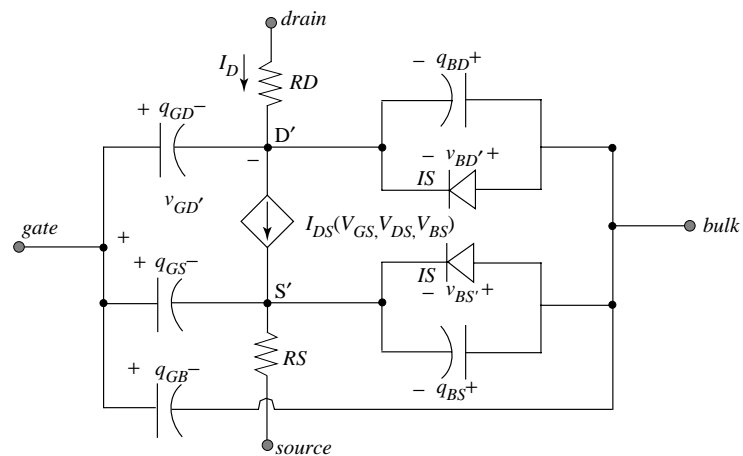

## 2. Many considerations in circuit design:

- multiple performance specs:
  - in analog systems: gain, bandwidth, power consumption, swing, noise, etc.
  - in digital systems: propagation delay, power, ease of logic synthesis, noise, etc.
- need to be immune to temperature variations and device parameter variations (*i.e.*: differential amplifier)
- must choose suitable technology: CMOS, BJT, CBJT, BiCMOS, etc.
- must avoid costly components (*i.e.*: resistors, capacitors)

## 3. Trade-offs:

- gain-bandwidth trade-off in amplifiers (*i.e.*: Miller effect)
- performance-power trade-off (*i.e.*: delay in logic circuits, gain in amplifiers)
- performance-cost trade-off (cost=design complexity, Si area, more aggressive technology)
- accuracy-complexity trade-off in modeling

□ Exciting times ahead in Si IC technology:

- *analog electronics* (since  $\sim 50's$ ): amplifiers, mixers, oscillators, DAC, ADC, etc.
- *digital electronics* (since  $\sim 60's$ ): computers, micro-controllers, random logic, DSP
- *solid-state memory* (since  $\sim 60's$ ): dynamic random-access memory, non-volatile RAM
- *energy conversion* (since  $\sim 70's$ ): solar cells, photodetectors
- *power control* (since  $\sim 70's$ ): "smart" power
- *communications* (since  $\sim 80's$ ): VHF, UHF, RF front ends, modems, fiber-optic systems
- *sensing, imaging* (since  $\sim 80's$ ): CCD cameras, CMOS cameras, many kinds of sensors
- *micro-electro-mechanical systems* (since  $\sim 90's$ ): accelerometers, movable mirror displays
- *biochip* (from  $\sim 2000$ ): DNA sequencing,  $\mu$ fluidics
- *vacuum microelectronics* (from  $\sim 2000?$ ): field-emitter displays
- ???????? (microreactors, microturbines, etc.)

□ Exciting times ahead in circuit design too:

- Numbers of transistors available outstrips ability to design by 3 to 1!
- Operational frequency of logic, analog, and communications circuits increasing very fast.
- Operational voltage shrinking quickly.
- New device technologies: GaAs HEMT, InP HBT, etc.

## More subjects in microelectronics at MIT

- *6.152J - Microelectronics Processing Technology.* Theory and practice of IC technology. Carried out in clean rooms of Microsystems Technology Laboratories. Fulfills Institute or EECS Lab requirement. Fall and Spring.
- *6.301 - Solid-State Circuits.* Analog circuit design. Design project. Spring.
- *6.334 - Power Electronics.* Power electronics devices and circuits. Spring. H-level.
- *6.374 - Analysis and Design of Digital Integrated Circuits.* Digital circuit design. Design projects. Fall. H-level.
- *6.720J - Integrated Microelectronic Devices.* Microelectronic device physics and design. Emphasis on MOSFET. Design project. Fall. H-level.