

PSET 9 solutions

P9.7 (a) $V_{out} = 0 \Rightarrow V_A = 0.7V$

$V_{BIAS} - V_A = V_{GS}$


$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$ & ignoring λ_n

$150\mu A = \frac{100\mu A}{2} \cdot \frac{20}{5} (V_{GS} - V_{TH})^2 \Rightarrow V_{GS} - V_{TH} = 0.866 \quad \therefore V_{GS} = 1.566V$

$\therefore V_{BIAS} = V_{GS} + V_A = 1.566 + 0.7 = \underline{2.266(V)}$

(b) $V_A = 0.7V$

(c)

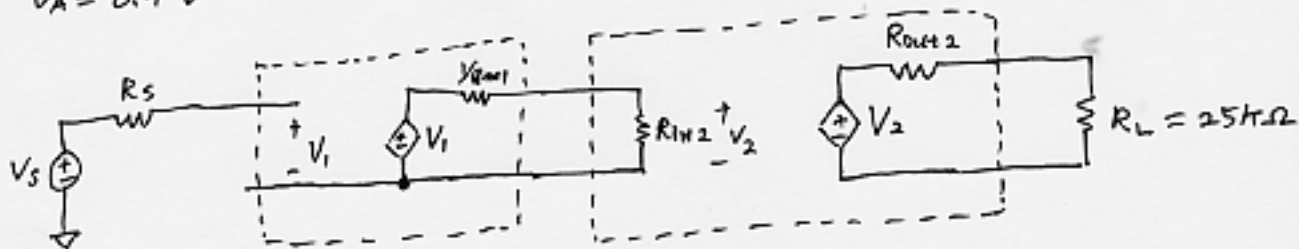

$g_{m1} = \sqrt{2 \cdot \mu_n C_{ox} \frac{W}{L} \cdot I_D} = 346.4 \mu A/V \quad \therefore \frac{1}{g_{m1}} = \underline{2.8868 k\Omega}$

$R_{in2} = r_{\pi 2} + \beta_0 (r_{o2} \parallel V_{oc} \parallel R_L)$

$g_{m2} = \frac{I_C}{V_{TH}} = \frac{150\mu A}{25mV} = 6 \mu A/V, \quad r_{\pi 2} = \frac{\beta_0}{g_{m2}} = 12.5 k\Omega$

$V_{oc} = \frac{V_A}{I_C} = \frac{50}{150\mu A} = 333.3 k\Omega$

$\therefore R_{in2} = 12.5 k\Omega + 75 \times (333.3 k\Omega \parallel 500 k\Omega \parallel 25 k\Omega) = \underline{1.679 M\Omega}$

$R_{out2} = \frac{1}{g_{m2}} + \frac{1}{g_{m1}} \cdot \frac{1}{\beta_0} = \underline{205.16 \Omega}$

(d) $\frac{V_{out}}{V_s} = \frac{1.679 M\Omega}{1.679 M\Omega + 2.8868 k\Omega} \cdot \frac{25 k\Omega}{25 k\Omega + 205.16 \Omega} \approx 0.99$

P9.8 (a) $V_{GS} = V_A - V_{out} = V_A \quad \therefore V_{out} = 0$

$\frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 = 150\mu A \Rightarrow V_{GS} - V_{TH} = 0.866$


$V_A = 0.866 + V_{TH} = 1.566V$

$V_{BIAS} - V_A = V_{BE}$

$\therefore V_{BIAS} = 0.7 + 1.566 = 2.266(V)$

P9.8 (b) $V_A = 1.566 \text{ (V)}$


(c)

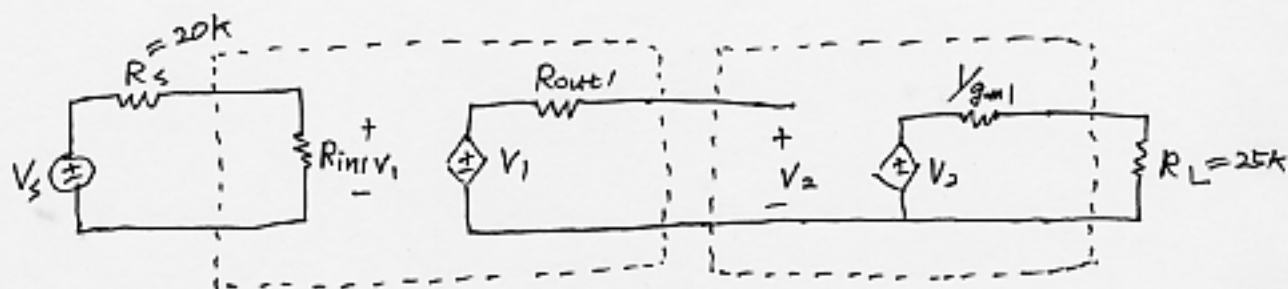

$R_{in1} = 1.679 \text{ M}\Omega$ $R_{out1} = 205.16 \Omega$ $\frac{1}{g_{m1}} = 2.8868 \text{ k}\Omega$
 ↳ from P9.7

(d) $\frac{V_{out}}{V_s} = \frac{1.679 \text{ M}\Omega}{1.679 \text{ M}\Omega + 20 \text{ k}\Omega} \cdot \frac{25 \text{ k}\Omega}{2.8868 \text{ k}\Omega + 25 \text{ k}\Omega} = 0.886$

P9.9 (a)

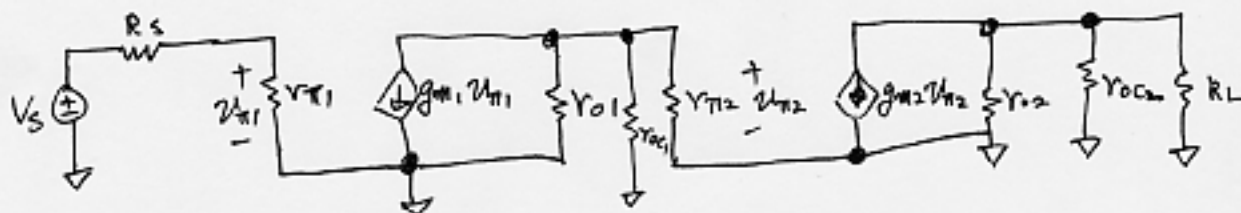

$g_{m1} = \frac{100 \text{ }\mu\text{A}}{25 \text{ mV}} = 4 \text{ mA/V}$

$g_{m2} = \frac{250 \text{ }\mu\text{A}}{25 \text{ mV}} = 10 \text{ mA/V}$

$r_{\pi1} = 25 \text{ k}\Omega$

$r_{\pi2} = 10 \text{ k}\Omega$

$r_{o1} = 200 \text{ k}\Omega$

$r_{o2} = 80 \text{ k}\Omega$

(b) $R_{in} = r_{\pi1} = 25 \text{ k}\Omega$

(c) $R_{out} = r_{o2} \parallel r_{oc} = 80 \text{ k}\Omega \parallel 250 \text{ k}\Omega = 60.61 \text{ k}\Omega$

(d) $A_{v, \text{intrinsic}} = g_{m1} (r_{o1} \parallel r_{oc1} \parallel r_{\pi2}) \cdot g_{m2} (r_{o2} \parallel r_{oc2})$
 $= 4 \text{ mA/V} (9.434 \text{ k}\Omega) \cdot 10 \text{ mA/V} \cdot (60.61 \text{ k}\Omega)$
 $= 22.87 \times 10^3$

(e) $A_v = \left(\frac{r_{\pi1}}{R_s + r_{\pi1}} \right) g_{m1} (r_{o1} \parallel r_{oc1} \parallel r_{\pi2}) g_{m2} \cdot (r_{oc2} \parallel r_{oc2} \parallel R_L)$
 $= 0.5 \times 4 \text{ mA/V} \times 9.434 \text{ k}\Omega \times 10 \text{ mA/V} \times 8.854 \text{ k}\Omega$
 $= 1.67 \times 10^3$

P 9.14

(a) $R_S \approx g_{m1} \cdot r_{o1} \cdot r_{o2}$

$$g_{m1} = \sqrt{2 \mu_p C_{ox} \frac{W}{L} \cdot I_D} = \sqrt{2 \times 20 \mu \times 10 \times 100 \mu} = 400 \mu A/V$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_p \cdot I_D} = \frac{1}{0.03 \times 100 \mu} = 333.3 \text{ k}\Omega$$

$\therefore R_S \approx 44.4 \text{ M}\Omega$

(b) $\frac{W}{L}$ for $M_{2B} = 10$ & doesn't change

$$\frac{W}{L} \text{ for } M_2 = 10/5 = 2$$

(c) $g_{m1} = \sqrt{2 \times 20 \mu \times 10 \times 20 \mu} = 178.29 \mu A$

$$r_{o1} = r_{o2} = \frac{1}{0.03 \times 20 \mu} = 1.667 \text{ M}\Omega$$

$\therefore R_S \approx 497.1 \text{ M}\Omega$

P 9.17 Ignore the channel length modulation for the bias point calculation.

(a) $I_D = \frac{\mu_p C_{ox}}{2} \frac{W}{L} (V_{SG} + V_{TP})^2$

$$V_D = V_G = I_D \times 6 \text{ k}\Omega - 3 \text{ V} = 0 \text{ V}$$

$\therefore V_{SG} = 3 \text{ V}$

$$500 \mu A = \frac{25 \mu}{2} \times \frac{W}{L} \times (3 - 0.7)^2$$

$\therefore \frac{W}{L} = 7.56$

(b) $I_{D3} = \frac{25 \mu}{2} \times \frac{100}{2} \times (V_{SG} - 0.7)^2 = 500 \mu A$

$\therefore (V_{SG} - 0.7)^2 = 0.8$


$V_{SG} = 1.6$, $V_S = 0 \text{ V}$ $\therefore V_G = -1.6 \text{ (V)}$

(c) $500 \mu A = \frac{50 \mu}{2} \times \frac{40}{2} \times (V_{GS} - V_{TM})^2$

$V_{GS} - V_{TM} = 1$ $\therefore V_{GS} = 1 + 0.7 = 1.7 \text{ V}$

$V_G = 1.7 - 3 = -1.3 \text{ (V)} = V_{BIAS}$

P 9.17 (d)

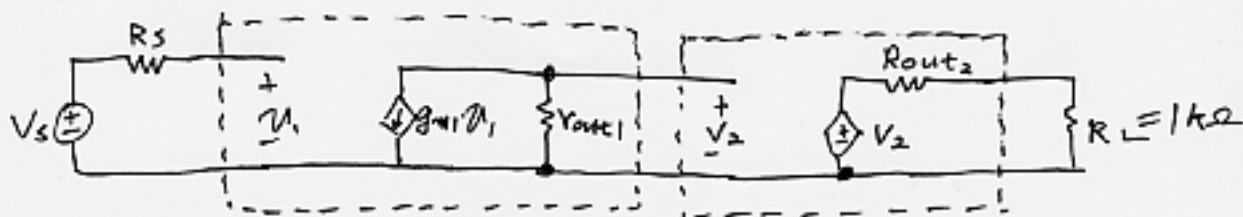

$$g_{m1} = \sqrt{2 \cdot \mu_n C_{ox} \frac{W}{L} \cdot I_D} = \sqrt{2 \times 50 \mu\text{A} \times \frac{40}{2} \times 50 \mu\text{A}} = 1 \text{ mA/V}$$

$$R_{out1} = r_{o1} \parallel r_{o2} = \frac{1}{\lambda_n I_D + \lambda_p I_D} = 33.3 \text{ k}\Omega$$

$$R_{out2} = \frac{1}{g_{m3}} = \frac{1}{\sqrt{2 \cdot \mu_p C_{ox} \frac{W}{L} \cdot I_D}} = 632.46 \Omega$$

(e)

$$A_v = -g_{m1} \cdot R_{out1} \cdot \frac{R_L}{R_L + R_{out2}}$$

$$= -1 \text{ mA/V} \times 33.3 \text{ k}\Omega \times \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 632.46 \Omega}$$

$$= -20.4$$

(f) $R_{out2, \text{new}}$ should be $\frac{1}{2} \times R_{out, \text{original}}$.

∴ g_{m3} must be twice.

∴ $\frac{W}{L}$ must be 4 times