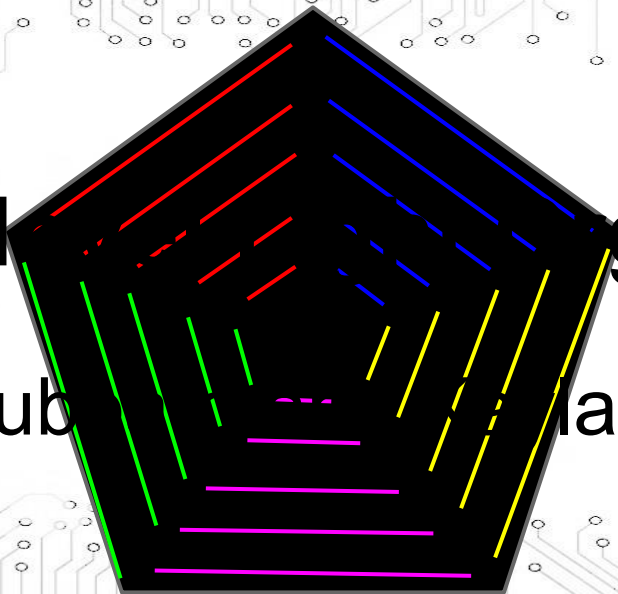


A Negan


Xavier Hubla Statham



Overview




Block Diagram

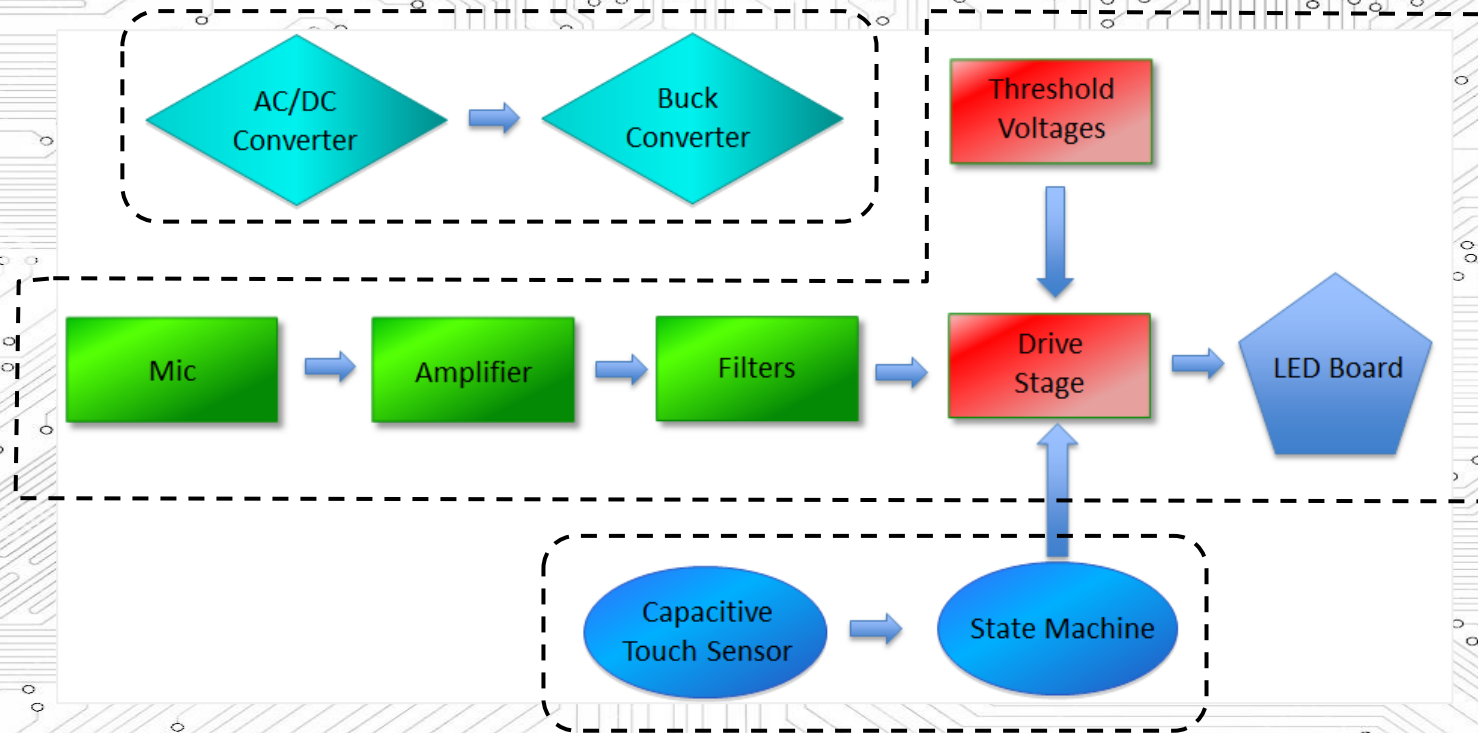


Choosing Frequency Bands

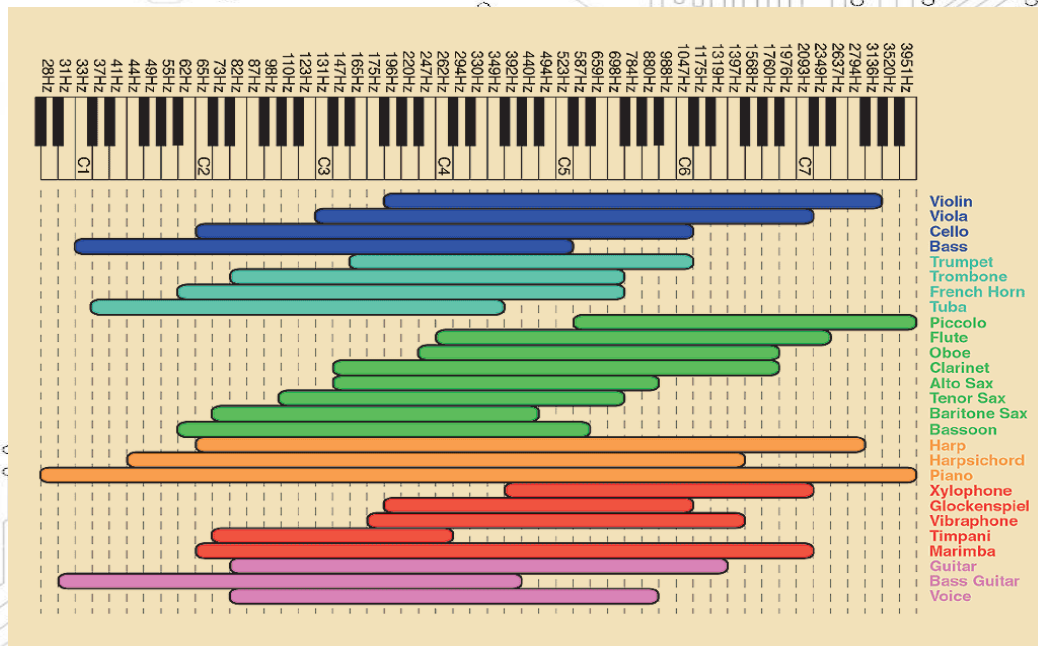- Well populated midrange & sparsely populated highs and lows
- Selected Frequency Bands:
 - 0 - 131Hz
 - 132-262Hz
 - 263-523Hz
 - 524-1047Hz
 - 1048-3951Hz




Filtering

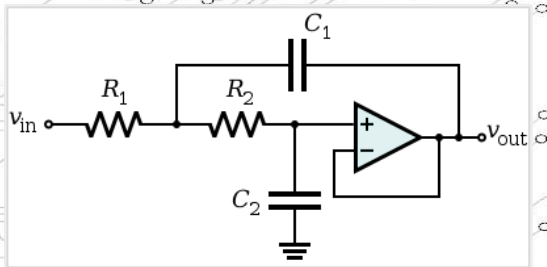
- Sallen-Key Topology for 2nd order response
- Lowpass, Highpass and Bandpass used.


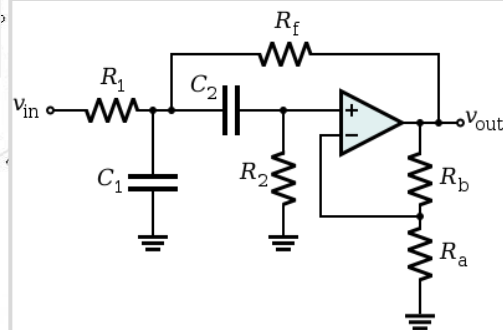
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{s^2 + s \left(\frac{1}{R_2 C_1} + \frac{1}{R_1 C_1} \right) + \frac{1}{R_1 C_1 R_2 C_2}}$$



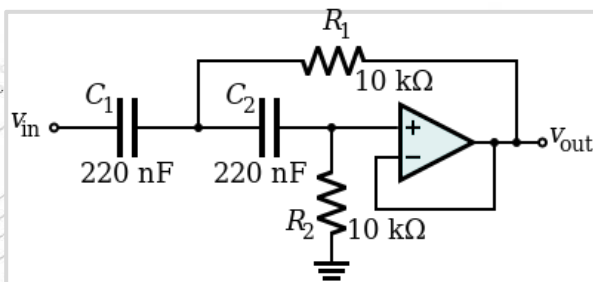
$$H(s) = \frac{\left(1 + \frac{R_b}{R_a}\right) \frac{s}{R_1 C_1}}{s^2 + \underbrace{\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{R_b}{R_a R_1 C_1}\right)}_{2\zeta\omega_0 = \frac{\omega_0}{Q}} s + \underbrace{\frac{R_1 + R_f}{R_1 R_f R_2 C_1 C_2}}_{\omega_0^2 = (2\pi f_0)^2}}$$




$$H(s) = \frac{C_1 C_2 s^2}{1/R_1 R_2 + s C_2 / R_2 + s C_1 / R_2 + C_1 C_2 s^2}$$

Amplification!

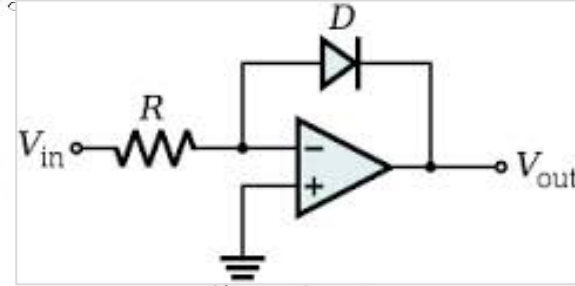- Raise Voltage Levels to drive MOSFETs
- Humans Hear on a Logscale
- Amplifier/LogAmplifier
- Not a lot of current draw!




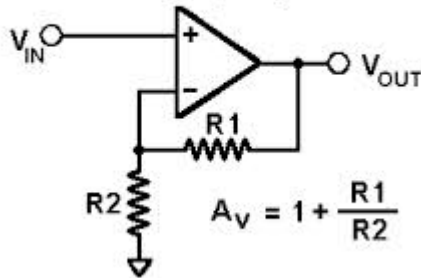
$$V_{out} = K \ln \frac{V_{in}}{V_{ref}}$$





$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

Light Organ: Driving and Board

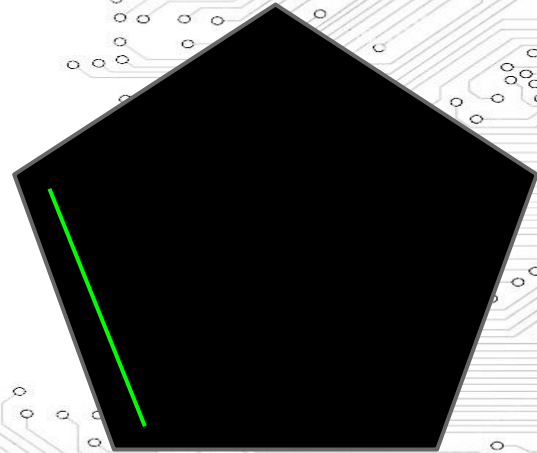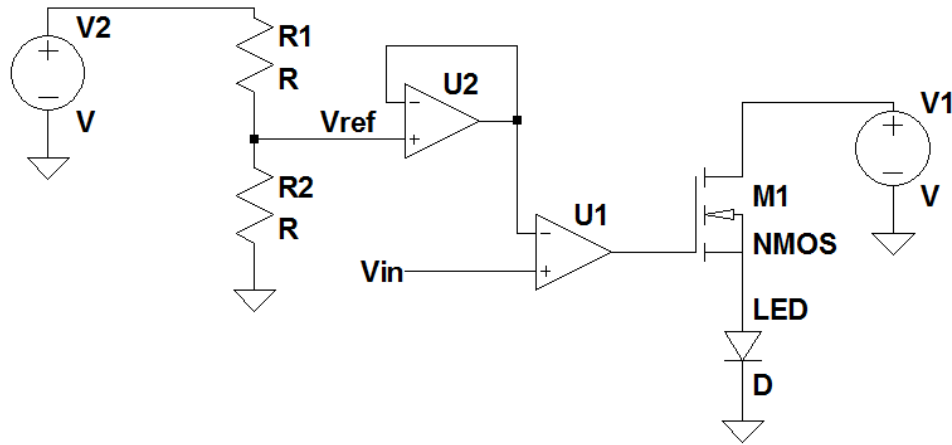


LED Strips

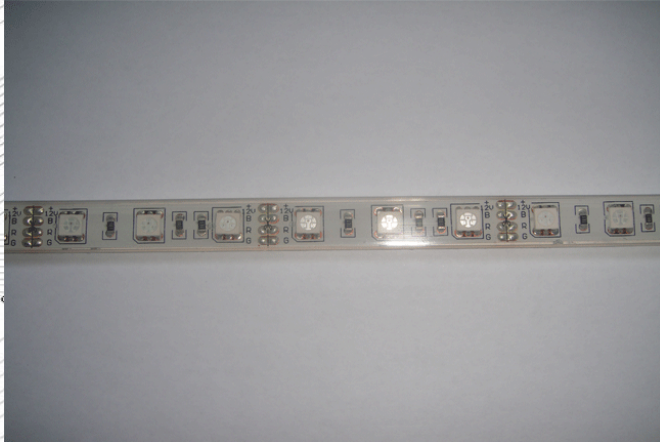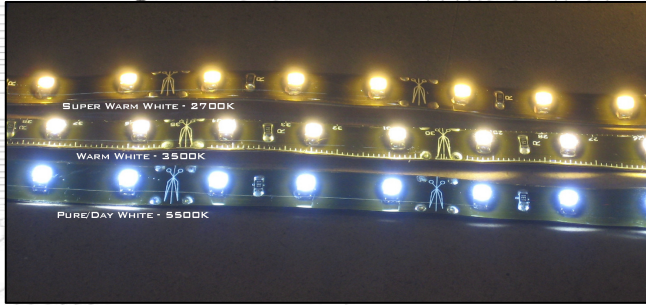


Power Supply

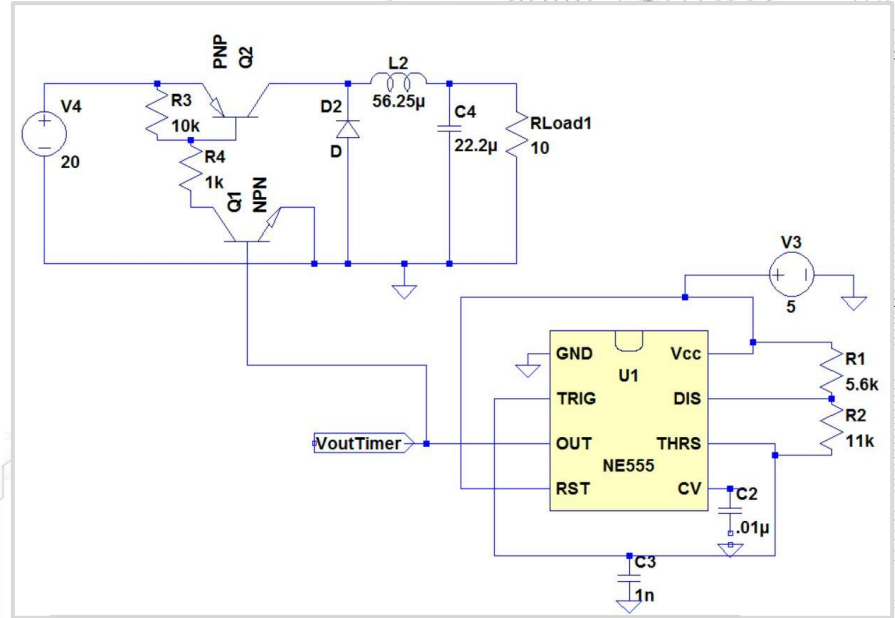- Using a simple laptop charger to create 20VDC from wall outlet
- Buck Converter will provide us with 12V DC for driving LED Strips
- LM805 Regulator will be used to power the 555




Capacitive Touch

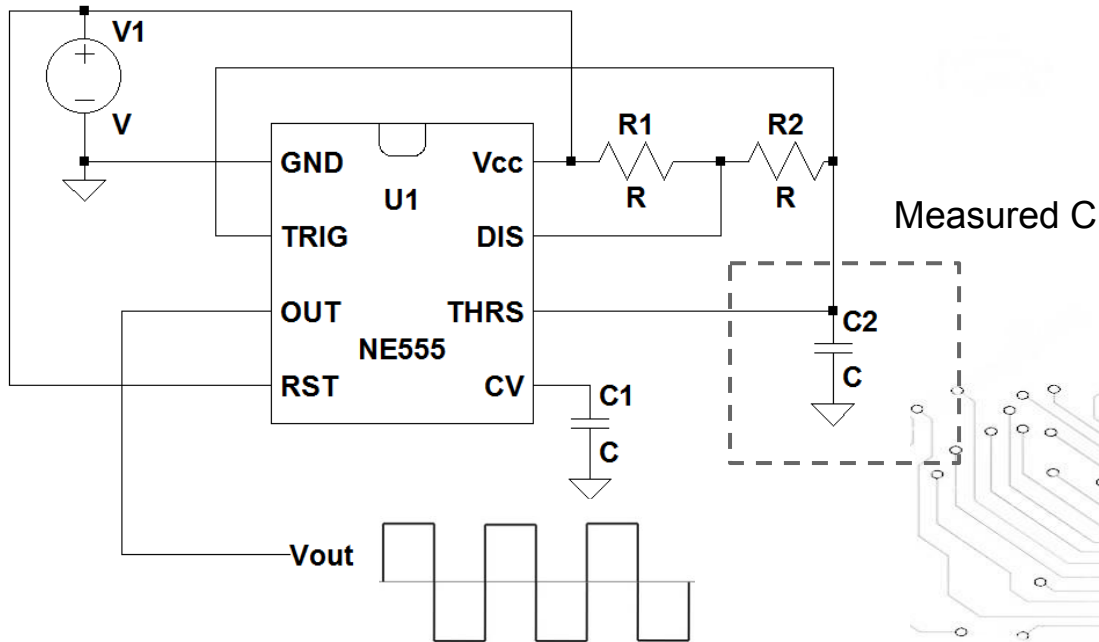

$$F \propto 1/C$$

Detect change in
frequency to
toggle on/off

Timeline

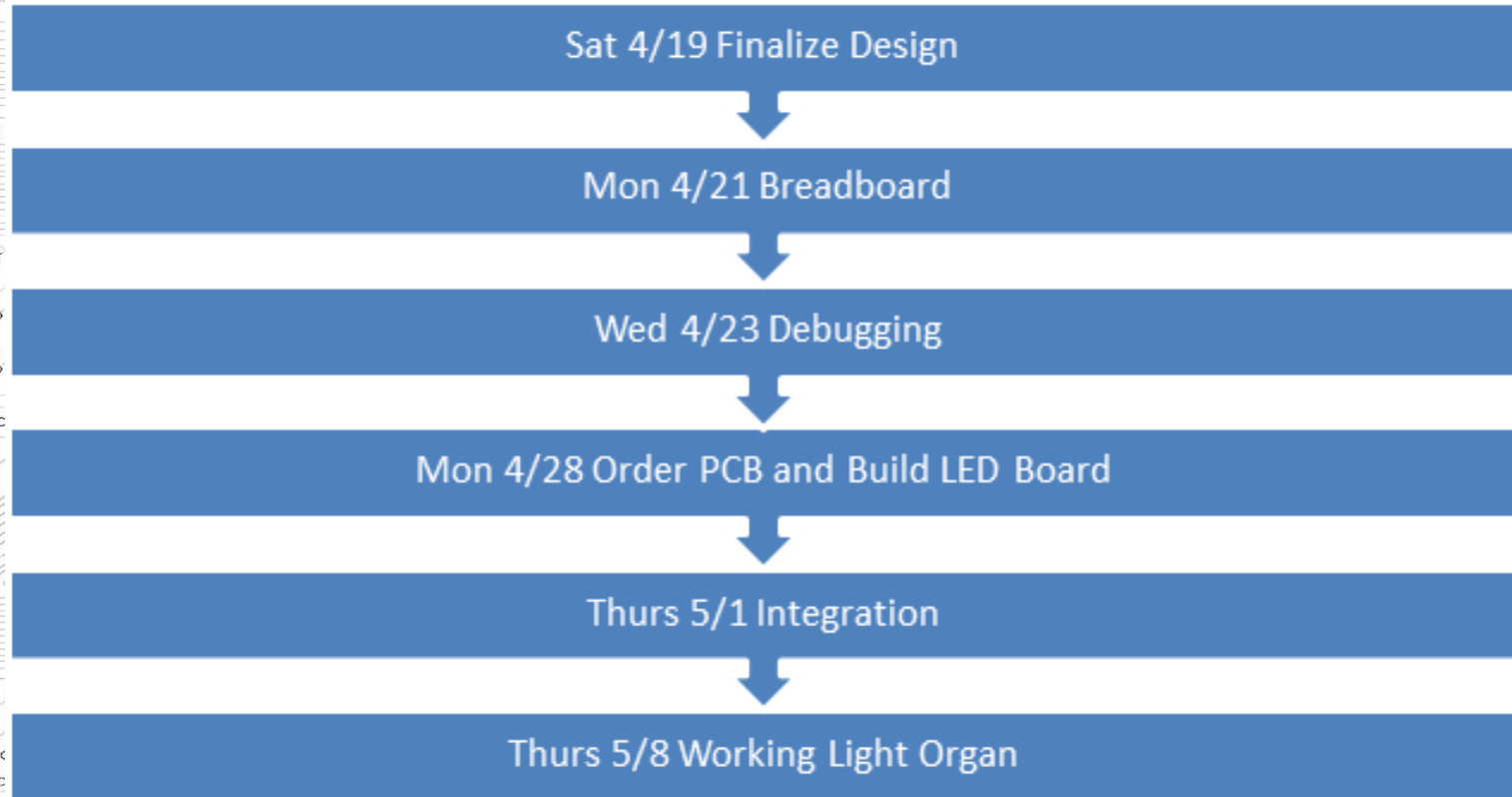

Potential Hiccups

- Many Op Amp comparators used so sizing will be difficult
- Current draw from power stage needs to be carefully monitored
- Designing an analog on/off toggle that works with the capacitive touch stage
- Choosing material for LED board

Looking Forward

- Creating multiple LED boards that are hot-swappable
- Using capacitive touch to control the brightness of the LEDs
- Using batteries as an optional power supply



Questions
?