

Modular Analog Synthesizer

Lauren Gresko

Elliott Williams

Elaine McVay

What is a Analog Synth?


- First Purely Electronic Instrument
- Collection of modules
- Produce, Modify, and Control Music Signals
- Unlimited Sounds




Why Build an Analog Synth?

- Resurgence in Popularity
- Introduction to Music Engineering
- Interesting Application of a Wide Range of EE Concepts
- Personal Interest

Overall System Design

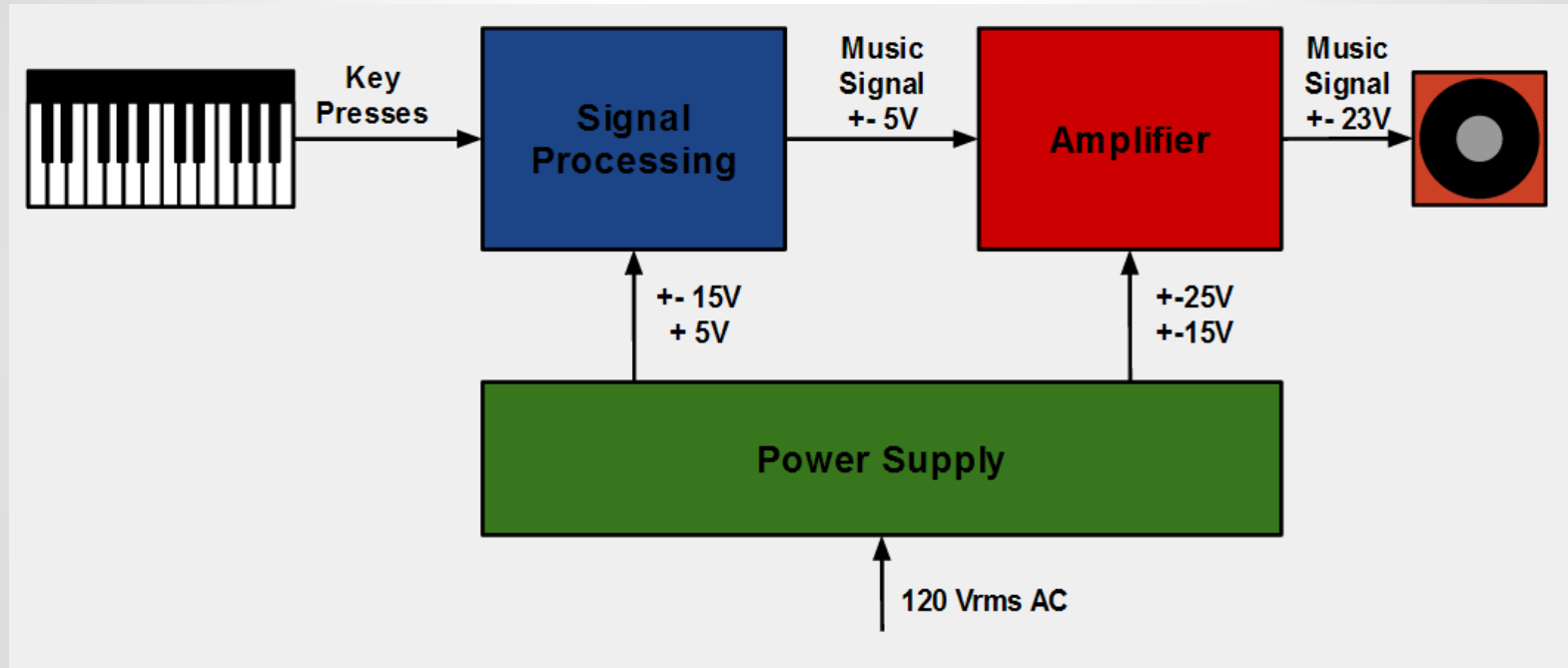

Signal Processing System

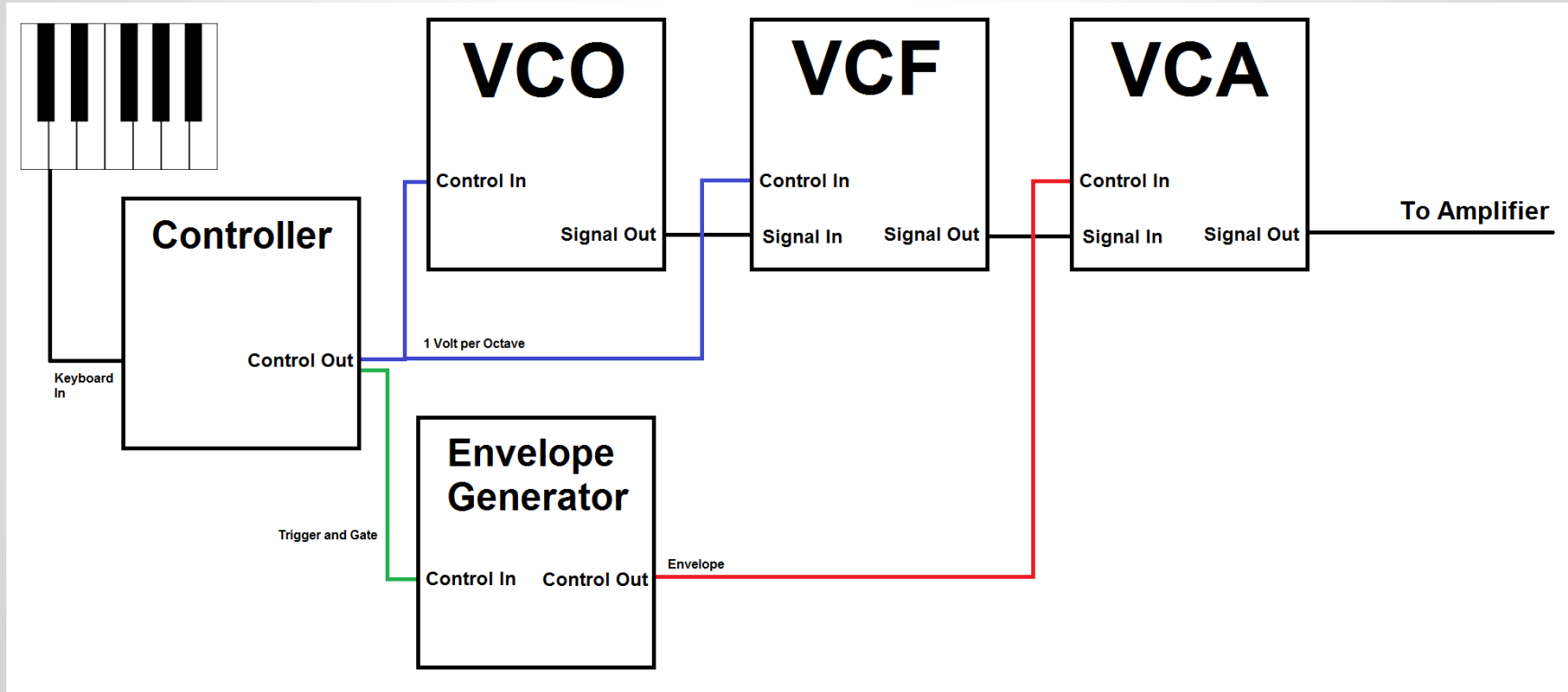


Signal Processing Modules

- Controller
- Voltage Controlled Oscillator
- Voltage Controlled Filter
- Voltage Controlled Amplifier
- Envelope Generator

Module I/O Signal Types


- Music Signal
 - -5V to +5V
- Control Signal
 - Gate, Trigger, Envelope
 - 1V per Octave
 - 0 to +5V

Example Patch

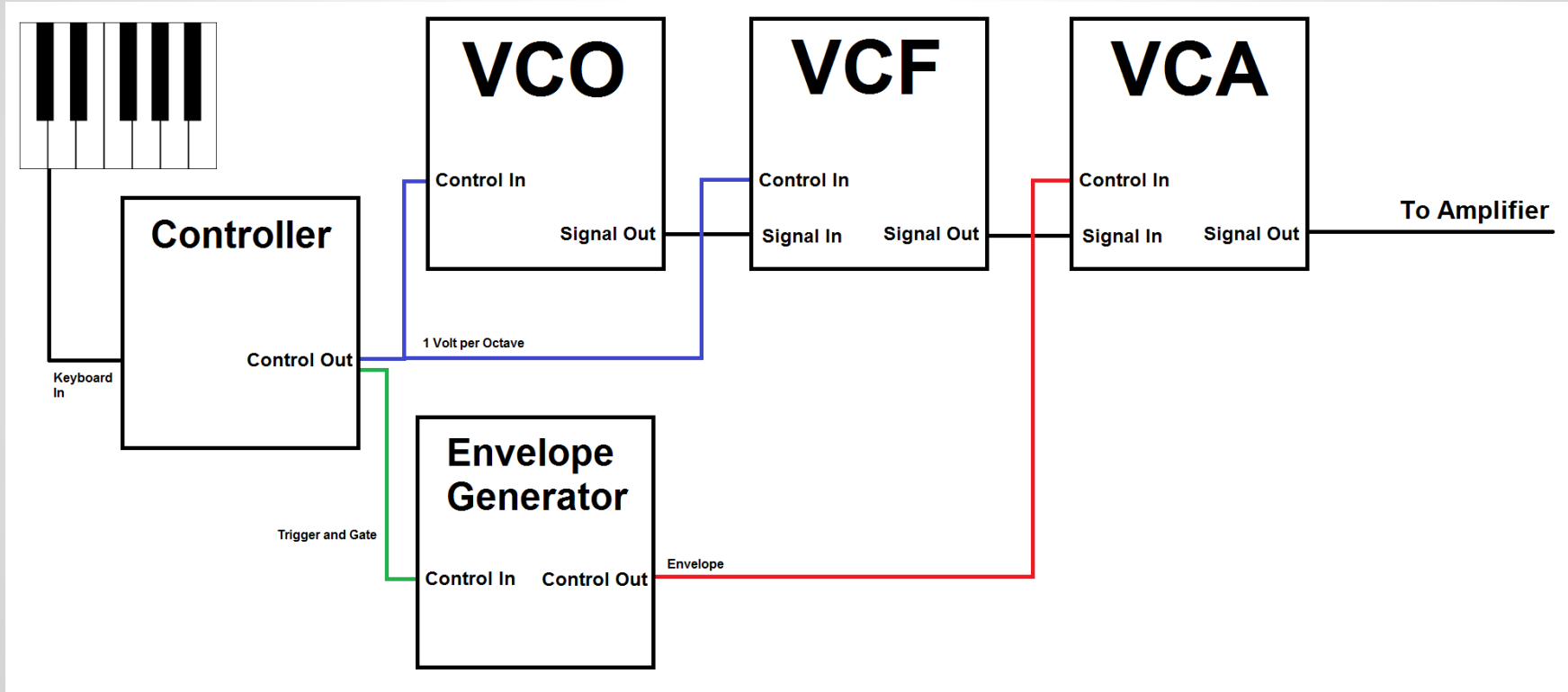


The Power Amplifier

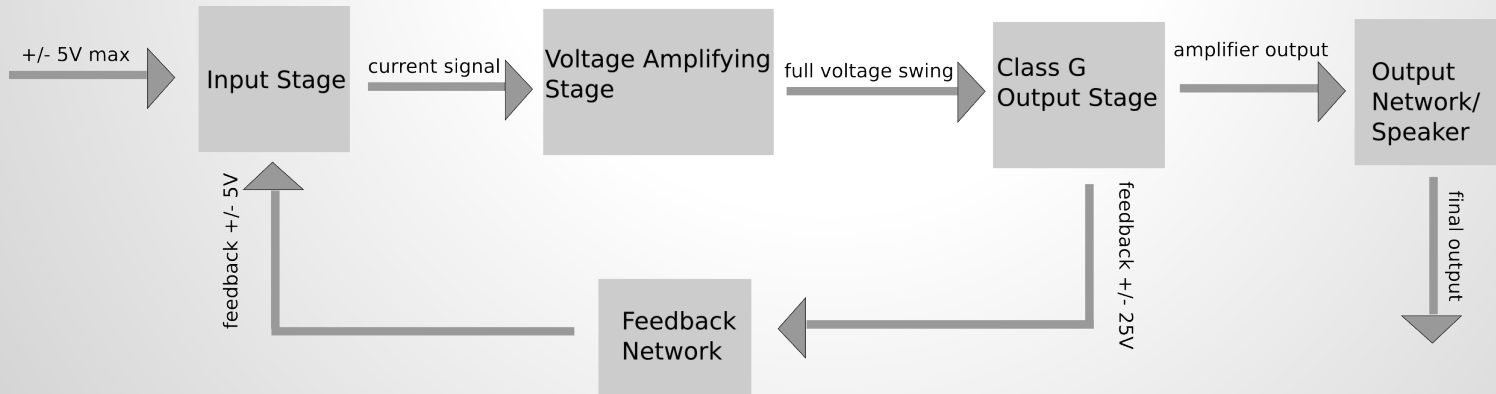- Gain of 4.5
- Bandwidth of 20Hz - 20kHz
- High Slew Rate, Maintain Linearity, Stability, Low Distortion




Class G Amplifier

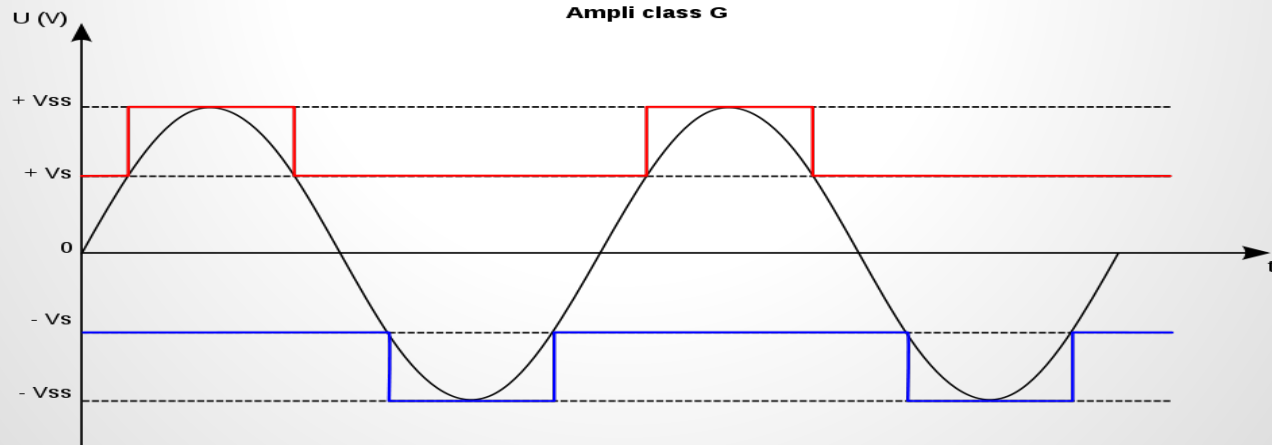- Utilizes two sets of supply rails in the output stage, reducing the power consumption but maintaining linearity.




Input Stage

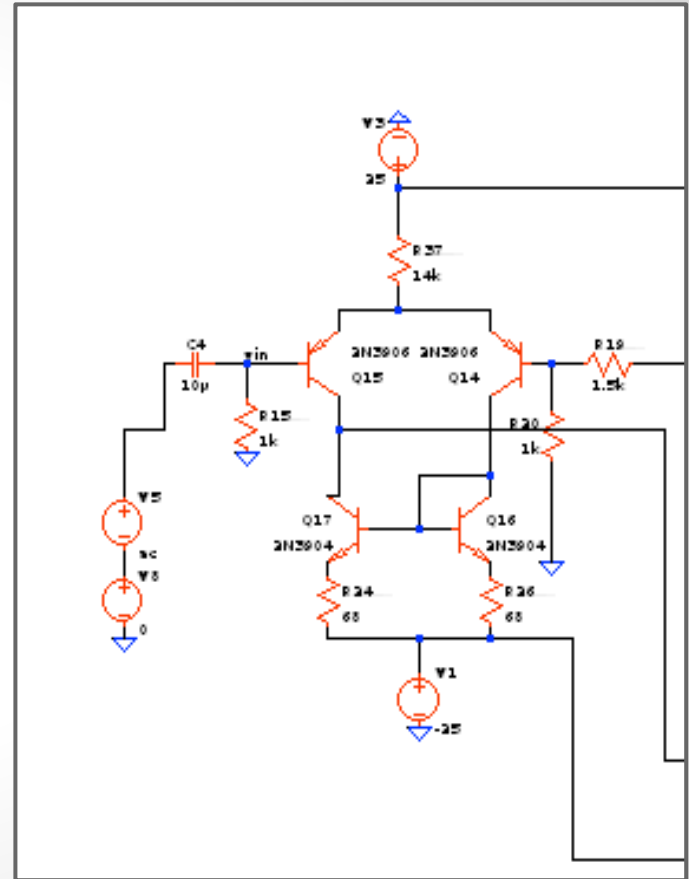- Allows for feedback from the output, improving linearity.
- Slew Rate is determined in the Input Stage: ICC/C_{dom} .





Voltage Amplifying Stage

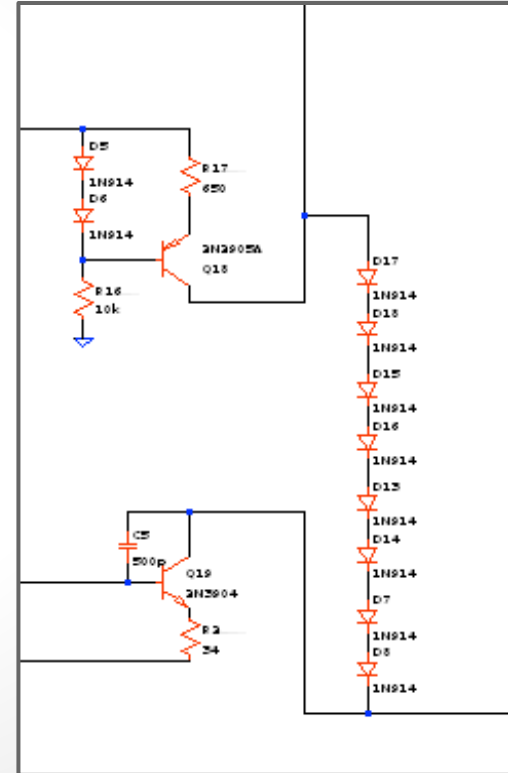- Need to set the dominant pole (Cdom). Bandwidth = $gm1 / (2 * \pi * Cdom * gain)$.
- Want open loop gain to fall below unity before enough phase accumulates.




Class G Output Stage

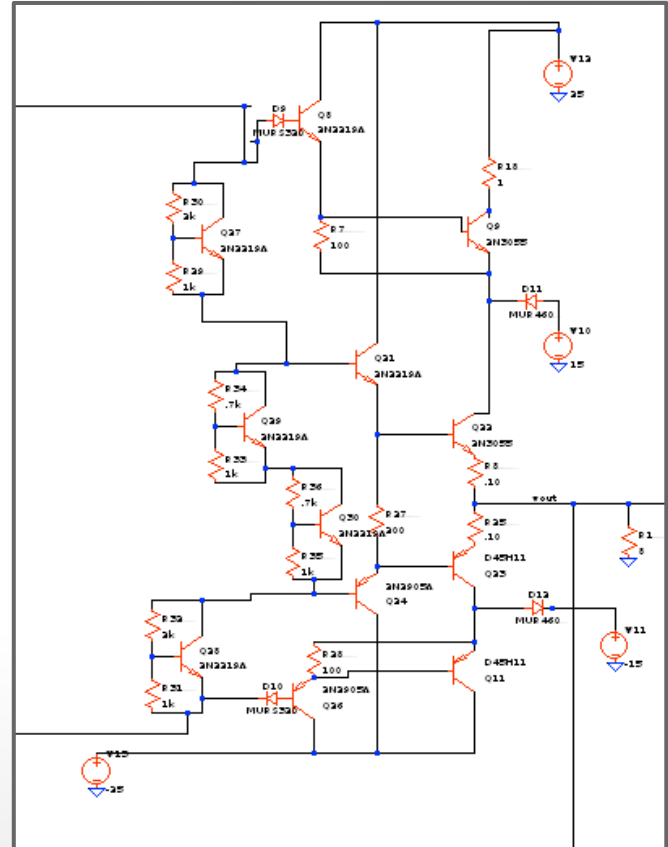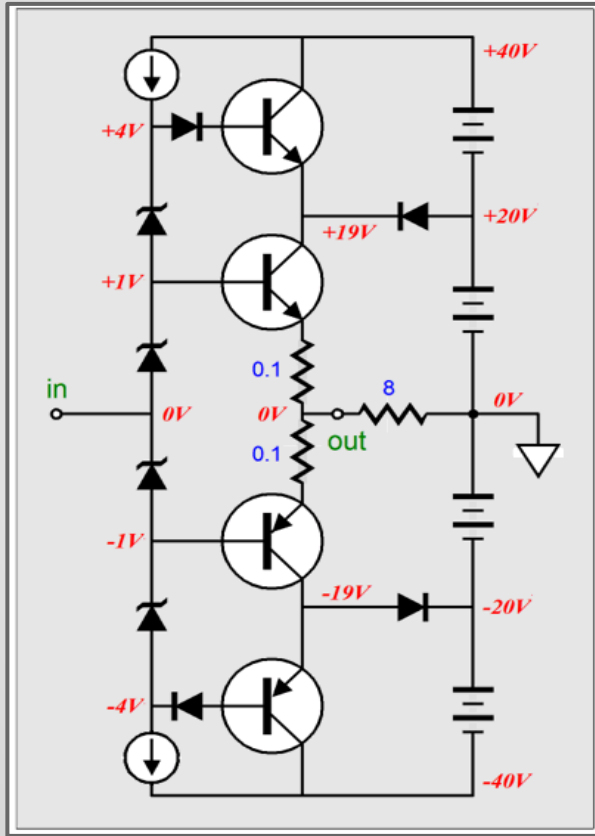


Output Network, Feedback


Possible Feedback Adjustment

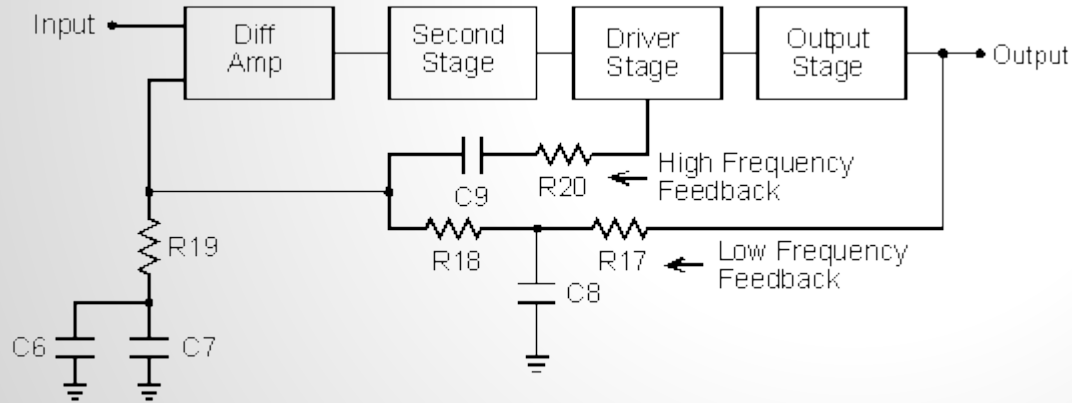

Output Network

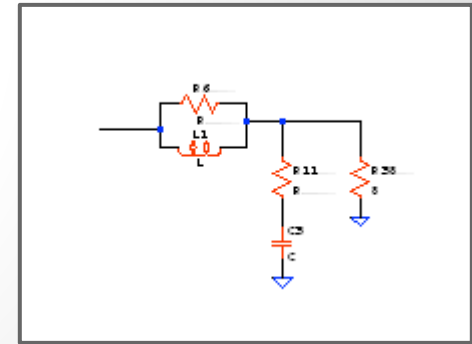

AC/DC Power Supply

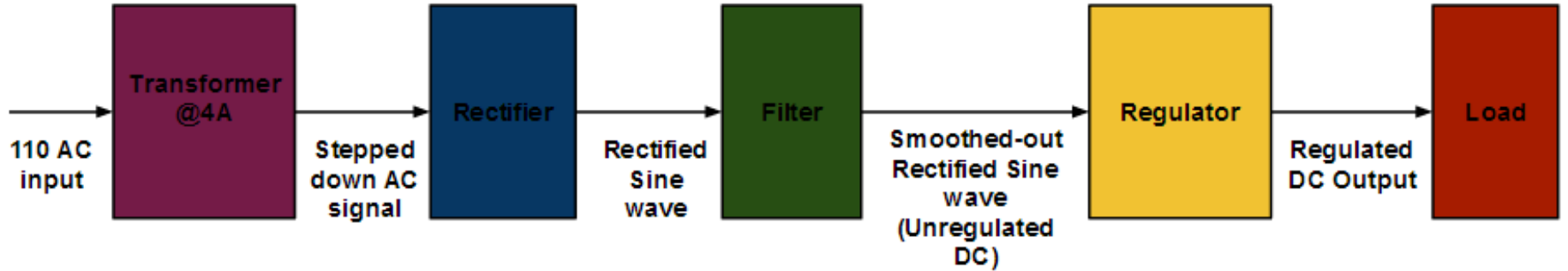


+/-25V

Bridge Rectifier

Smoothing
Capacitor

Voltage Regulator

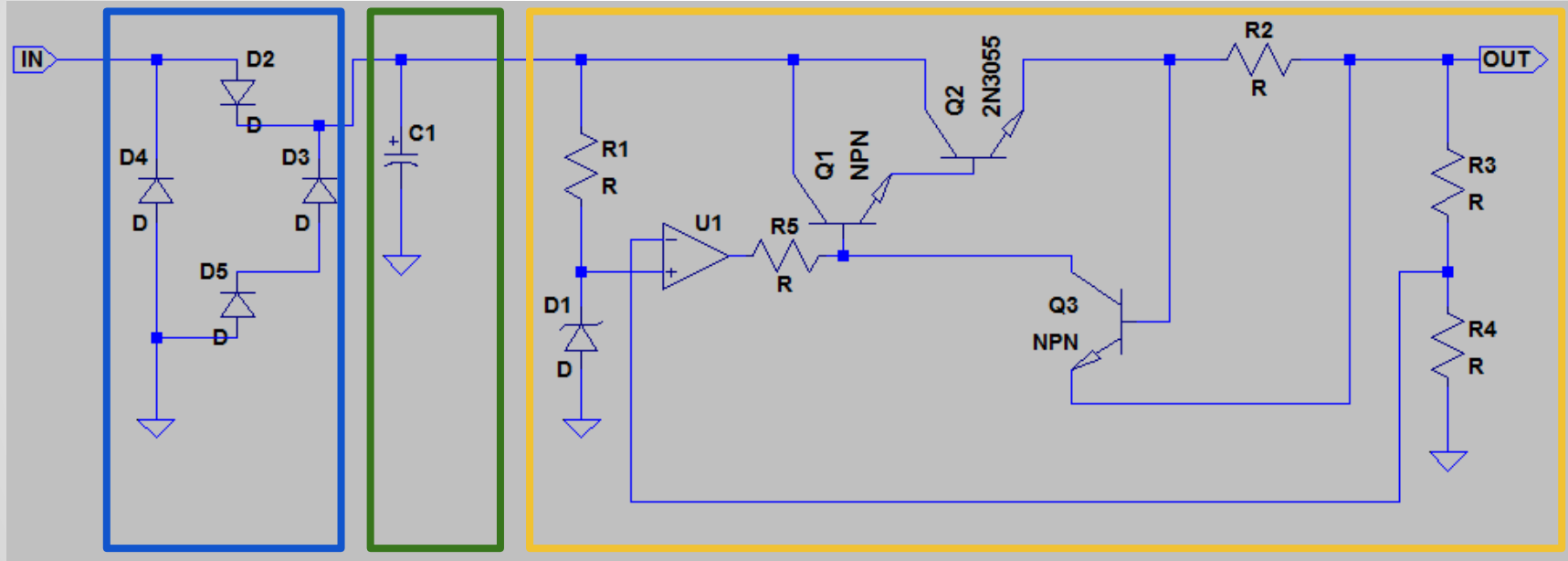

Specifications + Challenges

Supplying 25V@3.2A

Supplying 15V@4A

Limited selection of transformers


Voltage drop of Regulation Circuitry

Heatsinking



+/-15V & +/-10V

Voltage Regulator

Bridge Rectifier

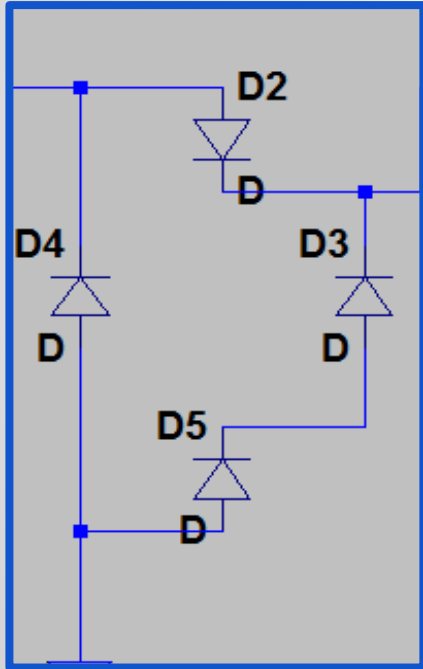

Smoothing Capacitor

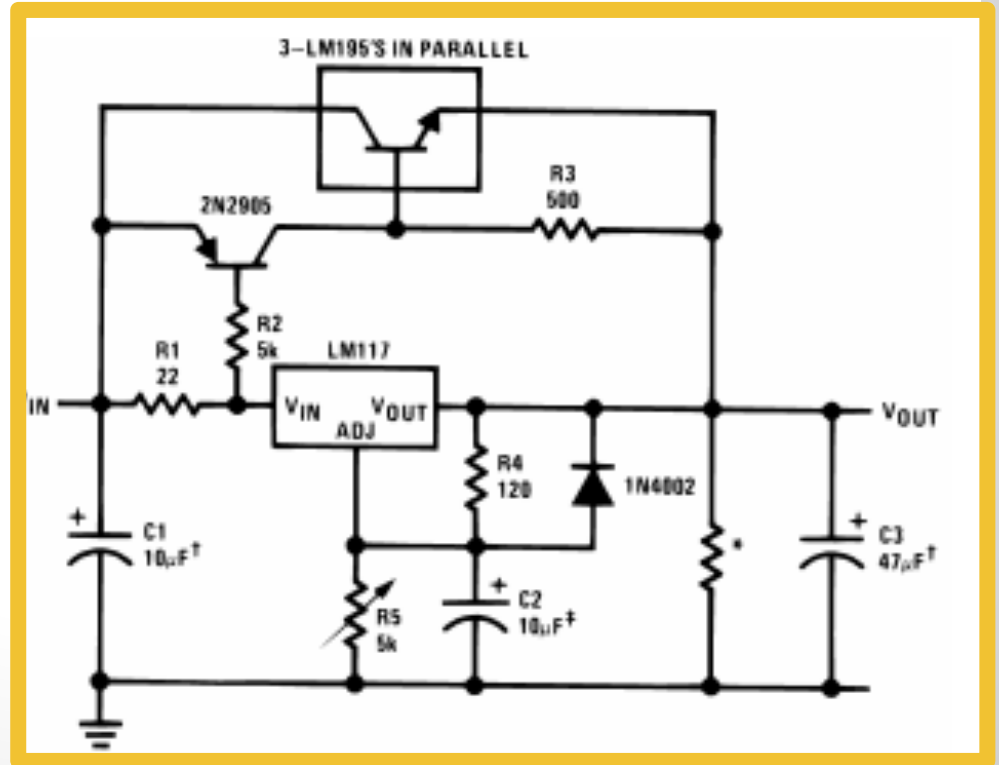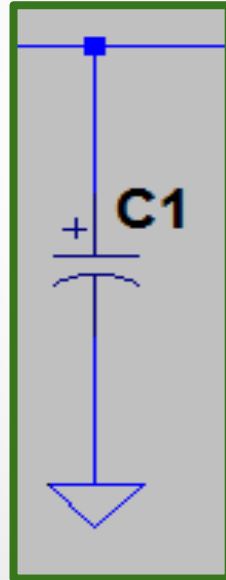

Timeline

- Week of the:
 - 3/31- Design modules
 - 4/7 - Breadboard + Test
 - 4/14 - Finalize Designs, Order Parts + Testing
 - 4/28- Order parts and a PCB + Build Controller, Power Supply, and Amplifier
 - 5/5 - Test + Construct PCB + Integrate

Conclusion

- An Analog Synthesizer is a fun project that will provide us with valuable experience in addition to a nice final product.